

EECS 42 Introduction Digital Electronics

Andrew R. Neureuther

Quiz 10/30 and Midterm 10/6


Lecture # 18 Logic Transients (Handout)

- A) Review: Quiz 10/30 and Midterm 11/6
- B) Transient as Capacitor Charging
- C) Equivalent Resistance for MOS
- D) Inverter Propagation Delay
- E) Complementary MOS Operation

<http://inst.EECS.Berkeley.EDU/~ee42/>

Copyright 2003, Regents of University of California

Midterm #2 Coverage

- Logic Functions and Timing Diagrams  Quiz 10/30
- Analysis of vanilla circuits with dependent sources
- Ideal Op-Amps
- Analysis of circuits using dependent sources to improve characteristics
- Static analysis of logic gates

	V_t (V)	$V_{OUT-SAT}$ (V)	k' ($\mu\text{A}/\text{V}^2$)
NMOS	0.43	0.63	100
PMOS	0.4	1	25

Minimum sized devices have $W/L = 2$

$$I_{OUT-SAT-n} = k'_n \left(\frac{W}{L} \right)_n (V_{IN} - V_{Tn}) V_{OUT-SAT-n}$$

$$I_{OUT-SAT-p} = k'_p \left(\frac{W}{L} \right)_p (V_{DD} - V_{IN} - |V_{Tp}|) V_{OUT-SAT-p}$$

Copyright 2003, Regents of University of California


**Logical Synthesis
Guided by DeMorgan's Theorem**

DeMorgan's Theorem :

$$A + B + C = \overline{\overline{A} \overline{B} \overline{C}} \quad \text{or} \quad \overline{A} + \overline{B} + \overline{C} = \overline{[A B C]}$$

 Example of Using DeMorgan's Theorem:


$$F = A \bullet B + C \bullet D \bullet E = \overline{\overline{A B} \bullet \overline{C D E}}$$



Thus any sum of products expression can be immediately synthesized from NAND gates alone

EFFECT OF GATE DELAY

Cascade of Logic Gates

 

Inputs have different delays, but we ascribe a single worst-case delay τ to every gate

How many "gate delays for shortest path? ANSWER : 2


How many gate delays for longest path? ANSWER : 3

TIMING DIAGRAMS

Version Date 10/28/03

Show transitions of variables vs time

 
Glitching: temporary switching to an incorrect value



Copyright 2003, Regents of University of California

Version Date 10/28/03

 EXAMPLE CIRCUIT: INCREASED INPUT RESISTANCE



Analysis: apply i_{TEST} and evaluate v_{TEST}

$$v_{IN} = R_{IN} i_{TEST} \quad v_{TEST} = R_{IN} i_{TEST} + v_E$$

KCL $\frac{v_E}{R_E} + \frac{v_E}{R_O} - i_{TEST} - G_m R_{IN} i_{TEST} = 0$


Check for special case for R_O infinite $\frac{v_{TEST}}{i_{TEST}} = R_{IN} + (1 + G_m R_{IN}) R_E$

Similar to the homework

Intuitive Explanation: R_E puts R_{IN} on a node whose voltage increases in response to current in R_{IN} .

Copyright 2003, Regents of University of California

Composite I_{OUT} vs. V_{OUT} for CMOS

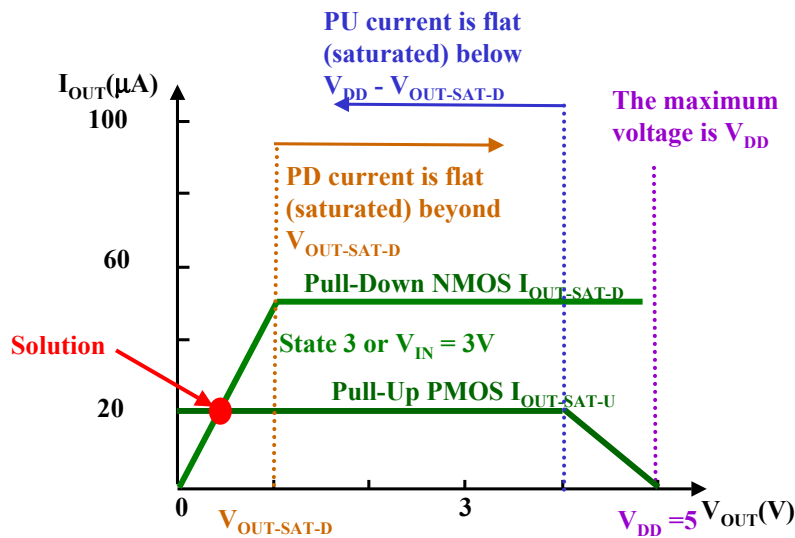

Copyright 2003, Regents of University of California

Method for Finding V_M

At V_M ,

- 1) $V_{OUT} = V_{IN} = V_M$
- 2) Both devices are in saturation
- 3) $I_{OUT-SAT-D} = I_{OUT-SAT-U}$

$$I_{OUT-SAT-D} = k_D (V_{IN} - V_{TD})^2 V_{OUT-SAT-D}$$

$$= I_{OUT-SAT-U} = k_U (V_{DD} - V_{IN} - V_{TU})^2 V_{OUT-SAT-U}$$


Substitute V_M

Solve for V_M

 
Example Result: When $k_D = k_U$, $V_{OUT-SAT-D} = V_{OUT-SAT-U}$ and $V_{TD} = V_{TU}$, then $V_M = V_{DD}/2$

Copyright 2003, Regents of University of California


Voltage Transfer Function for the Complementary Logic Circuit



 Transient Gate Problem: Discharging and Charging Capacitance on the Output



Output Propagation Delay High to Low

 


When V_{IN} goes High V_{OUT} starts decreases with time

Assume that the necessary voltage swing to cause the next downstream gate to begin to switch is $V_{DD}/2$ or $2.5V$.

That is the propagation delay τ_{HL} for the output to go from high to low is the time to go from $V_{DD} = 5V$ to to $V_{DD}/2 = 2.5V$

Copyright 2003, Regents of University of California

 Output Propagation Delay High to Low (Cont.)



When $V_{OUT} > V_{OUT-SAT-D}$ the available current is $I_{OUT-SAT-D}$

For this circuit when $V_{OUT} > V_{OUT-SAT-D}$ the available current is constant at $I_{OUT-SAT-D}$ and the capacitor discharges.

The **propagation delay** is thus

$$\Delta t = \frac{C_{OUT}\Delta V}{I_{OUT-SAT-D}} = \frac{C_{OUT}V_{DD}}{2I_{OUT-SAT-D}} = \frac{50\text{fF} \cdot 2.5V}{100\mu A} = 1.25\text{ns}$$

Copyright 2003, Regents of University of California

Switched Equivalent Resistance Model

The above model assumes the device is an ideal constant current source.


- 1) This is not true below $V_{OUT-SAT-D}$ and leads to inaccuracies.
- 2) Combining ideal current sources in networks with series and parallel connections is problematic.

Instead define an equivalent resistance for the device by setting $0.69R_D C$ equal to the Δt found above

$$\Delta t = \frac{C_{OUT} V_{DD}}{2I_{OUT-SAT-D}} = 0.69R_D C_{OUT}$$



This gives
 
$$R_D = \frac{V_{DD}}{2 \cdot (0.69)I_{OUT-SAT-D}} \approx \frac{3}{4} \frac{V_{DD}}{I_{OUT-SAT-D}} = \frac{3}{4} \frac{5V}{100\mu A} = 37.5k\Omega$$



Each device can now be replaced by this equivalent resistor.

  $R_D = \frac{3}{4} V_{DD}/I_{SAT}$ has a Physical Interpretation



$\frac{3}{4} V_{DD}$ is the average value of V_{OUT}

Approximate the NMOS device curve by a straight line from $(0,0)$ to $(I_{OUT-SAT-D}, \frac{3}{4} V_{DD})$.

Interpret the straight line as a resistor with

$$\text{slope} = 1/R = \frac{3}{4} V_{DD}/I_{SAT}$$

Switched Equivalent Resistance Values

The resistor values depend on the properties of silicon, geometrical layout, design style and technology node.

n-type silicon has a carrier mobility that is 2 to 3 times higher than p-type.

The resistance is inversely proportion to the gate width/length in the geometrical layout.

Design styles may restrict all NMOS and PMOS to be of a predetermined fixed size.


The current per unit width of the gate increases nearly inversely with the linewidth.

For convenience in EE 42 we assume
 $R_D = R_U = 10 \text{ k}\Omega$ for $V_{DD} = 5\text{V}$ and
 $R_D = R_U = 10 \text{ k}\Omega$ for $V_{DD} = 5\text{V}$

Copyright 2003, Regents of University of California

Inverter Propagation Delay

Discharge (pull-down)

 

$$\Delta t = 0.69R_D C_{OUT} = 0.69(10\text{k}\Omega)(50\text{fF}) = 345 \text{ ps}$$


Discharge (pull-up)

$$\Delta t = 0.69R_U C_{OUT} = 0.69(10\text{k}\Omega)(50\text{fF}) = 345 \text{ ps}$$

Copyright 2003, Regents of University of California

NMOS and PMOS use the same set of input signals


CMOS Logic Gate

 

PMOS only in pull-up
 PMOS conduct when input is low
 PMOS do not conduct when $A + (BC)$
 NMOS only in pull-down
 NMOS conduct when input is high.
 NMOS conduct for $A + (BC)$
 Logic is Complementary and produces $F = \overline{A + (BC)}$

CMOS Logic Gate: Example Inputs


A = 0
 B = 0
 C = 0

 

PMOS all conduct
 Output is High
 $= V_{DD}$
 NMOS do not conduct
 Logic is Complementary and produces $F = 1$

CMOS Logic Gate: Example Inputs

A = 0
B = 1
C = 1

 

PMOS A conducts; B and C Open

Output is High



= 0

NMOS B and C conduct; A open

Logic is Complementary and produces $F = 0$

Copyright 2003, Regents of University of California

Switched Equivalent Resistance Network

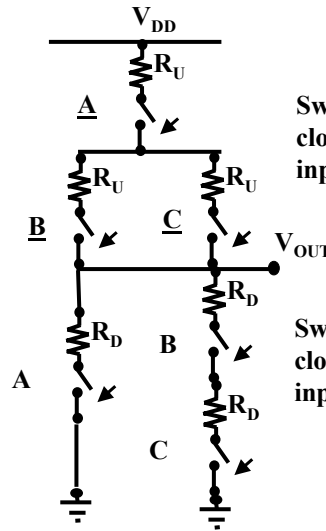 

Switches close when input is low.

Switches close when input is high.

Copyright 2003, Regents of University of California