

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 18: 10/28/03 A.R. Neureuther
Version Date 10/28/03

EECS 42 Introduction Digital Electronics

Andrew R. Neureuther

Quiz 10/30 and Midterm 10/6

Lecture # 18 Logic Transients (Handout)

- A) Review: Quiz 10/30 and Midterm 11/6
- B) Transient as Capacitor Charging
- C) Equivalent Resistance for MOS
- D) Inverter Propagation Delay
- E) Complementary MOS Operation

<http://inst.EECS.Berkeley.EDU/~ee42/>

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 18: 10/28/03 A.R. Neureuther
Version Date 10/28/03

Midterm #2 Coverage

- Logic Functions and Timing Diagrams ↔ Quiz 10/30
- Analysis of vanilla circuits with dependent sources
- Ideal Op-Amps
- Analysis of circuits using dependent sources to improve characteristics
- Static analysis of logic gates

	$V_T(V)$	$V_{OUT-SAT}(V)$	$k'(\mu A/V^2)$
NMOS	0.43	0.63	100
PMOS	0.4	1	25

Minimum sized devices have $W/L = 2$

$$I_{OUT-SAT-n} = k_n \left(\frac{W}{L}\right)_n (V_{IN} - V_{Tn})^2 V_{OUT-SAT-n}$$

$$I_{OUT-SAT-p} = k_p \left(\frac{W}{L}\right)_p (V_{DD} - V_{IN} - |V_{Tp}|)^2 V_{OUT-SAT-p}$$

Copyright 2003, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 18: 10/28/03 A.R. Neureuther
Version Date 10/28/03

Logical Synthesis

Guided by DeMorgan's Theorem

DeMorgan's Theorem :

$$A + B + C = \overline{\overline{A} \overline{B} \overline{C}} \quad \text{or} \quad \overline{A} + \overline{B} + \overline{C} = \overline{[A B C]}$$

Example of Using DeMorgan's Theorem:

$$F = A \cdot B + C \cdot D \cdot E = \overline{\overline{A \cdot B} \cdot \overline{C \cdot D \cdot E}}$$

Thus any sum of products expression can be immediately synthesized from NAND gates alone

Copyright 2003, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 18: 10/28/03 A.R. Neureuther
Version Date 10/28/03

EFFECT OF GATE DELAY

Cascade of Logic Gates

Inputs have different delays, but we ascribe a single worst-case delay τ to every gate

How many "gate delays for shortest path? ANSWER : 2

How many gate delays for longest path? ANSWER : 3

Copyright 2003, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 18: 10/28/03 A.R. Neureuther
Version Date 10/28/03

TIMING DIAGRAMS

Show transitions of variables vs time

Glitching: temporary switching to an incorrect value

Note - becomes valid one gate delay after B switches

Note that - becomes valid two gate delays after B&C switch, because the invert function takes one delay and the NAND function a second.

No change at $t = 3\tau$

Copyright 2003, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 18: 10/28/03 A.R. Neureuther
Version Date 10/28/03

EXAMPLE CIRCUIT: INCREASED INPUT RESISTANCE

Add resistor R_E

The output has been assumed to be shorted $v_{OUT} = 0$

Analysis: apply i_{TEST} and evaluate v_{TEST}

$$v_{IN} = R_{IN} i_{TEST} \quad v_{TEST} = R_{IN} i_{TEST} + v_E$$


Similar to the homework

KCL $\frac{v_E}{R_E} + \frac{v_E}{R_0} - i_{TEST} - G_m R_{IN} i_{TEST} = 0$

Check for special case for R_0 infinite $\frac{v_{TEST}}{i_{TEST}} = R_{IN} + (1 + G_m R_{IN}) R_E$

Intuitive Explanation: R_E puts R_{IN} on a node whose voltage increases in response to current in R_{IN} .

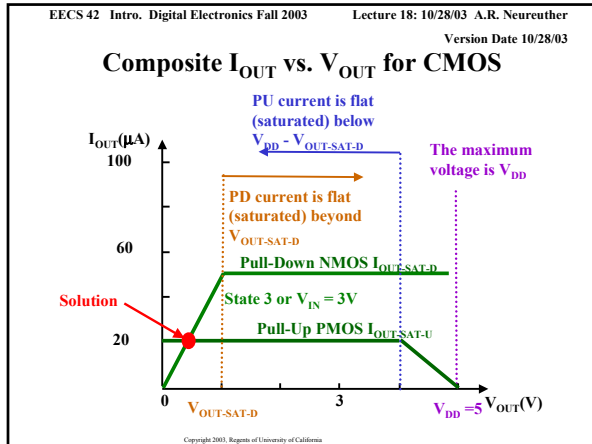Copyright 2003, Regents of University of California



EECS 42 Intro. Digital Electronics Fall 2003 Lecture 18: 10/28/03 A.R. Neureuther
Version Date 10/28/03

Method for Finding V_M

At V_M ,

- $V_{OUT} = V_{IN} = V_M$
- Both devices are in saturation
- $I_{OUT-SAT-D} = I_{OUT-SAT-U}$

$$I_{OUT-SAT-D} = k_D (V_{IN} - V_{TD})^2$$





$$= I_{OUT-SAT-U} = k_U (V_{DD} - V_{IN} - V_{TU})^2$$

Substitute V_M

Solve for V_M

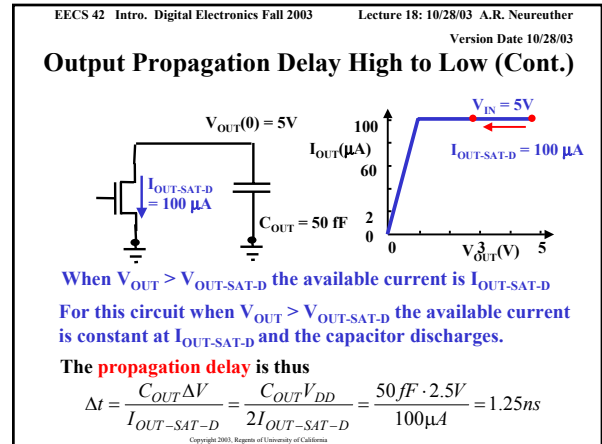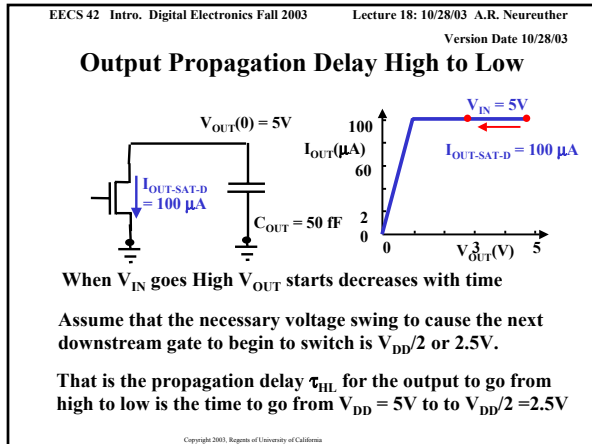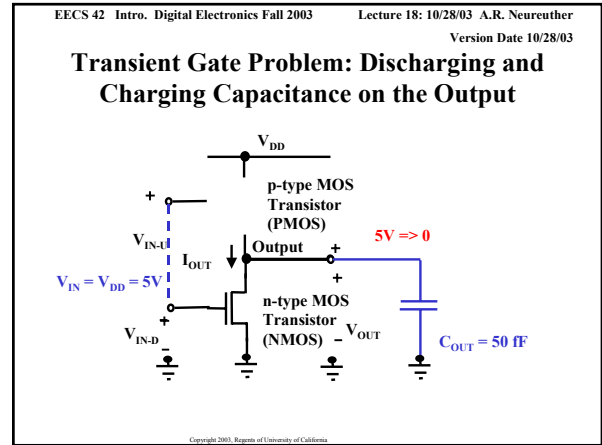 Example Result: When $k_D = k_U$, $V_{OUT-SAT-D} = V_{OUT-SAT-U}$ and $V_{TD} = V_{TU}$, then $V_M = V_{DD}/2$

Copyright 2003, Regents of University of California



EECS 42 Intro. Digital Electronics Fall 2003 Lecture 18: 10/28/03 A.R. Neureuther
Version Date 10/28/03

Switched Equivalent Resistance Model

The above model assumes the device is an ideal constant current source.

- 1) This is not true below $V_{OUT-SAT-D}$ and leads to inaccuracies.
- 2) Combining ideal current sources in networks with series and parallel connections is problematic.

Instead define an equivalent resistance for the device by setting $0.69R_D C$ equal to the Δt found above

$$\Delta t = \frac{C_{OUT} V_{DD}}{2 I_{OUT-SAT-D}} = 0.69 R_D C_{OUT}$$

This gives

$$R_D = \frac{V_{DD}}{2 \cdot (0.69) I_{OUT-SAT-D}} \approx \frac{3}{4} \frac{V_{DD}}{I_{OUT-SAT-D}} = \frac{3}{4} \frac{5V}{100\mu A} = 37.5k\Omega$$

Each device can now be replaced by this equivalent resistor.

Copyright 2003, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 18: 10/28/03 A.R. Neureuther
Version Date 10/28/03

$R_D = \frac{3}{4} V_{DD}/I_{SAT}$ has a Physical Interpretation

$\frac{3}{4} V_{DD}$ is the average value of V_{OUT}

Approximate the NMOS device curve by a straight line from $(0,0)$ to $(I_{OUT-SAT-D}, \frac{3}{4} V_{DD})$.

Interpret the straight line as a resistor with slope $= 1/R = \frac{3}{4} V_{DD}/I_{SAT}$

Copyright 2003, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 18: 10/28/03 A.R. Neureuther
Version Date 10/28/03

Switched Equivalent Resistance Values

The resistor values depend on the properties of silicon, geometrical layout, design style and technology node.

- n-type silicon has a carrier mobility that is 2 to 3 times higher than p-type.
- The resistance is inversely proportion to the gate width/length in the geometrical layout.
- Design styles may restrict all NMOS and PMOS to be of a predetermined fixed size.
- The current per unit width of the gate increases nearly inversely with the linewidth.

For convenience in EE 42 we assume
 $R_D = R_U = 10 k\Omega$ for $V_{DD} = 5V$ and
 $R_D = R_U = 10 k\Omega$ for $V_{DD} = 5V$

Copyright 2003, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 18: 10/28/03 A.R. Neureuther
Version Date 10/28/03

Inverter Propagation Delay

Discharge (pull-down)

$$\Delta t = 0.69 R_D C_{OUT} = 0.69(10k\Omega)(50fF) = 345 ps$$

Discharge (pull-up)

$$\Delta t = 0.69 R_U C_{OUT} = 0.69(10k\Omega)(50fF) = 345 ps$$

Copyright 2003, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 18: 10/28/03 A.R. Neureuther
Version Date 10/28/03

CMOS Logic Gate

NMOS and PMOS use the same set of input signals

- PMOS only in pull-up
- PMOS conduct when input is low
- PMOS do not conduct when $A+(BC)$
- NMOS only in pull-down
- NMOS conduct when input is high.
- NMOS conduct for $A+(BC)$

Logic is Complementary and produces $F = A+(BC)$

Copyright 2003, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 18: 10/28/03 A.R. Neureuther
Version Date 10/28/03

CMOS Logic Gate: Example Inputs


$A = 0$
 $B = 0$
 $C = 0$

- PMOS all conduct
- Output is High $= V_{DD}$
- NMOS do not conduct
- Logic is Complementary and produces $F = 1$

Copyright 2003, Regents of University of California


CMOS Logic Gate: Example Inputs

A = 0
B = 1
C = 1

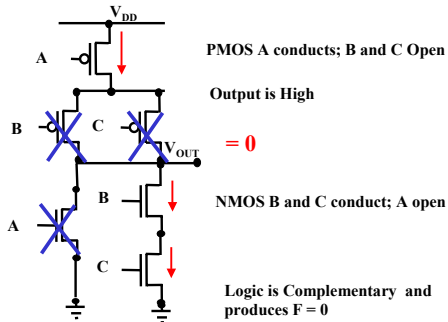

Copyright 2003, Regents of University of California

Switched Equivalent Resistance Network

 

Copyright 2003, Regents of University of California