

EECS 42 Intro. Digital Electronics Fall 2003      Lecture 20: 11/4/03 A.R. Neureuther  
Version Date 11/01/03

## EECS 42 Introduction to Electronics for Computer Science

### Andrew R. Neureuther

### Lecture # 20 Logic Transients

Handout of Monday Lecture.

A) 2<sup>nd</sup> Midterm Review (Cont.)  
B) Internal Path Propagation Delay  
C) Cascade CMOS elements  
D) Logic Feedback creates memory

<http://inst.EECS.Berkeley.EDU/~ee42/>

Copyright 2003, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003      Lecture 20: 11/4/03 A.R. Neureuther  
Version Date 11/01/03

## OP-AMP AND USE OF FEEDBACK

A very high-gain differential amplifier can function in an extremely linear fashion as an operational amplifier by using negative feedback.

EXAMPLE      Circuit Model

Negative feedback  $\Rightarrow$  **Stabilizes** the output

We can show that for  $A \rightarrow \infty$  and  $R_1 \rightarrow \infty$ ,

$$V_0 \approx V_{IN} \cdot \frac{R_1 + R_2}{R_1} \quad \text{Stable, finite, and independent of the properties of the OP AMP!}$$

Copyright 2003, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003      Lecture 20: 11/4/03 A.R. Neureuther  
Version Date 11/01/03

## IDEAL OP-AMPS ANALYSIS TECHNIQUE

Assumption 1: The potential between the op-amp input terminals,  $v_{(+)} - v_{(-)}$ , equals zero.

Assumption 2: The currents flowing into the op-amp's two input terminals both equal zero.

EXAMPLE

Copyright 2003, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003      Lecture 20: 11/4/03 A.R. Neureuther  
Version Date 11/01/03



## CASCADE OP-AMP CIRCUITS







How do you get started on finding  $V_0$ ?

**Hint: Identify Stages**  
**Hint:  $I_{IN}$  does not affect  $V_{O1}$**


See the further examples of op-amp circuits in the reader

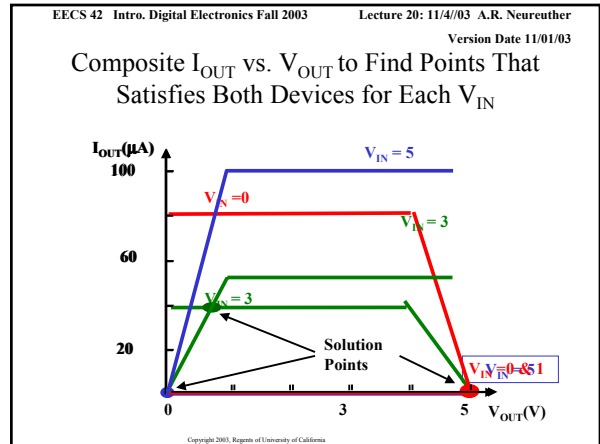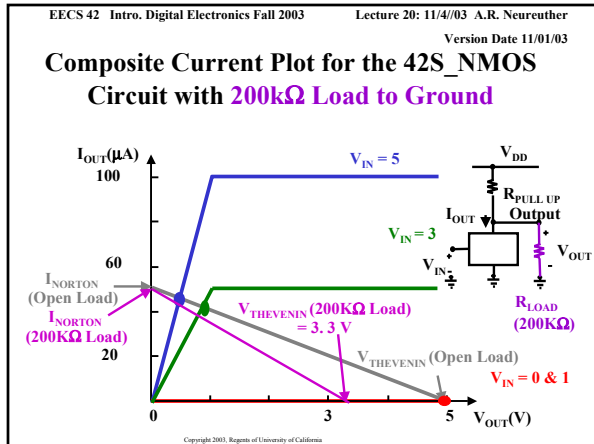Copyright 2003, Regents of University of California



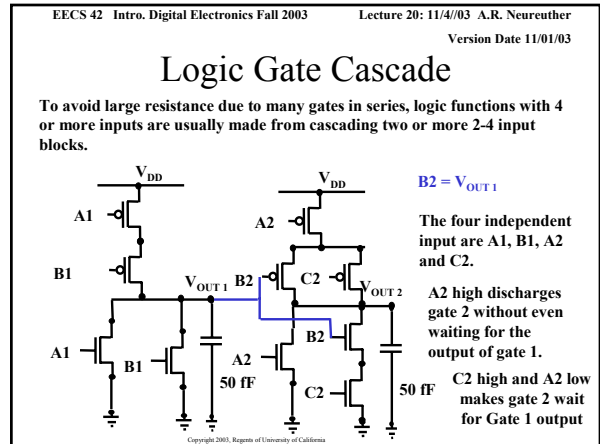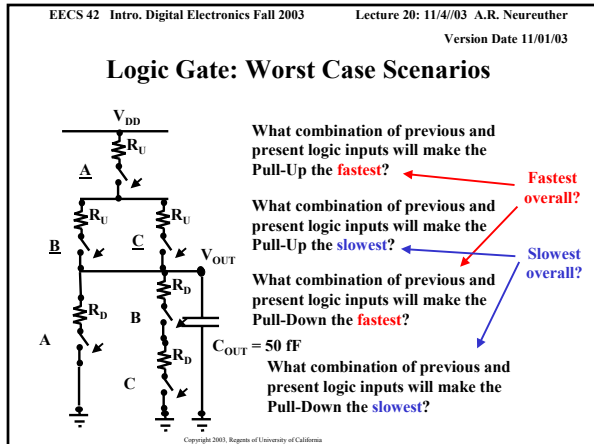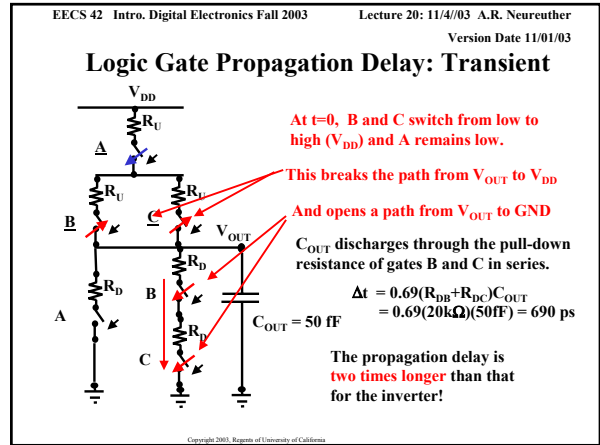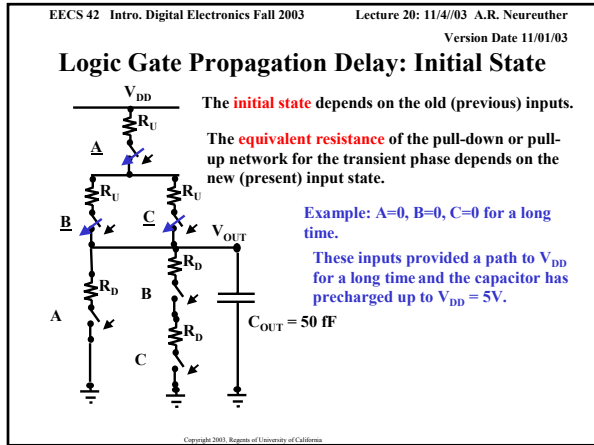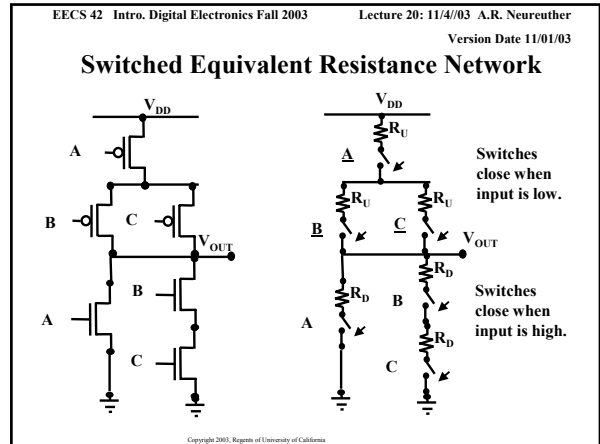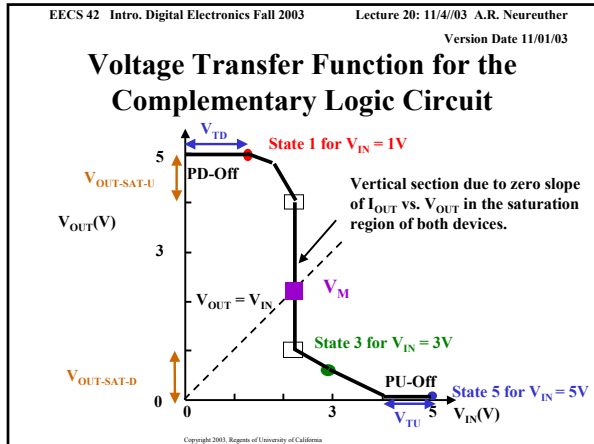


### Feedback Can Provide Memory

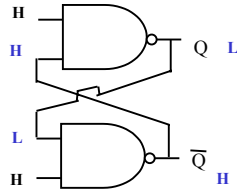


Copyright 2003, Regents of University of California

### Example of the Opposite State

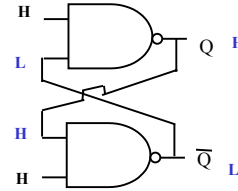

Copyright 2003, Regents of University of California


### Adding Memory Controls

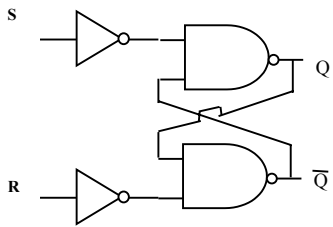

Set-Reset Flip-Flop

Copyright 2003, Regents of University of California

### Adding a Clock

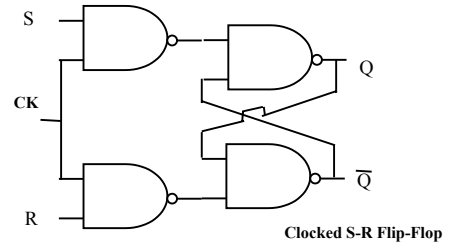

Clocked S-R Flip-Flop

Copyright 2003, Regents of University of California