

EE 42 – Introduction to Electronics for Computer Science



Fall 2003,
Dept. EECS, 510 Cory
UC Berkeley
Course Web Site

neureuth@eecs.berkeley.edu
Office Hours M1, Tu, Tu 10:30-11:30, F 1
<http://www-inst.eecs.berkeley.edu/~ee42/>

Prof. A. R. Neureuther

Problem Set # 9

Due: 1 PM Nov 5th, 2003 in box in 240 Cory

Midterm Thursday November 6th

In class, Closed Book, Closed Notes, Device Equations Provided


Review Session #1: 5 PM Tuesday Nov 4th, meet at 241 Cory

Review Session #2: 6 PM Wednesday Nov 5th, meet at 241 Cory

 9.1 Delay in Transistor Circuits

Use the logic circuit to the right with $R_{PU} = 20k\Omega$, $R_{PD} = 10k\Omega$, and $C = 20fF$.

- For a transition from high voltage to low voltage, where $V_{DD} = 5V$, determine the delay in the system.
- For a transition from low to high voltage, determine the delay in the system.
- What could you do to improve worst case delay by a factor of 2?




9.2 More Delay, and Delay Compensation

Take the following model of a logic circuit. $C = 20fF$.

- Determine the truth table for this circuit. What kind of logic gate is this? (Suppose A & B are input voltages controlling the switches. On pull-up, if control is low, you close the switch. On pull-down, if control is high, you close the switch. Otherwise, the switch is open)
- Given that all resistors are $10k\Omega$, determine worst case delay from low to high voltage. Assume the pull-up and pull-down networks never “pull” at the same time.
- Determine the worst case delay from high to low voltage.
- What could you do to equalize the worst case delays? (Hint adjust the W/L to adjust the resistance.)

 9.3 Review on Op-Amps


For the Op-Amp circuit to the right find V_{OUT1} and V_{OUT2} as a function of V_{IN1} . Be sure to show your fundamental assumptions. (Watch out this circuit may not be very useful.)



 9.4 Review on Three Terminal Devices

Use the EE42 Device Equations. $V_{DD} = 3V$ and $R = 60k\Omega$.

- Plot the I_{OUT} vs. V_{OUT} graph for the circuit external to the NMOS.
- Determine the NMOS current and voltage when $V_{IN} = 0, 1, 2$, and $3V$.
- Sketch a rough plot of V_{OUT} vs. V_{IN} from your data in b).



$$I_{OUT-SAT-n} = k'_n \left(\frac{W}{L} \right)_n (V_{IN} - V_{Tn}) V_{OUT-SAT-n}$$

$$I_{OUT-SAT-p} = k'_p \left(\frac{W}{L} \right)_p (V_{DD} - V_{IN} - |V_{Tp}|) V_{OUT-SAT-p}$$

| | $V_T(V)$ | $V_{OUT-SAT}(V)$ | $k'(\mu A/V^2)$ |
|------|----------|------------------|-----------------|
| NMOS | 0.43 | 0.63 | 100 |
| PMOS | 0.4 | 1 | 25 |

For a minimum sized device $W/L = 2$