

10/16/03

EE 42 – Introduction to Electronics for Computer Science

Fall 2003,
Dept. EECS, 510 Cory
UC Berkeley
Course Web Site

Prof. A. R. Neureuther
neureuth@eecs.berkeley.edu 642 - 4590
Office Hours M1, Tu, Th 10:30-11:30, F 11
[http://www - inst.eecs.berkeley.edu/~ee42/](http://www-inst.eecs.berkeley.edu/~ee42/)

Problem Set # 10

Due: 1 PM Nov 20th, 2003 in box outside 240 Cory


Announcement:

Reading Week #10: Review Schwarz and Oldham 11.2, 11.3, Class Handouts

Topics: Logic functions, Average Resistances.

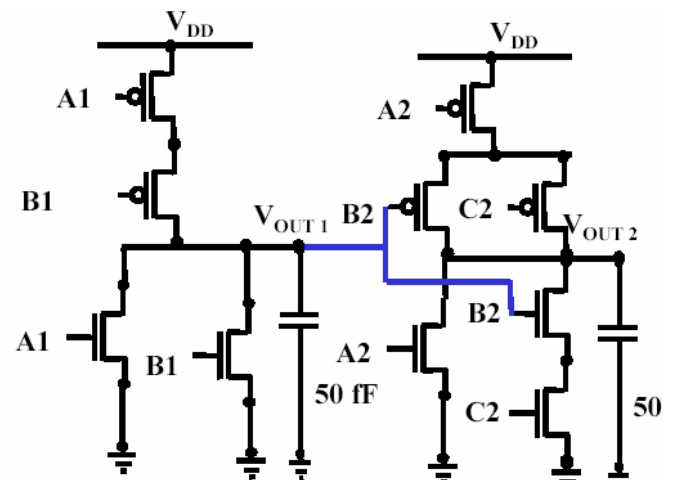10.1 Logic Functions Use the circuit to the right.


- Write the logic function for Vout1
- Write the logic function for Vout2
- What are the propagation delays of this circuit in terms of inverter delays?



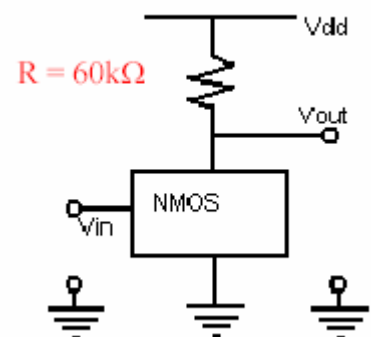10.2 Average Resistances Use the circuit to the right.

- Evaluate the equivalent resistance of the pull down network for Vdd=5V, Vth=1V, Vin=2V and Vout_sat=1V
- Evaluate the equivalent resistance for Vdd=3V, Vth=0.43V, Vin=2V and Vout_sat=0.63V

NMOS: $K'_n = 100 \mu\text{A}/\text{V}^2$ and $W/L = 2$



$$I_{OUT-SAT-n} = k'_n \left(\frac{W}{L} \right)_n (V_{IN} - V_{Tn}) V_{OUT-SAT-n}$$
$$I_{OUT-SAT-p} = k'_p \left(\frac{W}{L} \right)_p (V_{DD} - V_{IN} - |V_{Tp}|) V_{OUT-SAT-p}$$