UNIVERSITY OF CALIFORNIA, BERKELEY College of Engineering Department of Electrical Engineering and Computer Sciences

Last modified on October 14, 2003 by Eric Chung (e_chung@uclink.berkeley.edu)

Prof. Neureuther

EECS 42 Fall 2003

Homework	6	Solutions
----------	---	-----------

Problem 6.1. Logic and Truth Table from Circuit Symbols

a) Write algebraic expressions for the logic functions X and Y.

$$X = A + \overline{B}$$
$$Y = \overline{BC}$$

b) Combine these logic functions to find F.

F =	\overline{XY}
F =	$\overline{(A+\overline{B})\bullet(\overline{BC})}$

c) Truth Table

А	В	С	Х	Y	F
0	0	0	1	1	0
0	0	1	1	1	0
0	1	0	0	1	1
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	1	1	0
1	1	0	1	1	0
1	1	1	1	0	1

Problem 6.2. Synthesis via Sum of Products.

А	В	С	Х	Y	F
0	0	0	1	1	0
0	0	1	1	1	0
0	1	0	0	1	1
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	1	1	0
1	1	0	1	1	0
1	1	1	1	0	1

To apply the sum of products method for the variable F, we identify rows that have 1's in the F column. We continue by creating three product terms ABC and placing a NOT over each of the variables that have a corresponding zero in the column of the variable.

$$F = \overline{A}B\overline{C} + \overline{A}BC + ABC$$

Note: ABC is a single product term. A NOT is placed over any of the variables that have a corresponding zero in the truth table.

Problem 6.3. Synthesis of your own logic function.

Arbitrary logic function: F = AB + CD + E

a) Draw a circuit that realizes your sum of products form in NAND gates. To generate a circuit using only NAND gates, it helps to apply DeMorgan's law to function F.

 $F = \overline{\overline{AB + CD + E}} = \overline{\overline{AB} \bullet \overline{CD} \bullet \overline{E}}$

Note that this expression expresses all the terms using NAND functions The gate equivalent is shown below:



b) Apply a DeMorgan's law to convert the sum to a product $F = AB + CD + E = \overline{AB + CD + E} = \overline{\overline{AB \bullet CD \bullet E}}$

c) Apply the other DeMorgan's law to convert the initial products that still appear in b) to sums.

$$F = AB + CD + E = \overline{AB + CD + E} = \overline{AB} \bullet \overline{CD} \bullet \overline{E} = (\overline{A} + \overline{B}) \bullet (\overline{C} + \overline{D}) \bullet E$$

d) The NOR gate representation:



Any NOR or NAND gate with a signal tied to both of its inputs will produce the inverted input signal as its output.



