


Transistors/Transistors switches/DTL/TTL

Today: (13.3, 15.1, 15.2)

- Bipolar Transistor (nnp and pnp)
- Transistor switches
- DTL and TTL Logic Circuits

Semiconductors

 
- Materials - silicon crystal
- Electrical conduction in semiconductors can take place when negative charged electrons or positive charged holes (absent of electrons) move through the crystal.



- Material contain primarily free electrons is known as n-type semiconductor
- Material contain primarily holes is known as p-type semiconductor


Diodes

 - When p-type and n-type materials are placed in contact, the result structure is called pn junction.



- In p-type material, holes are the majority carriers, electrons are minority carriers.
- In n-type material, electron are the majority carriers, holes are minority carriers.
- Three phenomena: (1) one way conduction; (2) injection of minority carriers when forward biased; (3) collection of minority carriers when zero or reverse biased.


Forward Bias/Reverse Bias

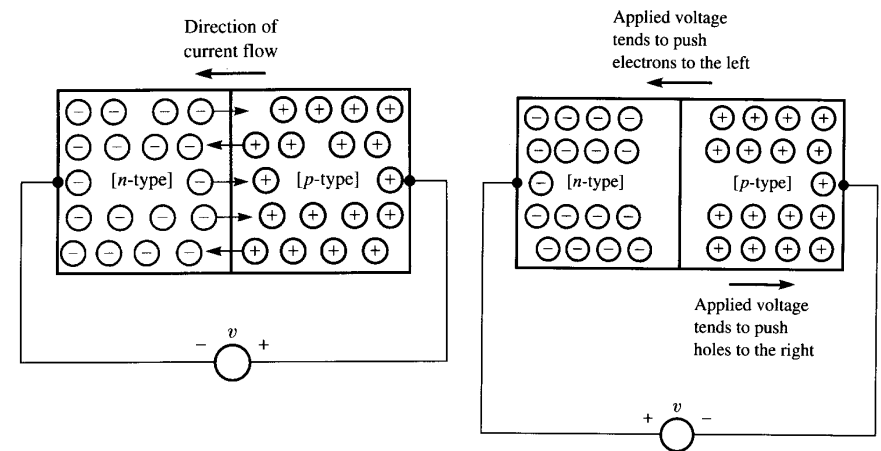

I-V characteristic of pn junction

- Ideal pn junction obeys the equation

$$i = I_s \left(e^{qv/kT} - 1 \right)$$

 

Where i and v are defined as shown in the diagram on the right q is the electronic charge, k is Boltzmann's constant

T is temperature in degree Kelvin kT/q has a dimension of voltage, V_{to} (thermal voltage) $=kT/q$ V_{to} (300K or room temperature) is 0.026V.



I_s is saturation current constant (but depends on the size of the junction, impurity concentration, and temperature)

I-V characteristic of pn junctions

$$i = I_s \left(e^{qv/kT} - 1 \right)$$



With $I_s = 10^{-13}A$

  Vertical scale: 1mA per large division
Horizontal scale: 1V per large division



Bipolar Transistor (nnp/pnp transistors)


Two pn junctions make a npn transistor

  

Forward bias

Reverse bias

Bipolar transistors (nnp)

 


$$i_1 \approx i_2, i_1 \gg i_3$$

Most emitter electrons flow into the collector (emitter current i_1 and collector current i_2 are approx. the same) and small amount flow out of the base as i_3 .

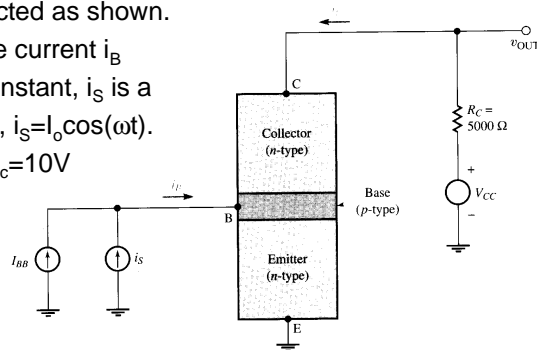Example

- A bipolar transistor is connected as shown. Assume i_C is related to the base current i_B according to $i_C = 100i_B$. I_{BB} is constant, i_S is a small time varying input current, $i_S = I_0 \cos(\omega t)$. Find v_{out} if $I_{BB} = 10\mu A$, $I_0 = 4\mu A$, $V_{CC} = 10V$



Based on Ohm's law:

$$v_{out} = V_{CC} - R_C i_C = V_{CC} - R_C (100i_B)$$


$$v_{out} = V_{CC} - R_C 100(I_{BB} + i_S)$$

$$v_{out} = V_{CC} - (5000)100(10 \times 10^{-6} + 4 \times 10^{-6} \cos \omega t)$$

$$v_{out} = 5 - 2 \cos(\omega t) V$$

Conventions & symbols

 The arrow indicates the direction of the current flow.




By KCL:

$$i_E + i_B + i_C = 0$$


By KVL:

$$V_{EB} + V_{BC} + V_{CE} = 0$$

 

Bipolar transistor in active mode

 
Active mode of transistor means emitter injects electrons into the base--base-emitter (pn junction) is forward biased.



V_{BE} must be sufficiently positive to make the sufficient current flow in the base-emitter junction.


Most electrons injected by the emitter are collected by the collector, the fraction are defined as α . $i_C = -\alpha i_E$

 (-ve sign because the actual i_E is going the opposite direction)



(npn transistor biased in active mode)

 The circuit showing a appropriate polarity for active mode operation.




Another relationship:

$$i_C = \beta i_B$$

$$\text{where } \beta = \frac{\alpha}{1 - \alpha}$$

 Typically, $\left\{ \begin{array}{l} \alpha \approx 1 \\ 50 < \beta < 1000 \end{array} \right\}$ (when transistors are in active mode)



(Continue)



In active mode, base-emitter junction acts like a forward biased pn junction

$$i_E = -I_{ES} \left(e^{qV_{BE}/kT} - 1 \right) \approx -I_{ES} \left(e^{qV_{BE}/kT} \right)$$

I_{ES} is a constant determined by the design of the transistor. -1 is dropped because at active mode, $\exp(qV/kT) \gg 1$.

Any small change in V_{BE} can lead to large change in i_E and i_C . (e.g. For active mode, V_{BE} is changed by 0.018V, i_E is doubled.

  Bias polarities for transistors operating in active modes






(polarity)

Parameters	npn	pnp
V_{CE}	positive	negative
V_{BE}	positive	negative
V_{CB}	positive	negative
i_E	negative	positive
i_B	positive	negative
i_C	positive	negative

Graphical Characteristics

   
- Common emitter connection (the emitter is common or connected to both the input and the output ports)



Output characteristic of a npn transistor in the common emitter configuration.¹⁵

Input characteristic of a npn silicon transistor in common emitter configuration.

Active, Saturation, Cutoff regions

 

Active region: $V_{CE} > 0.7V$, i_C is independent of V_{CE}
Cutoff region: $i_B = 0$, i_C is small.
Saturation region: Typically when V_{CE} is less than 0.7V. Low value of V_{CE} means that the collector base junction has lost its reverse bias -- the collector lost its ability to collect electrons, i_C becomes less than βi_B . (undesirable in amplifier, but useful in digital circuits)

Saturation region

- How saturation comes?
- Applies Ohm's law to the ckt as shown:


$$v_{CE} = v_{CC} - i_C R_C$$

In active mode, $i_C = \beta i_B$

$$v_{CE} = v_{CC} - \beta i_B R_C$$


As we increase i_B , V_{CE} decreases, eventually approach 0.7V. Collector junction lost its reverse bias and the transistor enter saturation mode. Any increase in i_B does not result in proportional increase in i_C ($i_C \neq \beta i_B$). V_{CE} decreases to a minimum value of approximately 0.2V.

 In Saturation mode: (1) $i_B > i_C/\beta$ (2) $V_{CE} = V_{CE}(\text{Sat}) \approx 0.2V$



 Example

Find the collector current of the transistor for the following 3 values of i_1 : 0, 5, and $20\mu A$, Assume the transistor is a "typical" transistor who's characteristic is given in Figure 13.29, 13.30.



Use graphical load-line method. Assume a imaginary break is made in the circuit as shown in the right.


From KVL: $v_C = V_2 - i_R R$

Solutions:


$V_C=5V, i_1=0\mu A, i_C=0mA$ (cutoff)

$V_C=2.5V, i_1=5\mu A, i_C=i_R, i_C=0.5mA$ (active region)

 $V_C=0.25V=V_{CE}, i_1=20\mu A, i_C=0.95mA$ (Saturation region)




Digital Circuits/Transistor Switches

 

Mode of transistor switch. The position of the switch is determined by whether V_{in} is "low" or "high".


For a inverter circuit, a "low" V_{in} will disconnect the switch. ($V_{out}=V_{CC}$)

 Assume high range is 4-5V. Low range is 0-0.5V. $V_{CC}=5V$



Bipolar transistor inverter

 Assume high range is 4-5V. Low range is 0-0.5V. $V_{CC}=5V$




Assume $R_B=1k\Omega$, with V_{IN} = low, results in an operating point where the load line meet the characteristic corresponding to $i_B=0$. (transistor in cutoff)


When V_{IN} = high, the base-emitter junction is forward biased.

$$i_B = \frac{V_{IN} - 0.7}{R_B}$$

 Assume $i_B = 1mA$, average high voltage is 4.5V $\Rightarrow R_B=3.8k\Omega$



(continue)

 

When V_{in} is low ($V_{in} < 0.5V$)
 $V_{CE} = \text{High (5V, transistor in cutoff)}$

When V_{in} is high ($4 < V_{in} < 5V$)
 $V_{CE} = \text{low (0.2V, transistor in saturation)}$

Notice V_{CE} is independent of i_B .
 Whether i_B equals $150\mu A$ or $1mA$
 still gives approximately $V_{CE} = 0.2V$

When the input to the inverter in "high", it is important that the base current be large enough to drive the transistor to saturation.

For saturation, $i_B > i_C/\beta$, $i_C = \frac{V_{CC} - V_{OUT}}{R_C}, V_{OUT} = V_{CE}$


(Continue)

$$i_B > \frac{i_C}{\beta} = \frac{V_{CC} - V_{CE}}{\beta R_C}$$

$$V_{CE} = V_{CE(SAT)}$$

$$i_B > \frac{i_C}{\beta} = \frac{V_{CC} - V_{CE(SAT)}}{\beta R_C}$$

 Multiple Stages Digital Circuits (loaded circuit)



Until now, we have been ignoring the current coming from the next stage. (no load effect until now)


In the circuit above, when V_{out} is "low", i_{out} will normally be positive. Since i_{out} is not zero, we need to take it into account in our load calculation. By KCL:

$$i_C = \frac{V_{CC} - V_{CE(SAT)}}{\beta R_C} + i_{OUT} \Rightarrow i_B > \frac{i_C}{\beta} = \frac{V_{CC} - V_{CE(SAT)}}{\beta R_C} + \frac{i_{OUT}}{\beta}$$

∴ Larger i_B must be supplied when load currents are expected.

DTL (Diode Transistor Logic Circuits)

NAND DTL circuit

 

To simplify the analysis, we will approx. the voltage of a forward biased pn junction to be 0.7V.

Since we don't know which diode is forward bias/reverse bias, let's start by guessing the result, then check for consistency.

Let v_A and $v_B = 0V$, D_A and D_B are forward biased $\Rightarrow V_X = 0.7V$

Since it takes V_X to be 2.1V to turns on D_1 , D_2 , and $T_1 \Rightarrow D_1, D_2$, and T_1 are cutoff $\Rightarrow i_B = 0. \Rightarrow V_{output} = V_{CC} = 5V$.

D_A, D_B on, D_1, D_2 , and T_1 off, consistency check out ok.

DTL NAND gate summary

Output corresponding to the various inputs for the DTL NAND gate.


v_A	v_B	v_X	Conduction?			v_F
			D_A	D_B	$D_1 D_2 T_1$	
0	0	0.7	Yes	Yes	No	5
0	0.3	0.7	Yes	No	No	5
0.2	4.5	0.9	Yes	No	No	5
4.8	4.1	2.1	No	No	Yes	0.2

NAND truth table

v_A	v_B	v_F
Low	Low	High
Low	High	High
High	Low	High
High	High	Low

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

 TTL (Transistor Transistor Logic Circuits)



2 inputs connect to high, 1 input to low.


TTL NAND gate (different cases)

Case 1: one or more input are "low", output is high.

E_1 is connected to low, E_2 and E_3 are connected to high.

Since E_1 is connected to low T_1 is on, $V_X = 0.7V$,

$$i_{B1} \cong (V_{CC} - 0.7) / R_1$$

 

Notice that i_{C1} is flowing into T_1 and flowing from the base of T_2 . This means T_2 (npn) is reverse biased. Since reverse bias current are small, $i_{B1} \gg i_{C1}/\beta \Rightarrow T_1$ is saturated $\Rightarrow V_{CE1} = V_{CE(SAT)} \cong 0.2V. \Rightarrow V_Y \cong 0.2V$ (T_2 and T_3 are performing the same function as D_1, D_2, T_1 in DTL) V_Y is smaller than 1.4V, the required voltage to activate T_2 and $T_3 \Rightarrow T_2$ and T_3 are turn off $\Rightarrow V_F = V_{CC}$.

\therefore one or more input are "low", output is high.

TTL NAND gate (different cases continue)


Case 2: All inputs are "high", output is low.

E_1, E_2 and E_3 are connected to high.

If T_1 were forward biased, $V_X = 0.7V + V_{CC}$ But V_X can not be higher than V_{CC} .

There is current flowing from V_{CC} thru R_1 into the base of T_1 (reverse biased) into the base of T_2 and T_3 .

 $V_X = 2.1V, V_Y = 1.4V, T_3$ is saturated (because the emitter of T_2 is driving the base of T_3) $\Rightarrow V_{out} = \text{low}$.



Summary

- Fundamental circuit of digital logic is the transistor switch, or inverter.
- Saturating bipolar transistor switches are used in diode-transistor logic (DTL) and transistor-transistor logic (TTL). The transistor acts as a switch that connects or disconnects the collector and the emitter. The switch is closed when sufficient base current is applied to saturate the transistor.
- Sufficient base current must be applied to BJT inverters to guarantee saturation under all load conditions.
- Logic family in different forms known as logic families.
- Blocks in the same family are compatible and can be interconnected.
- The TTL family and CMOS/BiCMOS family are the frequent used logic families.