


Review of charging and discharging in RC Circuits (an enlightened approach)

- *Before* we continue with formal circuit analysis - lets review RC circuits
- Rationale: Every node in a circuit has capacitance to ground, like it or not, and it's the charging of these capacitances that limits real circuit performance (speed)


Relevance to digital circuits:

We communicate with pulses

We send beautiful pulses out

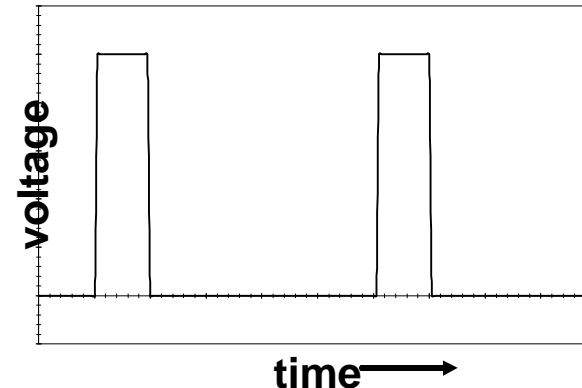

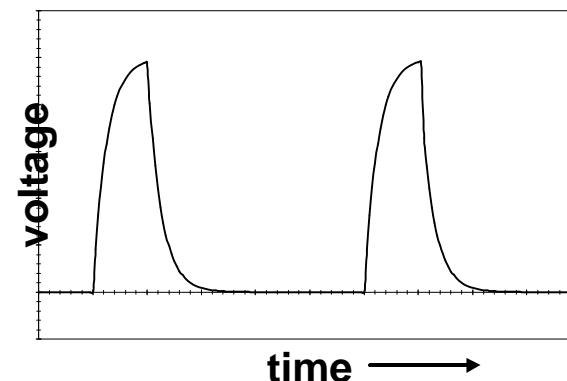But we receive lousy-looking pulses
and must restore them




RC charging effects are responsible So lets review them.

Simplification for time behavior of RC Circuits

- Before any input change occurs we have a dc circuit problem (that is we can use dc circuit analysis to relate the output to the input).
- Long after the input change occurs things “settle down” Nothing is changing So again we have a dc circuit problem.


We call the time period during which the output changes the *transient*

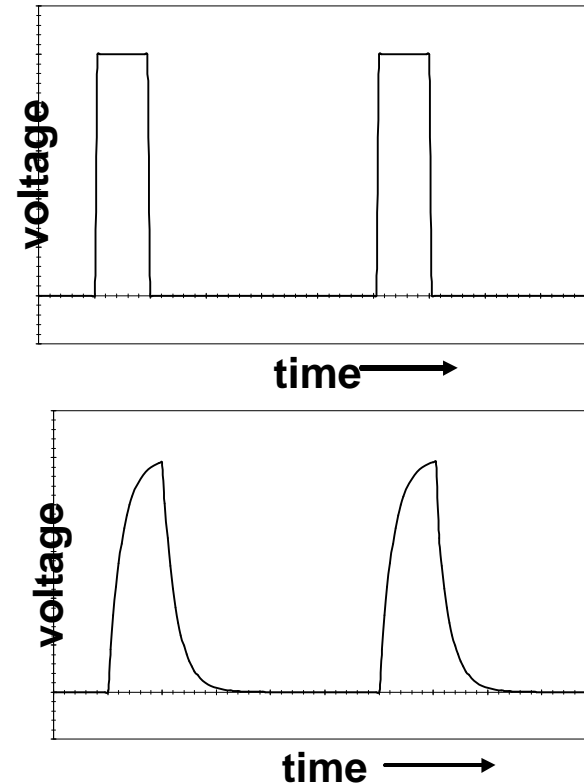We can predict a lot about the transient behavior from the pre- and post-transient dc solutions



What environment do pulses face?

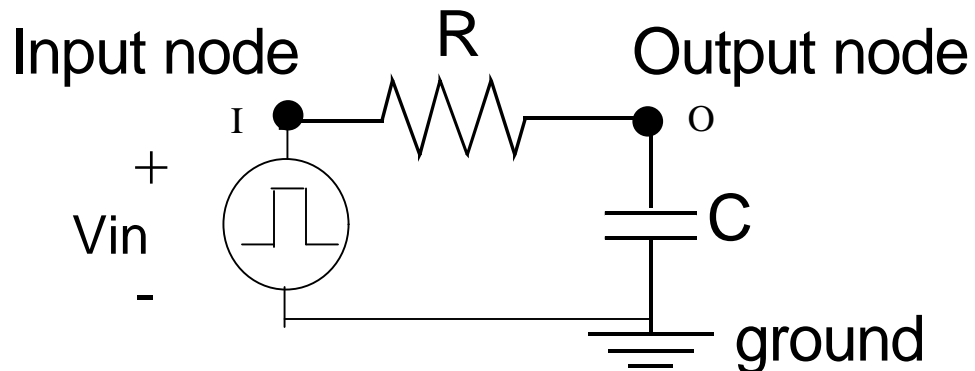- Every wire in a circuit has resistance.
- Every junction (called *nodes*) has capacitance to ground and other nodes.
- The active circuit elements (transistors) add additional resistance in series with the wires, and additional capacitance in parallel with the node capacitance.




A pulse originating at **node I** will arrive delayed and distorted at **node O** because it takes time to charge C through R

If we focus on the circuit which distorts the pulses produced by V_{in} , it consists simply of R and C . (V_{in} is just the time-varying source which produces the input pulse.)

The RC Circuit to Study


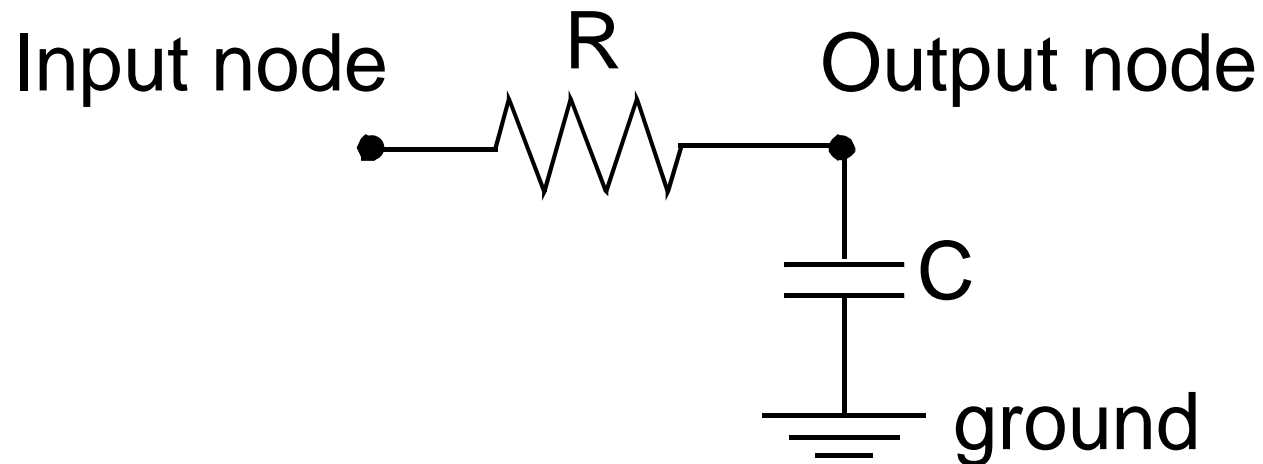
(All single-capacitor circuits reduce to this one)



- R represents total resistance (wire plus whatever drives the input node)
- C represents the total capacitance from node to the outside world (from devices, nearby wires, ground etc)

RC RESPONSE

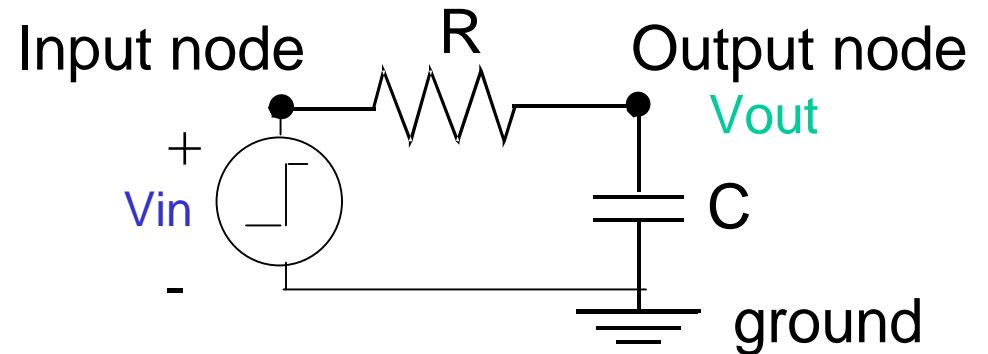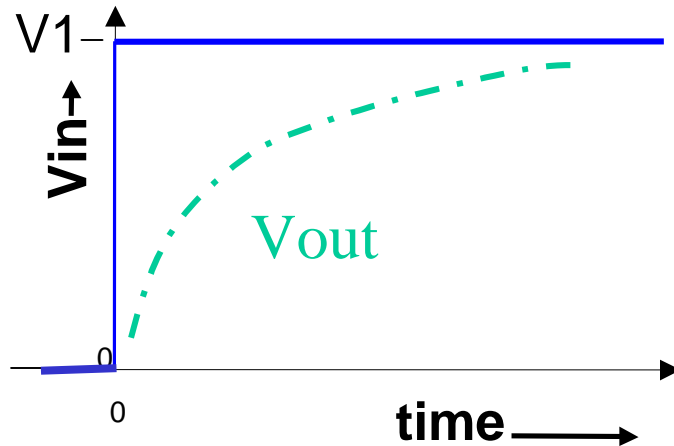Case 1 – Rising voltage. Capacitor uncharged: Apply + voltage step



- V_{in} “jumps” at $t=0$, but V_{out} cannot “jump” like V_{in} . Why not?



☞ Because an instantaneous change in a capacitor voltage would require instantaneous increase in energy stored ($\frac{1}{2}CV^2$), that is, infinite power. (Mathematically, V must be differentiable: $I=CdV/dt$)

V does not “jump” at $t=0$, i.e. $V(t=0^+) = V(t=0^-)$

Therefore the dc solution before the transient tells us the capacitor voltage at the beginning of the transient.

RC RESPONSE

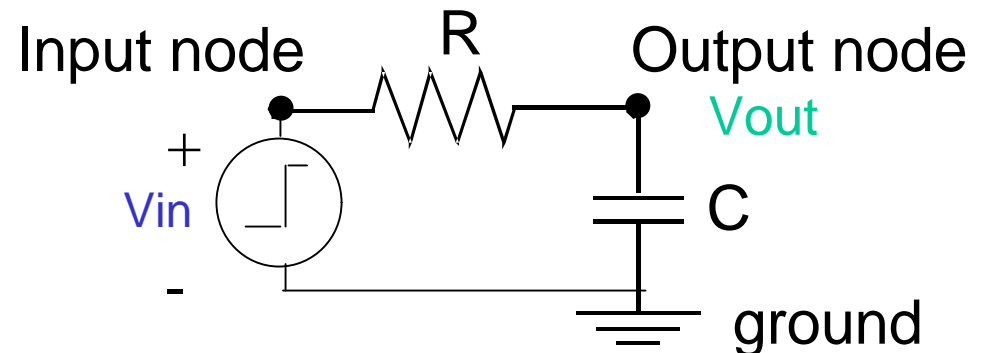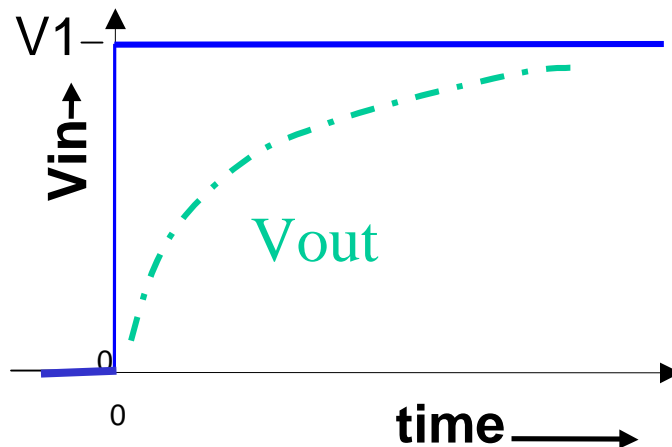Case 1 – Capacitor uncharged: Apply voltage step



- V_{out} approaches its final value asymptotically (It never quite gets to V_1 , but it gets arbitrarily close). Why?



After the transient is over (nothing changing anymore) it means $d(V)/dt = 0$; that is all currents must be zero. From Ohm's law, the voltage across R must be zero, i.e. $V_{in} = V_{out}$.

☞ That is, $V_{out} \rightarrow V_1$ as $t \rightarrow \infty$. (Asymptotic behavior)

Again the dc solution (after the transient) tells us (the asymptotic limit of) the capacitor voltage during the transient.

RC RESPONSE

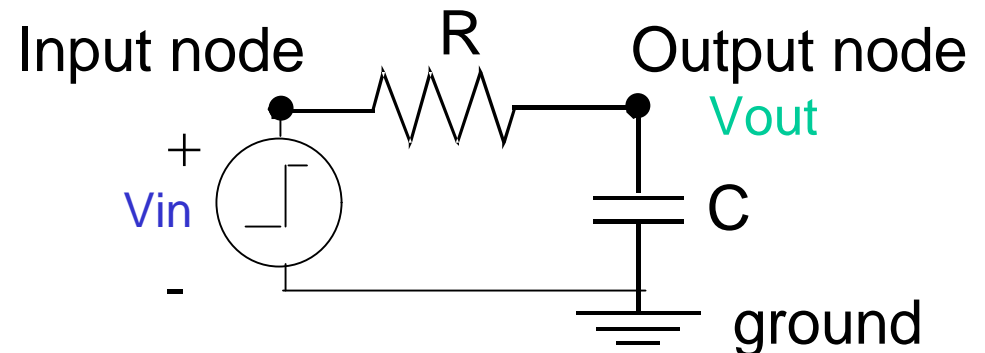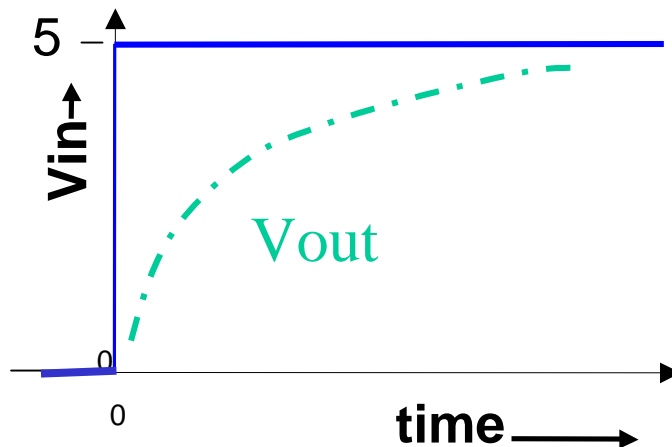
Example – Capacitor uncharged: Apply voltage step of 5 V




- Clearly V_{out} starts out at 0V (at $t = 0^+$) and approaches 5V.
- We know this because of the pre-transient dc solution ($V=0$) and post-transient dc solution ($V=5V$).

So we know a lot about V_{out} during the transient - namely its initial value, its final value , *and we know the general shape* .

RC RESPONSE: Case 1 (cont.)


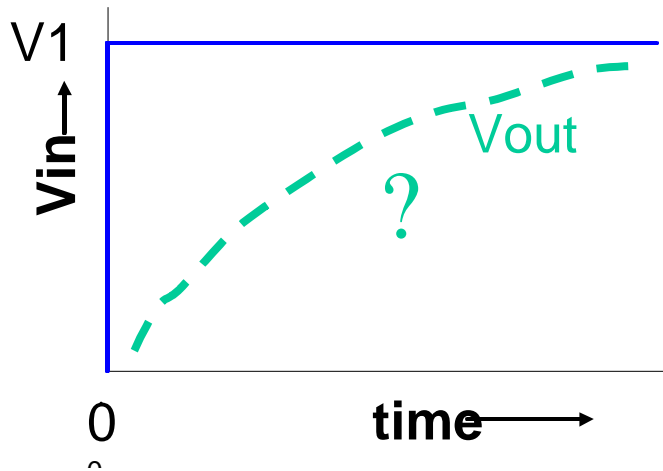


Exact form of V_{out} ?

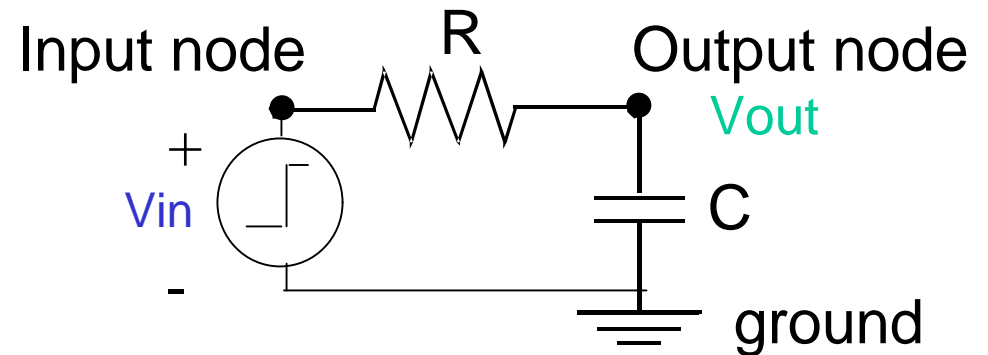

Equation for V_{out} : Do you remember general form?

$$V_{out} = V_1(1 - e^{-t/\tau})$$

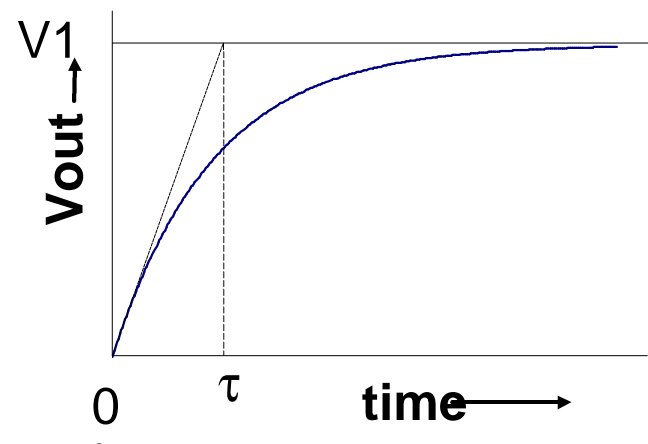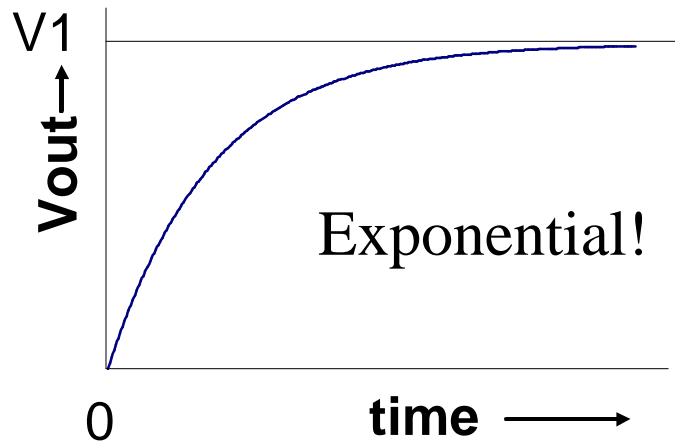


Review of simple exponentials.

Rising Exponential from Zero

$$V_{\text{out}} = V_1(1 - e^{-t/\tau})$$

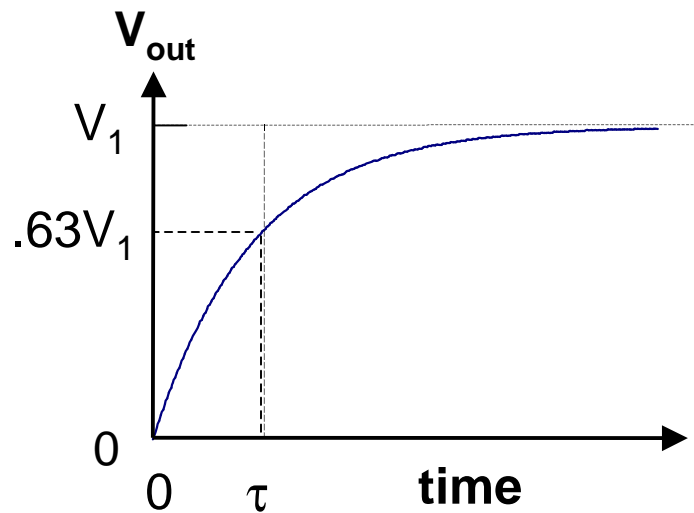
at $t = 0$, $V_{\text{out}} = 0$, and
at $t \rightarrow \infty$, $V_{\text{out}} \rightarrow V_1$ also
at $t = \tau$, $V_{\text{out}} = 0.63 V_1$



Falling Exponential to Zero

$$V_{\text{out}} = V_1 e^{-t/\tau}$$

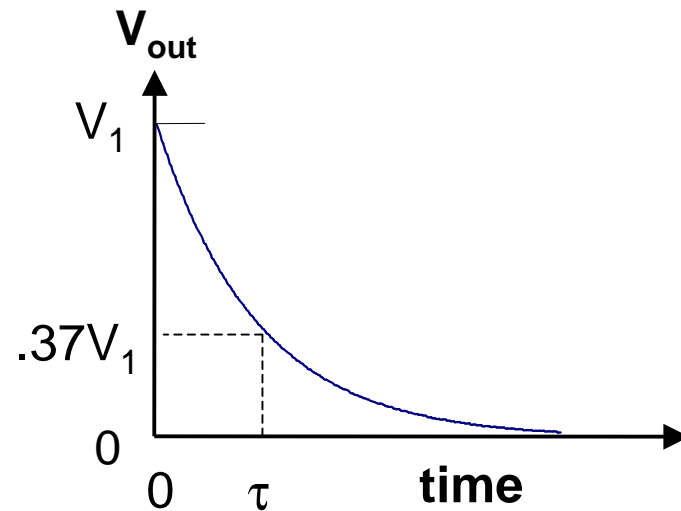at $t = 0$, $V_{\text{out}} = V_1$, and
at $t \rightarrow \infty$, $V_{\text{out}} \rightarrow 0$, also
at $t = \tau$, $V_{\text{out}} = 0.37 V_1$




Further Review of simple exponentials.

Rising Exponential from Zero

$$V_{\text{out}} = V_1(1 - e^{-t/\tau})$$

We can add a constant (positive or negative)

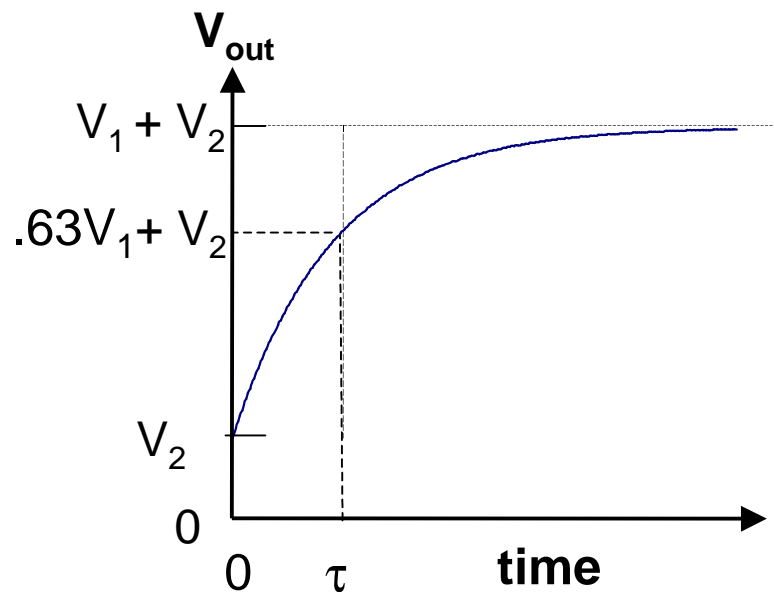
$$V_{\text{out}} = V_1(1 - e^{-t/\tau}) + V_2$$



Falling Exponential to Zero

$$V_{\text{out}} = V_1 e^{-t/\tau}$$
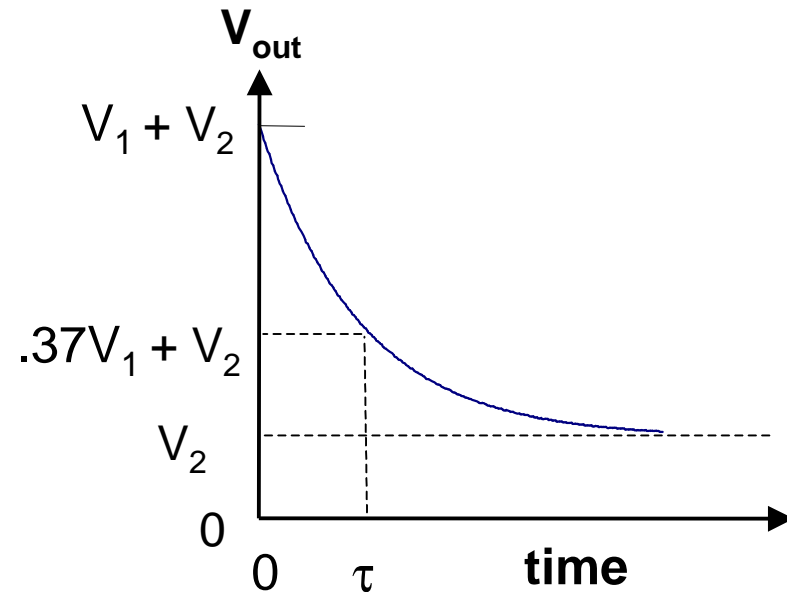
$$V_{\text{out}} = V_1 e^{-t/\tau} + V_2$$



Further Review of simple exponentials.

Rising Exponential

$$V_{\text{out}} = V_1(1 - e^{-t/\tau}) + V_2$$



Falling Exponential

$$V_{\text{out}} = V_1 e^{-t/\tau} + V_2$$


Both equations can be written in one simple form: $V_{\text{out}} = A + B e^{-t/\tau}$

Initial value ($t=0$): $V_{\text{out}} = A + B$. Final value ($t \gg \tau$): $V_{\text{out}} = A$

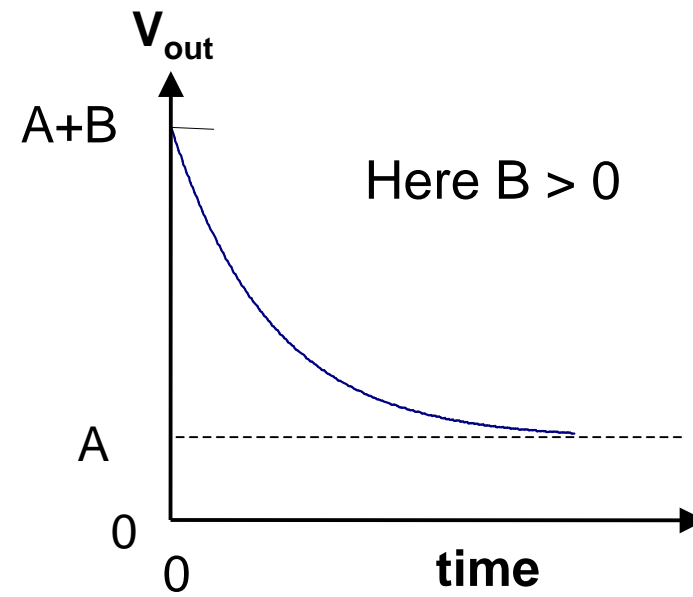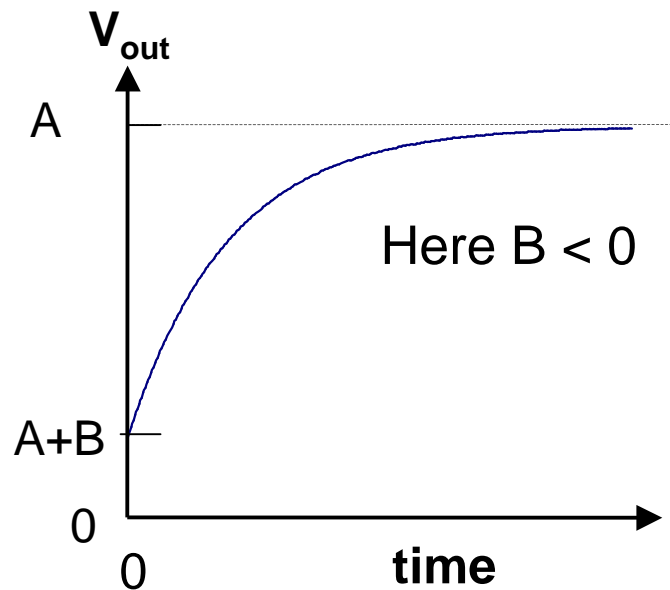Thus: if $B < 0$, rising exponential; if $B > 0$, falling exponential



RC RESPONSE: Case 1 (Rising exponential)

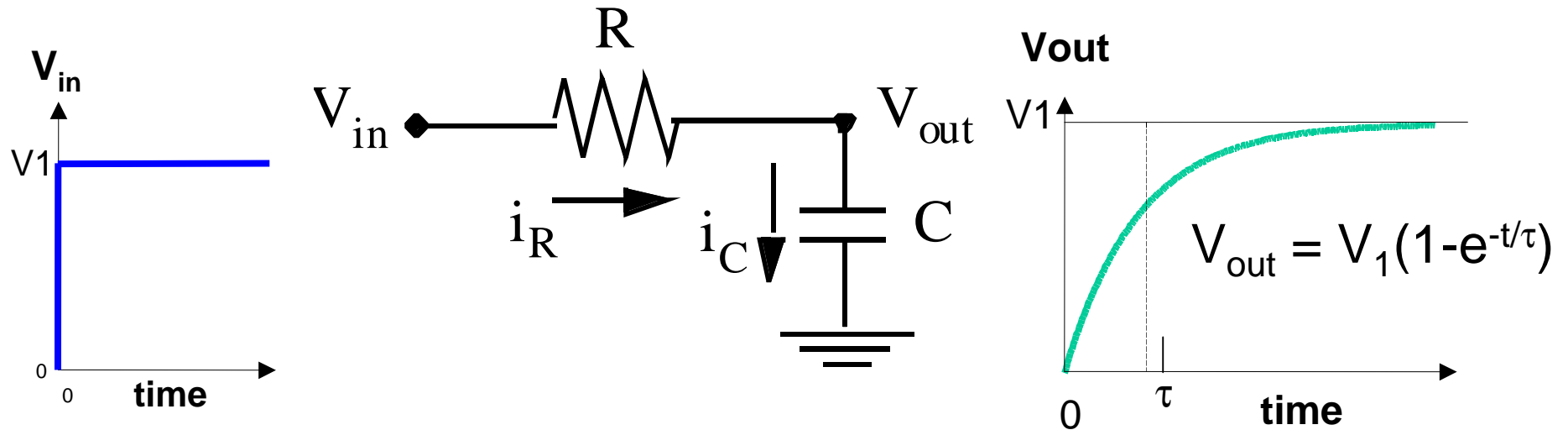

- How is τ related to R and C ?
 - If C is bigger, it takes longer ($\tau \uparrow$).
 - If R is bigger, it takes longer ($\tau \uparrow$).


~~✍~~ Thus, τ is proportional to RC .

☞ In fact, $\tau = RC$!

~~✍~~ Thus, $V_{out} = V_1(1 - e^{-t/\tau})$

RC RESPONSE: Case 1 (cont.)

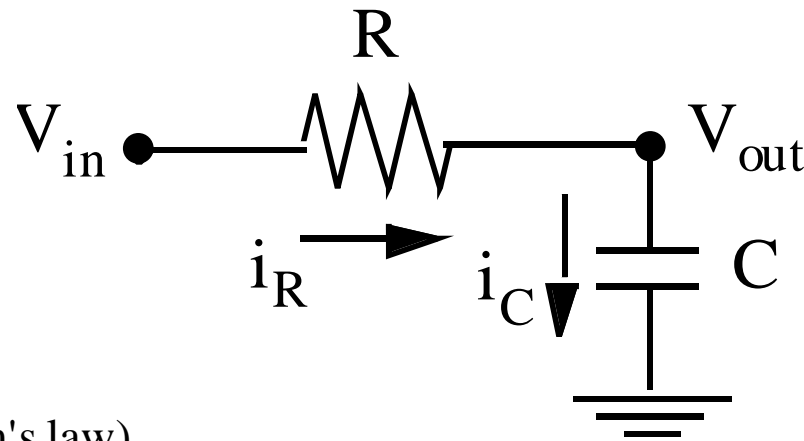Proof that $V_{\text{out}} = V_1(1 - e^{-t/RC})$



$$i_R = \frac{V_{\text{in}} - V_{\text{out}}}{R} \text{ (Ohm's law)}$$

$$i_C = C \frac{dV_{\text{out}}}{dt} \text{ (capacitance law)}$$

But $i_R = i_C$!

$$\text{Thus, } \frac{V_{\text{in}} - V_{\text{out}}}{R} = C \frac{dV_{\text{out}}}{dt}$$

or

$$\frac{dV_{\text{out}}}{dt} = \frac{1}{RC} (V_{\text{in}} - V_{\text{out}})$$

RC RESPONSE Case 1 (cont.)

Proof that $V_{\text{out}} = V_1(1 - e^{-t/RC})$

We have: $\frac{dV_{\text{out}}}{dt} = \frac{1}{RC}(V_{\text{in}} - V_{\text{out}})$

But $V_{\text{in}} = V_1 = \text{constant}$

and $V_{\text{out}} = 0$ at $t = 0^+$

I claim that the solution to this first-order linear differential equation is:

$$V_{\text{out}} = V_1(1 - e^{-t/RC})$$

Proof by substitution:

$$\frac{dV_{\text{out}}}{dt} \stackrel{?}{=} \frac{1}{RC}(V_{\text{in}} - V_{\text{out}})$$

↓

$$\cancel{\frac{V_1}{RC}} e^{-t/RC} \stackrel{?}{=} \frac{1}{RC}(V_1 \cancel{+} V_1(1 \cancel{-} e^{-t/RC}))$$

clearly


$$\frac{V_1}{RC} e^{-t/RC} = \frac{V_1}{RC} e^{-t/RC}$$

and

$$V_{\text{out}} = 0 \text{ at } t = 0^+ \quad \text{OK}$$

RC RESPONSE (cont.)

Generalization

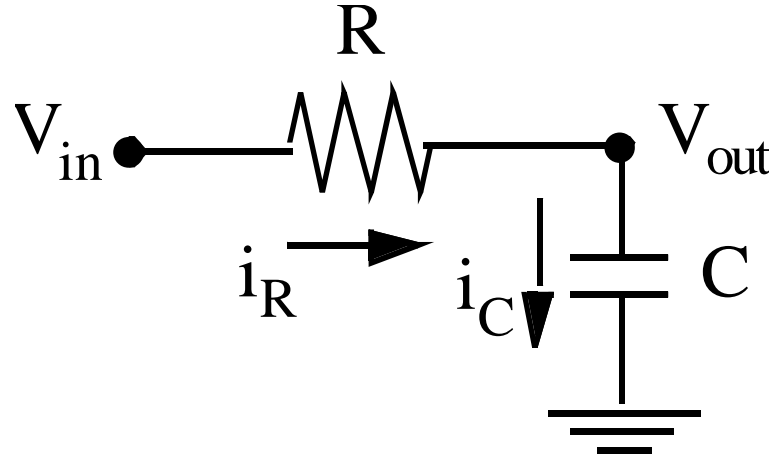

V_{in} switches at $t = 0$; then for any time interval $t > 0$, in which V_{in} is a constant, V_{out} is ***always*** of the form:

$$V_{out} = A + Be^{-t/\tau}$$

We determine A and B from the initial voltage on C , and the value of V_{in} . Assume V_{in} “switches” at $t=0$ from V_{co} to V_1 :

First, at $t = 0$ $V_C \equiv V_{co}$ initial voltage

➡ Thus, $A + B = V_{co}$

as $t \rightarrow \infty$, $V_C \rightarrow V_1$

➡ Thus, $A = V_1 \Rightarrow B = V_{co} - V_1$