



# EECS 42 – Introduction to Electronics for Computer Science

Spring 2003  
 Dept. EECS,  
 UC Berkeley  
 Course Web Site <http://www-inst.EECS.Berkeley.EDU/~ee42/>

Prof. A. R. Neureuther  
 510 Cory 642-4590  
 OH M, Tu, W, (Th), F 11

## Midterm #1 March 5th, 2003

**Closed Book, Closed Notes**  
**Write on the Exam paper**


Print Your Name: \_\_\_\_\_

Sign Your Name: \_\_\_\_\_

Show your work so that the method as well as the answer can be graded for correctness and completeness. Correct answers alone are only worth 70% of full credit.

Problem	Possible	Score
I	28	
II	22	
III	25	
IV	25	
<b>Total</b>	<b>100</b>	

### I (28 Points) Basic Circuit Analysis

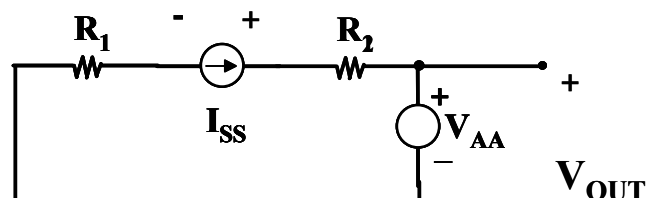

$$V_{AA} = 2V \quad I_{SS} = 1 \text{ mA}$$

$$R_1 = 1k\Omega \quad R_2 = 2k\Omega \quad R_3 = 3k\Omega$$

a) (7 points) Find  $R_{TH}$ .



b) (7 points) Find  $V_{OC}$ .

c) (7 points) Find the power delivered to the circuit by  $V_{AA}$ .

d) (7 points) Find the voltage on the current source  $I_{SS}$  in the direction shown on the diagram.
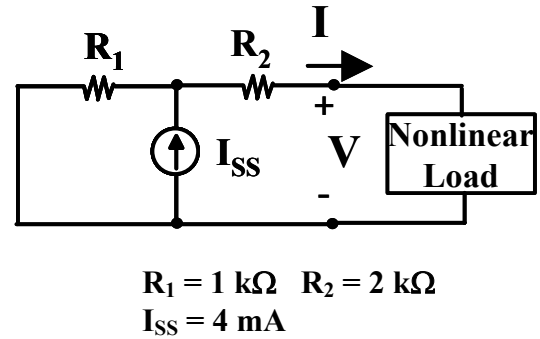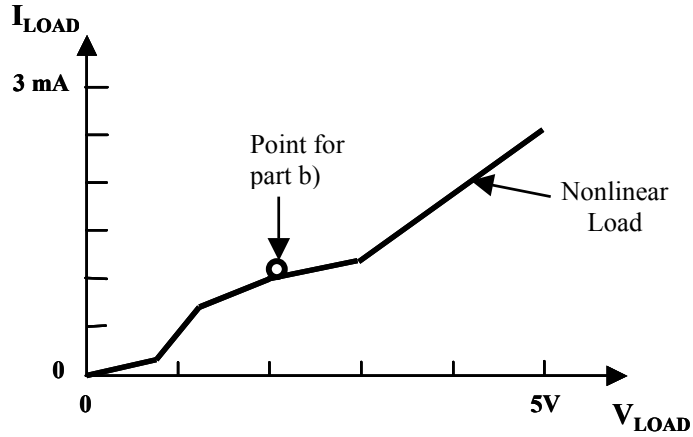
## II (22 Points) Load Lines

A linear circuit is connected to a nonlinear load.




- a) (12 points) Find the combination of current  $I$  and voltage  $V$  that satisfies both the circuit and the load.

- b) (10 points) Adjust  $R_2$  so that the solution passes through the point indicated on the device curve.

### III (25 Points) Transient

The switch in the circuit closes at  $t = 0$ . Just before switching the capacitor is charged to 2V.

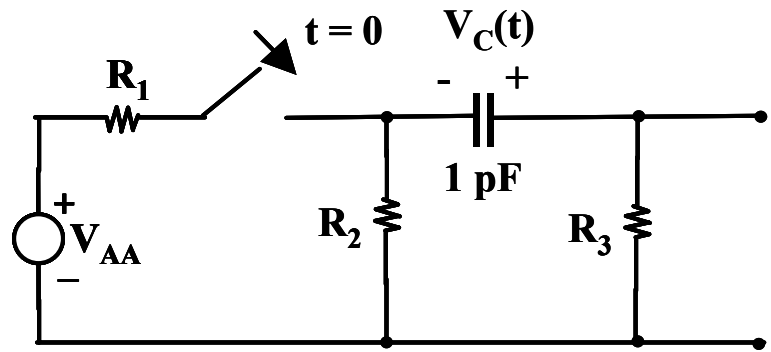
a) (18 points) Find the voltage on the capacitor  $V_C(t)$  for  $t > 0$ .



$$R_1 = 1\text{k}\Omega \quad R_2 = 2\text{k}\Omega \quad R_3 = 3\text{k}\Omega \\ V_{AA} = 5\text{V}$$

b) (7 points) Find  $dV_C(t)/dt$  just prior to the switch closing at  $t = 0$ .

### IV (25 Points) Node Equations

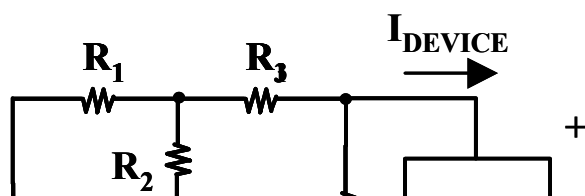

a) (15 points) Assign labels to the nodes and write a complete set of node equations for determining the node voltages. (These equations should contain only the node voltages themselves, resistances, source strengths and the device current.)

$$\mathbf{R_1 = 1k\Omega \quad R_2 = 2 k\Omega \quad R_3 = 3 k\Omega \quad R_3 = 3 k\Omega}$$
$$\mathbf{V_{AA} = 5 V \quad I_{SS} = 1 mA}$$

b) (10 points) Use **one** of your node equations from above to find the voltage on  $I_{SS}$  when the voltage on the device is 2V. (Hint: Substitute the device voltage to break the equations apart to avoid excessive algebra).