



EECS 42 – Introduction to Electronics for Computer Science

Spring 2003
Dept. EECS,
UC Berkeley
Course Web Site <http://www-inst.EECS.Berkeley.EDU/~ee42/>

Prof. A. R. Neureuther
510 Cory 642-4590
OH M, Tu, W, (Th), F 11

Midterm #2 April 16th, 2003

Closed Book, Closed Notes
Device Equations on Device Problem
Write on the Exam paper


Print Your Name: _____

Sign Your Name: _____

Show your work so that the method as well as the answer can be graded for correctness and completeness. Correct answers alone are only worth 70% of full credit.

Problem	Possible	Score
I	30	
II	35	
III	35	
Total	100	


I (30 Points) Logic and Timing Diagrams

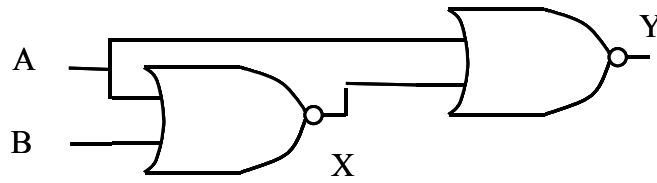


a) (12 points) Complete the truth table.

A	B	X	Y
0	0		
1	0		
0	1		
1	1		

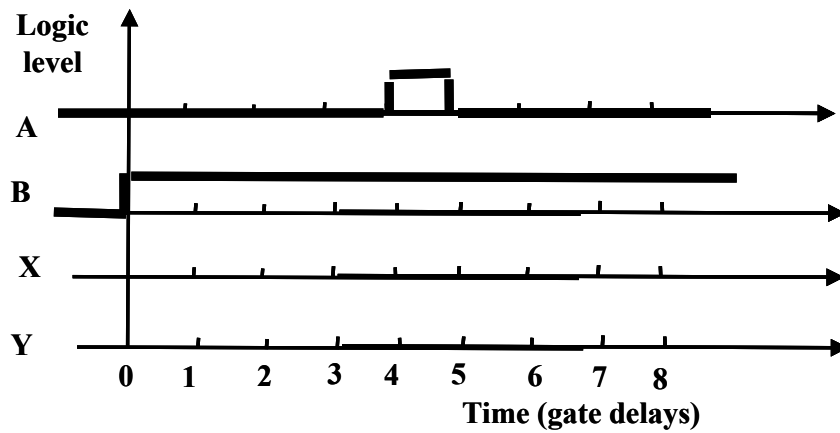b) (18 points) Complete the timing diagram for all eight gate delays.



II (35 Points) Dependent Sources

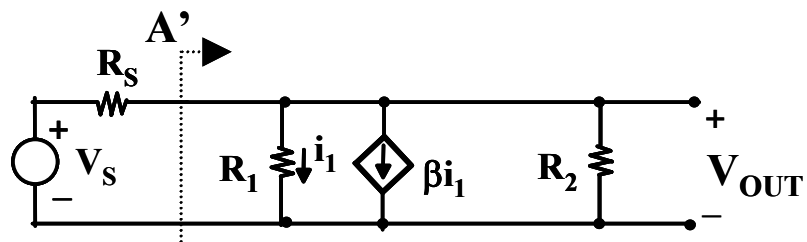

a) (15 points) Find V_{OUT} in terms of V_S , the resistors and the dependent source strength β .

b) (12 points) Find the resistance seen looking to the right of AA' in terms of the resistors and the dependent source strength β .

c) (8 points) Does increasing β raise or lower the resistance in part b)? Give a brief intuitive explanation of how this occurs.

III (35 Points) Logic Circuit with a EE42 Device

$$I_{OUT-SAT-D} = k_D (V_{IN} - V_{TD}) V_{OUT-SAT-D}$$

Values for this Exam

$$k_D = 40 \mu\text{A/V}^2$$

$$k_U = 30 \mu\text{A/V}^2$$

$$V_{TD} = 2\text{V}$$

$$V_{TU} = 1.5\text{V}$$


$$V_{OUT-SAT-D} = 0.5\text{V}$$

$$V_{OUT-SAT-U} = 1.5\text{V}$$

$$I_{OUT-SAT-U} = k_U (V_{DD} - V_{IN} - V_{TU}) V_{OUT-SAT-U}$$

↖ When in circuit attached to VDD.

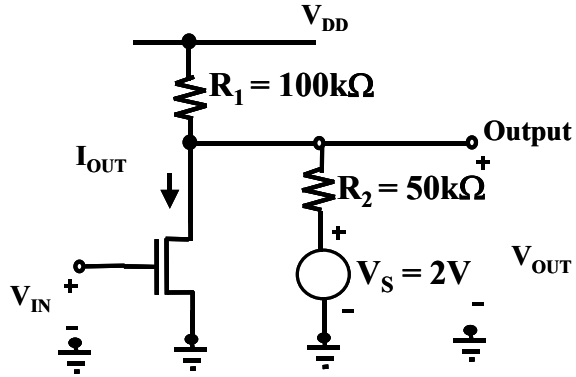a) (12 points) Remove the EE42 pull-down device from this circuit and consider the remaining circuit. Find the **open circuit voltage** and **short circuit current** that is seen looking out from the position of the pull-down EE42 device into the remaining circuit.



b) (11 points) Now consider the EE 42 device alone with the parameter values given. If V_{IN} is limited to a range of 0 to 5V and V_{OUT} is limited to a range of 0 to 5V, what will be the maximum current?

c) (12 points) Now consider the EE 42 device and circuit connected together. Find V_{OUT} when $V_{IN} = 3V$. You may use either a graphical or an algebraic method.

