



EECS 42 – Introduction to Electronics for Computer Science

Spring 2003
Dept. EECS,
UC Berkeley
Course Web Site <http://www-inst.EECS.Berkeley.EDU/~ee42/>

Prof. A. R. Neureuther
510 Cory 642-4590
OH M, Tu, W, (Th), F 11

Midterm #2 April 16th, 2003

Closed Book, Closed Notes
Device Equations on Device Problem
Write on the Exam paper


Print Your Name:_____Solution_____

Sign Your Name:_____

Show your work so that the method as well as the answer can be graded for correctness and completeness. Correct answers alone are only worth 70% of full credit.

Problem	Possible	Score
I	30	
II	35	
III	35	
Total	100	

I (30 Points) Logic and Timing Diagrams


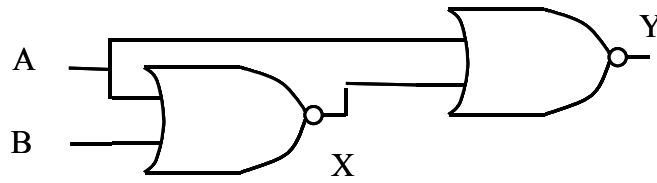


a) (12 points) Complete the truth table.


A	B	X	Y
0	0		
1	0		
0	1		
1	1		

A	B	X	Y
0	0	1	0
1	0	0	0
0	1	0	1
1	1	0	0

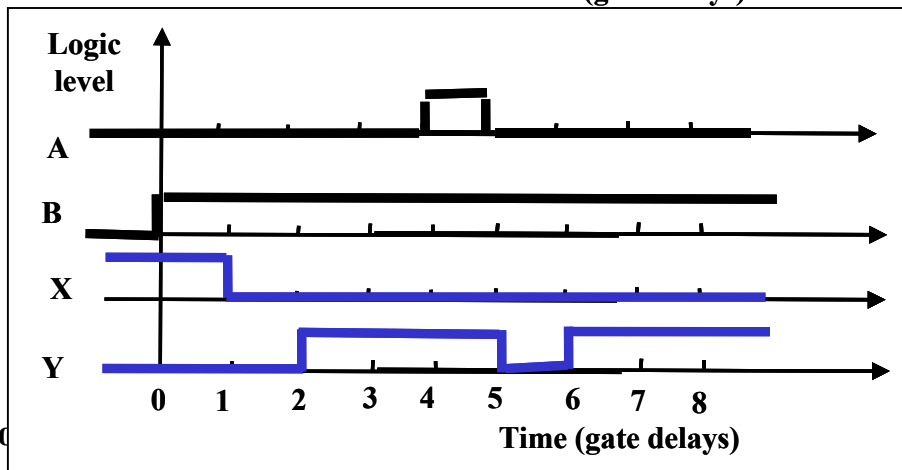 b) (18 points) Complete the timing diagram for all eight gate delays.



II (35 Po

 

a) (15 points) Find V_{OUT} in terms of V_S , the resistors and the dependent source strength β .

$$i_b = V_{OUT} / R_1$$

$$\beta i_b = \beta V_{OUT} / R_1$$

$$V_{OUT} \left(\frac{1}{R_1} + \beta \frac{1}{R_1} + \frac{1}{R_2} \right) + \frac{(V_{OUT} - V_S)}{R_S} = 0$$

$$V_{OUT} = V_S \frac{\frac{1}{R_S}}{\left(\frac{1}{R_1} + \beta \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_S} \right)}$$

b) (12 points) Find the resistance seen looking to the right of AA' in terms of the resistors and the dependent source strength β .

Apply v_{TEST} to the input then find i_{TEST}

$$i_{TEST} = \frac{V_{TEST}}{R_1} + \beta \frac{V_{TEST}}{R_1} + \frac{V_{TEST}}{R_2} = V_{TEST} \left(\frac{\beta+1}{R_1} + \frac{1}{R_2} \right)$$

$$\frac{V_{TEST}}{I_{TEST}} = \frac{1}{\left(\frac{\beta+1}{R_1} + \frac{1}{R_2} \right)} = \left(\frac{R_1}{\beta+1} \right) \parallel R_2$$

c) (8 points) Does increasing β raise or lower the resistance in part b)? Give a brief intuitive explanation of how this occurs.

Raising β reduces the resistance as whatever current that flows into R1 is always matched by a β times larger current through the dependent source. This same current is exactly the same current that would flow through resistor R1 if it were $(\beta+1)$ times smaller. (This reduction is diluted somewhat by R2 being in parallel.)

III (35 Points) Logic Circuit with a EE42 Device

$$I_{OUT-SAT-D} = k_D (V_{IN} - V_{TD}) V_{OUT-SAT-D}$$

Values for this Exam

$$k_D = 40 \mu A/V^2$$

$$k_U = 30 \mu A/V^2$$

$$V_{TD} = 2V$$

$$V_{TU} = 1.5V$$


$$V_{OUT-SAT-D} = 0.5V$$

$$V_{OUT-SAT-U} = 1.5V$$

$$I_{OUT-SAT-U} = k_U (V_{DD} - V_{IN} - V_{TU}) V_{OUT-SAT-U}$$

↙ When in circuit attached to VDD.

 a) (12 points) Remove the EE42 pull-down device from this circuit and consider the remaining circuit. Find the **open circuit voltage** and **short circuit current** that is seen looking out from the position of the pull-down EE42 device into the remaining circuit.



$$V_{OC} = 2V + (5V - 2V) \frac{R_2}{R_1 + R_2} = 2V + 3V \frac{50k\Omega}{100k\Omega + 50k\Omega} = 3V$$


$$I_{SC_Downward} = \frac{5V}{100k\Omega} + \frac{2V}{50k\Omega} = 50\mu A + 40\mu A = 90\mu A$$

b) (11 points) Now consider the EE 42 device alone with the parameter values given. If V_{IN} is limited to a range of 0 to 5V and V_{OUT} is limited to a range of 0 to 5V, what will be the maximum current?

Highest is when $V_{IN} = 5V$ and $V_{OUT} = 5V$

$$I = (40\mu A / V^2) (5V - 2V)(0.5V) = 60\mu A$$

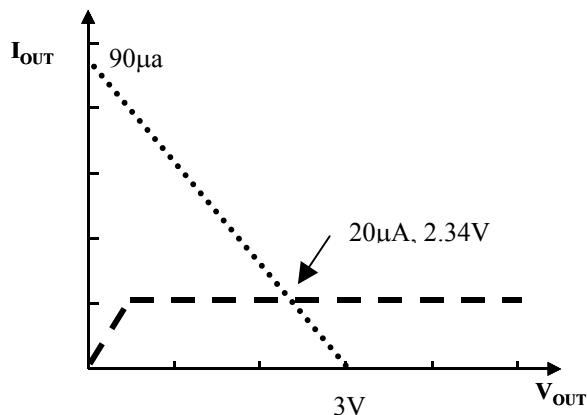c) (12 points) Now consider the EE 42 device and circuit connected together. Find V_{OUT} when $V_{IN} = 3V$. You may use either a graphical or an algebraic method.



For $V_{IN} = 3V$, $I_{SAT} = 40(3V - 2V)(0.5V) = 20\mu A$
KCL at the putput node gives

$$20\mu A = \frac{5V - V_{OUT}}{100k\Omega} + \frac{2V - V_{OUT}}{50k\Omega}$$

$$V_{OUT} = 70\mu A \frac{50k\Omega \cdot 100k\Omega}{50k\Omega + 100k\Omega} = 2.34V$$