



EECS 42 – Introduction to Electronics for Computer Science

Spring 2003,
Dept. EECS,
UC Berkeley
Course Web Site <http://www-inst.EECS.Berkeley.EDU/~ee42/>


Prof. A. R. Neureuther
510 Cory 642-4590
OH M, Tu, W, (Th), F 11

Quiz #2 April 9th, 2003


Show your work so that the method can be graded for correctness and completeness and all of the points do not depend on just the final numerical value.

I (25 Points) Logic Circuit

- a) Find a sum of products form for F.

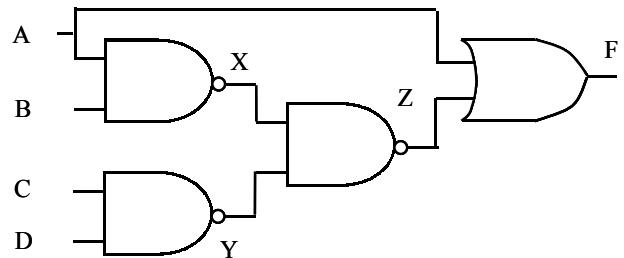

- b) Complete the timing diagram.

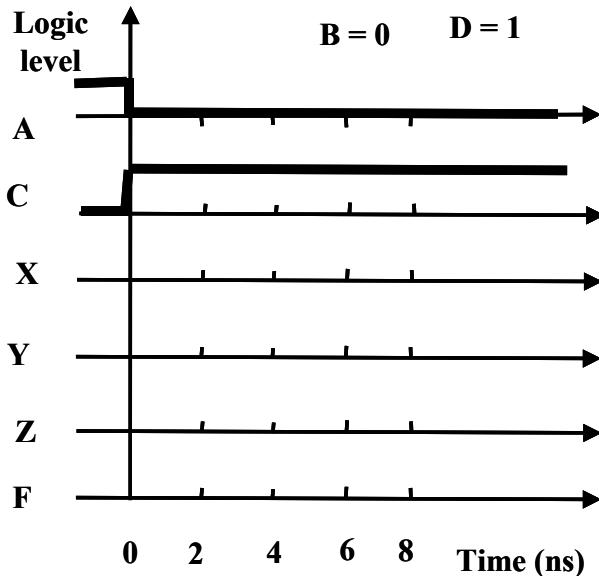

II (15 Points) Dependent Sources

Find the resistance seen looking into AA'.

