



● ● ● | Lecture 13

Today we will


- Examine how the logic gate model (RC circuit) reacts to a sequence of input changes
- Relate these results to clocking speed
- Define propagation delay
- Introduce digital logic gates
- Examine how signals propagate through logic circuits

● ● ● | Sequential Switching

  - What if we step up the input to a logic circuit,
- wait for the output to respond,
- then bring the input back down to perform the next computation?





Pulse Distortion

 



We need to wait for the output to reach a recognizable logic level, before changing the input again.

This affects clock speed.

  

  Example

- Suppose that the capacitor is discharged at $t=0$.
- With $V_{in}(t)$ as shown, find $V_{out}(t)$.



● ● ● | Example

- First, $V_{\text{out}}(t)$ will approach 4 V exponentially.
- We write the equation for this part using:
 - Initial condition $V_{\text{out}}(0) = 0 \text{ V}$
 - Final value $V_{\text{out},f} = 4 \text{ V}$
 - Time constant $RC = (2.5 \text{ k}\Omega)(1 \text{ nF}) = 2.5 \mu\text{s}$

$$V_{\text{out}}(t) = V_{\text{out},f} - (V_{\text{out}}(0) - V_{\text{out},f})e^{-t/RC}$$

$$V_{\text{out}}(t) = 4 - 4e^{-t/2.5\mu\text{s}} \text{ V} \quad \text{for } 0 \leq t \leq 5 \mu\text{s}$$

● ● ● | Example

- Then, at $5 \mu\text{s}$, $V_{\text{out}}(t)$ will approach 0 V exponentially.
- We write the equation for this part using:
 - Initial condition $V_{\text{out}}(5 \mu\text{s}) = ?$
Use equation from previous step, since V_{out} is continuous.


$$V_{\text{out}}(5\mu\text{s}) = 4 - 4e^{-5\mu\text{s}/2.5\mu\text{s}} = 3.44 \text{ V}$$

- Final value $V_{\text{out},f} = 0 \text{ V}$
- Time constant $RC = (2.5 \text{ k}\Omega)(1 \text{ nF}) = 2.5 \mu\text{s}$

$$V_{\text{out}}(t) = V_{\text{out},f} - (V_{\text{out}}(t_0) - V_{\text{out},f})e^{-(t-t_0)/RC}$$

$$V_{\text{out}}(t) = 3.44e^{-(t-5\mu\text{s})/2.5\mu\text{s}} \quad \text{for } t > 5 \mu\text{s}$$

Example

 

$$V_{out}(t) = \begin{cases} 4 - 4e^{-t/2.5\mu\text{s}} & \text{for } 0 \leq t \leq 5 \mu\text{s} \\ 3.44e^{-(t-5\mu\text{s})/2.5\mu\text{s}} & \text{for } t > 5 \mu\text{s} \end{cases}$$


Design Issues

- How long between successive inputs?
 - Need output to reach recognizable logic level
 - Output must be at this level long enough to serve as input to next logic gate
- How many consecutive logic gates does signal go through before being “cleaned up” or saved in static memory cell?
 - Eventually the signal gets really bad
 - But adding hardware adds cost and delay

● ● ● | Propagation Delay

- Suppose an input goes from some initial voltage to some final voltage.
- In our examples, the input switch is immediate, but in practice it is not.
- Propagation delay is officially defined as:
(time when output is halfway to final value) **minus**
(time when input is halfway to final value)

● ● ● | Illustration

 

Using our equation for $V_{\text{out}}(t)$, we can find:

$t_{P,HL}$
(time when $V_{\text{out}}(t) = 2 \text{ V}$, as it goes from 0 V to 4 V) – 0 s

$t_{P,LH}$
(time when $V_{\text{out}}(t) = 1.72 \text{ V}$, as it goes from 3.44 V to 0 V) – 5 μs

● ● ● Propagation Delay

- It's not a coincidence that the propagation delays were the same.
- For a general RC circuit that has an input voltage switch at $t = t_0$,

$$V_{\text{out}}(t) = V_{\text{out,f}} - (V_{\text{out}}(t_0) - V_{\text{out,f}})e^{-(t-t_0)/RC}$$

- The time when $V_{\text{out}}(t)$ is $\frac{1}{2}(V_{\text{out,f}} + V_{\text{out}}(t_0))$ is given by


$$\frac{1}{2}(V_{\text{out,f}} + V_{\text{out}}(t_0)) = V_{\text{out,f}} - (V_{\text{out}}(t_0) - V_{\text{out,f}})e^{-(t-t_0)/RC}$$
- Simplifying,

$$\frac{1}{2} = e^{-(t-t_0)/RC} \quad t = (\ln 2)(RC) + t_0$$
- The propagation delay, the difference between this time and t_0 , is

$$t_p = (\ln 2)(RC) \quad \text{Depends only on time constant!}$$

● ● ● Graphing Propagation through Multiple Logic Gates

 
- We will want to examine how these RC-related delays affect a signal going through multiple logic gates.
- The math involved in putting an RC output (decaying exponential) into another RC circuit is not so easy.
- So, when analyzing a circuit with many logic gates, we will use the following simplification:



● ● ● | Logic Gates

- We have been using a simple RC circuit to model a logic gate.
- In each case, the final value of V_{out} was V_{in} .
- This will not always be true; sometimes, the output will go to logic 0 when the input is logic 1 and vice-versa.
- To determine what the final value of a logic gate output will be, we need to learn the types of logic gates.

● ● ● | Logic Gates

 

● ● ● | Logic Functions: Truth Tables

We specify what a logic circuit does by listing the output for each possible input. This listing is called a **truth table**.

A	\overline{A}
0	1
1	0

NOT

A	B	A·B	$\overline{A \cdot B}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

AND NAND

● ● ● | Logic Functions: Truth Tables

A	B	A+B	$\overline{A+B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0


OR NOR

A	B	A ⊕ B	$\overline{A \oplus B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

XOR XNOR

● ● ● | Timing Diagrams

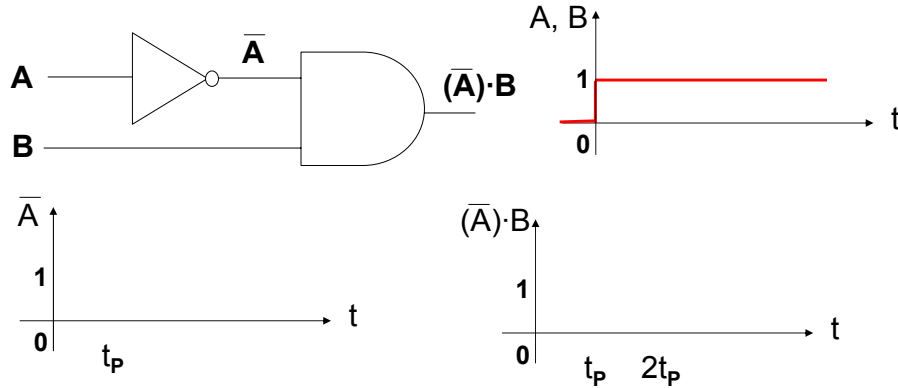- Now let's look at how signals propagate through logic gates, taking delay into consideration.
- Sketch the output for each logic gate in a more complicated circuit.





● ● ● | Strategy for Timing Diagrams

To find the output for a particular gate,

- Graph the inputs for that gate
- Graph the result of the logic gate using the input graphs
- Shift right by one t_p

● ● ● | **Example**

  

● ● ● | **Example**

