



## Lecture 16

Today we will

- Learn how to solve diode circuits
- Become proficient in the application of the different diode I-V models
- Gain experience “guessing” the correct diode mode for faster analysis




## Notes on Use of Models


- Most of the diode models are piecewise defined:
  - One function for reverse bias
  - Another for forward bias
- You will need to:
  - “Guess” that diode is reverse (or forward) biased
  - Solve for  $V$ ,  $I$  according to your guess
  - If this results in an impossibility, guess again
- Rarely, both guesses may lead to impossibility.
  - Use a more detailed model
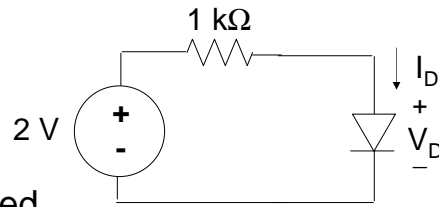
## Example 1: Ideal Diode Model

Find  $I_D$  and  $V_D$  using the ideal diode model.




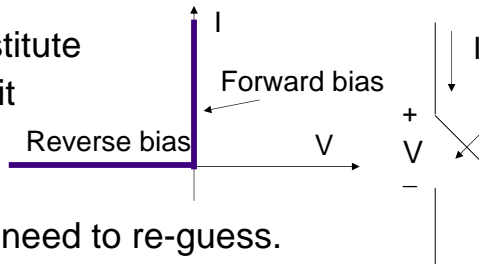- Is the diode reverse biased or forward biased?
- Make a guess, substitute corresponding circuit for diode.
- “Reality check” answer to see if we need to re-guess.


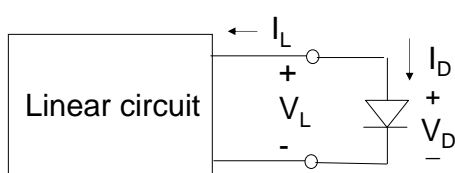
## Guessing the Diode Mode: Graphing

- Look at the diode circuit as a Thevenin equivalent linear circuit attached to a diode.




$$V_L = V_D$$

$$I_L = -I_D$$

- Graph the diode I-V curve and the linear circuit I-V curve on the same graph, both in terms of  $I_D$  and  $V_D$ .
- This means draw the diode I-V curve normally, and draw the linear I-V curve flipped vertically ( $I_L = -I_D$ ).
- See where the two intersect—this gives you  $I_D$  and  $V_D$ .


## Example 1: Ideal Diode Model

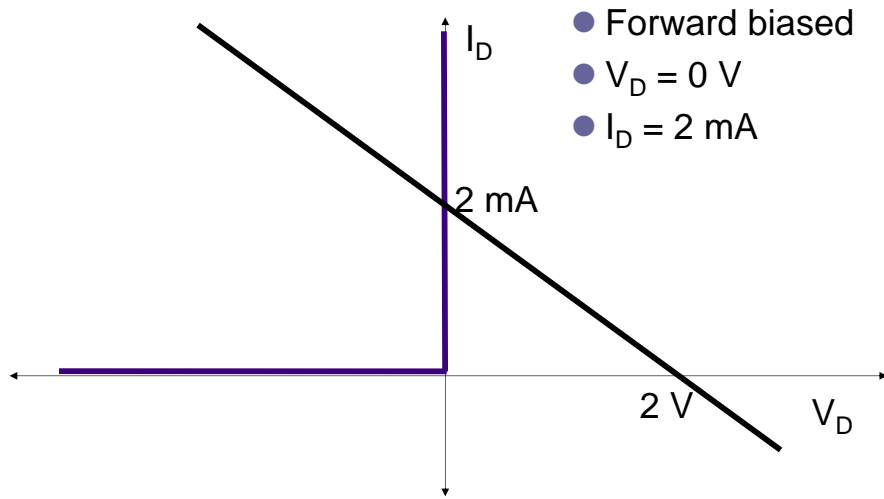
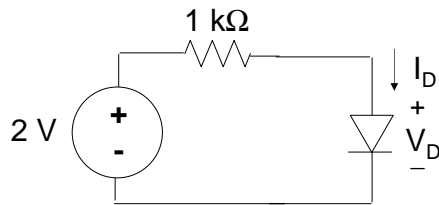
## Guessing the Diode Mode: “Common Sense”

We may notice:

- Polarity of the  $2 \text{ V}$  falling over the resistor and diode
- The  $2 \text{ V}$  is in same direction as  $V_D$
- Diode is probably forward biased




## Guessing the Diode Mode: When in Doubt...

- It's generally easier to guess **reverse bias** since it is easy to check.
- No matter what piecewise model we use, reverse bias is always open circuit.
- So when you don't know what to do, put in open circuit for the diode, and see if it violates reverse bias conditions (zero current, negative voltage).
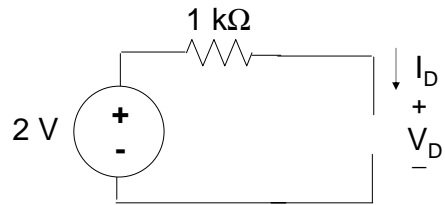
## Example 1: Ideal Diode Model

- Guess reverse bias:
- Since no current is flowing,  
 $V_D = 2 \text{ V}$  (by KVL)
- This is impossible for reverse bias (must have negative  $V_D$ )
- So the diode must be forward biased




## Example 1: Ideal Diode Model

- We know diode is forward biased:

- $V_D = 0 \text{ V}$

- $I_D = 2 \text{ V} / 1 \text{ k}\Omega = 2 \text{ mA}$

- Same as what we got graphically.

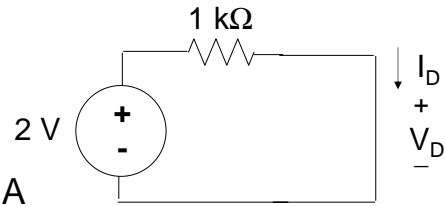

## Example 2: Large-Signal Diode Model


- Use the large-signal diode model with  $V_F = 0.7$  to find  $I_D$  and  $V_D$ .

- To be in forward bias mode, the diode needs 0.7 V.

- The source only provides 0.5 V.


- The resistor cannot add to the voltage since the diode could only allow current to flow clockwise.

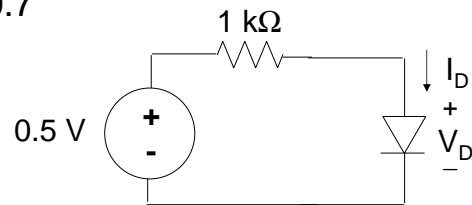- Reverse bias  $\Rightarrow$  open circuit  $\Rightarrow I_D = 0 \text{ A}$ ,  $V_D = 0 \text{ V}$



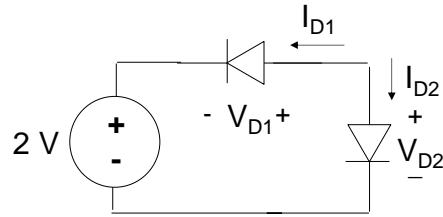
### Example 3: Large-Signal Diode Model

- Use the large-signal diode model with  $V_F = 0.7$  to find  $I_D$  and  $V_D$ .



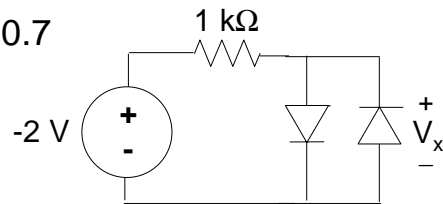
### Example 4: Large-Signal Diode Model

- Use the large-signal diode model with  $V_F = 0.7$  to find  $V_x$ .


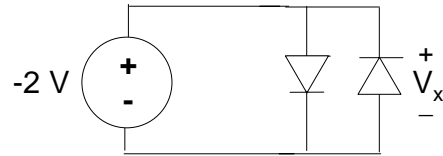
## Example 5: Ideal Diode Model

- Use the ideal diode model to find  $V_x$ .



## Example 6: Realistic Diode Model

- Using the realistic diode model with  $I_0 = 10^{-6}\text{ A}$  and  $V_T = 0.026\text{ V}$ , compute  $I_D$  and  $V_{\text{OUT}}$ .

