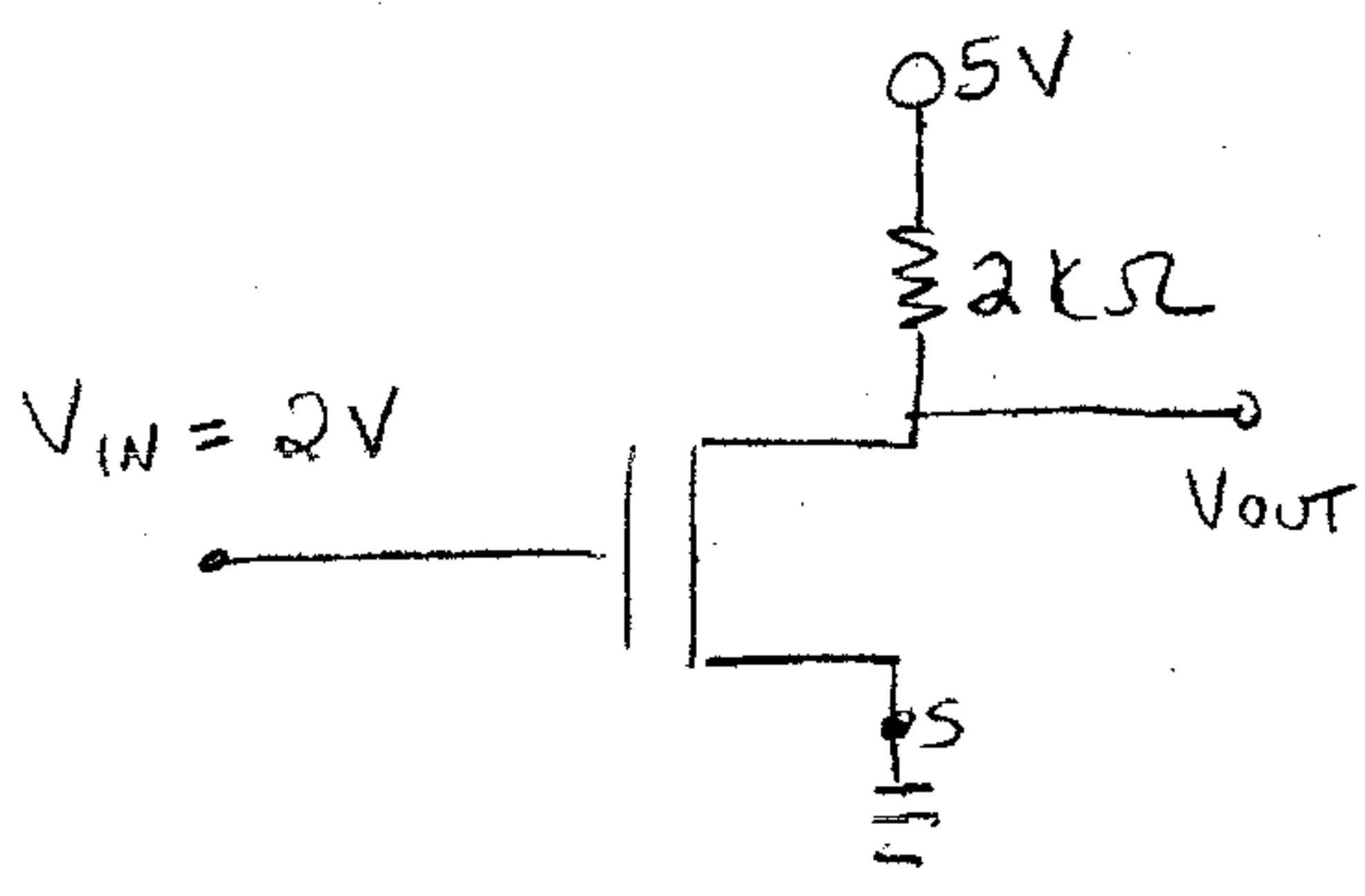


$V_{TH(n)} = 1V$
 $\lambda_n = 0$
 $\frac{W}{L} \mu_n C_{ox} = 1mA/V^2$

Find V_{GS} , V_{DS} , I_D , and V_{out} .

- $V_{GS} = V_{G1} = V_{in} = \boxed{5V}$
 $V_{GS} > V_{TH} \Rightarrow$ not cutoff mode.
- Assume saturation mode. (i.e. $V_{DS} > V_{GS} - V_{TH}$).
 Then, $i_D = \frac{1}{2} \cdot (1mA/V^2) \cdot (\underbrace{V_{GS} - V_{TH}}_{=4V})^2 = 8mA$.
 $\Rightarrow V_{out} = 5 - (2k\Omega)(8mA) = 5 - 16 = -11V$.
 \Rightarrow not saturation mode.

- Assume ~~cutoff~~ **triode mode**. Then, $V_{DS} < V_{GS} - V_{TH} = 4V$.
 $i_D = (1mA/V^2) (V_{GS} - V_{TH} - V_{DS}/2) V_{DS}$, and
 ~~$i_D = \frac{5 - V_{DS}}{2k}$~~
 ~~$\frac{5 - V_{DS}}{2k} = (1mA/V^2) (4 - V_{DS}/2) V_{DS}$~~
 $5 - V_{DS} = (8 - V_{DS}) \cdot V_{DS} \Rightarrow V_{DS}^2 - 9V_{DS} + 5 = 0$
 $V_{DS} = \frac{9 + \sqrt{81 - 20}}{2} \approx \frac{9 \pm 7.8}{2}$. $V_{DS} < 4V \Rightarrow V_{DS} = \frac{9 - 7.8}{2} = \boxed{0.6V}$
 $\Rightarrow \boxed{V_{out} = 0.6V}$, $i_D = \frac{5 - 0.6}{2k} = \boxed{2.2mA}$



$$V_{TH(M)} = 1V$$

$$\lambda_n = 0$$

$$\frac{W}{L} \mu_n C_{ox} = 1mA/V^2$$

Find V_{GS} , V_{DS} , I_D & V_{OUT} .

- $V_{GS} = V_{in} = \boxed{2V}$

$V_{GS} > V_{TH} = 1V \Rightarrow$ not cutoff mode.

- Assume saturation mode. ($V_{DS} > V_{GS} - V_{TH} = 1V$).


Then,
$$i_D = \frac{1}{2} \cdot (1mA/V^2) \cdot \left(\frac{V_{GS} - V_{TH}}{1V} \right)^2 = \boxed{0.5mA}$$

$$V_{DS} = 5 - (2k)(0.5mA) = \boxed{4V}$$

$V_{DS} > V_{GS} - V_{TH}$ ✓ (saturation mode ✓)

So, $V_{out} = \boxed{4V}$

③

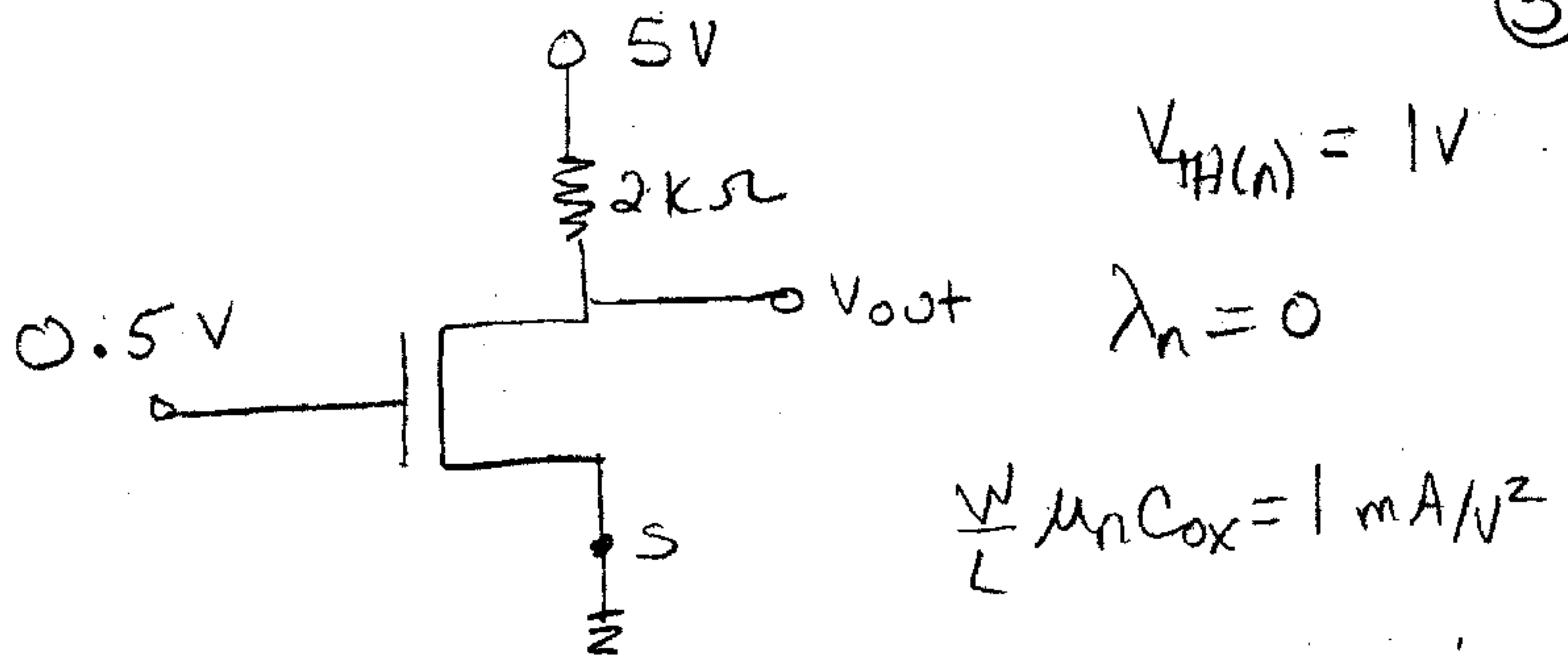

Find V_{GS} , V_{DS} , I_D & V_{out} .

$$V_{GS} = V_G - V_S = 0.5V - 0V = \boxed{0.5V}$$


$$V_{GS} = 0.5V < V_{TH} = 1V \Rightarrow \boxed{\text{cut-off mode}}$$

$$\text{cutoff mode} \Rightarrow i_D = \boxed{0A}$$

$$V_{out} = 5 - (2k)(0) = \boxed{5V}$$

$$V_{DS} = V_{out} = \boxed{5V}$$

(5)

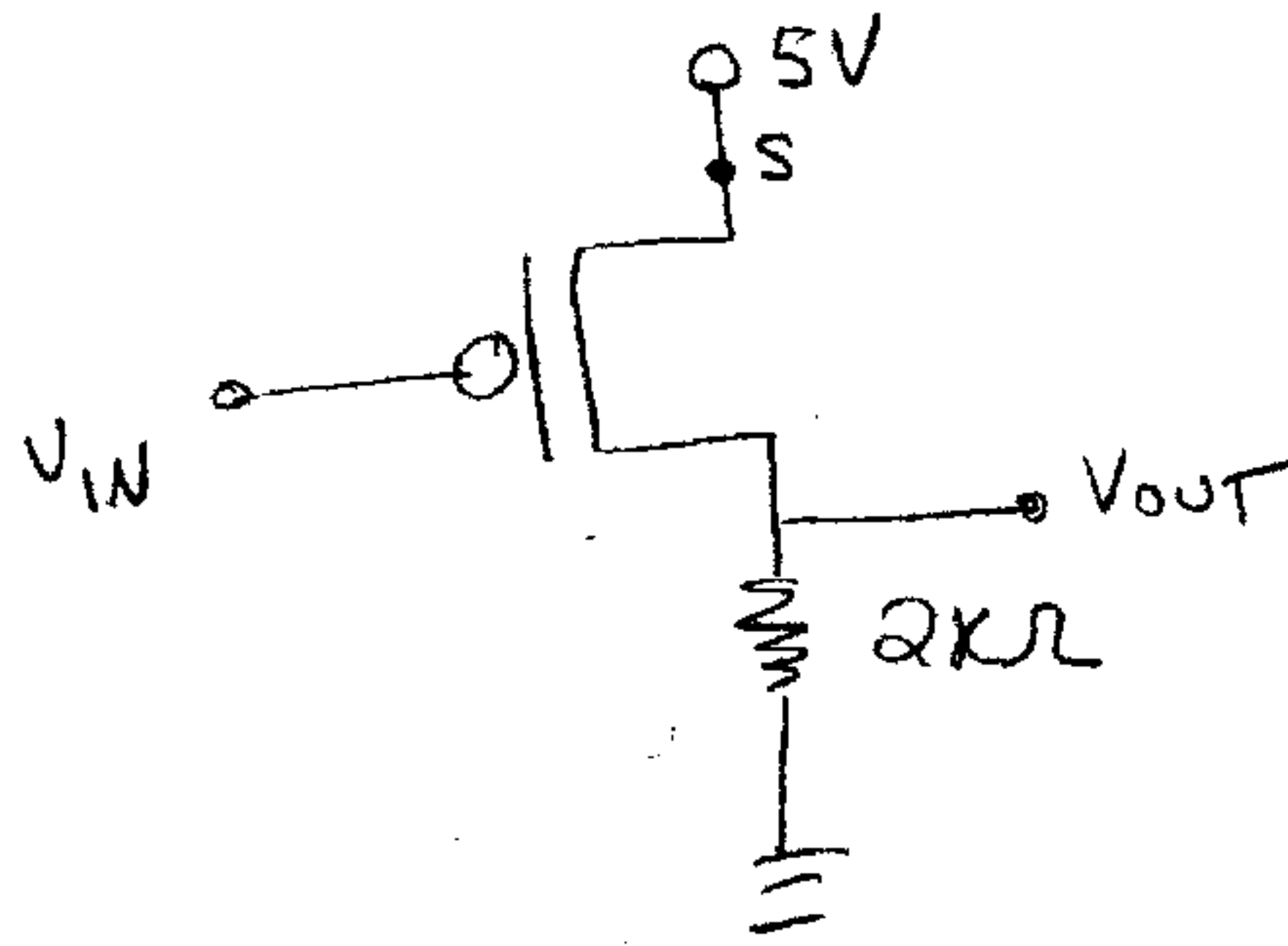

$$V_{TH(p)} = -1V$$

$$\lambda_p = 0$$

$$\frac{W}{L} \mu_p C_{ox} = 1 \frac{mA}{V^2}$$

This circuit is the complement of the NMOS inverter.

Find V_{out} for $V_{in} = 4.5V$, $3V$, and $0V$.

$$1) V_{in} = 4.5V \Rightarrow V_{GS} = V_G - V_S = 4.5 - 5 = -0.5V.$$

$$V_{GS} = -0.5V > V_{TH} = -1V \Rightarrow \text{cutoff mode} \Rightarrow i_D = 0A$$

$$\Rightarrow V_{out} = (2k\Omega)(0A) = \boxed{0V}$$

$$2) V_{in} = 3V \Rightarrow V_{GS} = 3 - 5 = -2V.$$


$V_{GS} < V_{TH} \Rightarrow$ not cutoff. Assume saturation. Then,

$$i_D = -\left(1 \frac{mA}{V^2}\right) \cdot \frac{1}{2} \left(\frac{V_{GS} - V_{TH}}{-2 - (-1)} \right)^2 = -0.5mA.$$

$$\Rightarrow V_{out} = V_D = (2k)(-0.5mA) = \boxed{-1V}$$

$$V_{DS} = V_D - V_S = -1 - 5 = -6V. < V_{GS} - V_{TH} \Rightarrow \text{indeed in saturation mode.}$$

5

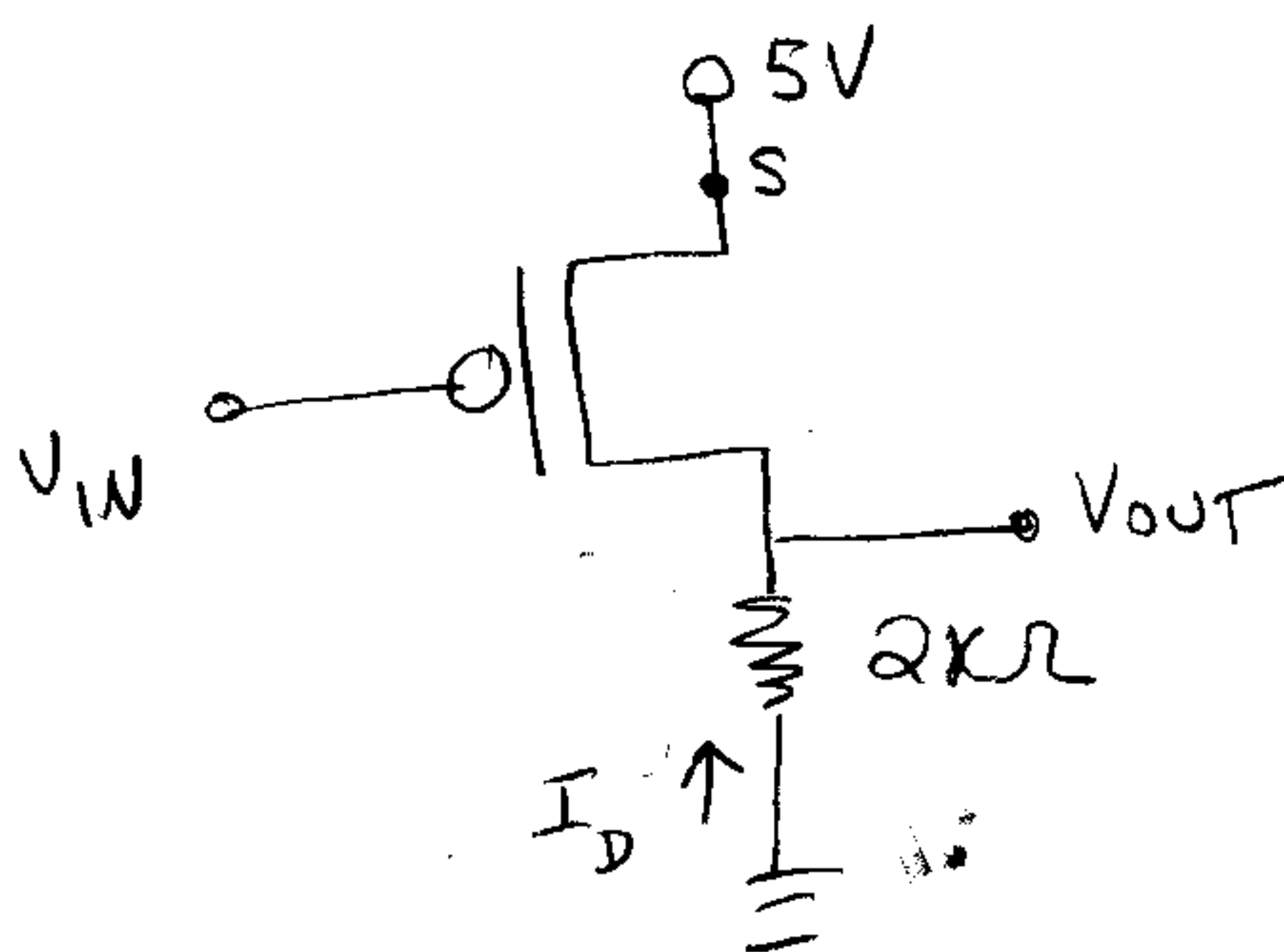

$$V_{TH(p)} = -1V$$

$$\lambda_p = 0$$

$$\frac{W}{L} \mu_p C_{ox} = 1 \frac{mA}{V^2}$$

This circuit is the complement of the NMOS inverter.

Find V_{OUT} for $V_{IN} = 4.5V, 3V,$ and $0V.$

$V_{IN} = 0: V_{GS} = 0V - 5V = -5V$ not cutoff

assume saturation $I_D = -1 \frac{mA}{V^2} (-5V - (-1V))^2 = -8mA$

$V_{DS} = -2kI_D - 5V = 11V$ not possible for PMOS

so triode mode:

$$I_D = -1 \frac{mA}{V^2} (-5V - (-1V) - \frac{V_{DS}}{2}) V_{DS}$$

KVL: $V_{DS} = -2kI_D - 5V \Rightarrow I_D = -\left(\frac{5V + V_{DS}}{2k}\right)$

Solve simultaneously to get


$V_{DS} = \{-0.6, -8.4\}$ not possible for triode mode

$$I_D = -\left(\frac{5V - 0.6}{2k}\right) = -2.2mA$$

$$V_{OUT} = -2kI_D = 4.4V$$

Our inverters had open outputs.

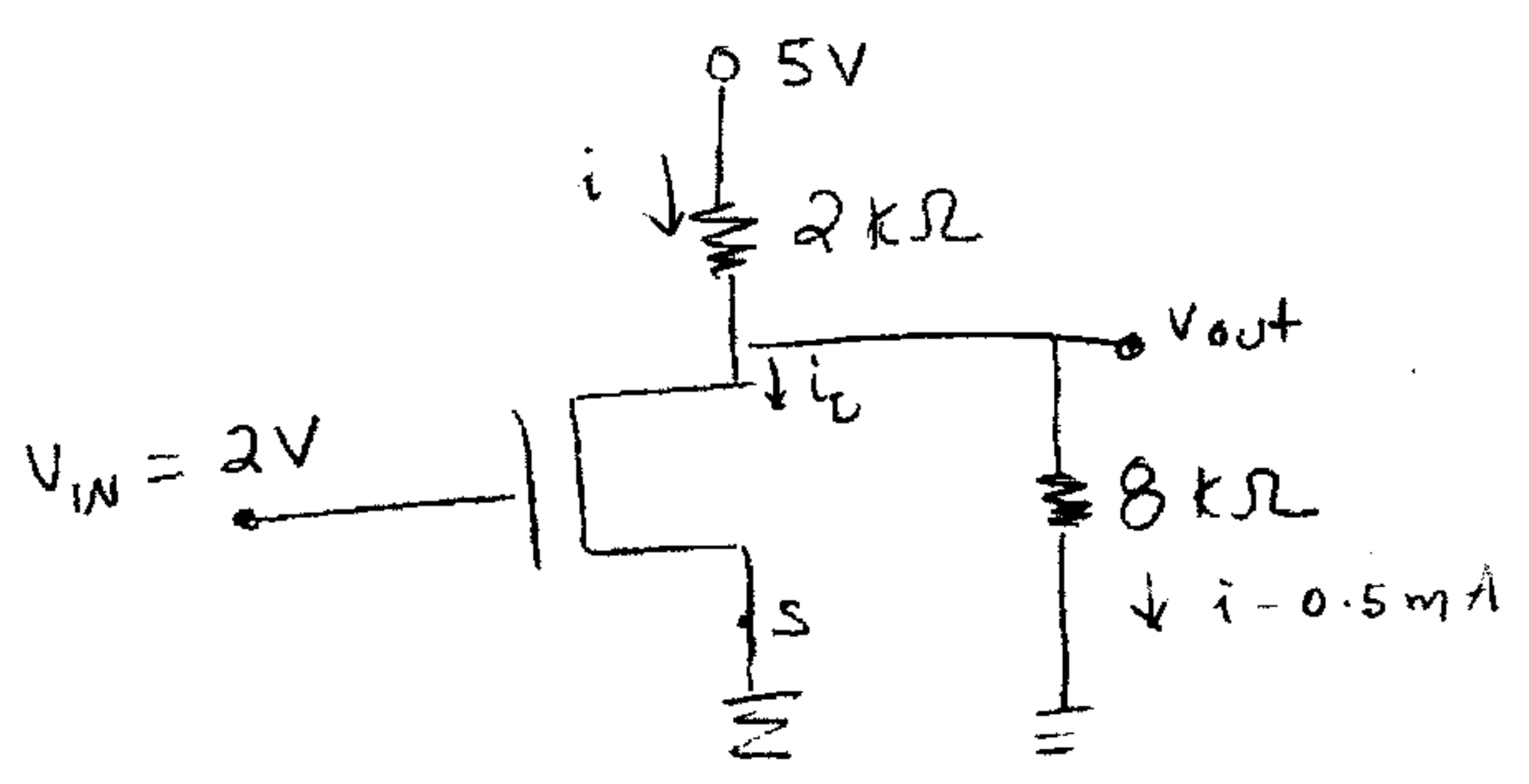If there is something (a "load") attached, the voltages & currents are different.



Find V_{GS} , V_{DS} , I_D & V_{out} .

- $V_{GS} = V_{G1} - V_S = 2 - 0 = 2V > V_{TH} = 1V \Rightarrow$ not cutoff.

Assume saturation mode. Then,

$$i_D = (1mA/V^2) \cdot \frac{1}{2} (V_{GS} - V_{TH})^2 = 0.5mA$$

KVL: $5V = 2k \cdot i + 8k (i - 0.5mA)$

$$5 = i \cdot 10k - 4$$

$$i = \frac{9}{10k} = 0.9mA \Rightarrow V_{out} = 8k (0.9mA - 0.5mA) = 8k (0.4mA)$$

$$V_{DS} = V_{out} = 3.2V > V_{GS} - V_{TH} = 1V$$

\Rightarrow saturation mode \checkmark