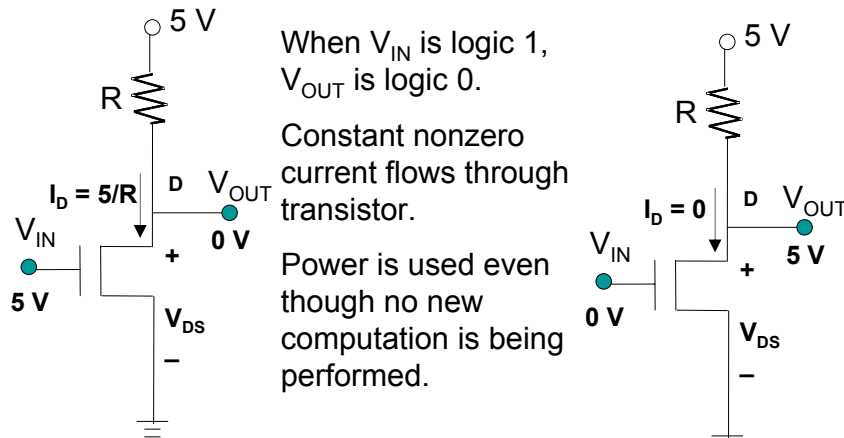


Lecture 20

Today we will


- Look at why our NMOS and PMOS inverters might not be the best inverter designs
- Introduce the CMOS inverter
- Analyze how the CMOS inverter works

NMOS Inverter



When V_{IN} changes to logic 0, transistor gets cutoff. I_D goes to 0. Resistor voltage goes to zero. V_{OUT} “pulled up” to 5 V.

PMOS Inverter

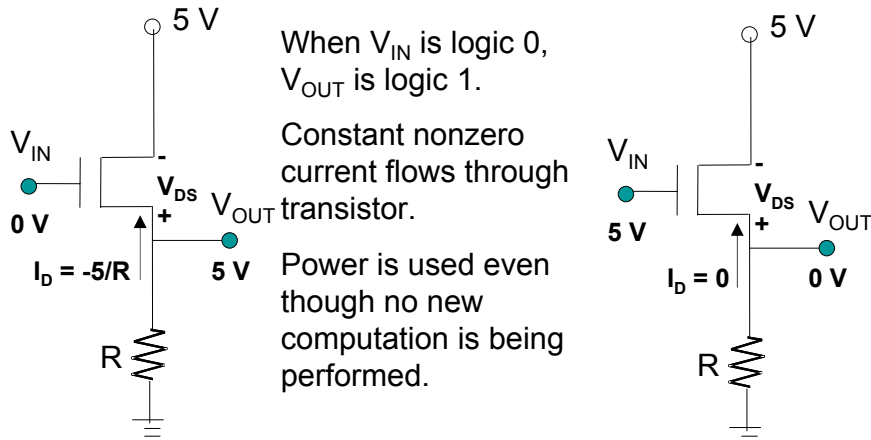


When V_{IN} is logic 0, V_{OUT} is logic 1.

Constant nonzero current flows through transistor.

Power is used even though no new computation is being performed.

When V_{IN} changes to logic 1, transistor gets cutoff. I_D goes to 0. Resistor voltage goes to zero. V_{OUT} “pulled down” to 0 V.

Analysis of CMOS Inverter

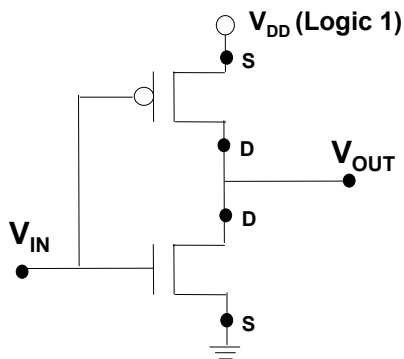


NMOS is “pull-down device”

PMOS is “pull-up device”


Each shuts off when not pulling

- We can follow the same procedure to solve for currents and voltages in the CMOS inverter as we did for the single NMOS and PMOS circuits.
- Remember, now we have **two transistors** so we write **two I-V relationships** and have **twice the number of variables**.
- We can roughly analyze the CMOS inverter graphically.


NMOS Inverter

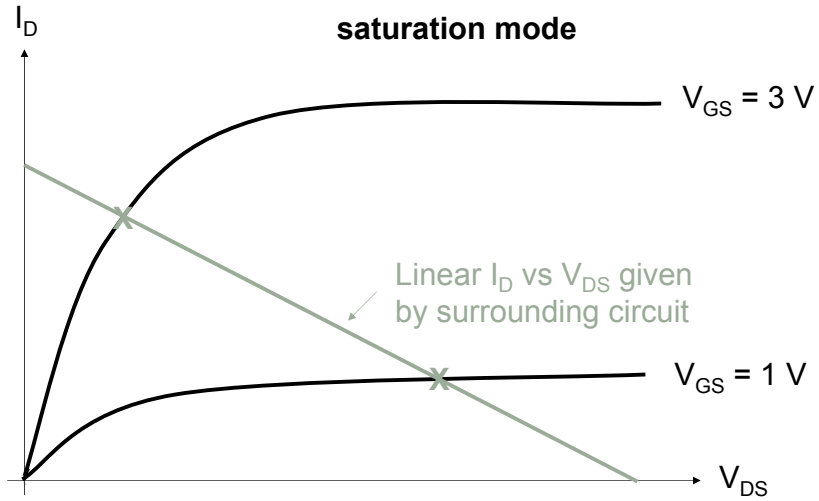


Linear KVL and KCL Equations

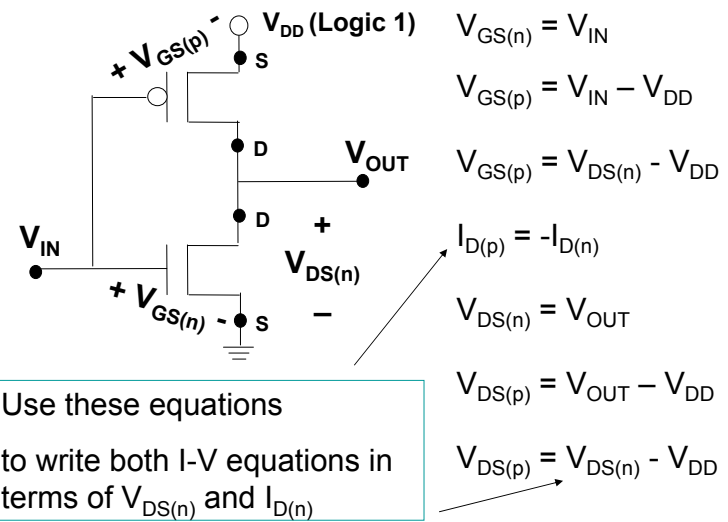


CMOS Analysis

 


CMOS Analysis

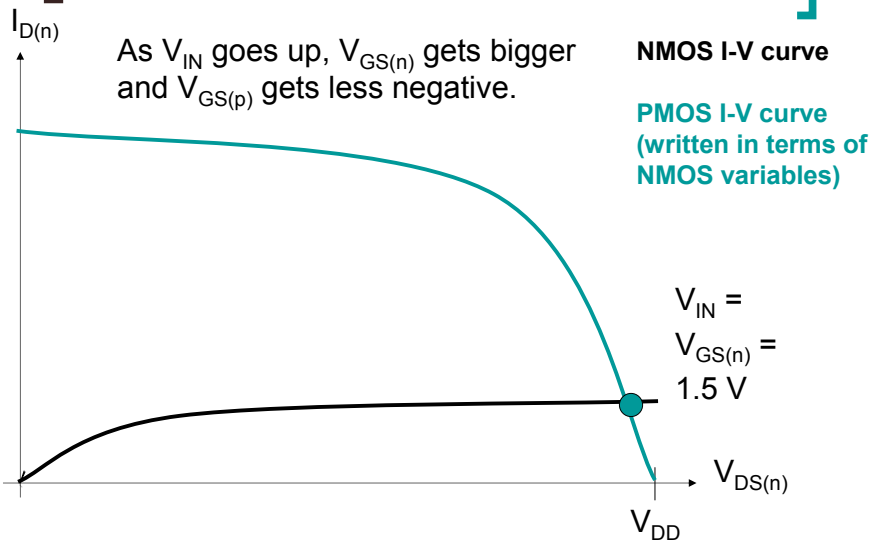


CMOS Analysis

 


CMOS Analysis

 


CMOS Analysis

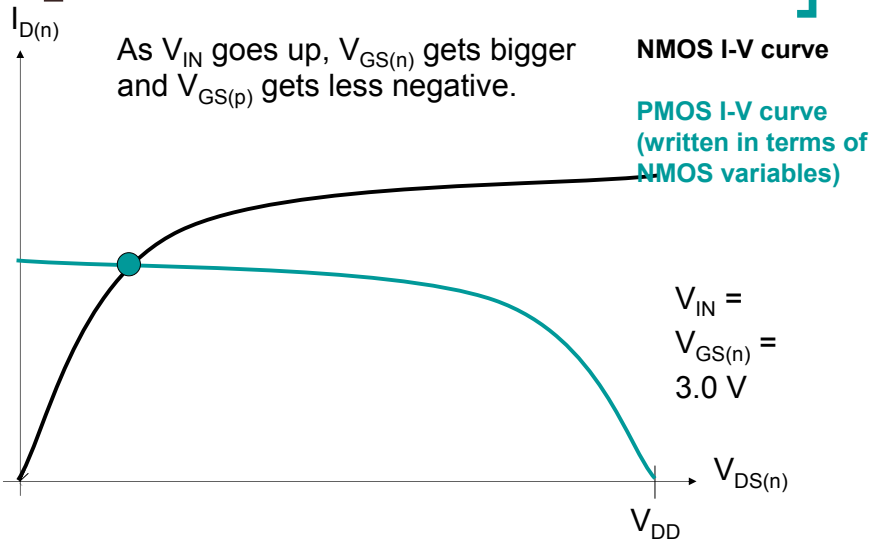


CMOS Analysis

 


CMOS Analysis

 

CMOS Inverter V_{OUT} vs. V_{IN}

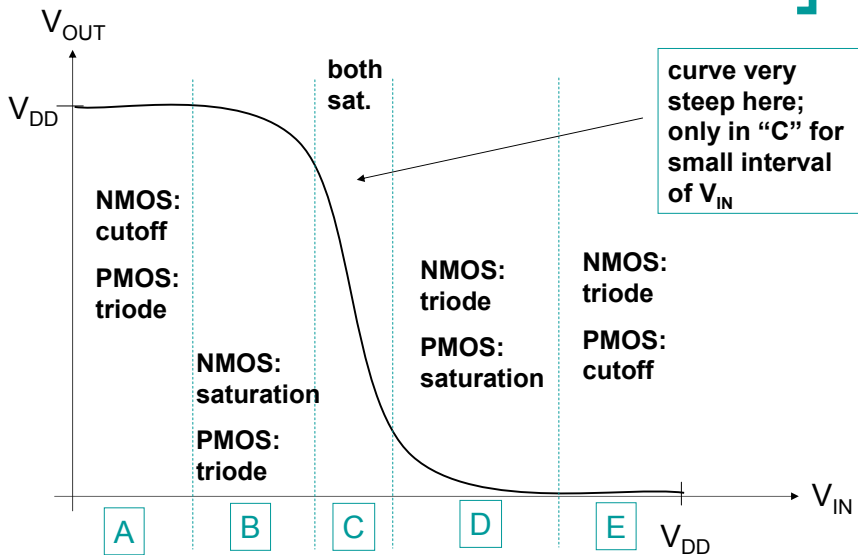

 

Important Points

- No I_D current flow in Regions A and E if **nothing** attached to output; current flows only during logic transition
- If another inverter (or other CMOS logic) attached to output, transistor gate terminals of attached stage do not permit current: current still flows only during logic transition

