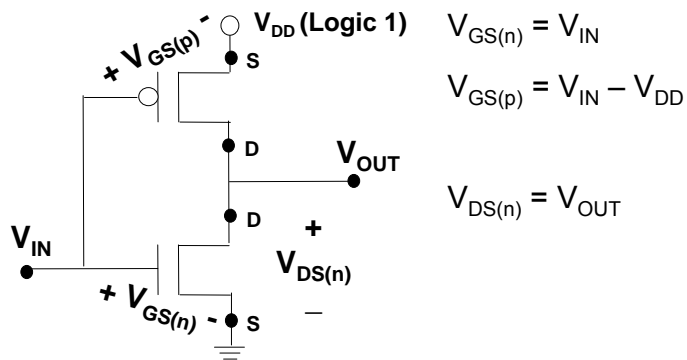


Lecture 21


Today we will

- Revisit the CMOS inverter, concentrating on logic 0 and logic 1 inputs
- Come up with an easy model for MOS transistors involved in CMOS digital computation
- Investigate the “complementary” nature of CMOS logic circuits
- Introduce CMOS NAND and NOR
- Determine the effective R and C for CMOS logic transitions


CMOS Inverter



CMOS Analysis


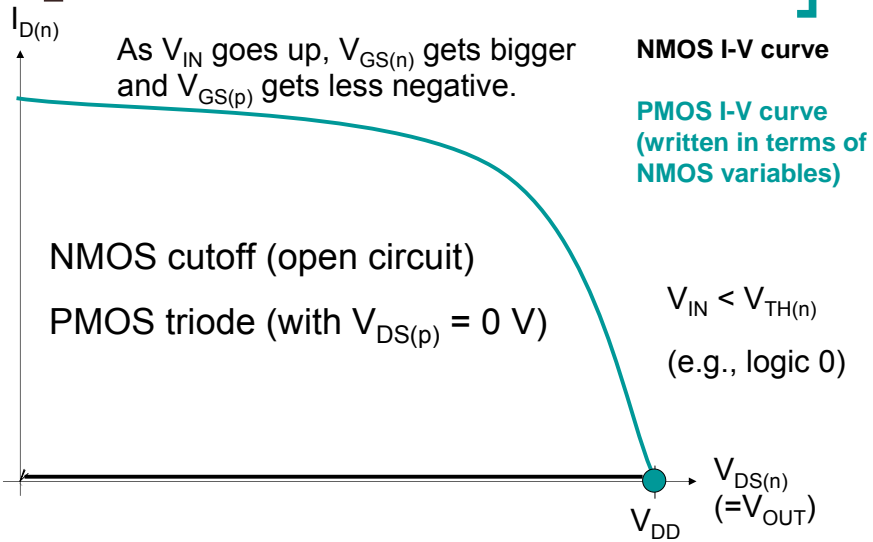


CMOS Analysis

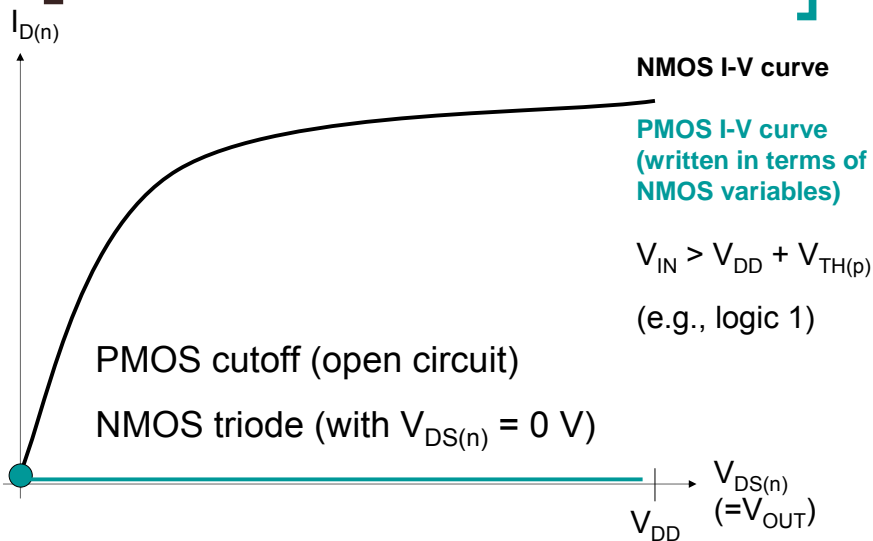



Model for Digital Computation

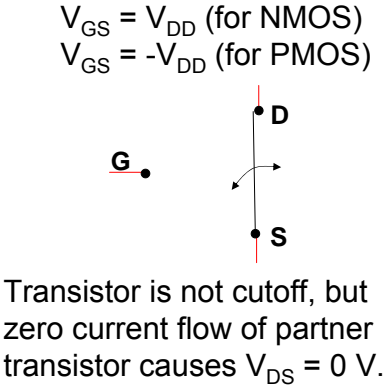 - This leads us to a simpler model for transistors in CMOS circuits, when V_{IN} is fully logic 0 or logic 1.




Practice

  - Use this model to find V_{OUT} for the circuits below.




CMOS NAND

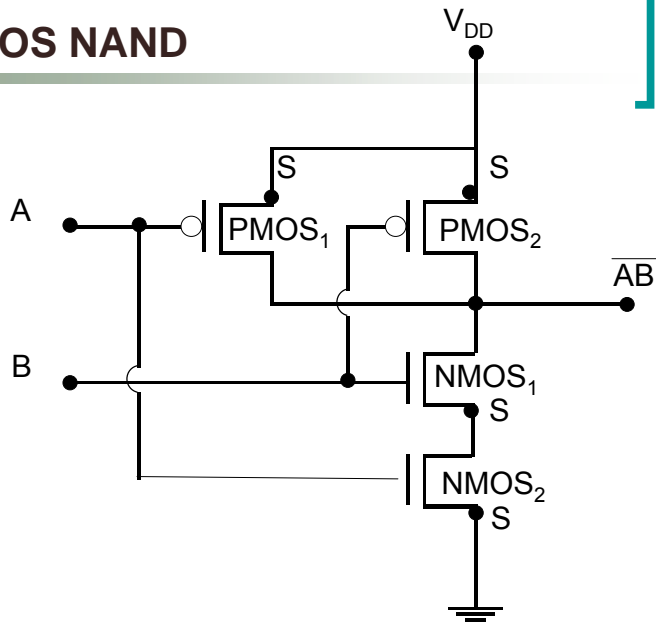


More Practice

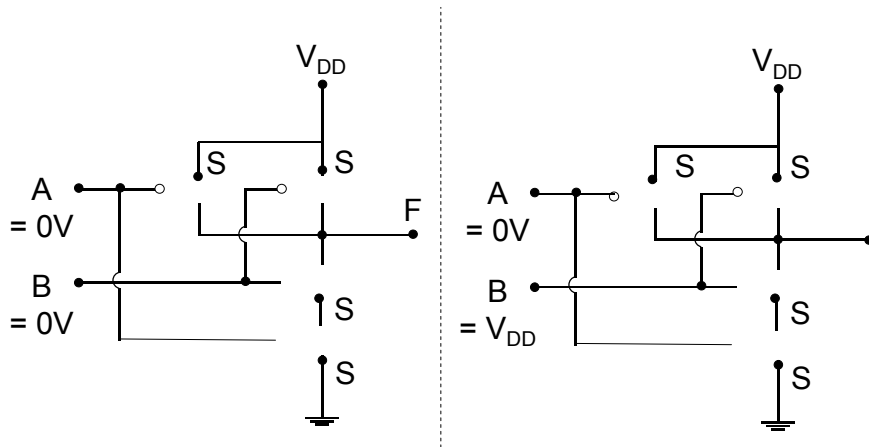Verify the logical operation of the CMOS NAND circuit:



More Practice

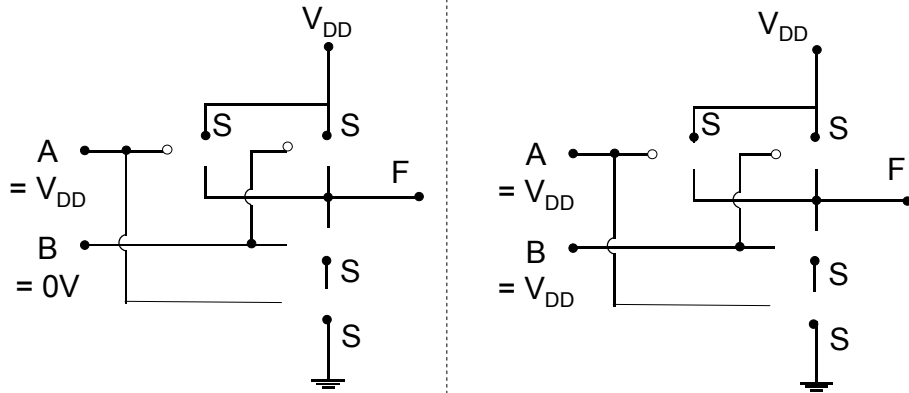
Verify the logical operation of the CMOS NAND circuit:



CMOS Networks

- Notice that V_{OUT} gets connected to either V_{DD} or ground by “active” (not cutoff) transistors.
- We say that these active transistors are “pulling up” or “pulling down” the output.
- NMOS transistors = **pull-down network**
- PMOS transistors = **pull-up network**
- These networks had better be **complementary** or V_{OUT} could be “floating”—or attached to both V_{DD} and ground at the same time.


CMOS NAND vs. NOR

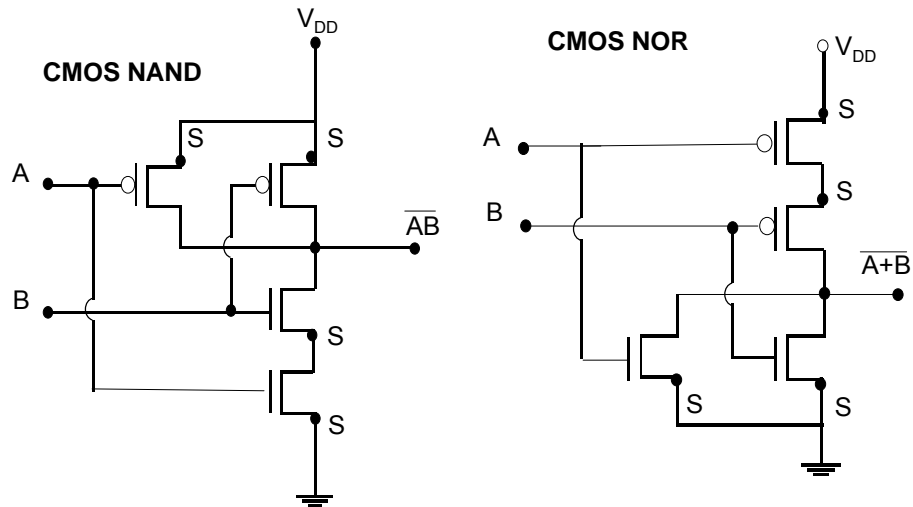

Complementary Networks


- If inputs A and B are connected to parallel NMOS, A and B must be connected to series PMOS.
- The reverse is also true.
- Determining the logic function from CMOS circuit is not hard:
 - Look at the NMOS half. It will tell you when the output is logic zero.
 - Parallel transistors: “like or”
 - Series transistors: “like and”

Resistance and Capacitance

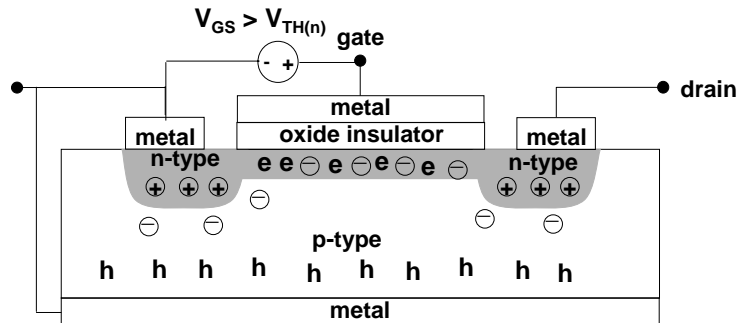


- The separation of charge by the oxide insulator creates a natural capacitance in the transistor from gate to source.
- The silicon through which I_D flows has a natural resistance.
- There are other sources of capacitance and resistance too.

Gate Delay—The Full Picture

 


- Suppose V_{IN} abruptly changed from logic 0 to logic 1.
- V_{OUT1} may not change quickly, since it is attached to the gates of the next inverter.
- These gates must collect/discharge electrons to change voltage.
- Each gate attached to the output contributes a capacitance.

Gate Delay—The Full Picture

 

- Where will these electrons come from/go to?
- No charges can pass through the cutoff transistor.
- Charges will go through the pull-down/pull-up transistors to ground. These transistors contribute resistance.


Computing Gate Delay

 

- Determine the capacitance of each gate attached to the output. These combine in parallel. Higher **fan-out** = more capacitance.
- Determine which transistors are pulling-up or pulling-down the output. Each contributes a resistance, and may need to be combined in series and/or parallel.
- The C from 1) and R from 2) are the RC for the V_{OUT1} transition.

[Example]

- Suppose we have the following circuit:

 

Logic 0 = 0 V
Logic 1 = 1 V
NMOS resistance
 $R_n = 1 \text{ k}\Omega$
PMOS resistance
 $R_p = 2 \text{ k}\Omega$
Gate capacitance
 $C_G = 50 \text{ pF}$

- If A and B both transition from logic 1 to logic 0 at $t = 0$, find the voltage at the NAND output, $V_{OUT}(t)$, for $t \geq 0$.