



Announcements

- Prof. Ross's office hours (in 477 Cory):
 - Tu Th 1:30 PM – 2:30 PM
 - Tu Th after class – 6:30 PM
 - additional appointments welcome!
- GSI Ashwin Ganesan's office hours (in 493 Cory):
 - M 4 PM – 5 PM
 - F 10 AM – 11 AM
- GSI Joe Makin's office hours (in 493 Cory):
 - To be announced
- Problems with Tuesday 11-12 discussion, will be held in 521 Cory next week (1/30/04) only; then likely to be rescheduled

1/22/2004

EE 42 Lecture 2



Cast of Characters

- Fundamental quantities
 - Charge
 - Current
 - Voltage
 - Power
- Fundamental concern
 - Current-Voltage Relationship
- Fundamental elements
 - Resistor
 - Voltage Source
 - Current Source

1/22/2004

EE 42 Lecture 2

Charge

- You are already familiar with the idea of **charge** from chemistry or physics.
- We say a proton has a positive charge, and an electron has a negative charge.
- Charge is measured in units called Coulombs, abbreviated C.

$$1 \text{ proton} = 1.6 \times 10^{-19} \text{ C}$$

$$1 \text{ electron} = -1.6 \times 10^{-19} \text{ C}$$

1 C is a whole lot of protons!

6.25×10^{18} protons in 1 C.


1/22/2004

EE 42 Lecture 2


Electric Field

- We know that opposite charges attract each other, and like charges repel.
- The presence of a charged particle creates an electric field. Other phenomena also create an electric field.
- The electric field is a lot like gravity. It can point in different directions and have different strength depending on location.

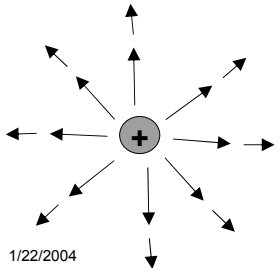Vector fields are like wind maps from your weather forecast.




1/22/2004

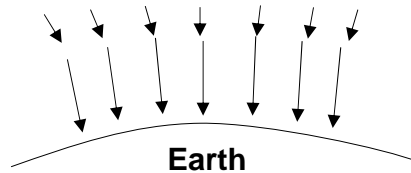

EE 42 Lecture 2

Voltage

- It takes energy to move a proton against the direction of an electric field (just like it takes energy to lift an object off the ground, against gravity).
- Suppose it takes (positive) energy to move a proton from point **a** to point **b**. Then we say point **b** is at a higher **electric potential** than point **a**.
- The difference in electric potential between two points is called **voltage**. Voltage, measured in Volts (V) indicates how much energy it takes to move a charge from point to point.

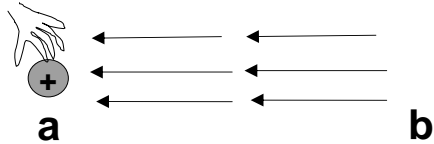


1/22/2004

EE 42 Lecture 2

Voltage Conventions

- Voltage is always measured between two points (just like distance). We need to specify the “start” and “finish”.
- We could write saying that **b** is 5 V higher than **a**.
- Or, we could write saying that **a** is -5 V higher than **b**.
- When we put down a + and a - to specify a voltage, it is simply a reference frame. We are not making a statement about which point **actually has** the higher potential, since the voltage in between can be negative!

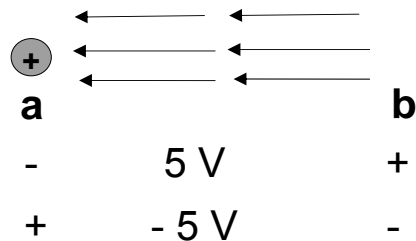


1/22/2004

EE 42 Lecture 2


Voltage Conventions: Notation

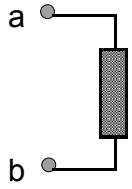- We can use subscript convention to define a voltage between two labeled points:



“ V_{ab} ” means the potential at “a” minus the potential at “b” (that is, the potential drop from “a” to “b”).

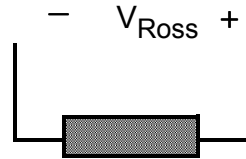- Remember, this is not saying that the potential at “a” is higher than the potential at “b”. The difference could be negative.
- We can make up voltages with any names we wish, as long as we provide a reference frame (+ and -).
- Here, V_{Ross} is the potential rise from left to right (or, the potential drop from right to left, or the right potential minus the left).




1/22/2004

EE 42 Lecture 2

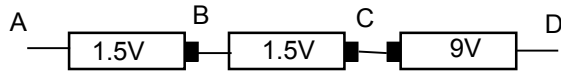
Examples

The flat end of the battery is at lower potential than the “bump” end.



What is V_{AD} ?

Find V_1 and V_x .

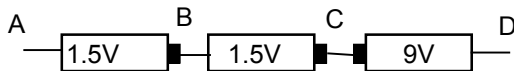

- V_1 +

- V_x +


1/22/2004

EE 42 Lecture 2

Voltage Conventions: Ground

- Many times, a common point will be used as the starting (-) point for several voltage measurements. This common point is called **common** or **ground**.
- We may define a voltage at point "a" *with respect to ground*. This refers to the voltage with + reference at "a" and - reference at ground (the voltage drop from "a" to ground).
- Voltages with respect to ground are often denoted using a single subscript:
- Notice the symbol for ground.

Also seen is

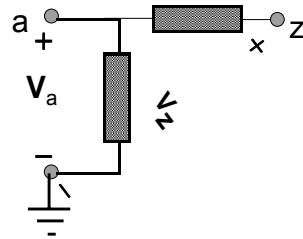

1/22/2004

EE 42 Lecture 2

Current: Moving Charge

- An electric field (or applied energy) can cause charge to move.
- The amount of charge per time unit moving past a point is called **current**.
- Current is measured in Coulombs per second, which are called Amperes (abbreviated A and called Amps for short).
- Mathematically speaking,

$$i = \frac{dq}{dt}$$

where i is current in A, q is charge in C, and t is time in s


- Even though it is usually electrons that do the moving, **current is defined as the flow of positive charge.**

1/22/2004

EE 42 Lecture 2

Current Reference Direction

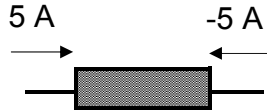- Current also needs a reference frame. To define a current, draw an arrow:



- This says “the current moving through the device from left to right is 5 A”.
- We could also say, “the current moving through the device from right to left is -5 A”.
- Drawing an arrow does not make a statement about the direction the current is actually going. It is just a reference frame. You can draw arrows however you want when you need to solve for currents.

Resistance

- Current is due the ability of electrons to break away from atoms and move around.
- In some materials, like metals, where there are few valence electrons, little energy is needed to break bonds and move an electron.
- In other materials, a strong electric field (voltage) must be applied to break the bonds. These materials are said to have a higher **resistance**.
- Resistance, measured in Ohms (Ω), indicates how much voltage is necessary to create a certain amount of current.

Power


- Power is the amount of energy absorbed or generated per unit time. It is the time derivative of energy, and it is measured in Watts (W).
- The power absorbed (or generated) by a device is equal to the product of the current through the device and the voltage over the device:
$$p = v i$$
 where p is power in W, v is voltage in V and i is current in A.
- Sometimes this equation gives you the power absorbed by the device, and sometimes it provides the power generated by the device.

1/22/2004

EE 42 Lecture 2

Power: Sign Convention

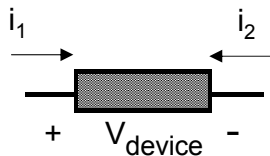- Whether “ $p = v i$ ” provides absorbed power or generated power depends on the relationship between the current and voltage directions.
- If the current i is referenced to flow from the “+” terminal of v to the “-” terminal of v , then “ $p = v i$ ” provides the power absorbed.
- When the opposite is true, “ $p = v i$ ” provides the power generated.



Power absorbed by
device = $(V_{\text{device}}) (i_1)$


Power generated by
device = $(V_{\text{device}}) (i_2)$

1/22/2004

EE 42 Lecture 2

Power Calculations

Find the power absorbed by each element.

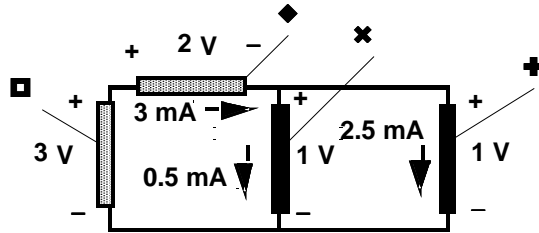

Element \square :

Element \diamond :

Element \times :

Element $+$:

Current-Voltage Relationship

- In this course, we deal with circuits that perform computations, where the numbers are voltages.
- Voltages appear at the input, and create current in the devices, which in turn changes the output voltage—and computation has taken place.
- The relationship between current and voltage in a device is fundamental. Circuit elements are characterized by their current-voltage relationships. It is these relationships that allow us to design and analyze circuits.
- We will now present current-voltage relationships (called i-v relationships for short) for basic circuit elements.

Basic Circuit Elements

- Resistor
 - Current is proportional to voltage (linear)
- Ideal Voltage Source
 - Voltage is a given quantity, current is unknown
- Wire (Short Circuit)
 - Voltage is zero, current is unknown
- Ideal Current Source
 - Current is a given quantity, voltage is unknown
- Air (Open Circuit)
 - Current is zero, voltage is unknown

1/22/2004


EE 42 Lecture 2

Resistor

- The resistor has a current-voltage relationship called Ohm's law:

$$v = i R$$

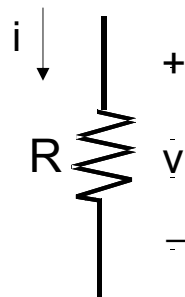where R is the resistance in Ω ,
 i is the current in A, and v is the voltage in V, with reference directions **as pictured**.




- If R is given, once you know i , it is easy to find v and vice-versa.
- Since R is never negative, a resistor always absorbs power...

1/22/2004

EE 42 Lecture 2

Ideal Voltage Source

- The ideal voltage source explicitly defines the voltage between its terminals.
 - Constant (DC) voltage source: $V_s = 5 \text{ V}$
 - Time-Varying voltage source: $V_s = 10 \sin(t) \text{ V}$
 - Examples: batteries, wall outlet, function generator, ...
- The ideal voltage source does not provide any information about the current flowing through it.
- The current through the voltage source is defined by the rest of the circuit to which the source is attached. Current cannot be determined by the value of the voltage.
- Do not assume that the current is zero!

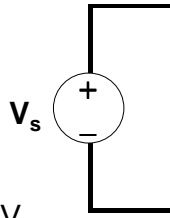


Wire

- Wire has a very small resistance.
- For simplicity, we will idealize wire in the following way: the potential at all points on a piece of wire is the same, regardless of the current going through it.
 - Wire is a 0 V voltage source
 - Wire is a 0 Ω resistor
- This idealization (and others) can lead to contradictions on paper—and smoke in lab.

Ideal Current Source

- The ideal current source sets the value of the current running through it.
 - Constant (DC) current source: $I_S = 2 \text{ A}$
 - Time-Varying current source: $I_S = -3 \sin(t) \text{ A}$
 - Examples: few in real life!
- The ideal current source has known current, but unknown voltage.
- The voltage across the voltage source is defined by the rest of the circuit to which the source is attached.
- Voltage cannot be determined by the value of the current.
- Do not assume that the voltage is zero!

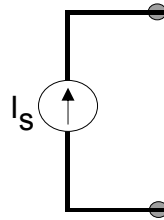

1/22/2004

EE 42 Lecture 2

Air

- Many of us at one time, after walking on a carpet in winter, have touched a piece of metal and seen a blue arc of light.
- That arc is current going through the air. So is a bolt of lightning during a thunderstorm.
- However, these events are unusual. Air is usually a good insulator and does not allow current to flow.
- For simplicity, we will idealize air in the following way: current never flows through air (or a hole in a circuit), regardless of the potential difference (voltage) present.
 - Air is a 0 A current source
 - Air is a very very big (infinite) resistor
- There can be nonzero voltage over air or a hole in a circuit!

1/22/2004

EE 42 Lecture 2