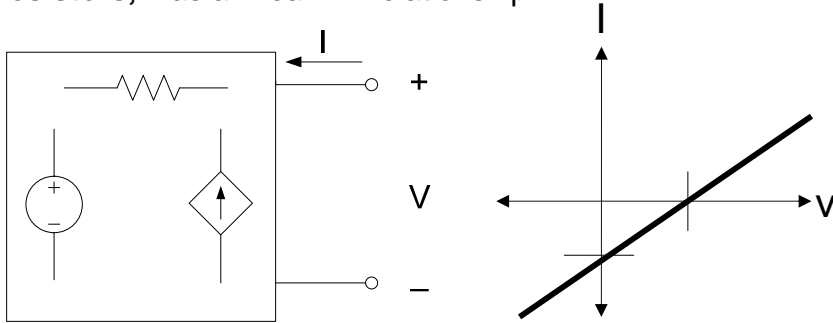


## Lecture 8: Linearity and Equivalent Circuits


Every circuit which is composed of **ideal independent voltage and current sources, linear dependent sources, and resistors**, has a linear I-V relationship.



There is a simpler circuit with the same I-V relationship.
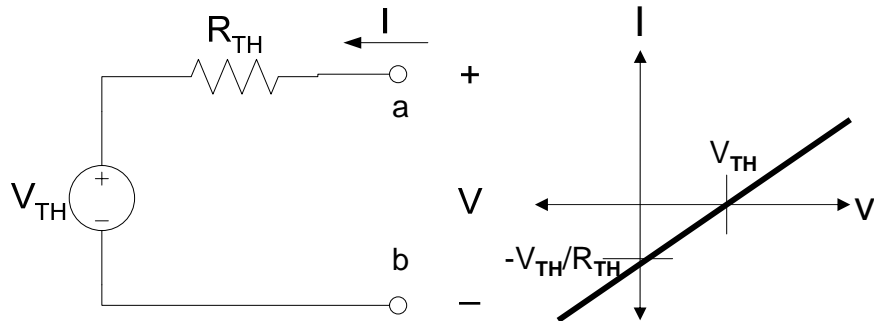
## Thevenin Equivalent Circuit


The **Thevenin equivalent** circuit is composed of a voltage source in series with a resistor:



It can model any circuit except a pure independent current source, through choice of  $V_T$  and  $R_T$ .
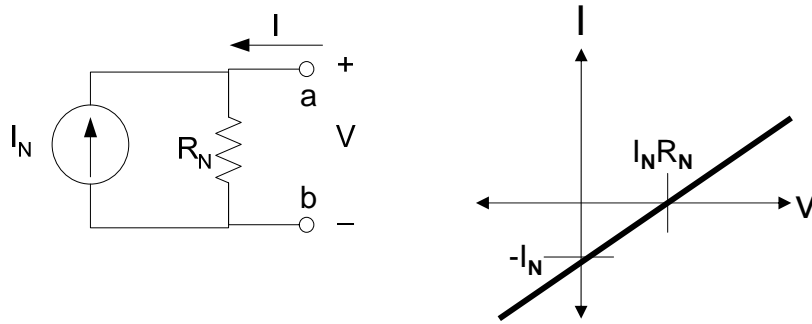
## Norton Equivalent Circuit

The **Norton equivalent** circuit is composed of a current source in parallel with a resistor:



It can model any circuit except a pure independent voltage source, through choice of  $I_N$  and  $R_N$ .

## Two Points Define a Line


To find the Thevenin or Norton equivalent for a circuit, all we need to do is:

- Find two points on the I-V graph for the circuit.
  - Set the voltage  $V$  and find the corresponding  $I$
  - Set the current  $I$  and find the corresponding  $V$
- Find the x-intercept and y-intercept of the graph.
- Find the  $V_{TH}$  and  $R_{TH}$ , or the  $I_N$  and  $R_N$  that replicate this line.

## Our Favorite Two Points on the I-V Graph

- We can find the x-intercept directly by finding the **V** that occurs when **I = 0**.
  - This means finding the V that occurs when there is air between the circuit terminals.
  - This voltage is called the **open-circuit voltage**,  $V_{OC}$ .
  - $V_{TH} = I_N R_N = V_{OC}$
- We can find the y-intercept directly by finding the **I** that occurs when **V = 0**.
  - This means finding the I that occurs when there is a wire between the circuit terminals.
  - This current is called the **short-circuit current**,  $I_{SC}$ .
  - $I_N = V_{TH} / R_{TH} = -I_{SC}$

## Useful Identities

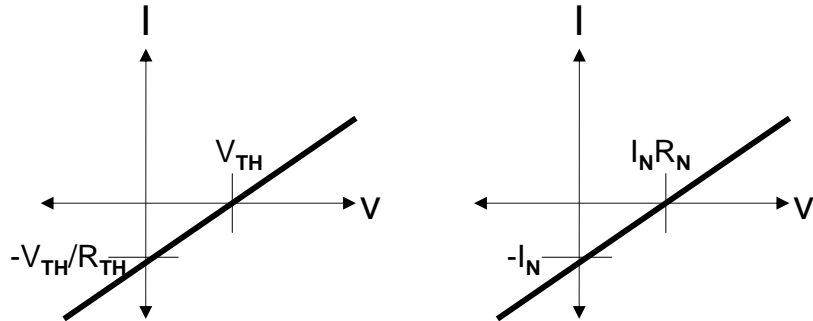

$$V_{TH} = I_N R_N$$


$$R_N = V_{TH} / I_N$$

$$R_{TH} = R_N$$

$$I_N = V_{TH} / R_{TH}$$


$$R_{TH} = V_{TH} / I_N$$

### Example (Nilsson & Riedel text)

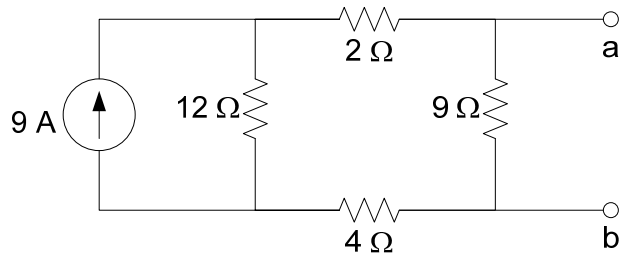

Find the  
Thevenin and  
Norton circuits.

### Example (Nilsson & Riedel text)

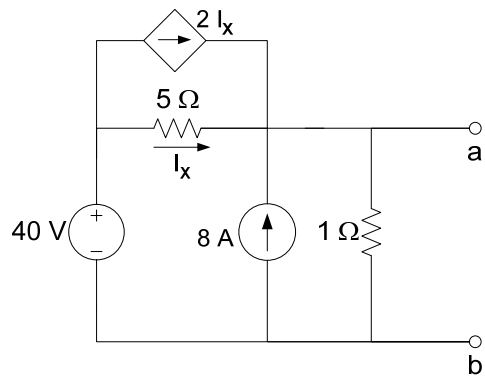

Find the Thevenin  
and Norton circuits.



## $V_{TH}$ and $I_N$ Come From Independent Sources


- If there are no independent voltage or current sources in a circuit,  $V_{TH} = 0 \text{ V}$  and  $I_N = 0 \text{ A}$ .
- If there is no independent voltage or current present in a circuit (only resistors and linear dependent sources), **all currents and voltages in the circuit are zero.**
- In this situation, you know that the I-V graph goes through the origin.
- However, the slope of the graph,  $1/R_{TH}$ , still must be determined. It cannot be found using  $R_{TH} = V_{TH} / I_N$ .



## No Independent Sources? Test for $R_{TH}$

- A simple example of a circuit with no independent sources is a resistor.
- One cannot determine the resistance by measuring voltage and current—a resistor has no voltage or current on its own.
- An ohmmeter applies a test voltage and measures the resulting current to find resistance.
- Do the same to find  $R_{TH}$ : Set  $V$  using an independent voltage source, and measure  $I$ .
- Or, set  $I$  using an independent current source, and measure  $V$ .
- $R_{TH} = V / I$
- Here, you are finding an additional point on the I-V graph.

## Example

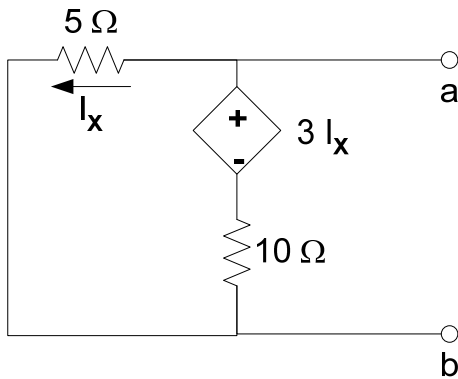


Find the Thevenin and Norton circuits.

## $R_{TH}$ Comes From Resistors and Linear Dependent Sources

- The value of  $R_{TH}$  does not depend on the values of independent voltage and current sources in a circuit.
- I can turn a 12 V source into a -12 V source, or a 0 V source, and the value of  $R_{TH}$  remains the same.
- When looking for  $R_{TH}$  in a circuit that has no dependent sources, it is often easier to:
  - Turn off all independent sources (change voltage sources to 0 V wire and current sources to 0 A air)
  - Simplify remaining resistors using series/parallel combinations to find  $R_{TH}$



## Example

Find  $R_{TH}$ .

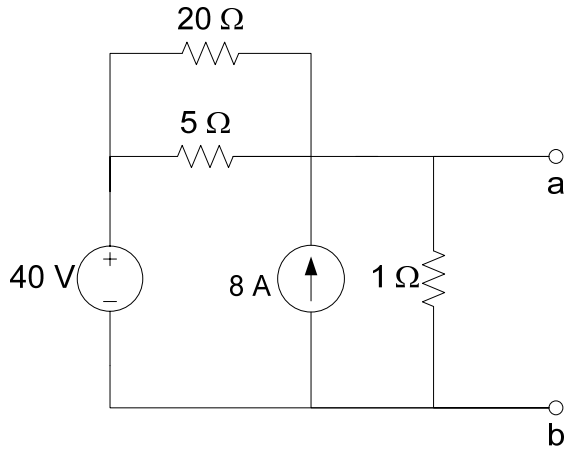

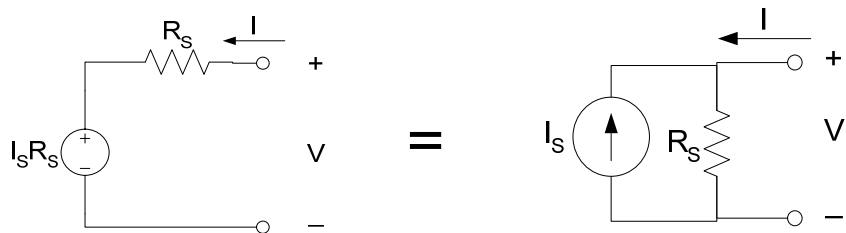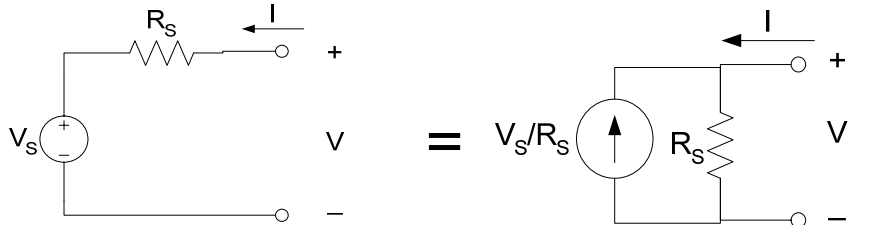
## Source Transformations

One can change back and forth between Thevenin and Norton:



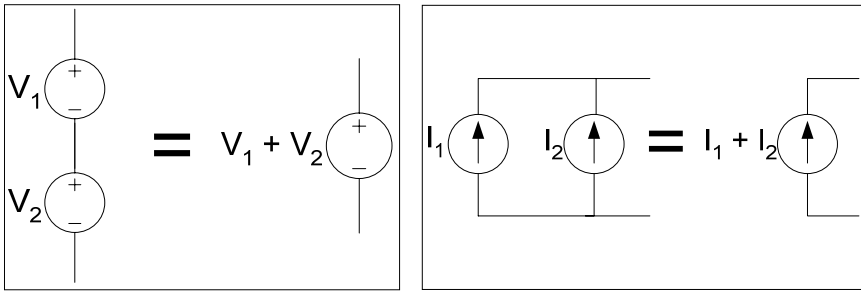
## Source Transformations

One can use source transformations to simplify a circuit just like using series/parallel rules to simplify resistors. Remember that:



## Example (Nilsson & Riedel text)

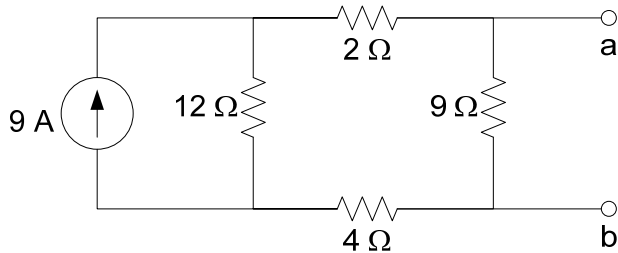

Find the  
Thevenin and  
Norton circuits.