

Name : _____

Name : _____

TA: _____

Section : _____

EECS 40/43

Lab Report: Device Operating Curves

1. Connect a $220\ \Omega$ resistor as the DUT. Sketch the curve displayed on the oscilloscope. Does it matches with the expected value. (Label your plot)
2. Connect the black box as the DUT. Sketch the I-V characteristic of the DUT. From the I-V curve, can you determine what is inside the black box? Check your answer with the TA.

