


Discussion Section 11

Sean Huang

April 16, 2021


Counter Blocks

 - Simple to implement
 - Just an add 1 every clock cycle!
- Register to remember the count



Counter Blocks

 - Simple to implement
 - Just an add 1 every clock cycle!
- Register to remember the count
- Adders are expensive
 - Too general
 - Do we really need an entire adder to just count by 1 each time?



Counter Blocks

- Determine next value combinationaly
- Use the same tools as encoding state machines to design next count logic
 - K-maps, Boolean algebra, Truth tables

a	b	c	d	a'	b'	c'	d'
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	1	0	1	0
1	0	1	0	1	0	1	1
1	0	1	1	1	1	0	0
1	1	0	0	1	1	0	1
1	1	0	1	1	1	1	0
1	1	1	0	1	1	1	1
1	1	1	1	0	0	0	0

Terminal Count (tc)

- Common output of counters
- Flag set when either the counter reaches its maximum/minimum value or a set threshold value
- Useful for using counters in state machines

Booth Recoding

- Do partial products every 2 bits instead of 1 for fewer operations
- Traditional partial products
 - 0
 - A
- Higher-radix has more partial products
 - 0
 - A
 - 2A
 - 3A

B_{k+1}	B_k	B_{k-1}	Action
0	0	0	Add 0
0	0	1	Add A
0	1	0	Add A
0	1	1	Add 2A
1	0	0	Sub 2A
1	0	1	Sub A
1	1	0	Sub A
1	1	1	Add 0

Booth Recoding

- Higher-radix has more partial products, which we can decompose as such
 - $-0 = 0$
 - $-A = A$
 - $-2A = 4A - 2A$
 - $-3A = 4A - A$
- $4A$ is simply A shifted 2 to the left, so this is the same as adding A to the next partial sum

B_{k+1}	B_k	B_{k-1}	Action
0	0	0	Add 0
0	0	1	Add A
0	1	0	Add A
0	1	1	Add 2A
1	0	0	Sub 2A
1	0	1	Sub A
1	1	0	Sub A
1	1	1	Add 0

Booth Recoding Example

- For first bit pair, implied $B_{k-1}=0$
- First pair is 11, $B_{k-1}=0$
 - Perform $4A - A$
 - Put down $-A$ for this partial product

11[0] Sub A

For first bit pair assume previous pair is 00

$$\begin{array}{r} 010101 \\ \times 01101100 \\ \hline -010101 \end{array}$$

Booth Recoding Example

- For first bit pair, implied $B_{k-1}=0$
- First pair is 11, $B_{k-1}=0$
 - Perform $4A - A$
 - Put down $-A$ for this partial product
- Next pair is 10, $B_{k-1}=1$
 - Perform $4A - 2A$
 - Put down $-A$ ($-2A + A$ from last partial)

11[0] Sub A
10[1] Sub A

For first bit pair assume previous pair is 00

$$\begin{array}{r}
 010101 \\
 \times 01101100 \\
 \hline
 -010101 \\
 -010101
 \end{array}$$

Booth Recoding Example

- For first bit pair, implied $B_{k-1}=0$
- First pair is 11, $B_{k-1}=0$
 - Perform $4A - A$
 - Put down $-A$ for this partial product
- Next pair is 10, $B_{k-1}=1$
 - Perform $4A - 2A$
 - Put down $-A$ ($-2A + A$ from last partial)
- Last pair 01, $B_{k-1}=1$
 - Perform $+2A$

11[0]	Sub A	-010101
10[1]	Sub A	-010101
01[1]	Add 2A	+010101
		01000110111

For first bit pair assume previous pair is 00

↓

	0	1	0	1	0	1	
×	0	1	1	0	1	1	0

Baugh-Wooley Multiplier

- Booth recoding does not really work well for signed multiplication

Baugh-Wooley Multiplier

- Must sign extend and subtract last partial for signed multiplication
- Can remove sign extension by adding a 1 at the MSB of each partial product
- Remember to subtract this constant at the end!

$$\begin{array}{r}
 \begin{array}{cccccccc}
 & & & & & & a_3 & a_2 & a_1 & a_0 \\
 & & & & & & \times & b_3 & b_2 & b_1 & b_0 \\
 \hline
 & & & & & & & a_2 b_0 & a_1 b_0 & a_0 b_0 \\
 + & & & & & & \overline{a_3 b_0} & a_2 b_0 & a_1 b_0 & a_0 b_0 \\
 + & & & & & & \overline{a_3 b_1} & a_2 b_1 & a_1 b_1 & a_0 b_1 \\
 + & & & & & & \overline{a_3 b_2} & a_2 b_2 & a_1 b_2 & a_0 b_2 \\
 - & & & & & & \overline{a_3 b_3} & a_2 b_3 & a_1 b_3 & a_0 b_3 \\
 - & & & & & & 1 & 1 & 1 & 1 \\
 \hline
 & & & & & & c_7 & c_6 & c_5 & c_4 & c_3 & c_2 & c_1 & c_0
 \end{array}
 \end{array}$$

Appendix A

Why the sign extension can be ignored in Baugh–Wooley

Baugh-Wooley Multiplier

- Consider both the case of a negative (2's complement) and positive number

101001

001001

Baugh-Wooley Multiplier

- Consider both the case of a negative (2's complement) and positive number
- Sign extend by a few bits

1111111111111111101001

000000000000000001001

Baugh-Wooley Multiplier

- Consider both the case of a negative (2's complement) and positive number
- Sign extend by a few bits
- Add 1 at the original sign bit

1111111111111111101001
+1

000000000000000001001
+1

Baugh-Wooley Multiplier

- In the positive case
 - Extension all 0, can ignore all except inverted sign bit
- In the negative case
 - 1 carries to next sign extension bit
 - Carry chains all the way until all sign extension bits are 0
 - Drop carry out (won't affect final sum)

← +1
11111111000000001001

101001
+1