

Discussion Section 4

Sean Huang

February 12, 2021

Karnaugh Map Example

Simplify this expression:

$$\begin{aligned} out = & a'b'c'd' + a'b'c'd + a'b'cd' + a'bc'd' + \\ & + a'bc'd + a'bcd + ab'c'd' + ab'cd' \\ & + ab'cd + abc'd + abcd' + abcd \end{aligned}$$

Karnaugh Map Example

Simplify this expression:

$$\begin{aligned} out = & a'b'c'd' + a'b'c'd + a'b'cd' + a'bc'd' + \\ & + a'bc'd + a'bcd + ab'c'd' + ab'cd' \\ & + ab'cd + abc'd + abcd' + abcd \end{aligned}$$

a	b	c	d	out
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Karnaugh Map Example

Simplify this expression:

$$\begin{aligned} out = & a'b'c'd' + a'b'c'd + a'b'cd' + a'bc'd' + \\ & + a'bc'd + a'bcd + ab'c'd' + ab'cd' \\ & + ab'cd + abc'd + abcd' + abcd \end{aligned}$$

#	a	b	c	d	out
0	0	0	0	0	1
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	0
10	1	0	1	0	1
11	1	0	1	1	1
12	1	1	0	0	0
13	1	1	0	1	1
14	1	1	1	0	1
15	1	1	1	1	1

Karnaugh Map Example

- Truth Table maps to K-map
 - Can fill out K-map “in order”
- Squares in K-map not in same order as TT
 - Gray code sequencing inputs reorders terms
- Each box containing a 1 is a minterm

		CD			
		00	01	11	10
AB	00	0	1	3	2
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10


Karnaugh Map Example

$$\begin{aligned} & \begin{array}{cccc} & 0 & 1 & 2 & 4 \\ \text{out} = & a'b'c'd' & + a'b'c'd & + a'b'cd' & + a'bc'd' \\ & 5 & 7 & 8 & 10 \\ & + a'bc'd & + a'bcd & + ab'c'd' & + ab'cd' \\ & 11 & 13 & 14 & 15 \\ & + ab'cd & + abc'd & + abcd' & + abcd \end{array} \end{aligned}$$

		CD			
		00	01	11	10
AB	00	1	1	0	1
	01	1	1	1	0
	11	0	1	1	1
	10	1	0	1	1


Karnaugh Map Example

 - Group minterms together
 - Groups also called *implicants*
 - Each group is a simplified product term omitting one or more variable
 - Implicant groups can wrap around edges/corners
- $out = bd + b'd' + ac + a'c'$
- When all minterms are grouped and no bigger groups can be made, they are known as *prime implicants*




Karnaugh Maps and Glitches

 - Prime implicants that do not overlap are called *essential prime implicants*
 - Both terms cannot be true at the same time
- Output works fine if both AND gates are identical and arrive at OR at the same time
 - This is unrealistic. Real gates have varying delays




Karnaugh Maps and Glitches

 - Prime implicants that do not overlap are called *essential prime implicants*
 - Both terms cannot be true at the same time
- Creates possibility of a glitch
 - Also known as a *static hazard*
- If one term evaluates to false before the other term evaluates to true, output can momentarily glitch



Karnaugh Maps and Glitches

 
- Prime implicants that do not overlap are called *essential prime implicants*
 - Both terms cannot be true at the same time
- Creates possibility of a glitch
 - Also known as a *static hazard*
- If one term evaluates to false before the other term evaluates to true, output can momentarily glitch
- Can avoid with redundant terms
 - Output “covered” by additional term



Finite State Machines


Finite State Machines

 - Simple automata
- All sequential systems can be modeled as an FSM
- Useful abstraction of stateful behavior
- Represented with State Transition Diagrams
 - Describes trajectory of state machine depending on inputs
 - Usually traverse an edge every clock cycle




Simple Example (Traffic Lights)

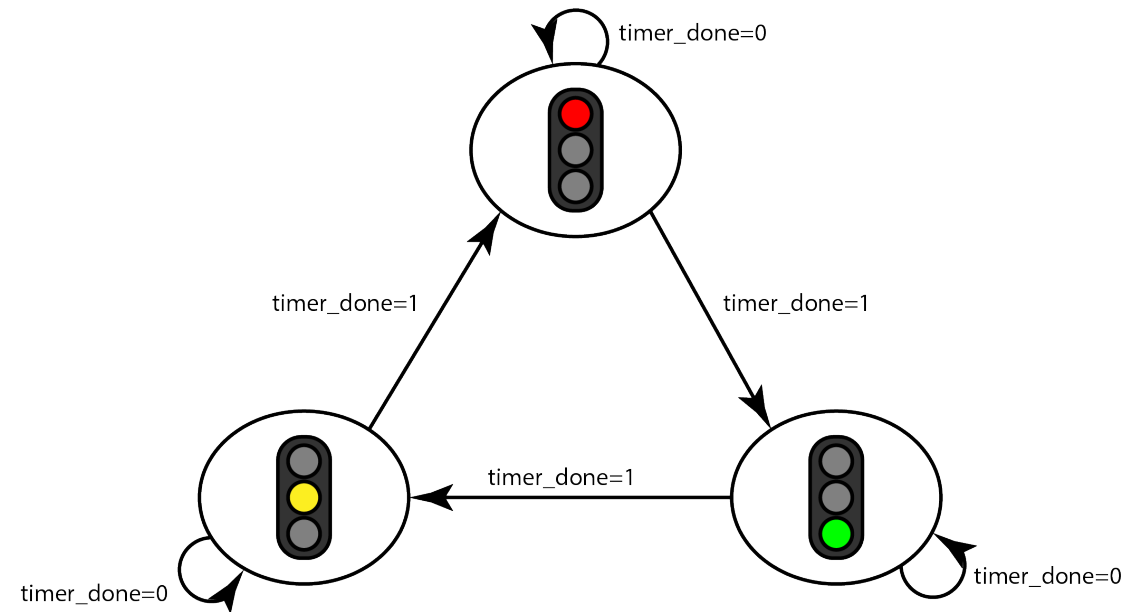- Simple timer-based traffic light system
- Each light is a particular state
 - Light changes once timer runs out
- Each edge depends on same input signal
 - Which state is next depends on current state



Less Simple Example (Traffic Lights)

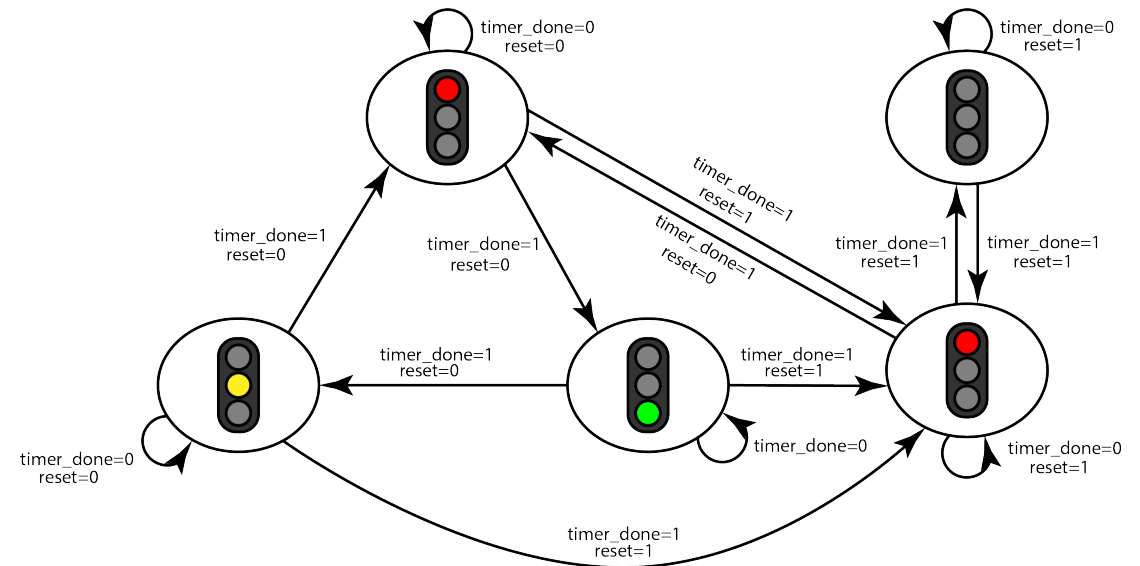- Reset to a flashing red light until reset goes low again
 - Add “off” state, and new “red_rst” state
 - New states flash back and forth until reset goes low
 - All other states reset to “red_rst” state until ready to continue normal operation





Implementing FSMs

- FSMs implemented in hardware with registers and logic
- How to keep track of current state?
- Could store a number in the registers
 - What format to use?
 - Binary
 - One-hot
 - Gray coding
 - Something else?


Binary Encoding

  - Probably first idea you come to
- Encode each state as binary number
- Next state depends on current state code and inputs
- Code efficiently uses registers 😊
 - Only need $\log_2(N_States)$ bits
- Per-bit logic can get complicated 😞
 - State transitions may involve changing several bits
 - Outputs may need to be decoded




Gray Code Encoding

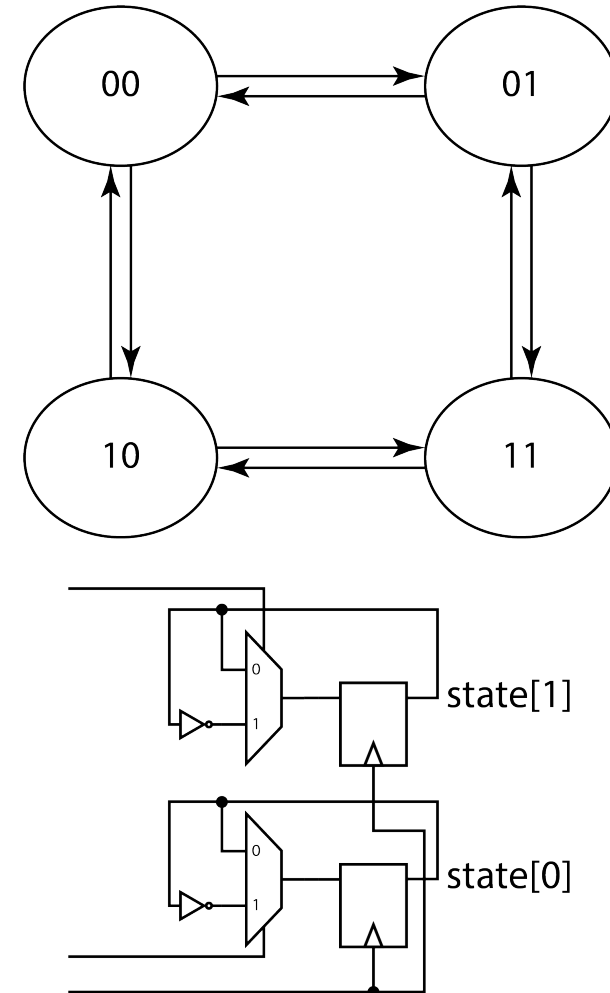- Modification on Binary Encoding
- Only allow one bit to change at a time
- Simpler per-bit logic 😊
 - Basically just decide which bit to change at each edge




Gray Code Encoding

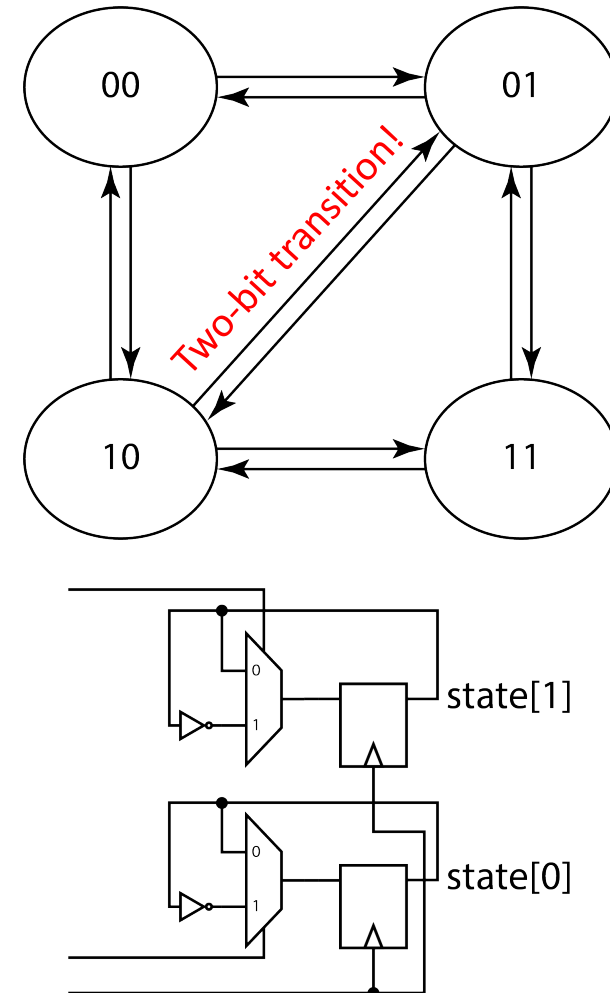- Modification on Binary Encoding
- Only allow one bit to change at a time
- Simpler per-bit logic 😊
 - Basically just decide which bit to change at each edge
- Not all state diagrams work 😞
 - Some state changes cannot be Gray coded





One-Hot Encoding

 - Only 1 wire high at a time
- Each wire represents a state
- Easier to design and debug 😊
 - Can design per-bit logic in isolation
 - Each register responsible for a state, easy to find current state from waveform/log
 - Maps well to FPGAs
- Not register efficient 😞
 - Per-bit logic can get even messier than binary
 - Needs N_{States} registers/wires



Counters and State Machines

 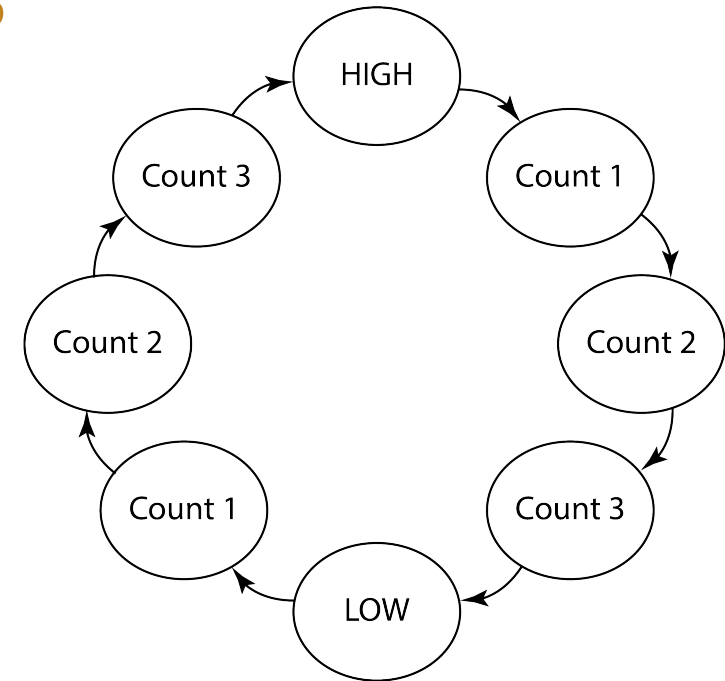- Divide-by-4 Clock Divider
 - Output toggles every 4 clock cycles
 - Many linear state transitions
- Do we really need a state for all the counting steps?



Counters and State Machines

- Replace counting states with a counter
 - Counter sets flag when finished counting
- Counters and Accumulators commonly used with state machines
 - Repetitive and linear steps can be delegated to a counter/accumulator

