

EECS 151/251A Homework 8

Due Monday, April 12th, 2021

For this Homework

Please include a short (1-2 sentence) explanation with your answer, unless otherwise noted.

Problem 1: Loop Unrolling

Let's take another look at the Parity Checker FSM from Lecture 7. Most FSMs are loops, so we can also apply the same loop unrolling method to them as well.

- (a) Modify the Parity Checker FSM to be a Mealy Machine implementation. Show a circuit diagram of your modified design.
- (b) The input to the Parity Checker now arrives 3 bits at a time. Apply the loop unrolling technique to increase the throughput of the design. Show a circuit diagram of your modified design.
- (c) The unrolled loop has a long critical path from the registered feedback value back to the input as this must pass through all the parity check stages. Is there a way you can modify the design to have a shorter critical path? Discuss how you would make the modification. (*Hint: Tree structures*)

Problem 2: C-Slowing

In digital signal processing, a common technique is to employ filter banks, which are bandpass filters used in parallel with the same input stream to decompose the input into its frequency components. One such filter topology is the biquad filter (Wikipedia Article), which is so named as its transfer function is the ratio of two quadratic functions (i.e. it has 2 poles and 2 zeroes). The filter bank in question is thus made up of several of these filters all working in parallel.

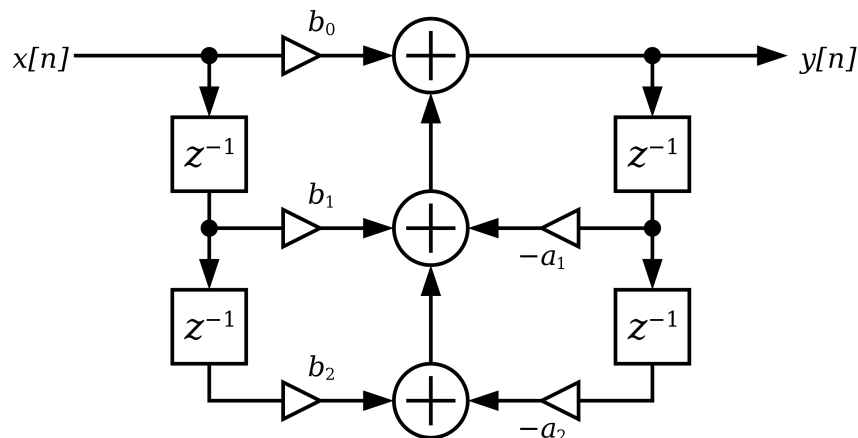


Figure 1: Block Diagram of a Digital Biquad Filter

Where z^{-1} represents 1 cycle of delay, and the triangle amplifiers represent multiplication.

- What is the critical path of the biquad filter design?
- Assuming the multipliers and adders cannot be pipelined, how would you apply C-slowness to maximize throughput? What is the optimal value for C?
- Show a block diagram of your design, including any additional blocks/circuits you need to achieve the C-slowness.

Problem 3: FIFO Redesign

A known issue with the basic FIFO design is that a naïve solution may have an intolerably long delay from clock edge to expressing the full/empty signal. This could potentially be an issue for both the producer and the consumer of the FIFO. On the producer side, the logic for generating the next data packet may be long enough that it needs to see a valid full flag near the beginning of the clock cycle. Likewise, the consumer may also need to know if the queue is empty early on in the clock cycle.

For the parts below, the memory blocks will be simple dual port (single asynchronous read, single synchronous write). The read/write pointers are implemented with a wrap-around counter that you should represent as a fixed block (i.e. the counter cannot be redesigned). The FIFO is instantiated with the following interface:

```

module fifo #(
    parameter N
) (
    input clk,
    input rst,
    input [N-1:0] enqueue_bits,
    output [N-1:0] dequeue_bits,

```

```
    input enqueue_val,
    output enqueue_rdy,
    output dequeue_val,
    input dequeue_rdy,
    output full,
    output empty
)
```

- (a) Show a block diagram of a naïve 8-bit wide, 16-entry deep FIFO that does address the long full/empty flag delay.
- (b) Modify your design from part (a) to solve the long delay problem. Explain your design decisions and the solution that your improved FIFO implements in 4-5 sentences.

Problem 4: Cache Review

Design a 64x64 fully associative memory with 64-bit words (1 word per line) using flip-flops and logic gates. The memory address is 8-bits long, however, so the processor may miss when requesting data or writing data to the memory. The memory will behave in the following way when encountering such a situation:

- In the case of a read miss, the memory is to express a `NO_DATA` flag to indicate to the processor that the memory address is invalid.
- Each memory location has a corresponding `valid` bit. When data is written to a memory location, its corresponding `valid` bit is set. The memory initializes with all `valid` unset.
- If the processor attempts to write to the memory, it will overwrite the first (in ascending order of memory line locations) non-`valid` line in the memory.
- On a write, if all the memory locations are valid, the memory will use a replacement policy called "not recently used" (an approximation of "least recently used"). The policy is implemented as follows:
 - Whenever a memory location is accessed for a read, a corresponding `used` bit will be set for that location.
 - A shift register will rotate through the memory locations in descending order, pointing to a single memory line at a time.
 - At the beginning of the clock cycle, the memory line that the shift register is pointing at will have its `used` bit unset.
 - When writing to a fully valid memory, the first (in ascending order) non-used line is overwritten.
- The "find first row" operation for both finding the first invalid line or first non-used line should happen combinationaly (i.e. within 1 clock cycle). *Note: You don't need to worry about the delay for this circuit, just make it as simple as possible.*

For this problem please turn in:

- A block diagram of your design. You may represent the flip-flops in the memory as a large block, but indicate how the flip-flops are distributed (data bits, valid/used bits, tag, etc.). The "find first row" operation logic should be drawn at the gate level using basic logic gates (4 input maximum) and MUXes. Also, be sure to indicate the input and output pins clearly.
- An overview (1-2 paragraphs) of how the memory operates, making note of the design decisions you made.