



**EECS 151/251A**

**Spring 2021**

**Digital Design and Integrated  
Circuits**

Instructor:

John Wawrzynek

**Lecture 14: RISC-V Part 2**


# Announcements

- Virtual Front Row today, 3/4:
  - *Tony Kam*
  - *Ben Tait*
  - *Robin Chu*
  - *Neil Kulkarni*
  - *Robert Puccinelli*
- HW6 posted (due Monday)
- Midterm Reminder
  - Format TBD
- No HW next week

	2/25	Circuit Timing Part 2 ( <a href="#">slides</a> )( <a href="#">video</a> )	
7	3/2	RISC-V Microarchitecture and Implementation	Discussion 7
	3/4	RISC-V Part 2	
8	3/9	Exam 1 Review	Discussion 8
	3/11	No Class - Exam 6-9PM	
9	3/16	Power and Energy	Discussion 9
	3/18	Memory Blocks 1	
10	3/23	Spring Recess	
	3/25	Spring Recess	

# Implementing Branches

*Uses the “B-type” instruction format*

 

- RISC-V Assembly Instruction, example:

**beq rs1, rs2, label**


*if rs1==rs2 pc ← pc + offset // offset computed by compiler/assembler and stored in the immediate field(s)*

*example:*


**beq x1, x2, L1**

- B-format is mostly same as S-Format, with two register sources (rs1/rs2) and a 12-bit immediate
- But now immediate represents values -4096 to +4094 in 2-byte increments
- The 12 immediate bits encode *even* 13-bit signed byte offsets (lowest bit of offset is always zero, so no need to store it)


# Review: Adding *sw* to datapath

 


# Adding branches to datapath

 

# Adding branches to datapath

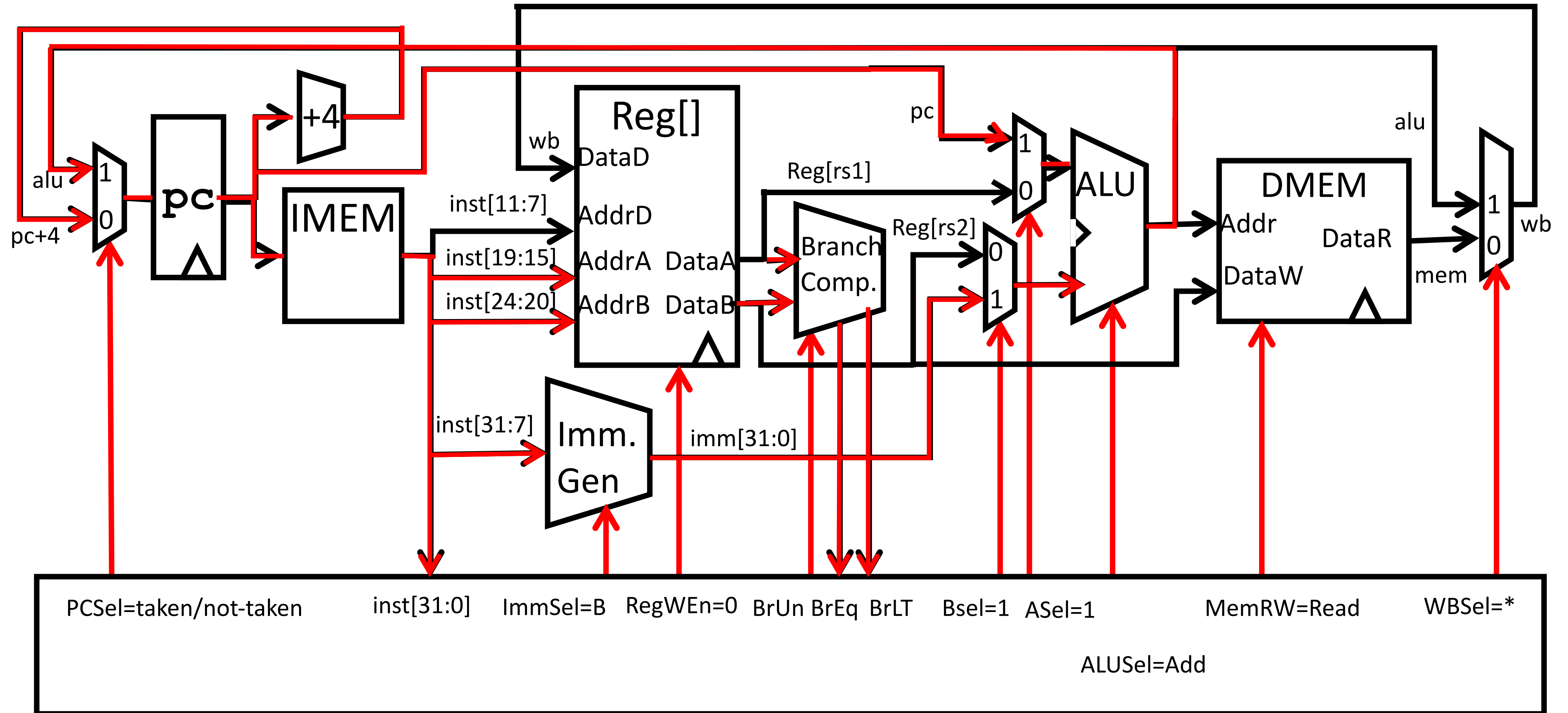


# Branch Comparator

 


- $\text{BrEq} = 1$ , if  $A=B$
- $\text{BrLT} = 1$ , if  $A < B$
- $\text{BrUn} = 1$  selects unsigned comparison for  $\text{BrLT}$ ,  $0=\text{signed}$
- BGE branch:  $A \geq B$ , if  $!(A < B)$

# RISC-V Immediate Encoding

## Instruction Encodings, inst[31:0]

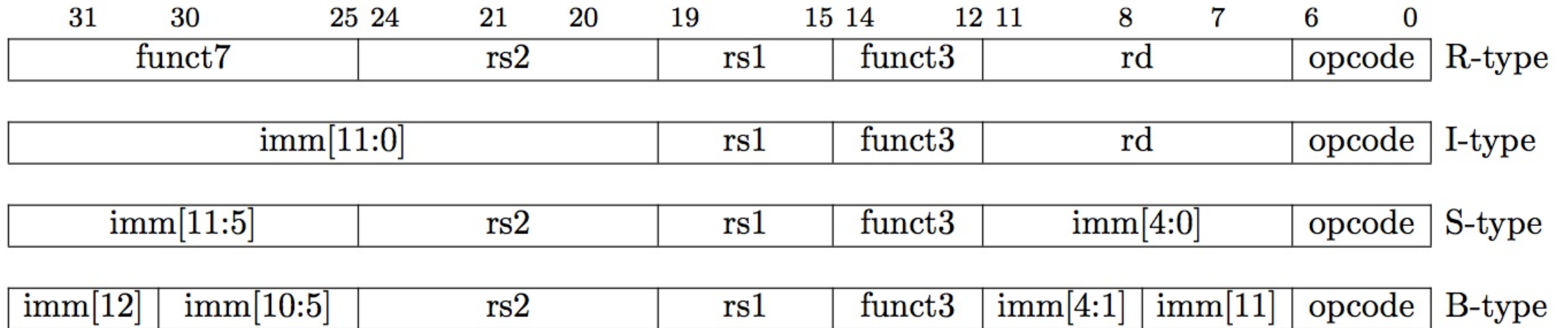

## 32-bit immediates produced, imm[31:0]

 


← Upper bits sign-extended from inst[31] always

Only bit 7 of instruction changes role in immediate between S and B



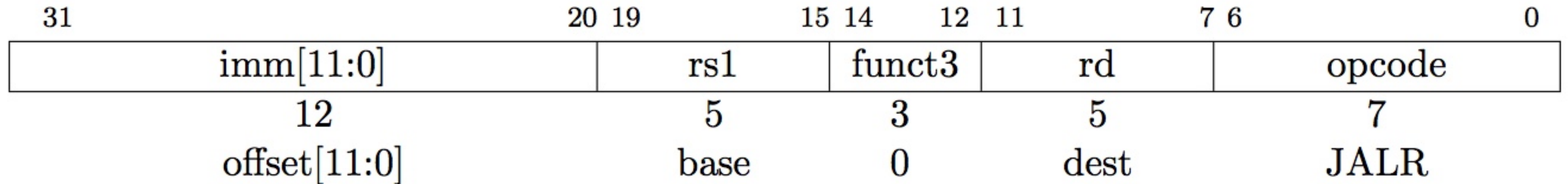
# Implementing JALR Instruction (I-Format)




- JALR rd, rs, immediate
  - Writes PC+4 to Reg[rd] (return address)
  - Sets PC = Reg[rs1] + offset
  - Uses same immediates as arithmetic and loads
    - **no** multiplication by 2 bytes


# Review: Adding branches to datapath

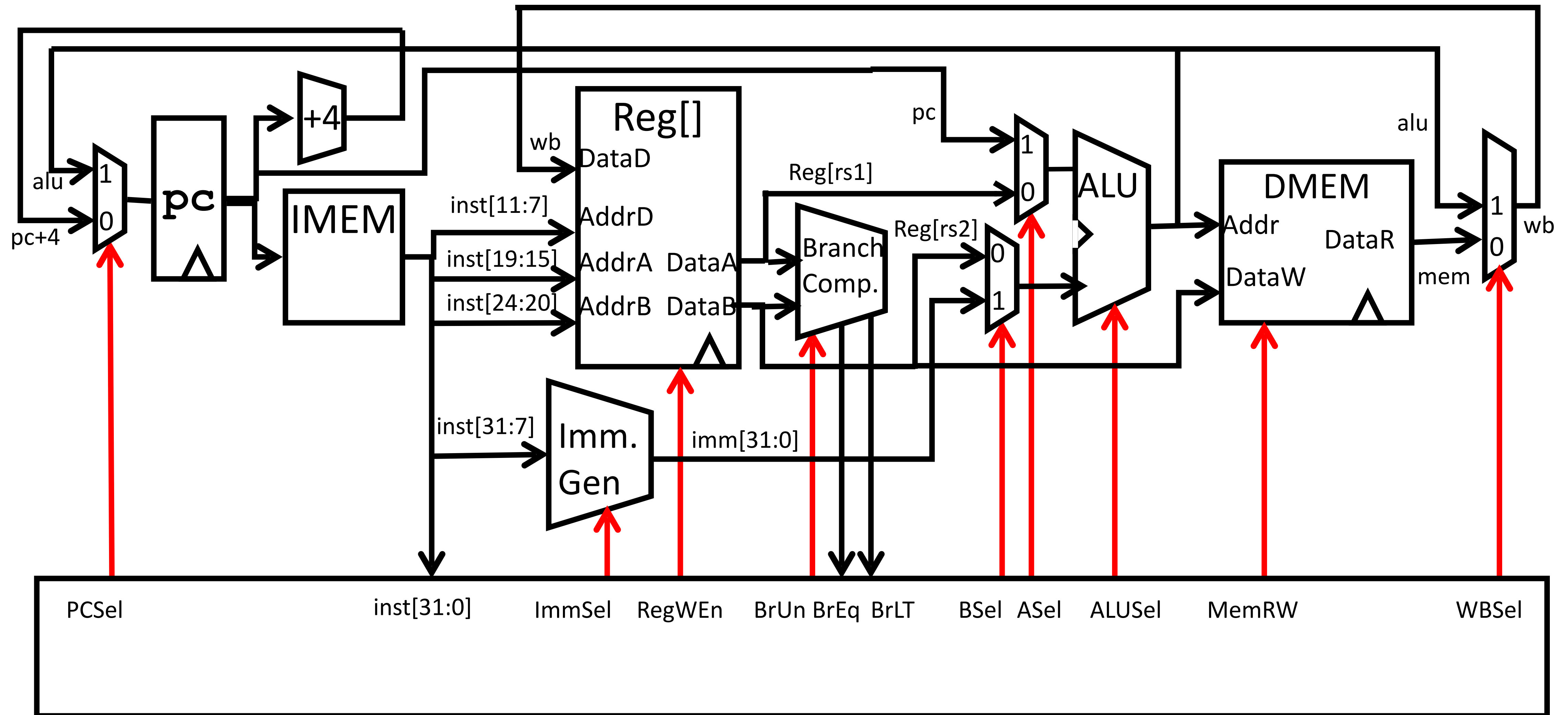

# Adding jalr to datapath

 


# Adding jalr to datapath

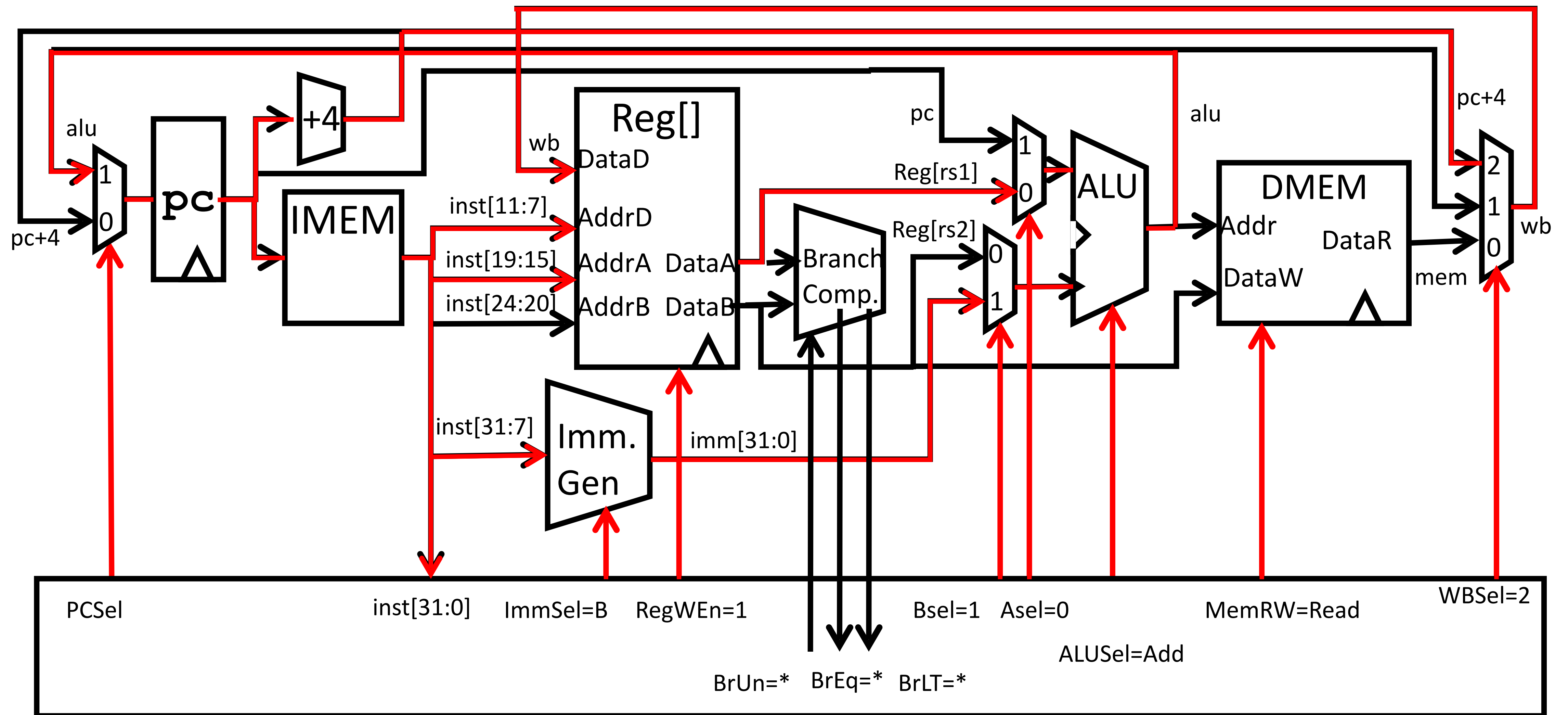


# Implementing jal Instruction

*Uses the “J-type” instruction format*

 


- JAL saves PC+4 in Reg[rd] (the return address)
- Set PC = PC + offset (PC-relative jump)
- Target somewhere within  $\pm 2^{19}$  locations, 2 bytes apart
  - $\pm 2^{18}$  32-bit instructions
- Immediate encoding optimized similarly to branch instruction to reduce hardware cost


# Adding jal to datapath

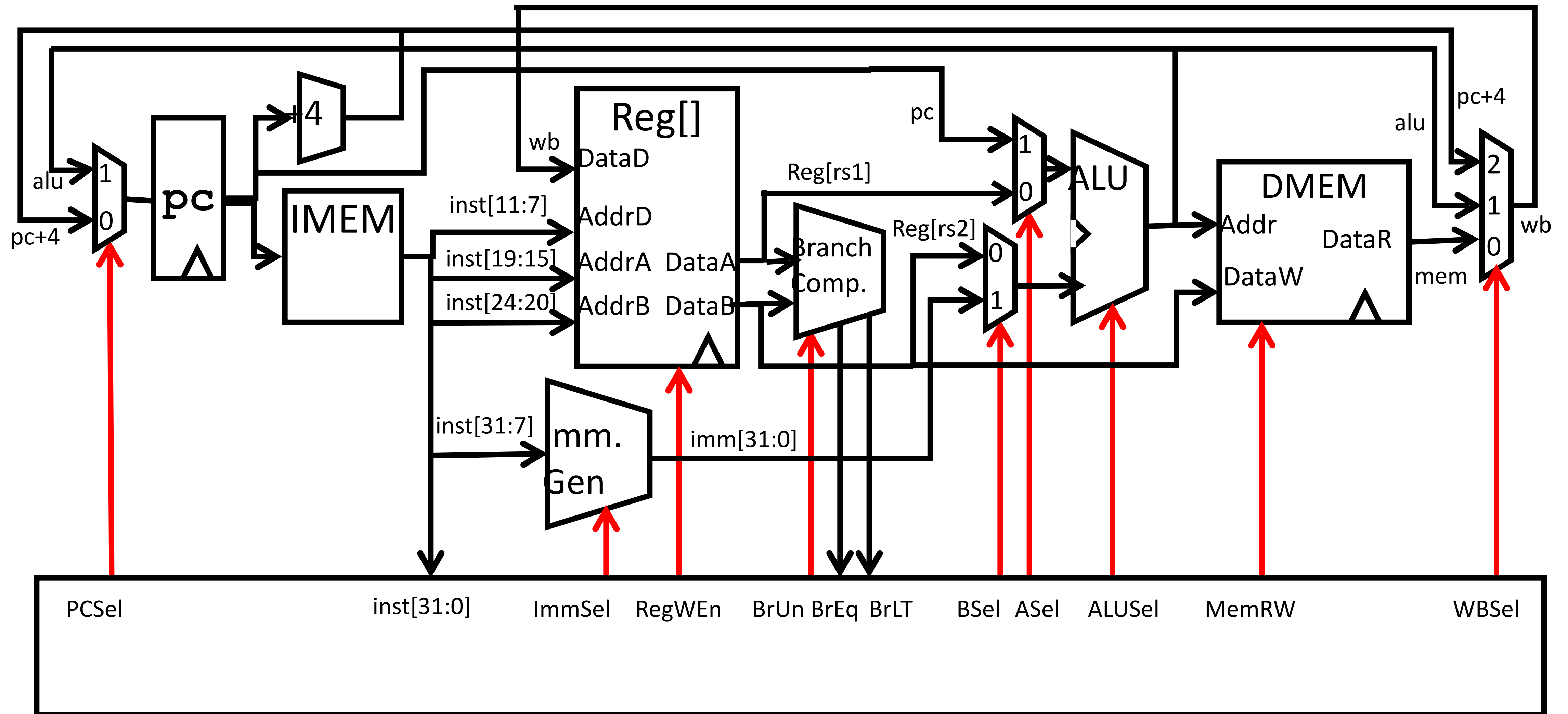

# Adding jal to datapath

 

# Single-Cycle RISC-V RV32I Datapath

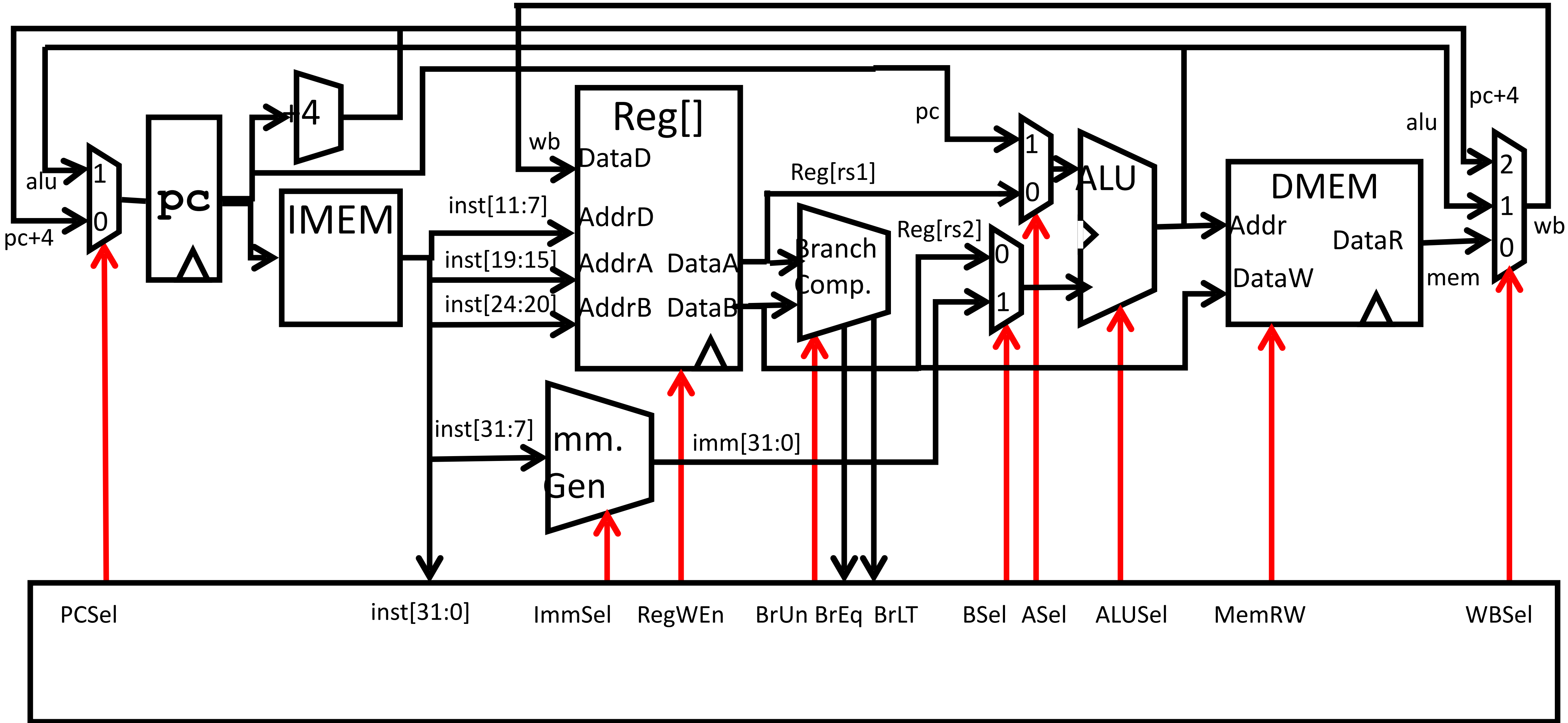



# Controller Implementation:

- Control logic works really well as a case statement...

```
always @* begin
    op = instr[26:31];
    imm = instr[15:0]; ...

    reg_dst = 1'bx;    // Don't care
    reg_write = 1'b0; // By default don't write
    ...
    case (op)
        6'b000000: begin reg_write = 1; ... end
        ...
    endcase
end
```



## Processor Pipelining

# **Review: Processor Performance**

**Program Execution Time**

**= (# instructions)(cycles/instruction)(seconds/cycle)**

**= # instructions x CPI x  $T_C$**



# Single-Cycle Performance

- *Single-cycle critical path:*

$$T_c = t_{q\_PC} + t_{mem} + \max(t_{RFread}, t_{sext} + t_{mux}) + t_{ALU} + t_{mem} + t_{mux} + t_{RFsetup}$$

- *In most implementations, limiting paths are:*

- *memory, ALU, register file.*


- $T_c = t_{q\_PC} + 2t_{mem} + t_{RFread} + t_{mux} + t_{ALU} + t_{RFsetup}$

# Pipelined Processor


- Use temporal parallelism
- Divide single-cycle processor into 5 stages:
  - Fetch
  - Decode
  - Execute
  - Memory
  - Writeback
- Add pipeline registers between stages

# Single-Cycle vs. Pipelined Performance



## Single-Cycle

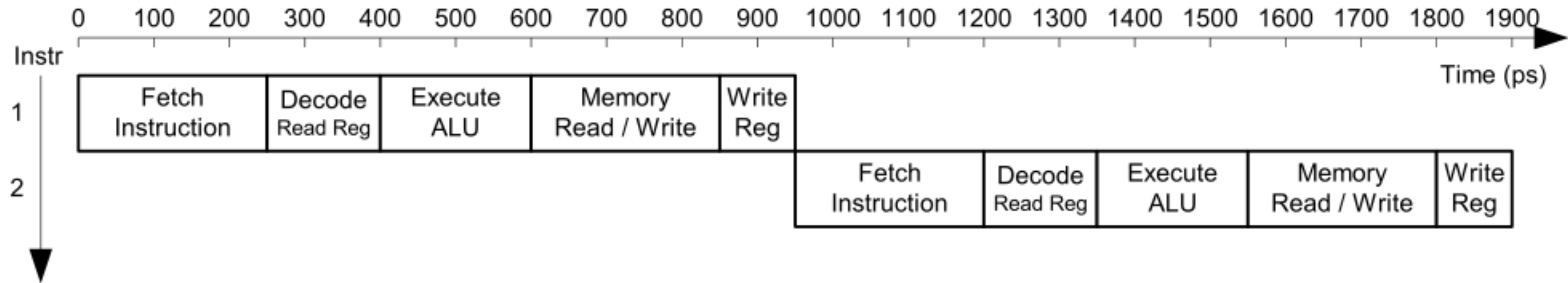

## Pipelined

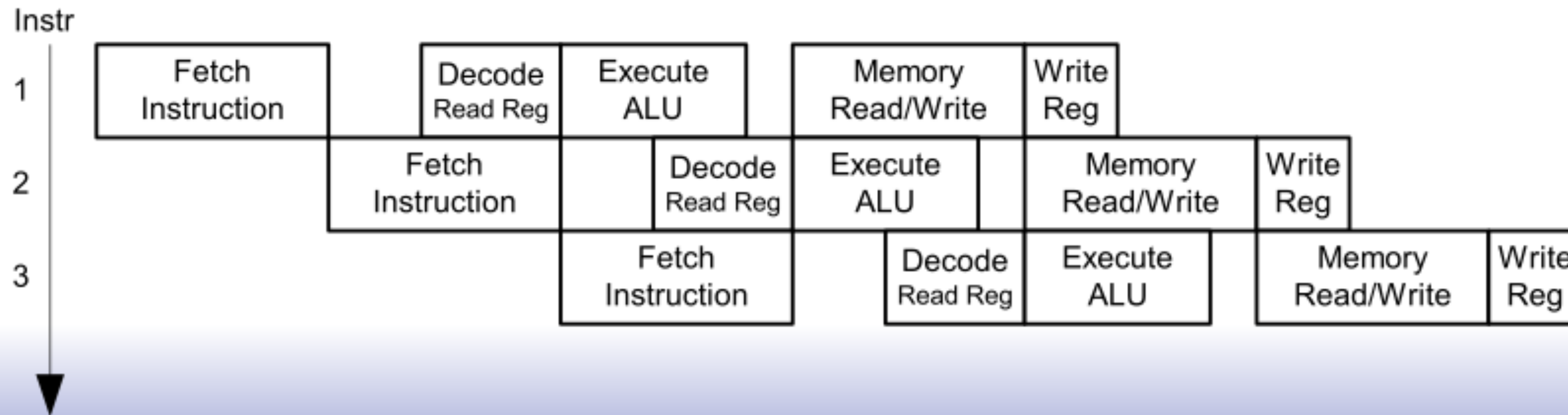


# Single-Cycle and Pipelined Datapath

 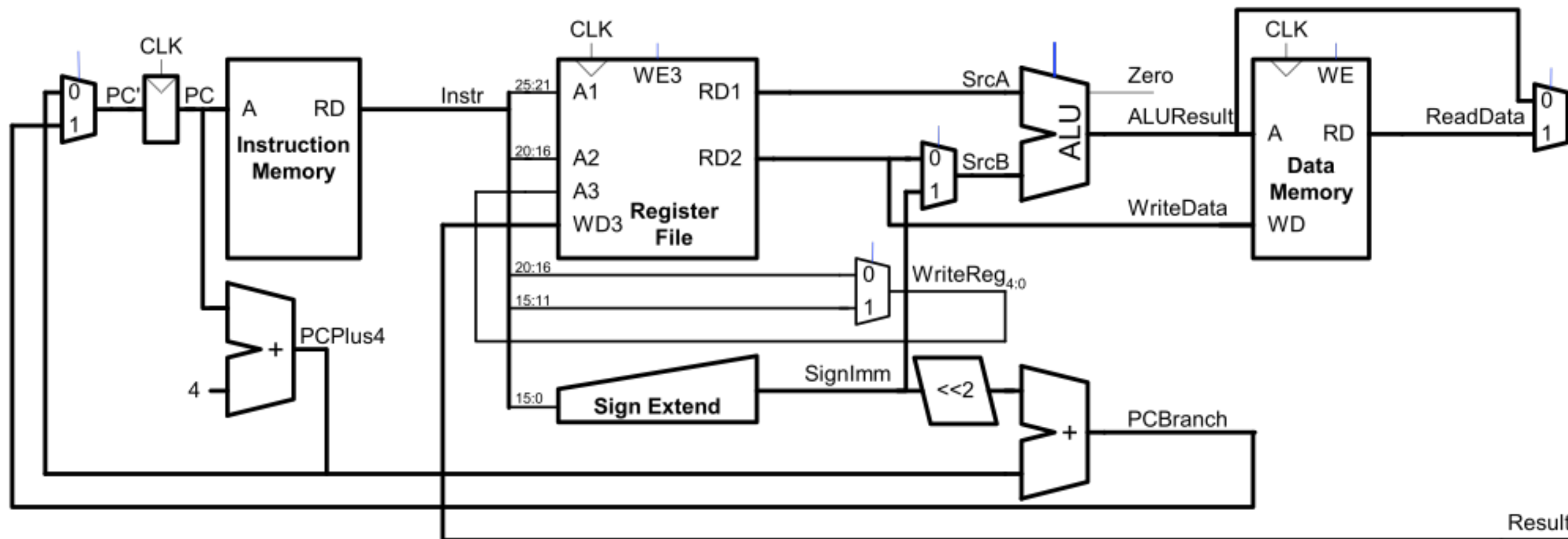


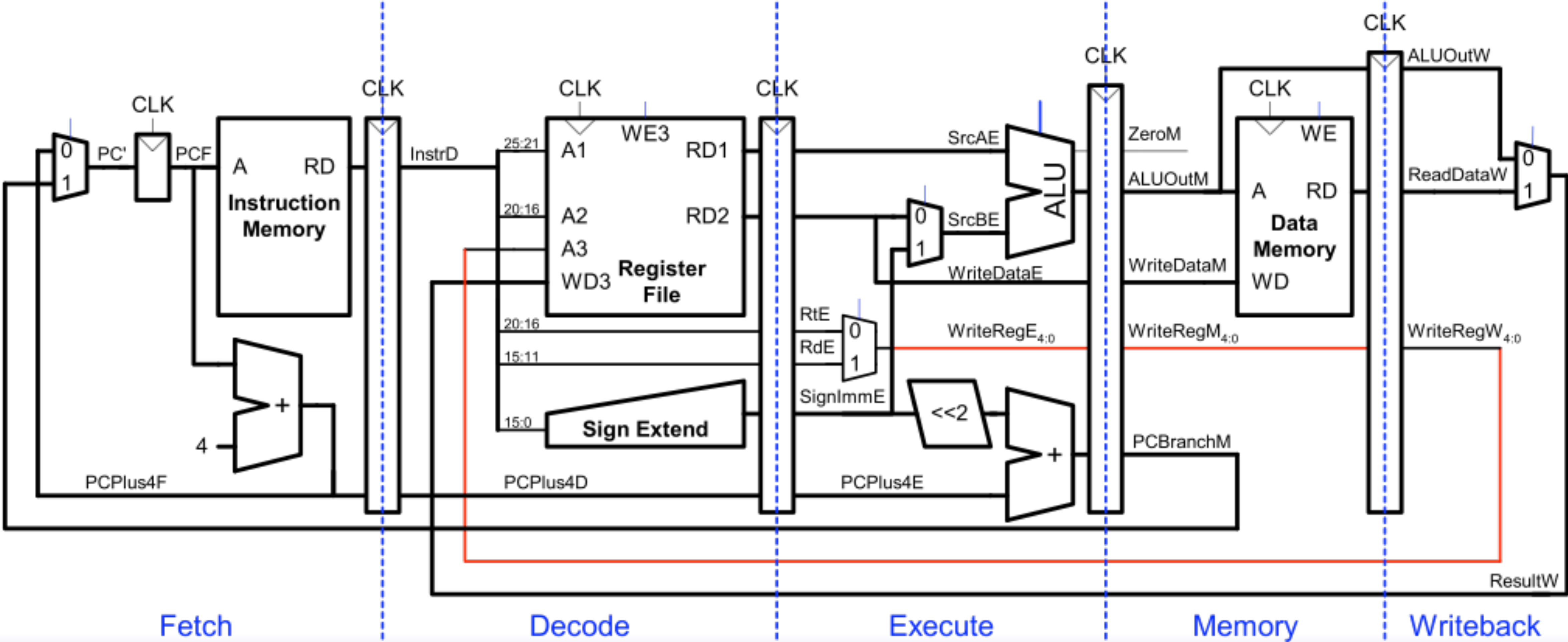
# Corrected Pipelined Datapath

- *WriteReg must arrive at the same time as Result*





# Pipeline Hazards

- ❑ Occurs when an instruction depends on results from previous instruction that hasn't completed.
- ❑ Types of hazards:
  - **Data hazard:** register value not written back to register file yet
  - **Control hazard:** next instruction not decided yet (caused by branches)

*We need to design ways to avoid hazards, else we pay the price in CPI (cycles per instruction) and processor performance suffers.*

# Processor Pipelining

*Deeper pipeline example.*

IF1	IF2	ID	X1	X2	M1	M2	WB	
	IF1	IF2	ID	X1	X2	M1	M2	WB

*Deeper pipelines => less logic per stage => high clock rate.*

*But*

*Deeper pipelines\* => more hazards => more cost and/or higher CPI.*

*Cycles per instruction might go up because of unresolvable hazards.*

*Remember, Performance = # instructions X Frequency<sub>clk</sub> / CPI*

*\*Many designs included pipelines as long as 7, 10 and even 20 stages (like in the [Intel Pentium 4](#)). The later "Prescott" and "Cedar Mill" Pentium 4 cores (and their [Pentium D](#) derivatives) had a 31-stage pipeline.*

*How about shorter pipelines ... Less cost, less performance (but higher cost efficiency)*



## 3-Stage Pipeline

# 3-Stage Pipeline (used for FPGA/ASIC project)

*The blocks in the datapath with the greatest delay are: IMEM, ALU, and DMEM. Allocate one pipeline stage to each:*



*Most details you will need to work out for yourself. Some details to follow ...  
In particular, let's look at hazards.*

# 3-stage Pipeline

## Data Hazard


add x5, x3, x4	I	X	M		
add x7, x6, x5		I	X	M	

*reg 5 value needed here!*

*reg 5 value updated here*

*The fix:*

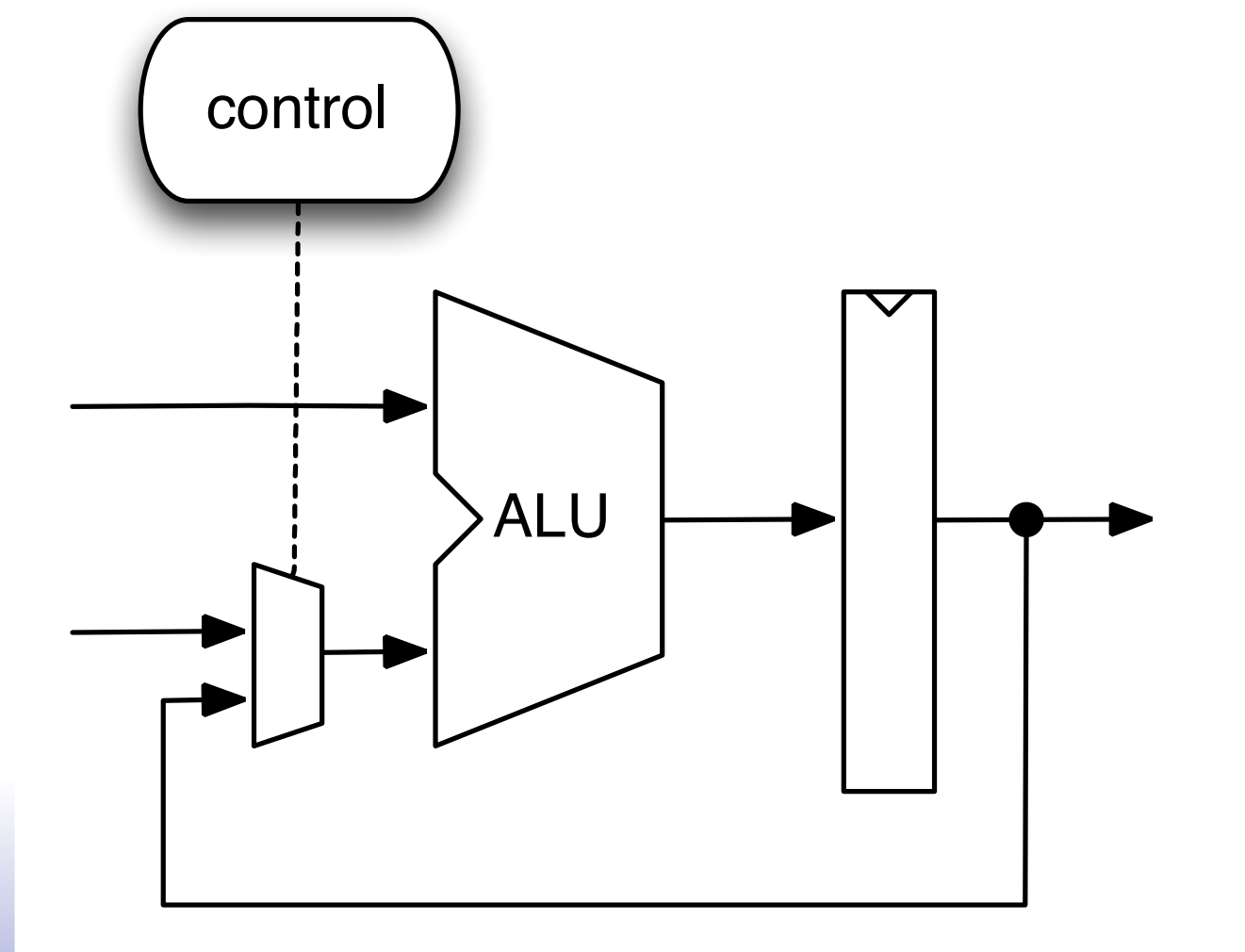Selectively forward ALU result back to input of ALU.



- *Need to add mux at input to ALU, add control logic to sense when to activate. Check reference for details.*

# 3-stage Pipeline

## Load Hazard

<b>lw x5, offset(x4)</b>	<b>I</b>	<b>X</b>	<b>M</b>		
<b>add x7, x6, x5</b>		<b>I</b>	<b>X</b>	<b>M</b>	

*value needed here!*

*Memory value known here. It is written into the regfile on this edge.*

*The fix: Delay the dependent instruction by one cycle to allow the load to complete, send the result of load directly to the ALU (and to the regfile). **No delay if not dependent!***

<b>lw x5, offset(x4)</b>	<b>I</b>	<b>X</b>	<b>M</b>		
<b>add x7, x6, x5</b>		<b>I</b>	<b>nop</b>	<b>nop</b>	
<b>add x7, x6, x5</b>			<b>I</b>	<b>X</b>	<b>M</b>



# 3-stage Pipeline

## Control Hazard

beq x1, x2, L1	I	X	M		
add x5, x3, x4		I	X	M	
add x6, x1, x2			I	X	M
L1: sub x7, x6, x5				I	X

*but needed here!*

*branch address ready here*

*Several Possibilities:\**

- The fix:*
- 1. Always delay fetch of instruction after branch*
  - 2. Assume branch “not taken”, continue with instruction at PC+4, and correct later if wrong.*
  - 3. Predict branch taken or not based on history (state) and correct later if wrong.*

- 1. Simple, but all branches now take 2 cycles (lowers performance)*
- 2. Simple, only some branches take 2 cycles (better performance)*
- 3. Complex, very few branches take 2 cycles (best performance)*

*\* MIPS defines “branch delay slot”, RISC-V doesn't*

# Predict “not taken”

## Control Hazard

Branch address ready at end of X stage:

- If branch “not taken”, do nothing.
- If branch “taken”, then kill instruction in I stage (about to enter X stage) and fetch at new target address (PC)


<u>bneq</u> x1, x1, L1	I	X	M		
add x5, x3, x4		I	X	M	
add x6, x1, x2			I	X	M
L1: sub x7, x6, x5				I	X

**Not taken**

<u>beq</u> x1, x1, L1	I	X	M		
add x5, x3, x4		I	nop	nop	
L1: sub x7, x6, x5			I	X	M

**Taken**
 
## EECS151 Project CPU Pipelining Summary



- Pipeline rules:
  - Writes/reads to/from DMem are clocked on the leading edge of the clock in the “M” stage
  - Writes to RegFile at the end of the “M” stage
  - Instruction Decode and Register File access is up to you.
- Branch: predict “not-taken”
- Load: 1 cycle delay/stall on *dependent* instruction
- Bypass ALU for data hazards
- More details in upcoming spec

# **End of Lecture 14**