



EECS 151/251A

Spring 2021

Digital Design and Integrated Circuits

Instructor:


John Wawrzynek

**Lecture 18:
Memory Circuits
and Blocks, Part 2**

Announcements


- ❑ Welcome back!
- ❑ Virtual Front Row for today 3/30:
 - ❑ *Bernard Chen*
 - ❑ *Matthew Tran*
 - ❑ *Jennifer Zhou*
 - ❑ *Suphakorn Lertruchtkul*
 - ❑ *Ruohan Yan*
- ❑ **Please ask question or make comments!**
- ❑ Homework assignment 7 (power & memory) posted.

(On-chip) SRAM Memory

 


ARM A5 Photo

SRAM read/write operations

 

SRAM Operation - Read

 1. Bit lines are “pre-charged” to VDD
2. Word line is driven high (pre-charger is turned off)
3. Cell pulls-down one bit line
4. Differential sensing circuit on periphery is activated to capture value on bit lines.




During read \bar{Q} will get slightly pulled up when WL first goes high, but ...

- *But by sizing the transistors correctly, reading the cell will not destroy the stored value*

SRAM Operation - Write

 1. Column driver circuit on periphery differentially drives the bit lines
2. Word line is driven high (column driver stays on)
3. One side of cell is driven low, flips the other side




For successful write the access transistor needs to overpower the cell pullup. The transistors are sized to allow this to happen.




Memory Periphery

Periphery

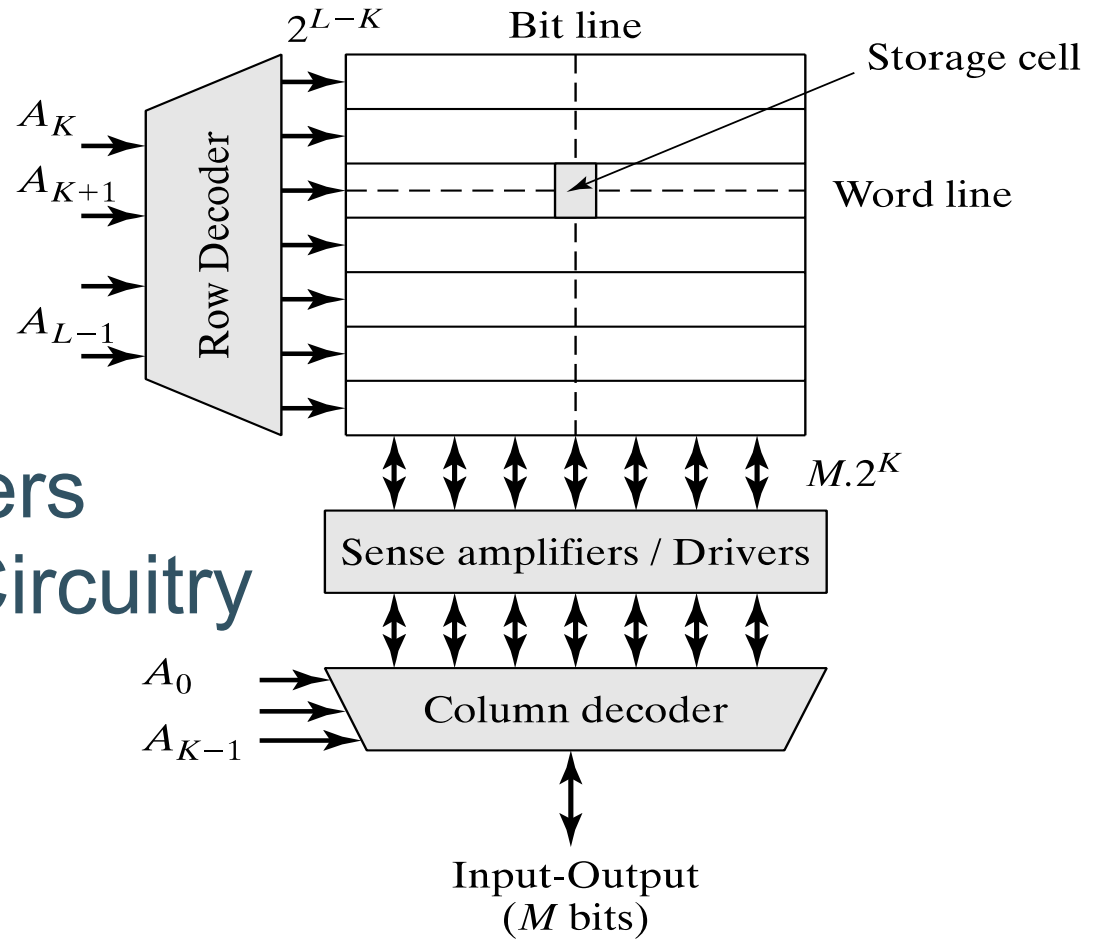- ❑ Decoders
- ❑ Sense Amplifiers
- ❑ Input/Output Buffers
- ❑ Control / Timing Circuitry



Row Decoder

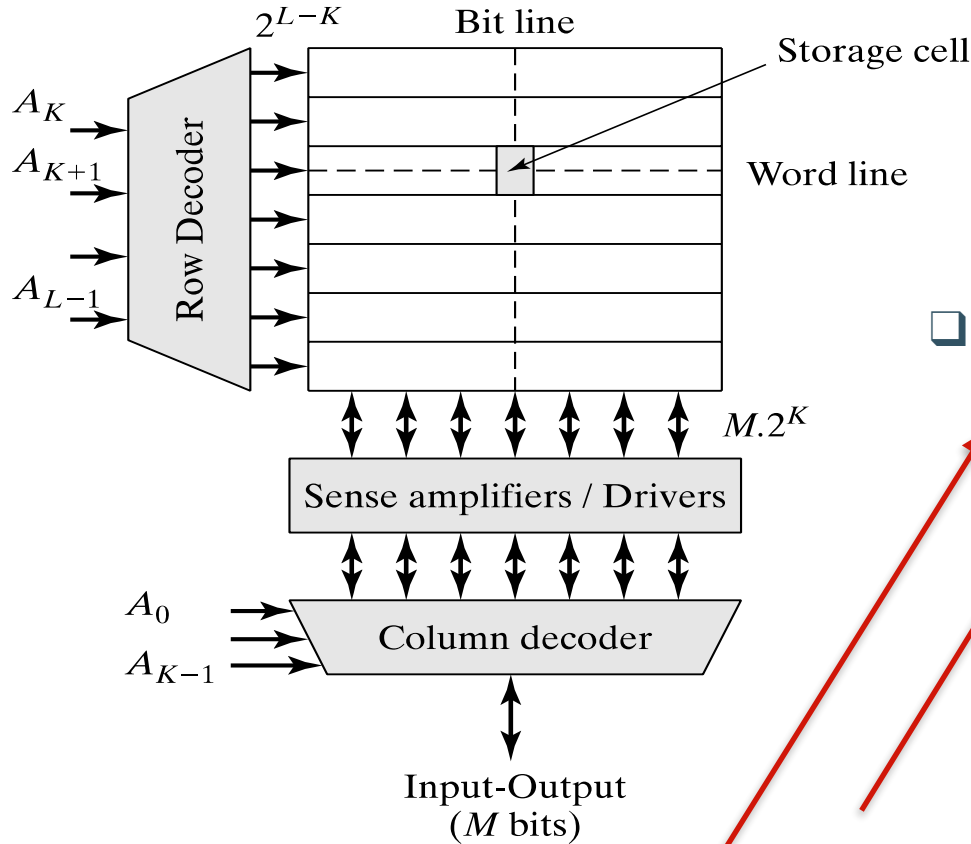

- L total address bits
- K for column decoding
- $L-K$ for row decoding
- Row decoder expands $L-K$ address lines into 2^{L-K} word lines
- M bits per word

□ Example: decoder for $8K \times 8$ memory block

- core arranged as 256×256 cells
- Need 256 AND gates, each driving one word line

each row has 32 8-bit words ($8 \times 32 = 256$)

$8K \times 8$ means $8K$ words of 8-bits each

In this case: $L=13$ total address bits ($2^L=8K$), $K=5$ ($2^K=32$), $L-K=8$ ($2^{L-K}=256$)

Row Decoders

(N)AND Decoder


$$WL_0 = A_0 A_1 A_2 A_3 A_4 A_5 A_6 A_7 A_8 A_9$$

$$WL_{511} = \bar{A}_0 A_1 A_2 A_3 A_4 A_5 A_6 A_7 A_8 A_9$$

NOR Decoder

$$WL_0 = \overline{A_0 + A_1 + A_2 + A_3 + A_4 + A_5 + A_6 + A_7 + A_8 + A_9}$$
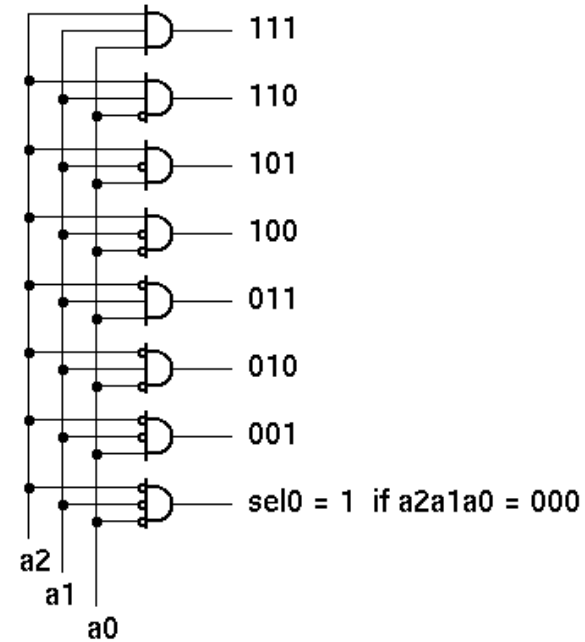
$$WL_{511} = \overline{A_0 + \bar{A}_1 + \bar{A}_2 + \bar{A}_3 + \bar{A}_4 + \bar{A}_5 + \bar{A}_6 + \bar{A}_7 + \bar{A}_8 + \bar{A}_9}$$



Collection of 2^{L-K} logic gates, but need to be dense and fast.

Naive solution would require $L-K$ input gates: *Too big to pitch match to storage cells and too slow.*

Predecoders

$\overline{a_5}$	$\overline{a_4}$	$\overline{a_3}$	$\overline{a_2}$	$\overline{a_1}$	$\overline{a_0}$
$\overline{a_5}$	$\overline{a_4}$	$\overline{a_3}$	$\overline{a_2}$	$\overline{a_1}$	a_0
$\overline{a_5}$	$\overline{a_4}$	$\overline{a_3}$	$\overline{a_2}$	a_1	$\overline{a_0}$
$\overline{a_5}$	$\overline{a_4}$	$\overline{a_3}$	$\overline{a_2}$	a_1	a_0
$\overline{a_5}$	$\overline{a_4}$	$\overline{a_3}$	a_2	$\overline{a_1}$	$\overline{a_0}$
$\overline{a_5}$	$\overline{a_4}$	$\overline{a_3}$	a_2	$\overline{a_1}$	a_0
$\overline{a_5}$	$\overline{a_4}$	$\overline{a_3}$	a_2	a_1	$\overline{a_0}$
$\overline{a_5}$	$\overline{a_4}$	$\overline{a_3}$	a_2	a_1	a_0


•
•
•

a_5	a_4	a_3	a_2	$\overline{a_1}$	$\overline{a_0}$
a_5	a_4	a_3	a_2	$\overline{a_1}$	a_0
a_5	a_4	a_3	a_2	a_1	$\overline{a_0}$
a_5	a_4	a_3	a_2	a_1	a_0


- ❑ Use a single gate for each of the shared terms
 - E.g., from $a_1, \overline{a_1}, a_0, \overline{a_0}$ generate four signals:
 - $\overline{a_1} \overline{a_0}, \overline{a_1} a_0, a_1 \overline{a_0}, a_1 a_0$
- ❑ In other words, we decode smaller groups of address bits first
 - And using the “predecoded” outputs to do the rest of the decoding

Predecoder and Decoder


Predecoders

 

Final Decoder

 

Column “Decoder”

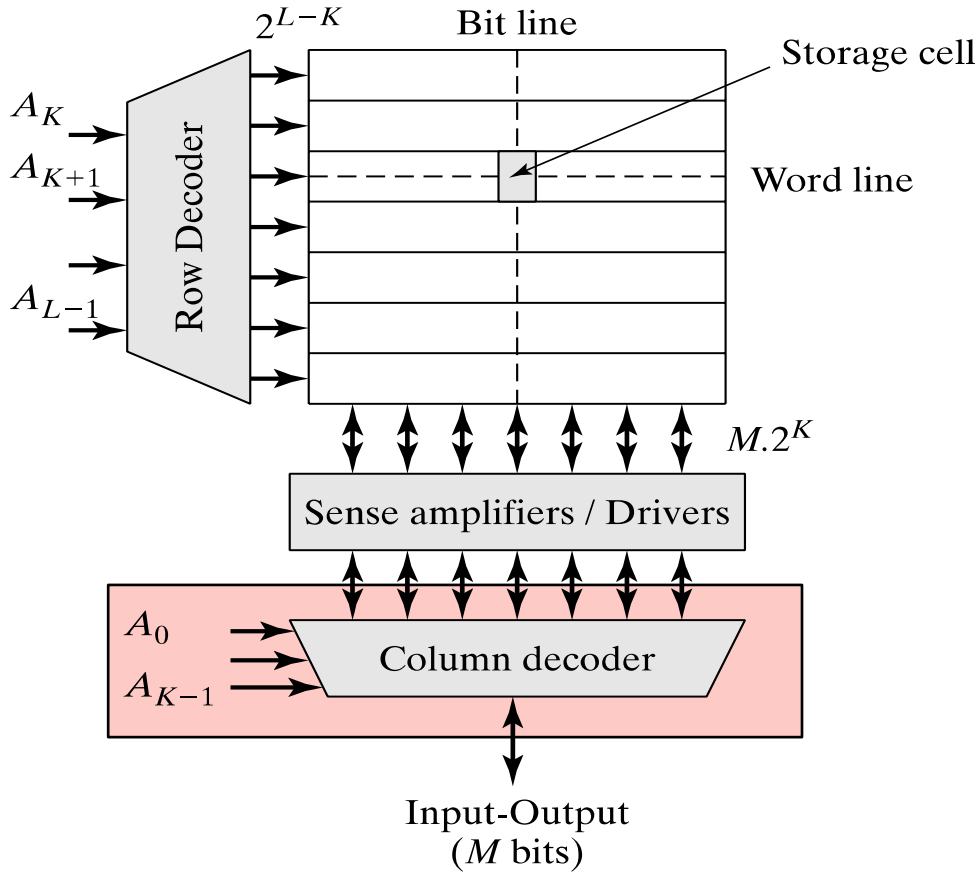


- ❑ Is basically a multiplexer
- ❑ Each row contains 2^K words each M bits wide.
- ❑ Bit of each of the 2^K are interleaved
 - ❑ ex: $K=2, M=8$



$d_7 c_7 b_7 a_7 d_6 c_6 b_6 a_6 d_5 c_5 b_5 a_5 d_4 c_4 b_4 a_4 d_3 c_3 b_3 a_3 d_2 c_2 b_2 a_2 d_1 c_1 b_1 a_1 d_0 c_0 b_0 a_0$

4 interleaved words A, B, C, D

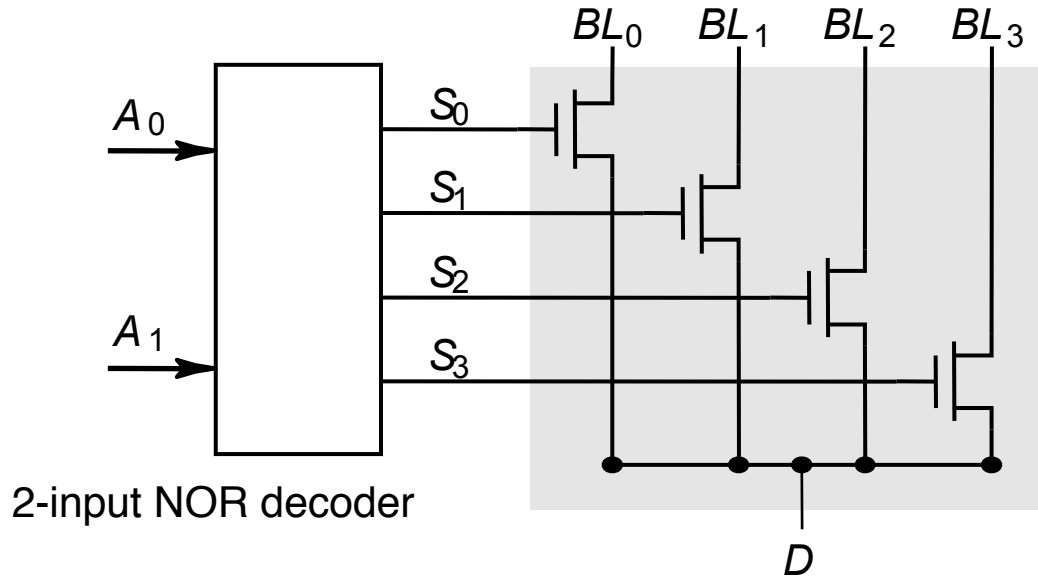4-input pass-transistor based Column Decoder (for read)



(actual circuit would use a “differential signaling”)

decoder shared across all $2^K \times M$ row bits

Advantages: speed (Only one extra transistor in signal path, share sense amp)

Sense Amplifiers Speed Reading


large Capacitance of bit lines

$$\tau_p \propto \frac{C \cdot \Delta V}{I_{av}}$$


make as small as possible

small

Idea: Use “Sense Amplifier”

 


Differential Sense Amplifier

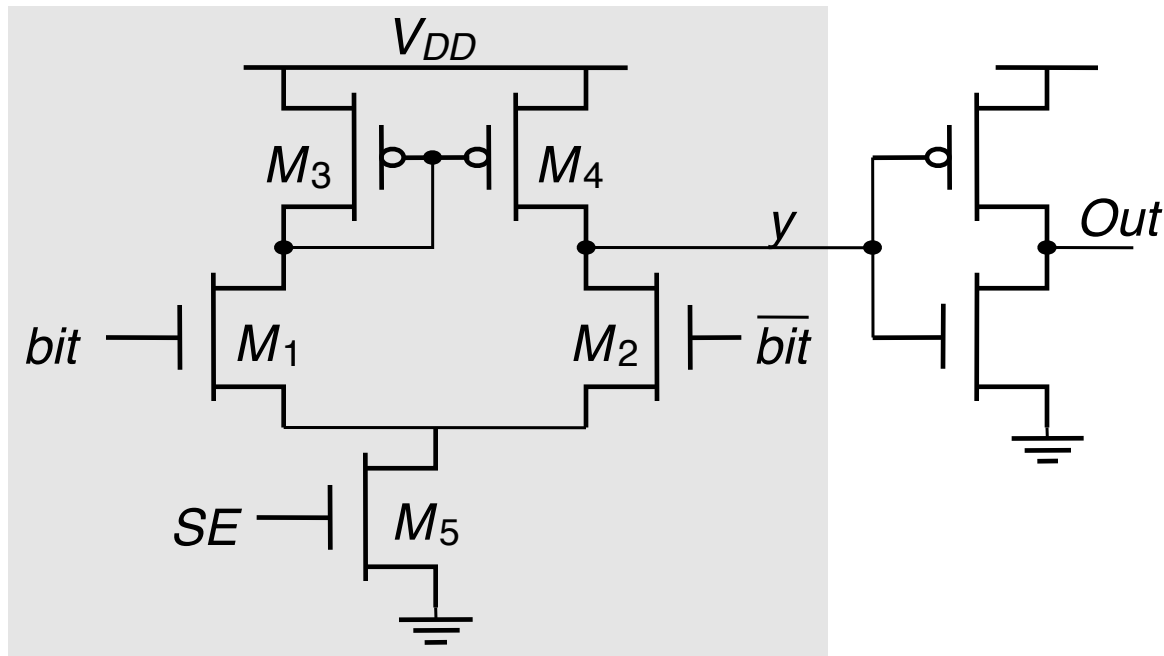

Classic Differential Amp structure - basis of opAmp


Differential Sensing – SRAM

 

(a) SRAM sensing scheme





DRAM

 

- ❑ Gets used for off-chip large inexpensive memories.
- ❑ Most commonly not compatible with logic processes. Requires special IC processing.

3-Transistor DRAM Cell

Can work with a normal logic IC process

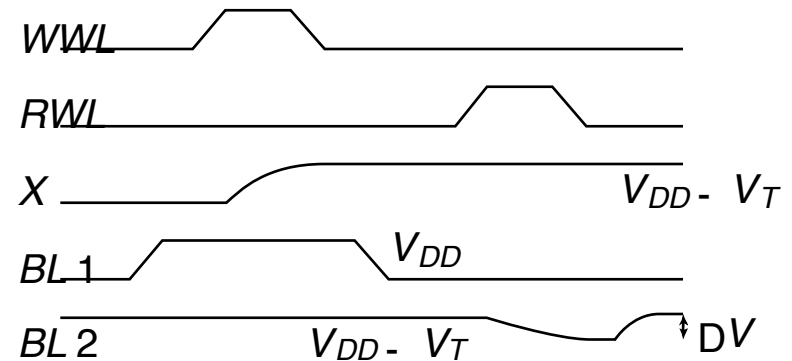 


No constraints on device ratios

Reads are non-destructive

Value stored at node X when writing a "1" = $V_{WWL} - V_{Tn}$

1-Transistor DRAM Cell

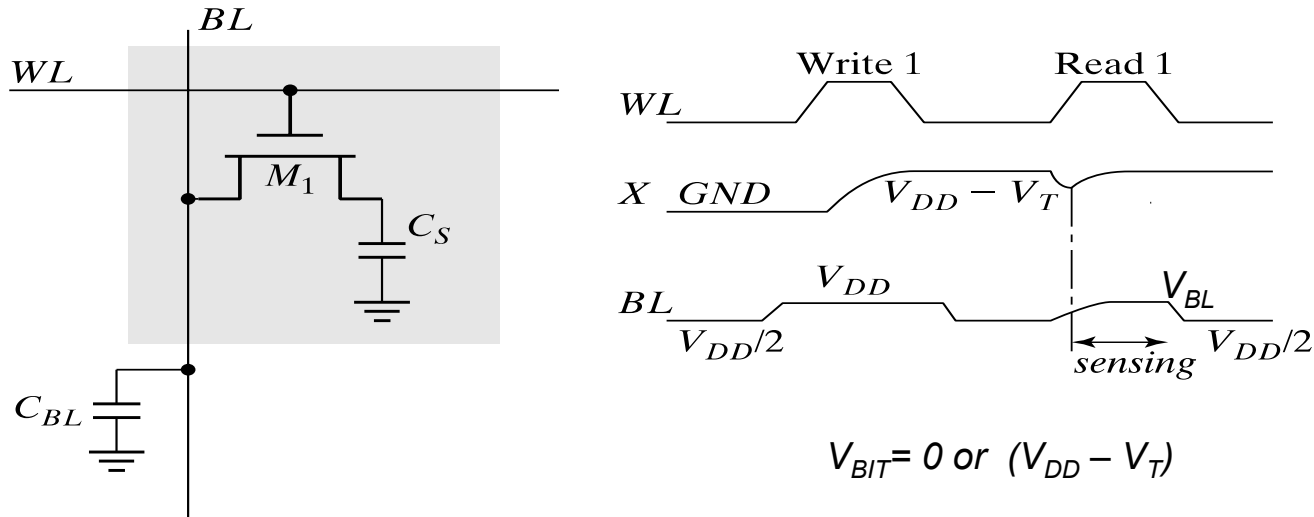


Write: C_S is charged or discharged by asserting WL and BL.

Read: Charge redistribution takes place between bit line and storage capacitance

$C_S \ll C_{BL}$ Voltage swing is small; typically around 250 mV or less.

- ❑ To get sufficient C_S , **special IC process is used**
- ❑ Cell reading is destructive, therefore read operation always is followed by a write-back
- ❑ Cell loses charge (leaks away in ms - highly temperature dependent),²⁰ therefore cells occasionally need to be “refreshed” using read/write cycle

Advanced 1T DRAM Cells

 

Cell Plate Si

Capacitor Insulator

Storage Node Poly


2nd Field Oxide

Refilling Poly

Si Substrate

Trench Cell


Not common

 

Stacked-capacitor Cell

Common

Latch-Based Sense Amplifier (DRAM)

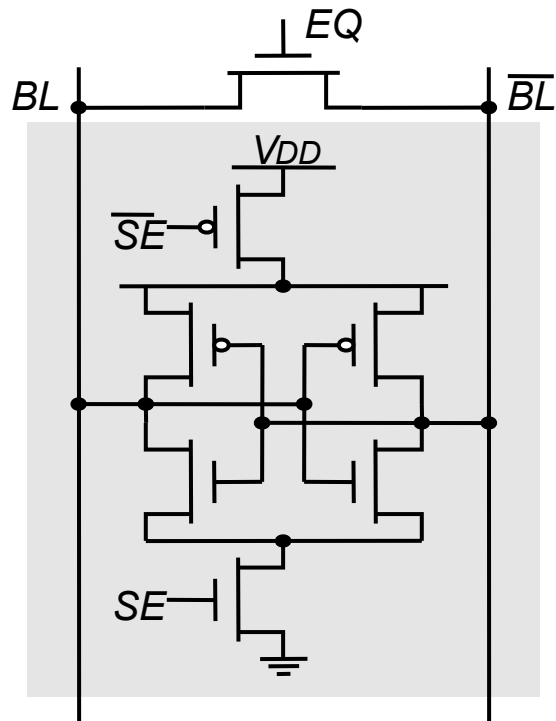

- Bit lines equalized, with EQ, and precharged to $V_{dd}/2$
- Sense amp initialized to its meta-stable point with EQ
- Once adequate voltage gap created, sense amp enabled with SE
- Positive feedback quickly forces output to a stable operating point.
- Bit line from inactive array below/above used as reference for differential sensing.



Memory Blocks


- ❑ Multi-ported RAM
- ❑ Combining Memory blocks
- ❑ FIFOs
- ❑ FPGA memory blocks
- ❑ Caches
- ❑ Memory Blocks in the Project



Multi-ported memory

Memory Architecture Review

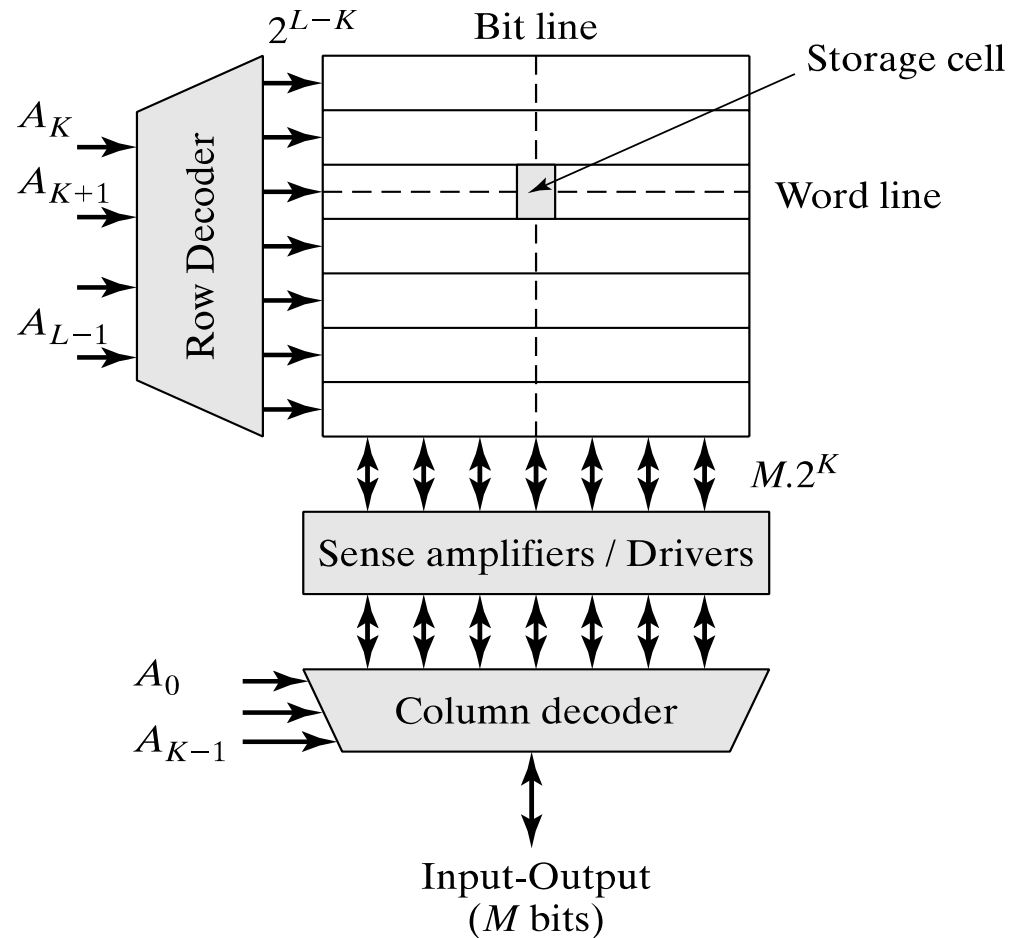
- ❑ **Word lines** used to select a row for reading or writing
- ❑ **Bit lines** carry data to/from periphery
- ❑ **Core aspect ratio** keep close to 1 to help balance delay on word line versus bit line
- ❑ **Address bits** are divided between the two decoders
- ❑ **Row decoder** used to select word line
- ❑ **Column decoder** used to select one or more columns for input/output of data



Multi-ported Memory

□ Motivation:

 - Consider CPU core register file:
 - 1 read or write per cycle limits processor performance.
 - Complicates pipelining. Difficult for different instructions to simultaneously read or write regfile.
 - Common arrangement in pipelined CPUs is 2 read ports and 1 write port.



– I/O data buffering:


disk or network interface




- dual-porting allows both sides to simultaneously access memory at full bandwidth.

Dual-ported Memory Internals

 - Add decoder, another set of read/write logic, bits lines, word lines:



- Example cell: SRAM

 


- Repeat everything but cross-coupled inverters.
- This scheme extends up to a couple more ports, then need to add additional transistors.



Combining Memory Blocks

Building Larger Memories

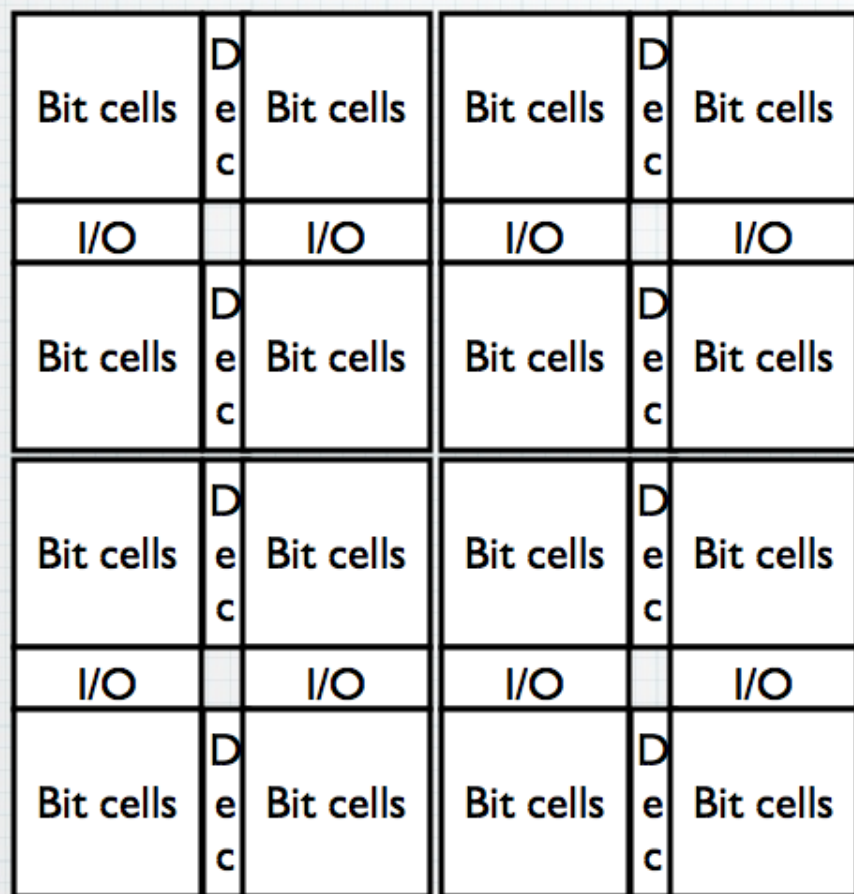


- Large arrays constructed by tiling multiple leaf arrays, sharing decoders and I/O circuitry
 - e.g., sense amp attached to arrays above and below
- Leaf array limited in size to 128-256 bits in row/column due to RC delay of wordlines and bitlines
- Also to reduce power by only activating selected sub-bank
- In larger memories, delay and energy dominated by I/O wiring

Cascading Memory-Blocks

How to make larger memory blocks out of smaller ones.

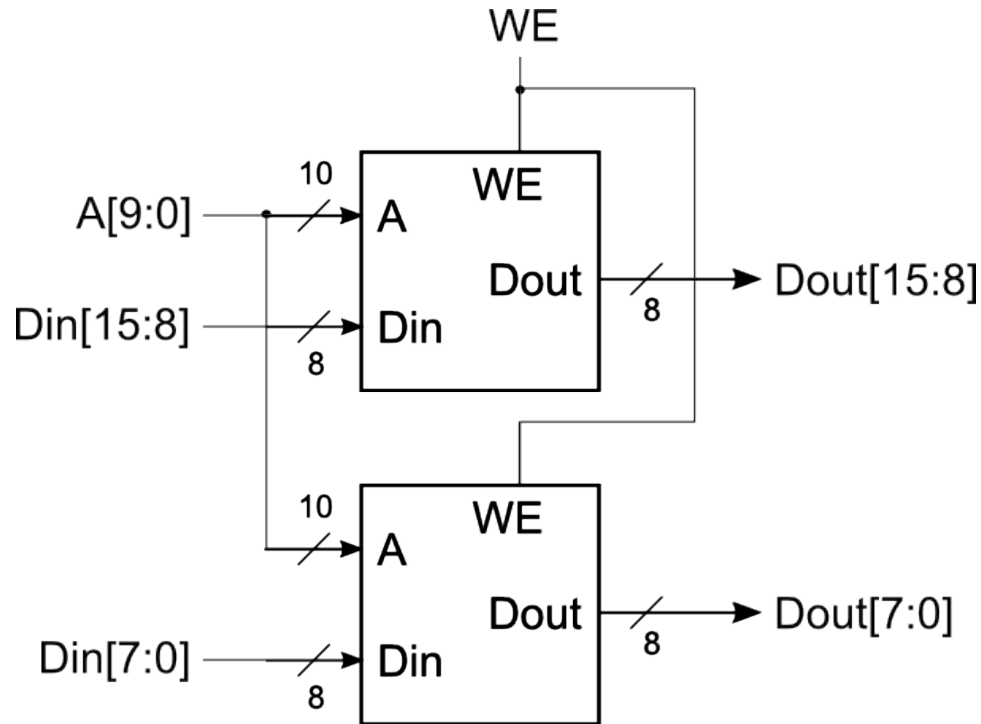
Increasing the width. Example: given 1Kx8, want 1Kx16



Cascading Memory-Blocks

How to make larger memory blocks out of smaller ones.

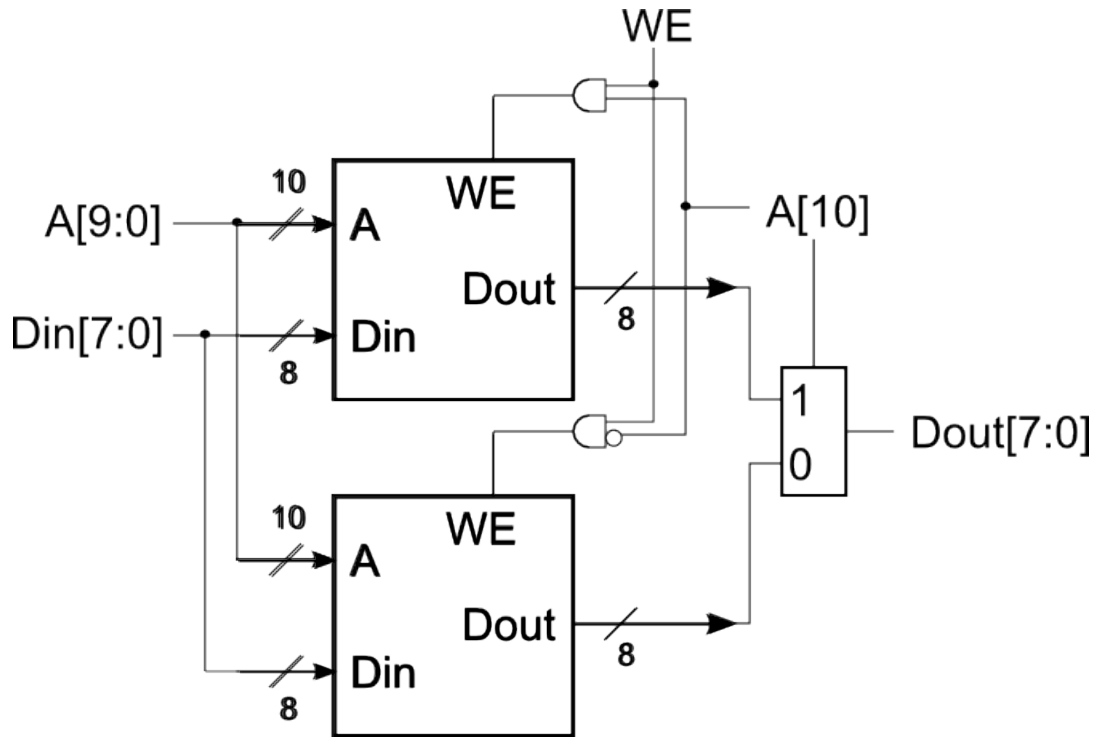
Increasing the depth. Example: given 1Kx8, want 2Kx8



Adding Ports to Primitive Memory Blocks

Adding a read port to a simple dual port (SDP) memory.

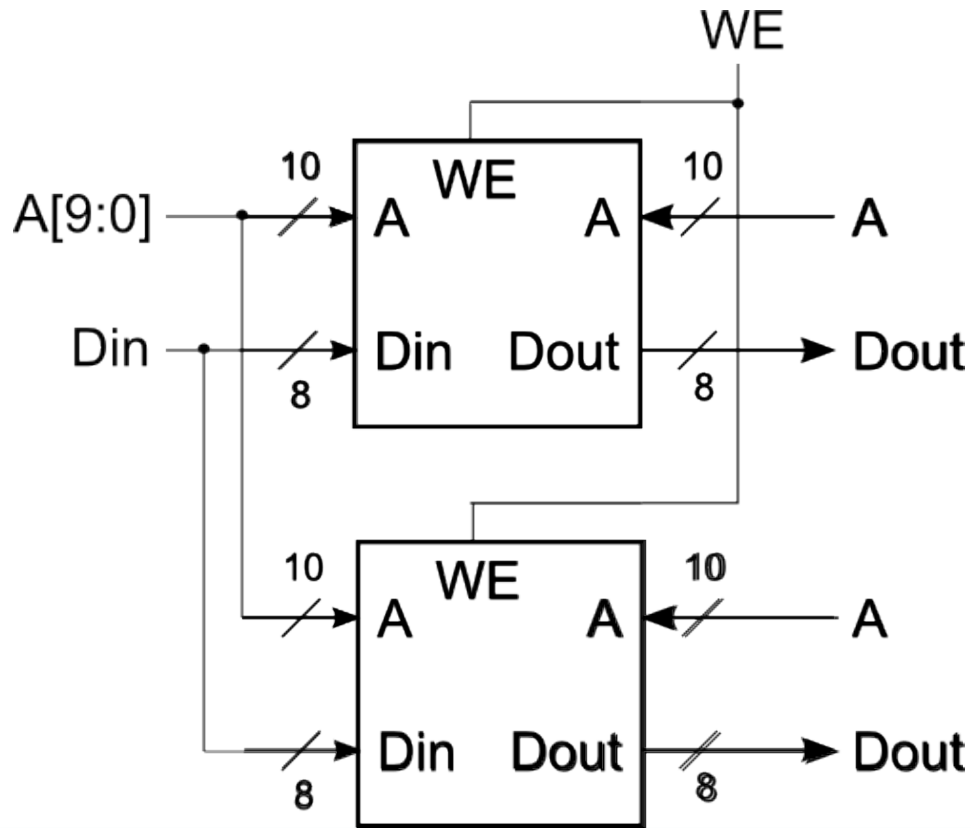
Example: given 1Kx8 SDP, want 1 write & 2 read ports.



Adding Ports to Primitive Memory Blocks

How to add a write port to a simple dual port memory.

 Example: given 1Kx8 SDP, want 1 read & 2 write ports.






FIFOs


First-in-first-out (FIFO) Memory

 - ❑ Used to implement *queues*.
- ❑ These find common use in computers and communication circuits.
- ❑ Generally, used to “decouple” actions of producer and consumer:



- *Producer can perform many writes without consumer performing any reads (or vis versa). However, because of finite buffer size, on average, need equal number of reads and writes.*
- *Typical uses:*
 - *interfacing I/O devices. Example network interface. Data bursts from network, then processor bursts to memory buffer (or reads one word at a time from interface). Operations not synchronized.*
 - *Example: Audio output. Processor produces output samples in bursts (during process swap-in time). Audio DAC clocks it out at constant sample rate.*


FIFO Interfaces

 


- ❑ After write or read operation, FULL and EMPTY indicate status of buffer.
- ❑ Used by external logic to control it's own reading from or writing to the buffer.
- ❑ FIFO resets to EMPTY state.
- ❑ HALF FULL (or other indicator of partial fullness) is optional.

“Circular buffer” implementation:

 
- *Address pointers are used internally to keep next write position and next read position into a dual-port memory.*



 - *If pointers equal after write \Rightarrow FULL:*



 
- *If pointers equal after read \Rightarrow EMPTY:*



Note: pointer incrementing is done “mod size-of-buffer”

Xilinx Virtex5 FIFOs

 - ❑ Virtex5 BlockRAMS include dedicated circuits for FIFOs.
- ❑ Details in User Guide (ug190).
- ❑ Takes advantage of separate dual ports and independent ports clocks.






Memory on FPGAs


Virtex-5 LX110T
memory blocks.

Distributed RAM
using LUTs
among the CLBs.

Block RAMs
in four
columns.

 


A SLICEM 6-LUT ... ("distributed RAM")

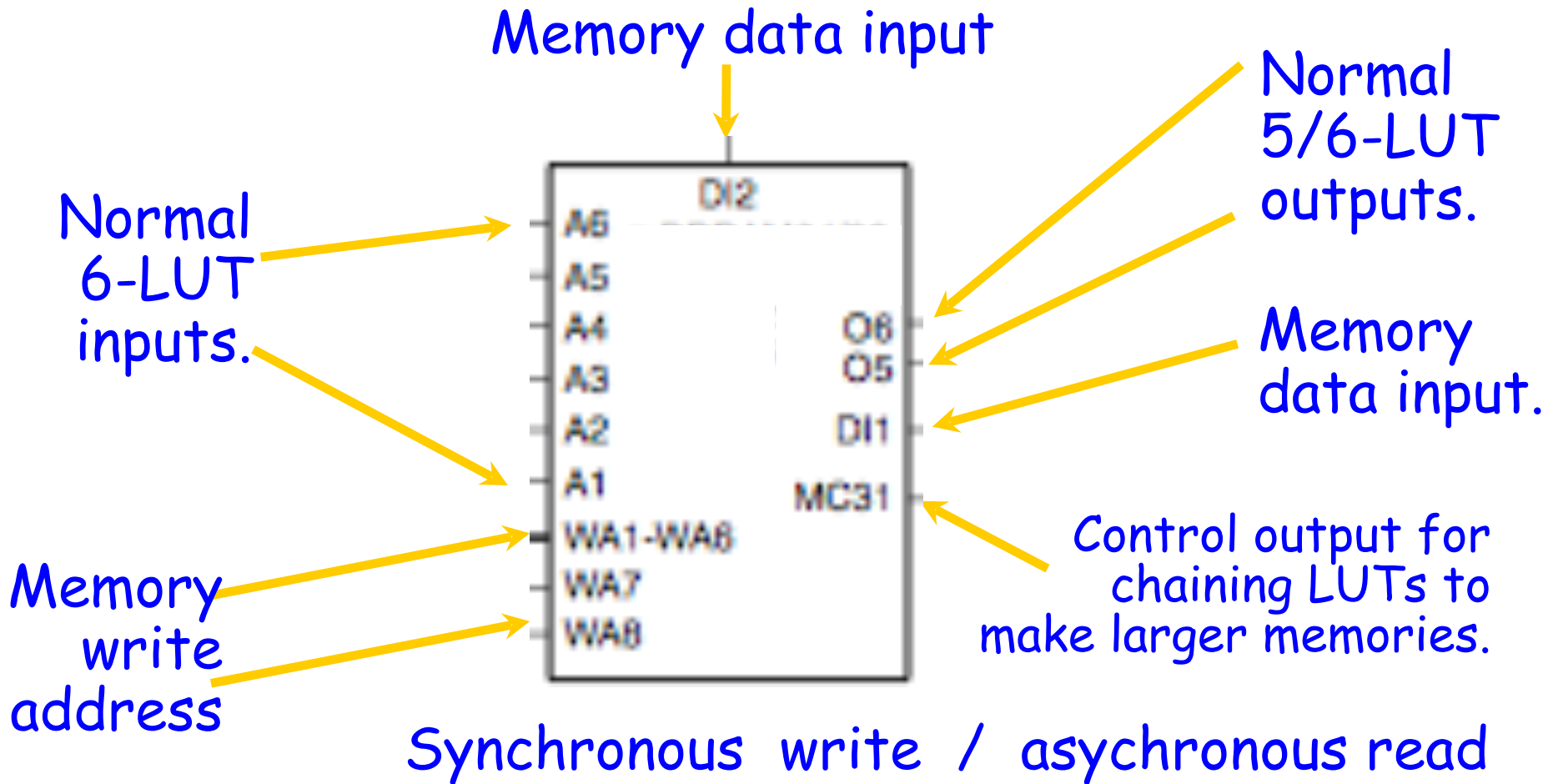

A 1.1 Mb distributed RAM can be made if all SLICEMs of an LX110T are used as RAM.


SLICEL vs SLICEM ...

SLICEL

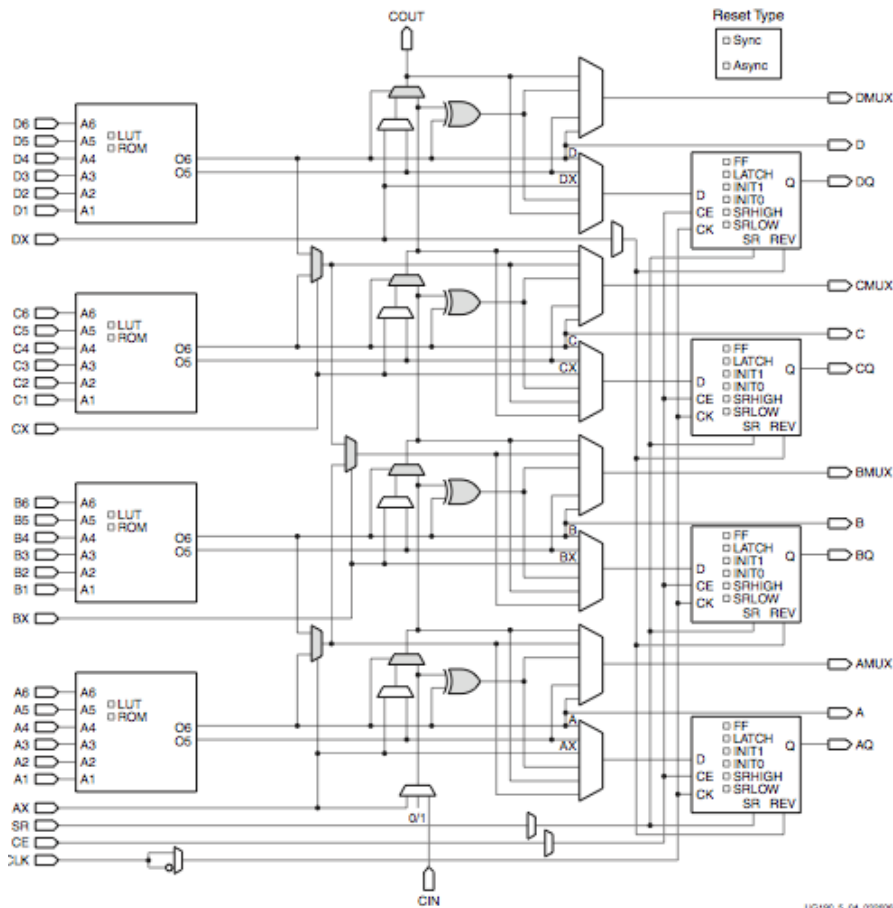

UG190 5.04 02/06

SLICEM

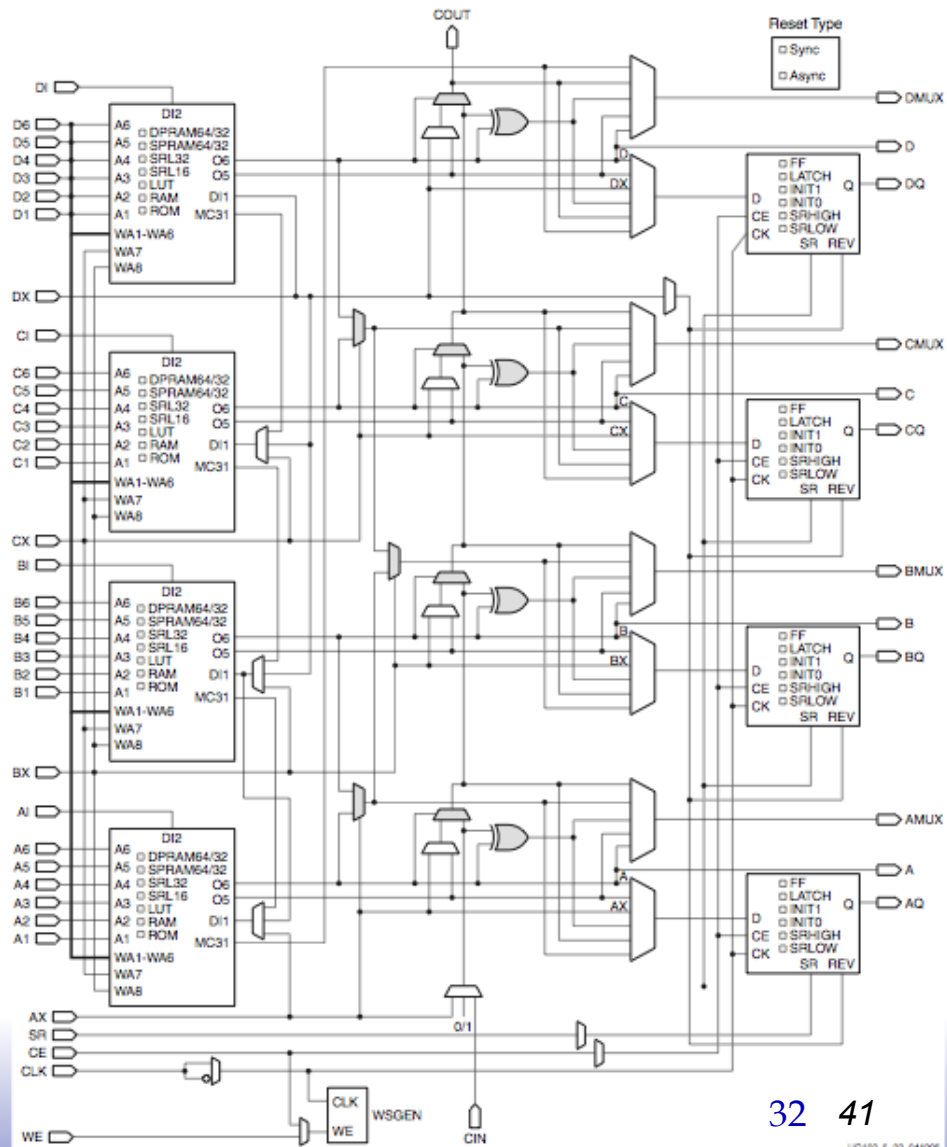

UG190 5.03 04/06

SLICEM adds memory features to LUTs, + muxes.

Example Distributed RAM (LUT RAM)

Example configuration:
Single-port 256b x 1,
registered output.


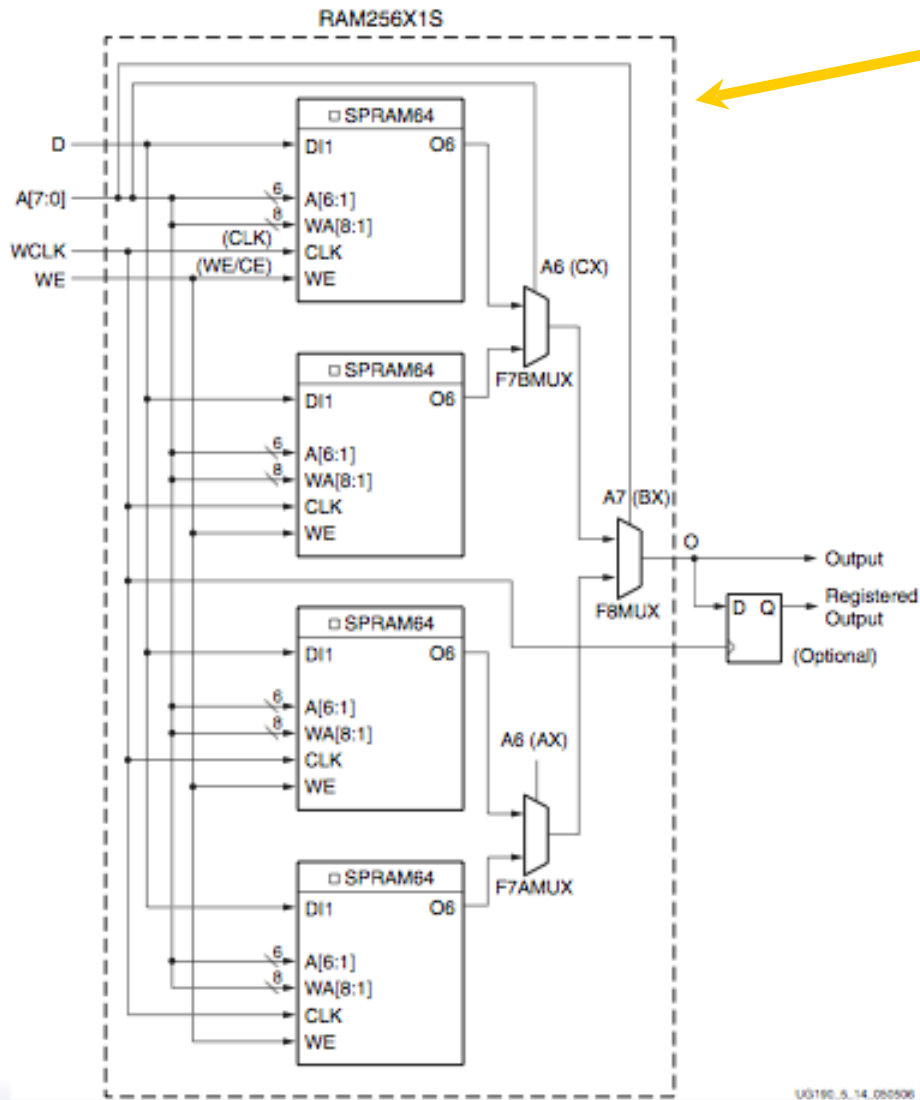


Figure 5-14: Distributed RAM (RAM256X1S)

Distributed RAM Primitives

 

- Single-Port 32 x 1-bit RAM
- Dual-Port 32 x 1-bit RAM
- Quad-Port 32 x 2-bit RAM
- Simple Dual-Port 32 x 6-bit RAM
- Single-Port 64 x 1-bit RAM
- Dual-Port 64 x 1-bit RAM
- Quad-Port 64 x 1-bit RAM
- Simple Dual-Port 64 x 3-bit RAM
- Single-Port 128 x 1-bit RAM
- Dual-Port 128 x 1-bit RAM
- Single-Port 256 x 1-bit RAM

All are built from a single slice or less.

Remember, though, that the SLICEM LUT is naturally only 1 read and 1 write port.

Distributed RAM Timing


 


Figure 5-27: Simplified Virtex-5 FPGA SLICEM Distributed RAM


Block RAM Overview

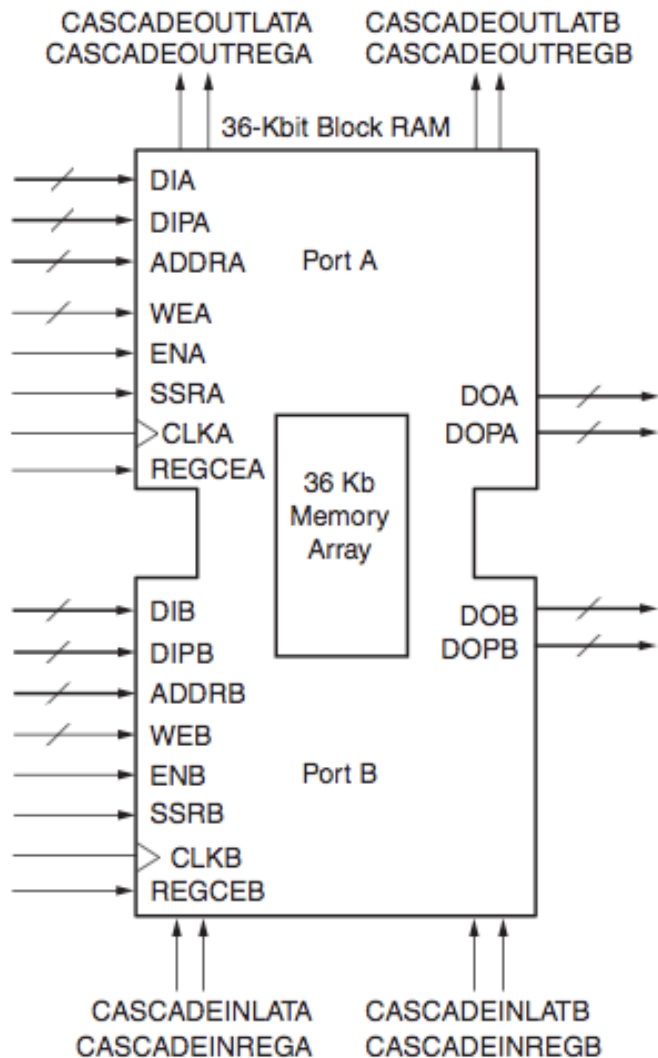

ug0190_4_01_032106

- 36K bits of data total, can be configured as:
 - 2 independent 18Kb RAMs, or one 36Kb RAM.
- Each 36Kb block RAM can be configured as:
 - 64Kx1 (when cascaded with an adjacent 36Kb block RAM), 32Kx1, 16Kx2, 8Kx4, 4Kx9, 2Kx18, or 1Kx36 memory.
- Each 18Kb block RAM can be configured as:
 - 16Kx1, 8Kx2, 4Kx4, 2Kx9, or 1Kx18 memory.
- Write and Read are synchronous operations.
- The two ports are symmetrical and totally independent (can have different clocks), sharing only the stored data.
- Each port can be configured in one of the available widths, independent of the other port. The read port width can be different from the write port width for each port.
- The memory content can be initialized or cleared by the configuration bitstream.

Block RAM Timing

 


ug190_4_03_032206

- ❑ Optional output register, would delay appearance of output data by one cycle.
- ❑ Maximum clock rate, roughly 400MHz.

Ultra-RAM Blocks

Table 2-1: Block RAM and UltraRAM Comparison


Feature	Block RAM	UltraRAM
Clocking	Two clocks	Single clock
Built-in FIFO	Yes	No
Data width	Configurable (1, 2, 4, 9, 18, 36, 72)	Fixed (72-bits)
Modes	SDP and TDP	Two ports, each can independently read or write (a superset of SDP)
ECC	64-bit SECDED Supported in 64-bit SDP only (one ECC decoder for port A and one ECC encoder for port B)	64-bit SECDED One set of complete ECC logic for each port to enable independent ECC operations (ECC encoder and decoder for both ports)
Cascade	<ul style="list-style-type: none"> Cascade output only (input cascade implemented via logic resources) Cascade within a single clock region 	<ul style="list-style-type: none"> Cascade both input and output (with global address decoding) Cascade across clock regions in a column Cascade across several columns with minimal logic resources
Power savings	One mode via manual signal assertion	One mode via manual signal assertion

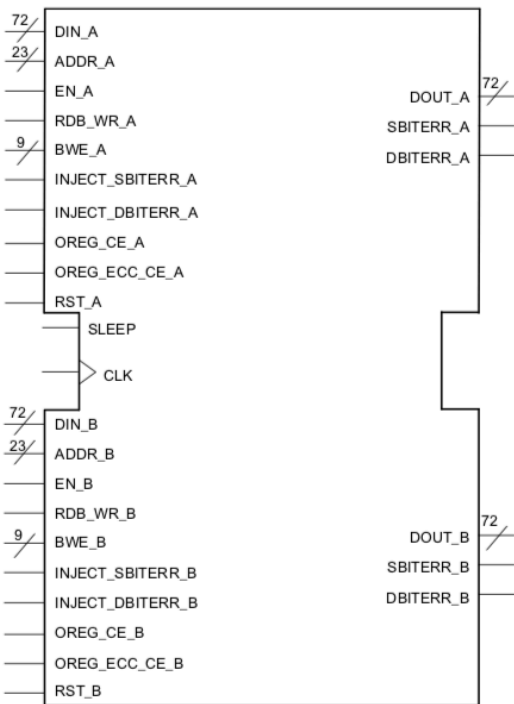

X171 82-012617

Figure 2-1: UltraRAM URAM288_BASE Primitive

State-of-the-Art - Xilinx FPGAs

 

Virtex Ultra-scale


Device Name	VU3P	VU5P	VU7P	VU9P	VU11P	VU13P	VU27P	VU29P	VU31P	VU33P	VU35P	VU37P	
System Logic Cells (K)	862	1,314	1,724	2,586	2,835	3,780	2,835	3,780	962	962	1,907	2,852	
CLB Flip-Flops (K)	788	1,201	1,576	2,364	2,592	3,456	2,592	3,456	879	879	1,743	2,607	
CLB LUTs (K)	394	601	788	1,182	1,296	1,728	1,296	1,728	440	440	872	1,304	
Max. Dist. RAM (Mb)	12.0	18.3	24.1	36.1	36.2	48.3	36.2	48.3	12.5	12.5	24.6	36.7	
Total Block RAM (Mb)	25.3	36.0	50.6	75.9	70.9	94.5	70.9	94.5	23.6	23.6	47.3	70.9	
UltraRAM (Mb)	90.0	132.2	180.0	270.0	270.0	360.0	270.0	360.0	90.0	90.0	180.0	270.0	
HBM DRAM (GB)	-	-	-	-	-	-	-	-	4	8	8	8	
HBM AXI Interfaces	-	-	-	-	-	-	-	-	32	32	32	32	
Clock Mgmt Tiles (CMTs)	10	20	20	30	12	16	16	16	4	4	8	12	
DSP Slices	2,280	3,474	4,560	6,840	9,216	12,288	9,216	12,288	2,880	2,880	5,952	9,024	
Peak INT8 DSP (TOP/s)	7.1	10.8	14.2	21.3	28.7	38.3	28.7	38.3	8.9	8.9	18.6	28.1	
PCIe [®] Gen3 x16	2	4	4	6	3	4	1	1	0	0	1	2	
PCIe Gen3 x16/Gen4 x8 / CCIX ⁽¹⁾	-	-	-	-	-	-	-	-	4	4	4	4	
150G Interlaken	3	4	6	9	6	8	6	8	0	0	2	4	
100G Ethernet w/ KR4 RS-FEC	3	4	6	9	9	12	11	15	2	2	5	8	
Max. Single-Ended HP I/Os	520	832	832	832	624	832	520	676	208	208	416	624	
GTY 32.75Gb/s Transceivers	40	80	80	120	96	128	32	32	32	32	64	96	
GTM 58Gb/s PAM4 Transceivers							32	48					
100G / 50G KP4 FEC							16 / 32	24 / 48					
Extended ⁽²⁾	-1 -2 -2L -3	-1 -2 -2L -3	-1 -2 -2L -3	-1 -2 -2L -3	-1 -2 -2L -3	-1 -2 -2L -3	-1 -2 -2L -3	-1 -2 -2L -3	-1 -2 -2L -3	-1 -2 -2L -3	-1 -2 -2L -3	-1 -2 -2L -3	-1 -2 -2L -3
Industrial	-1 -2	-1 -2	-1 -2	-1 -2	-1 -2	-1 -2	-1 -2	-1 -2	-	-	-	-	



Caches

1977: DRAM faster than microprocessors


 
TIMING:
6502 PROCESSOR'S
 Φ_1 CLOCK SHOWING
WHEN AND BY WHOM
MEMORY IS ACCESSED



Apple II (1977)

CPU: 1000 ns

DRAM: 400 ns

 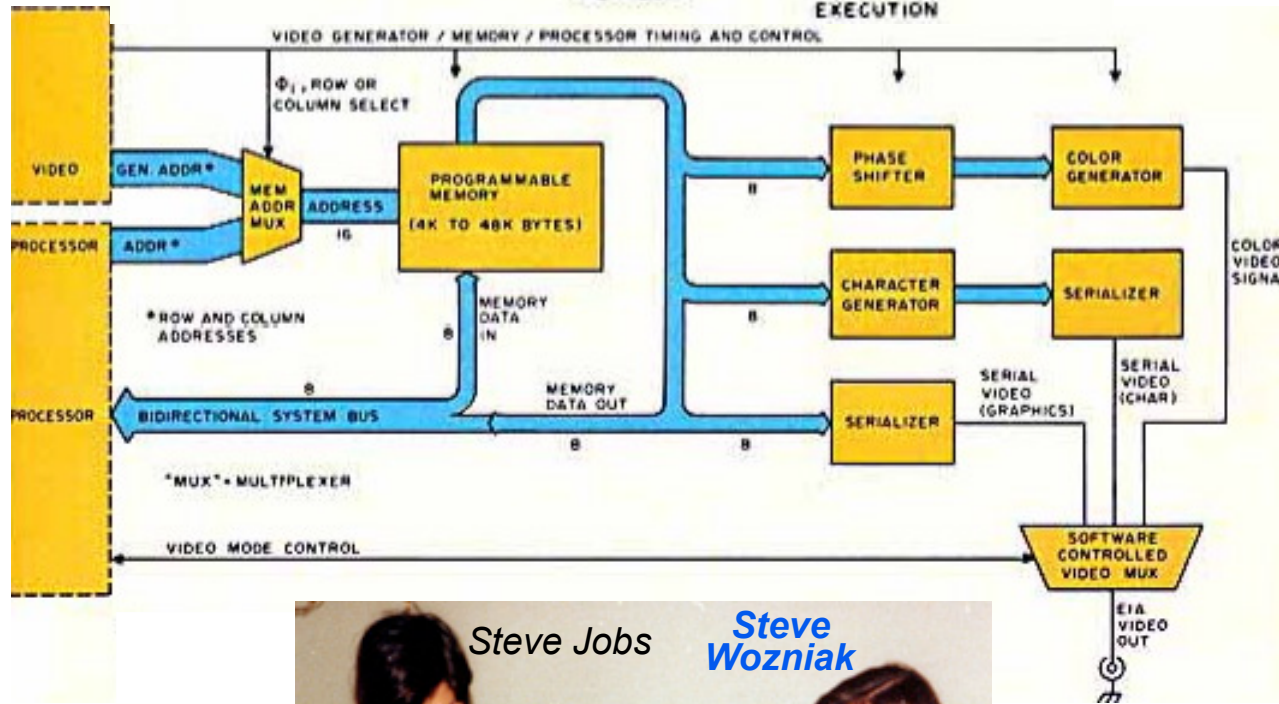

Steve Jobs

Steve Wozniak

RAM Complement	Apple II System
4K	\$ 1,298.00
48K	2,638.00


1980-2003, CPU speed outpaced DRAM ...

Q. How did architects address this gap?

A. Put smaller, faster **“cache”** memories between CPU and DRAM.

Create a **“memory hierarchy”**.

Performance
(1/latency)

 


Review from 61C

- ❑ **Two Different Types of Locality:**
 - **Temporal Locality (Locality in Time):** If an item is referenced, it will tend to be referenced again soon.
 - **Spatial Locality (Locality in Space):** If an item is referenced, items whose addresses are close by tend to be referenced soon.
- ❑ **By taking advantage of the principle of locality:**
 - **Present the user with as much memory as is available in the cheapest technology.**
 - **Provide access at the speed offered by the fastest technology.**
- ❑ **DRAM is slow but cheap and dense:**
 - **Good choice for presenting the user with a BIG memory system**
- ❑ **SRAM is fast but expensive and not very dense:**
 - **Good choice for providing the user FAST access time.**


CPU-Cache Interaction

(5-stage pipeline)

 

Cache Refill Data from Lower Levels of Memory Hierarchy

Nahalem Die Photo (i7, i5)

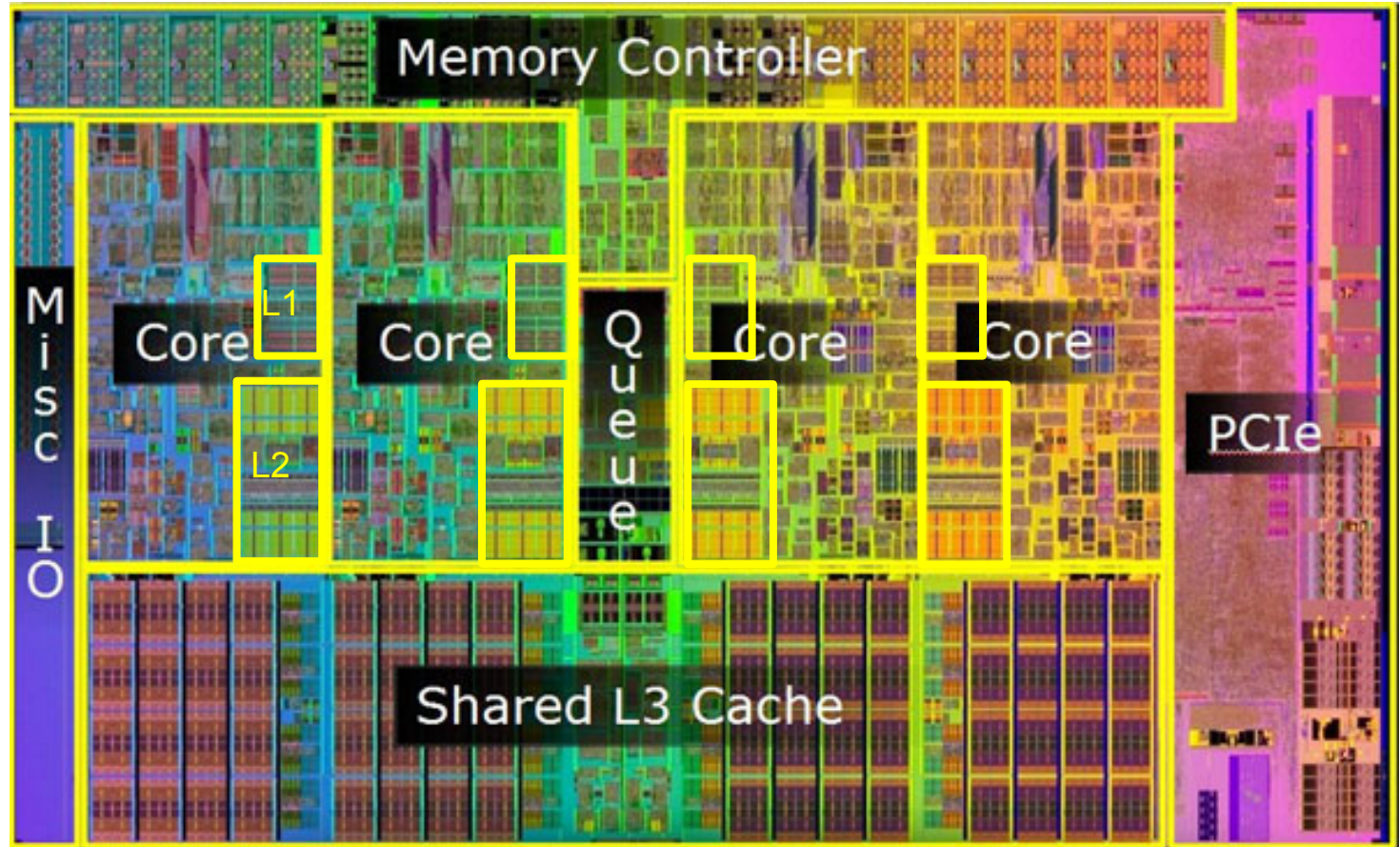

□ Per core:


- 32KB L1 I-Cache (4-way set associative (SA))
- 32KB L1 D-Cache (8-way SA)
- 256KB unified L2 (8-way SA, 64B blocks)
- Common L3 8MB cache

□ Common L3 8MB cache

Fully Associative

Fully Associative Cache

 - No Cache Index
- For read, compare the Cache Tags of all cache entries in parallel
- Example: Block Size = 32 B blocks, we need N 27-bit comparators




Set Associative Cache

N-way set associative: N entries for each Cache Index

- (N direct mapped caches operates in parallel)

 Example: Two-way set associative cache

- Cache Index selects a “set” from the cache
- The two tags in the set are compared to the input in parallel
- Data is selected based on the tag result





RAM Blocks and the Project

Processor Design Considerations (FPGA Version)

❑ Register File: Consider distributed RAM (LUT RAM)

- Size is close to what is needed: distributed RAM primitive configurations are 32 or 64 bits deep. Extra width is easily achieved by parallel arrangements.
- LUT-RAM configurations offer multi-porting options - useful for register files.
- Asynchronous read, might be useful by providing flexibility on where to put register read in the pipeline.

❑ Instruction / Data Memories : Consider Block RAM

- Higher density, lower cost for large number of bits
- A single 36kbit Block RAM implements 1K 32-bit words.
- Configuration stream based initialization, permits a simple “boot strap” procedure.

Processor Design Considerations (ASIC Version)

❑ **Register File: use synthesized RAM**

- At this size (1k bits) synthesized is competitive with dense RAM block
- Latch-based instead of flip-flop-based would save on area.
- Asynchronous read, might be useful by providing flexibility on where to put register read in the pipeline.

❑ **Instruction / Data Caches : Use generated dense Block RAM**

- Higher density, lower cost for large number of bits
- We will provide for you