



EECS151/251A

Spring 2021

Digital Design and Integrated Circuits

Instructor:
John Wawrzynek

Lecture 27:

Wrap-up

Outline



- ❑ *Important takeaways*
- ❑ *Exam Topics*

Why Study and Learn Digital Design?

- We expect that many of you will eventually be employed as designers.
 - **Digital design is not a spectator sport.** The only way to learn it, and to appreciate the issues, is to do it.
 - To a large extent, it comes with practice/experience (this course is just the beginning).
 - Another way to get better is to study other designs. Not time to do much of this during the semester, but a good practice for later.
- However, a significant percentage of our graduates will not be digital designers. What's in it for them?
 - Better manager of designers, marketers, field engineers, etc.
 - Better researcher/scientist/designer in related areas
 - Software engineers, fabrication process development, etc.
 - Even to become a better user of electronic systems.

In What Context Will You be Designing?

Engineers learn so that they can build.


Scientists build so that they can learn.

- Electronic design is a critical tool for most areas of pure science:
 - Astrophysics – special electronics used for processing radio antenna signals.
 - Genomics – special processing architectures for DNA string matching.
 - In general - sensor processing, control, and number crunching.
 - Machine Learning now relies heavily on special hardware.
 - In some fields, computation has replaced experimentation – particle physics, world weather prediction (fluid dynamics).
- In computer engineering, prototypes often designed, implemented, and studied to “prove out” an idea. Common within universities and industrial research labs. Lessons learned and proven ideas often transferred to industry through licensing, technical communications, or startup companies.
 - RISC processors were first proved out at Berkeley and IBM Research

Designs in Industry

- ❑ Of course, companies are the primary employer of designers. Provide some useful products to society or government and make a profit for the shareholders.
- ❑ Interesting recent shift
 - All software giants now have hardware design teams (embedded and chips)
 - Google, Amazon, Facebook, Microsoft, ...

 Global Electronic System Production
(\$1.62T, 2018F)



Source: IC Insights

Ten Big Ideas from EECS151

1. **Modularity and Hierarchy** is an important way to describe and think about digital systems.
2. **Parallelism** is a key property of hardware systems and distinguishes them from serial software execution.
3. **Clocking** and the use of state elements (latches, flip-flops, and memories) control the flow of data.
4. **Cost/Performance/Power tradeoffs** are possible at all levels of the system design.
5. **Boolean Algebra** and other logic representations.
6. **Hardware Description Languages (HDLs) and Logic Synthesis** are a central tool for digital design.
7. **Datapath + Controller** is a effective design pattern.
8. **Finite State Machines** abstraction gives us a way to model any digital system – used for designing controllers.
9. **Arithmetic circuits** are often based on “long-hand” arithmetic techniques.
10. **FPGAs + ASICs** give us a convenient and flexible implementation technology.

What We Didn't Cover

- ❑ Design Verification and Testing
 - Industrial designers spend more than half their time testing and verifying correctness of their designs.
 - Some of this covered in the lab and a bit in lecture. Didn't cover rigorous testing procedures.
 - Most industrial products are designed from the start for testability. Important for design verification and later for manufacturing test.
 - Related: Fault modeling and fault tolerant design.

- ❑ Other High-level Optimization Techniques
 - High-level Synthesis - now starting to catch on

- ❑ Other High-level Architectures: GPUs, video processing, network routers, ...

- ❑ Asynchronous Design

Most Closely Related Courses

- ❑ CS152 Computer Architecture and Engineering
 - Design and Analysis of Microprocessors
 - Applies basic design concepts from EECS151
- ❑ EE241B Digital Integrated Circuits
 - Transistor-level design of ICs
 - More on Advanced ASIC Tool use
- ❑ CS250 VLSI Systems Design
 - Advanced-undergrad/grad course
 - Design tradeoffs at the chip design level

Future Design Issues

- ❑ Automatic High-level synthesis (HLS) and optimization (with micro-architecture synthesis) and hardware/software co-design.
- ❑ Current practice is “system on a chip” (SOC) design methodology:
 - Pre-designed subsystems (processor cores, bus controllers, memory systems, network interfaces, etc.) connected with standard on-chip interconnect or bus.
 - Strong emphasis on “accelerators” for energy efficiency and performance.
- ❑ A number of alternatives to silicon VLSI have been proposed, including techniques based on:
 - Carbon nanotubes*, molecular electronics, quantum mechanics, and biological processes.
 - How will these change the way we design systems?

**In 2012, IBM produced a sub-10 nm carbon nanotube transistor that outperformed silicon on speed and power. "The superior low-voltage performance of the sub-10 nm CNT transistor proves the viability of nanotubes for consideration in future aggressively scaled transistor technologies", according to the abstract of the paper in [Nano Letters](#).*

Final Exam and Project Info

- ❑ **Exam held May 14th Friday 7-10PM.**
 - ❑ “Comprehensive” Final Exam
 - ❑ Emphasis on second half, but some coverage of first half
 - ❑ Same format as Exam 1. Open-book and notes. Zoom proctoring.
- ❑ FPGA project interviews: Wednesday of RRR week, 5/5.
- ❑ FPGA project final reports: Friday 5/7.

The exam will be a “take home exam” and take place Thursday April 30, 7-10PM. The exam comprises a set of questions with 1 point per expected minute of completion with a total of approximately 90 points. 251A students will be asked to complete extra questions. All students are allowed to refer to your notes, the class lecture notes, and any other reference materials that you have available. However, the problems are challenging and if you are not suitable familiar with the course topics, you may not have much time to look at notes. You are not allowed to speak with anyone on any topic related to the course during the exam period. After completing the exam, you will be asked to sign a statement attesting that you did not discuss the exam problems with anyone else. You will turn in your answers with Gradescope as you do your homework.

As with the first exam, clarification questions can be directed to the teaching staff via piazza.

Topics:


The final exam will be comprehensive and test all topics covered this semester. However, emphasis will be placed on topics covered after the midterm exam—those listed below.

- 1. How to Design a RISC-V Single-Cycle Processor from the ISA**
- 2. Processor Pipelining Hazards and Mechanisms**
- 3. Sources of Power and Energy consumption in Digital ICs**
- 4. Principles Behind Five Low-power Design Techniques**
- 5. How to Improve Energy Efficiency through Parallelism and Pipelining**
- 6. Memory Block Internal Architecture**
- 7. SRAM Cell and Read/Write Operation**
- 8. Memory Block Periphery Circuits**
- 9. Memory Decoder Design**
- 10. DRAM Cell and Read/Write Operation**
- 11. Dual-port Memory Architecture**
- 12. Cascading Memory blocks for More Width, Depth, and Ports**
- 13. FIFO Implementation**

- 14. Serialization versus Parallelization in Iterative Computations**
- 15. Principles of Pipelining and Restrictions of Loops**
- 16. C-Slow Technique for Pipelining Loops**
- 17. List Processor Design and Optimizations**
- 18. Modulo Scheduling**
- 19. Carry Select Adder Design**
- 20. Carry Lookahead and Parallel Prefix Adders**
- 21. Bit-Serial Addition**
- 22. Array Multiplier Design**
- 23. Carry Save Addition**
- 24. Signed Multiplication**
- 25. Bit-Serial Multiplication**
- 26. CSD Multiplier Design**
- 27. Booth Encoding Multiplication**
- 28. Log and Barrel Shifters Design and Analysis**
- 29. Use of Counters in Controller Design**
- 30. Effect of Clock Uncertainties on Maximum Clock Frequency**
- 31. Source of Clock Uncertainties**
- 32. Principles of Good Clock Distribution**
- 33. IR and dI/dt effects in Power distribution**
- 34. Types and Sources of Faults in ICs**
- 35. Hamming Codes**


How to Design a RISC-V Single-Cycle Processor from the ISA

Single-Cycle RISC-V RV32I Datapath

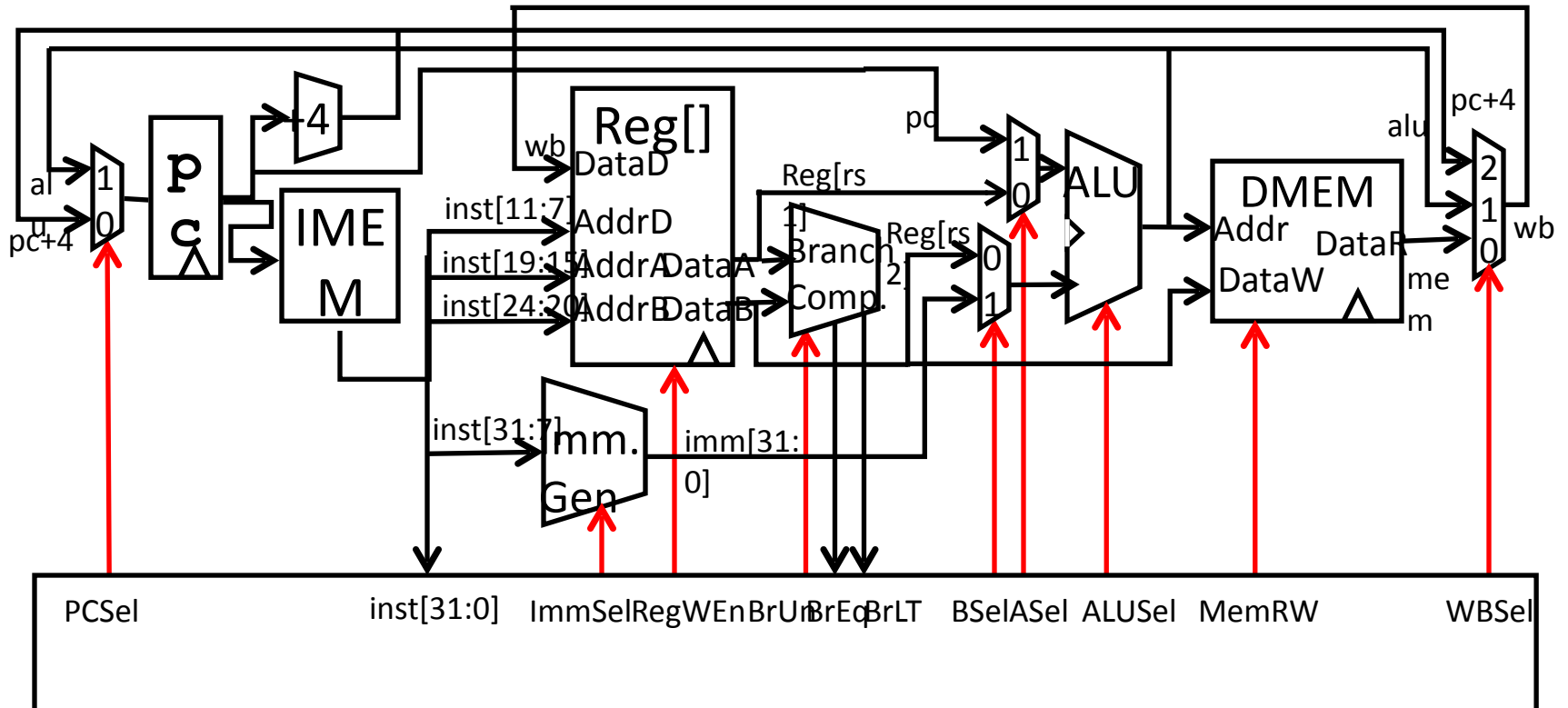


Processor Pipelining Hazards and Mechanisms

Pipelined Processor


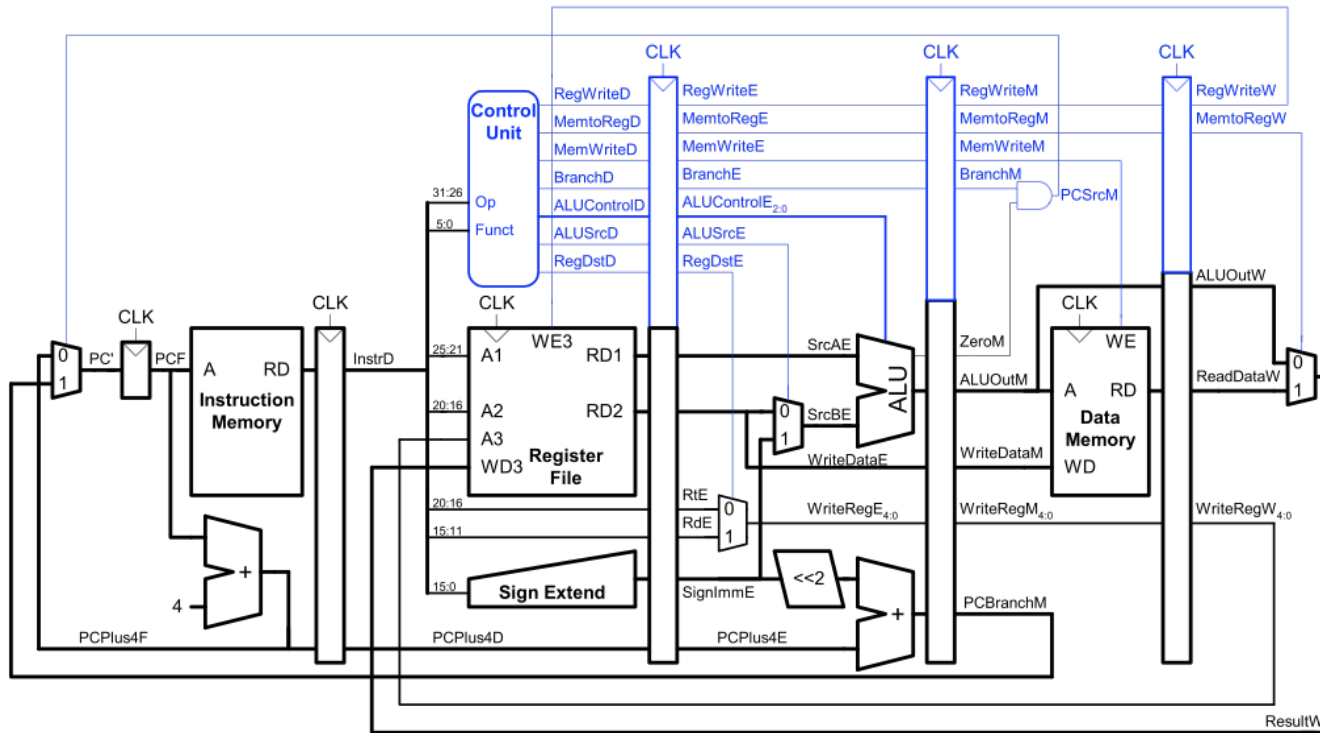


Sources of Power and Energy consumption in Digital ICs
 
$$\text{Total Power} = P_{\text{switching}} + P_{\text{short-circuit}} + P_{\text{leakage}}$$


  
$$I_{DSub} = k \cdot e^{\frac{-q \cdot V_T}{a \cdot k_a \cdot T}}$$




Some low-power design techniques

- * **Parallelism and pipelining**
- * **Power-down idle transistors**
- * **Slow down non-critical paths**
- * **Clock gating**
- * **Thermal management**

Principles Behind Five Low-power Design Techniques

And so, we can transform this:

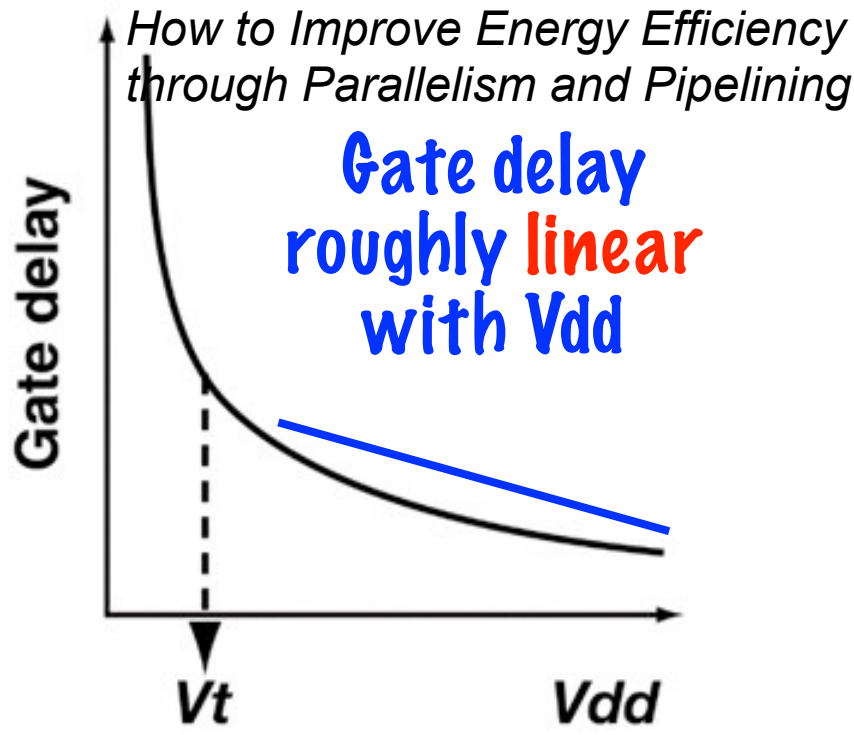

Vdd

Logic Block →

Freq = 1
 Vdd = 1
 Throughput = 1
 Power = 1
 Area = 1
 Pwr Den = 1

$P \sim F \times V_{dd}^2$
 $P \sim 1 \times 1^2$

Block processes stereo audio. 1/2 of clocks for "left", 1/2 for "right".

Into this:

Top block processes "left", bottom "right".

Vdd/2

Logic Block →

Freq = 0.5
 Vdd = 0.5
 Throughput = 1
 Power = 0.25
 Area = 2
 Pwr Den = 0.125

Logic Block →


$P \sim \#blks \times F \times V_{dd}^2$
 $P \sim 2 \times 1/2 \times 1/4 = 1/4$
 CV² power only

THIS MAGIC TRICK BROUGHT TO YOU BY CORY HALL ...

Memory Block Internal Architecture


Memory Architecture Overview

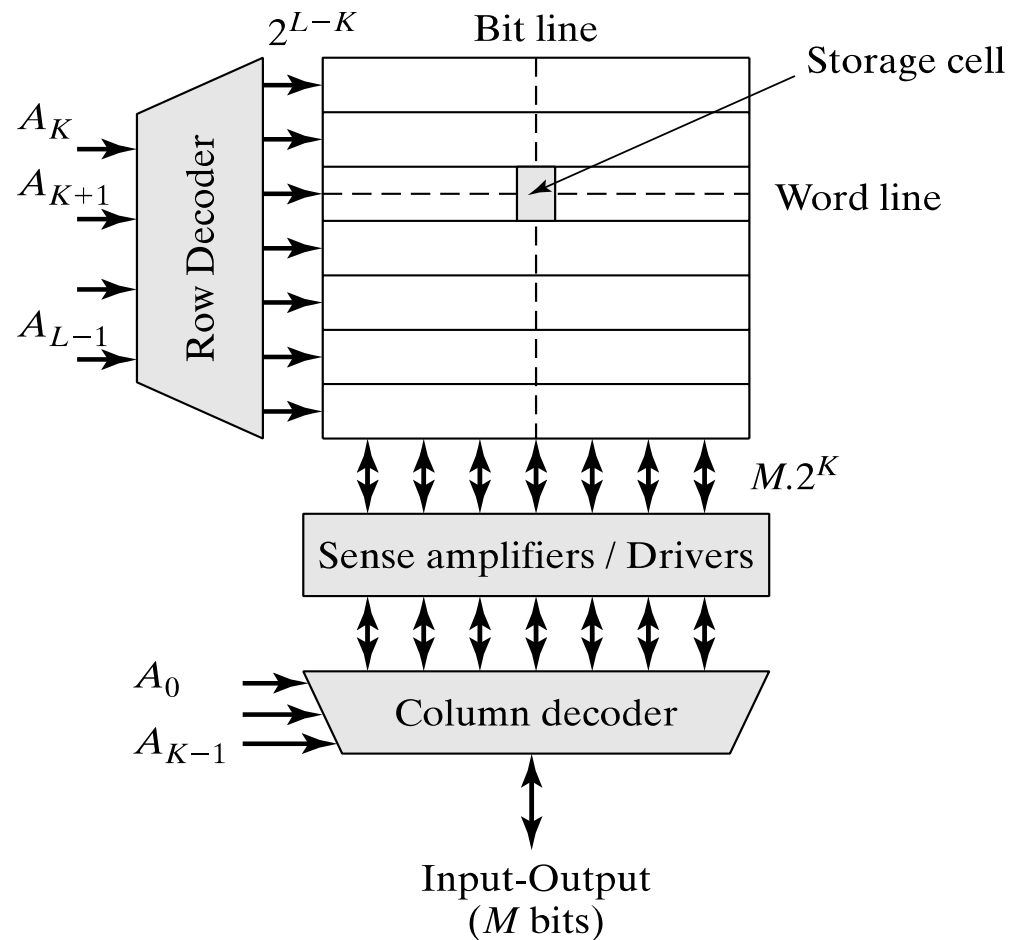- ❑ **Word lines** used to select a row for reading or writing
- ❑ **Bit lines** carry data to/from periphery
- ❑ **Core aspect ratio** keep close to 1 to help balance delay on word line versus bit line
- ❑ **Address bits** are divided between the two decoders
- ❑ **Row decoder** used to select word line
- ❑ **Column decoder** used to select one or more columns for input/output of data



SRAM Cell and Read/Write Operation

SRAM read/write operations

 


Periphery

- ❑ Decoders
- ❑ Sense Amplifiers
- ❑ Input/Output Buffers
- ❑ Control / Timing Circuitry

Memory Decoder Design

Row Decoder


 
- Expands $L-K$ address lines into 2^{L-K} word lines



- Example: decoder for 8Kx8 memory block
 - core arranged as 256x256 cells
 - Need 256 AND gates, each driving one word line

DRAM Cell and Read/Write Operation

1-Transistor DRAM Cell

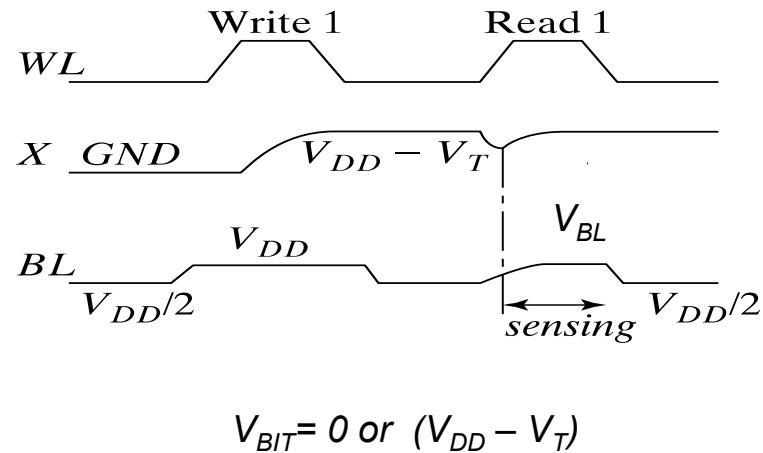 

Write: C_S is charged or discharged by asserting WL and BL.

Read: Charge redistribution takes place between bit line and storage capacitance


$C_S \ll C_{BL}$ Voltage swing is small; typically around 250 mV.

- ❑ To get sufficient C_S , special IC process is used
- ❑ Cell reading is destructive, therefore read operation always is followed by a write-back
- ❑ Cell loses charge (leaks away in ms - highly temperature dependent), therefore cells occasionally need to be “refreshed” - read/write cycle


Dual-port Memory Architecture

Dual-ported Memory Internals

 - Add decoder, another set of read/write logic, bits lines, word lines:



- Example cell: SRAM

 


- Repeat everything but cross-coupled inverters.
- This scheme extends up to a couple more ports, then need to add additional transistors.

Cascading Memory blocks for More Width, Depth, and Ports

Cascading Memory-Blocks

How to make larger memory blocks out of smaller ones.

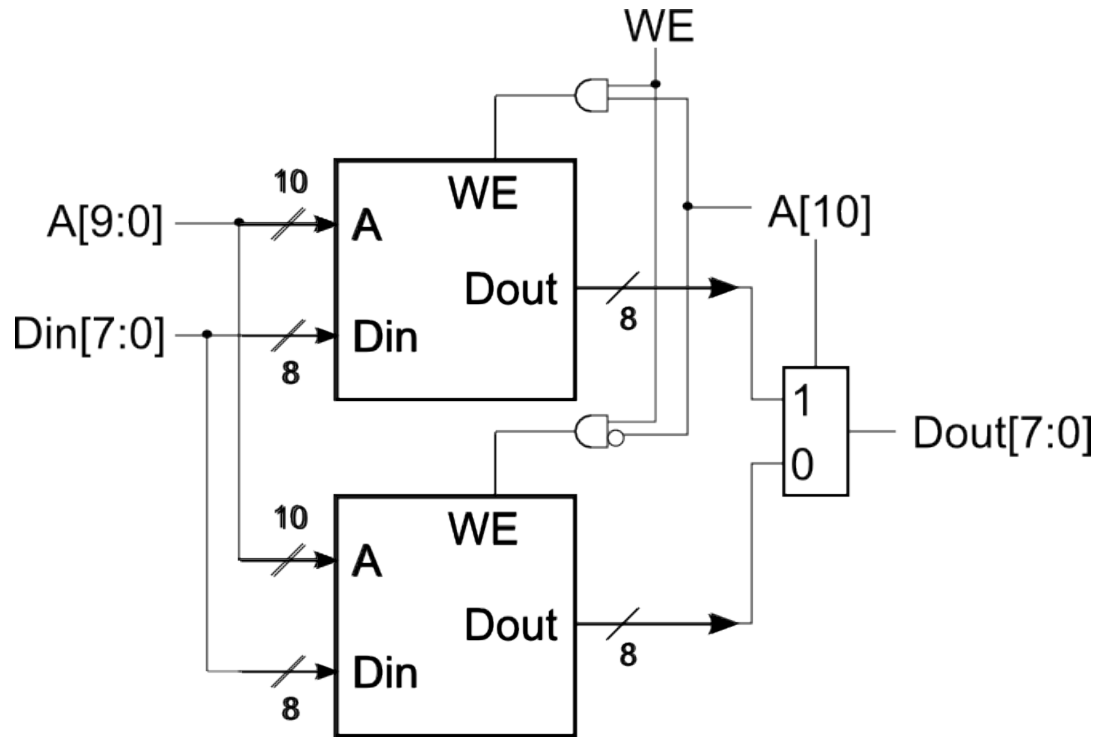Increasing the depth. Example: given $1K \times 8$, want $2K \times 8$



FIFO Implementation

FIFO Implementation Details

- Assume, dual-port memory with asynchronous read, synchronous write.
- Binary counter for each of read and write address. CEs (count enable) controlled by WE and RE.
- Equal comparator to see when pointers match.
- State elements for FULL and EMPTY flags:

WE	RE	equal*	EMPTY _i	FULL _i
0	0	0	0	0
0	0	1	EMPTY _{i-1}	FULL _{i-1}
0	1	0	0	0
0	1	1	1	0
1	0	0	0	0
1	0	1	0	1
1	1	0	0	0
1	1	1	EMPTY _{i-1}	FULL _{i-1}


- Control logic (FSM) with truth-table (draft) shown to left.

* Actually need 2 signals: “will be equal after read” and “will be equal after write”


Serialization versus Parallelization in Iterative Computations

Time-Multiplexing


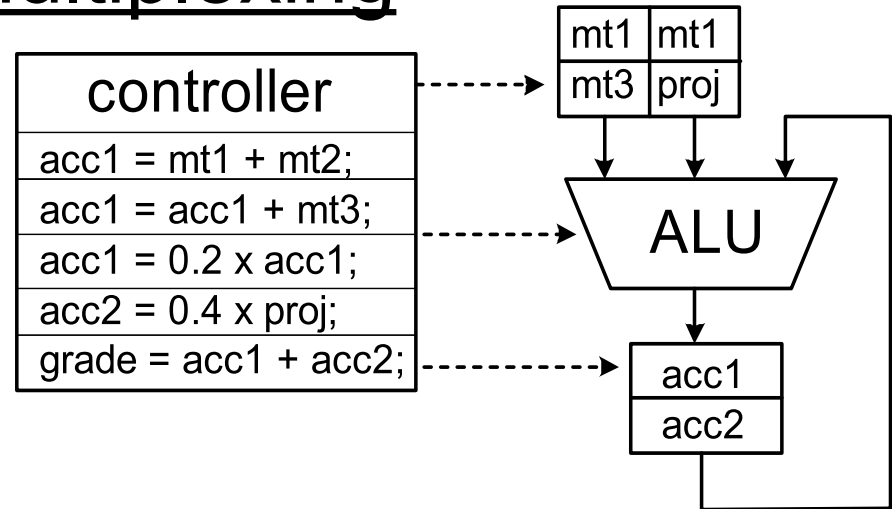
- *Time multiplex* single ALU for all adds and multiplies:
- Attempts to minimize cost at the expense of time.
 - Need to add extra register, muxes, control.



 - If we adopt above approach, we can then consider the combinational hardware circuit diagram as an *abstract computation-graph*.



  
Using other primitives, other coverings are possible.



- This time-multiplexing “covers” the computation graph by performing the action of each node one at a time. (Sort of *emulates* it.)

Limits on Pipelining

 - Without FF overhead, throughput improvement \propto # of stages.
- After many stages are added FF overhead begins to dominate:



- Other limiters to effective pipelining:
 - clock skew contributes to clock overhead
 - unequal stages
 - FFs dominate *cost*
 - clock distribution power consumption
 - **feedback (dependencies between loop iterations)**



Principles of Pipelining and Restrictions of Loops

Pipelining Loops with Feedback

“Loop carry dependency”


However, we can overlap the “non-feedback” part of the iterations:

  Add is associative and commutative. Therefore we can reorder the computation to shorten the delay of the feedback path:



“Shorten” the feedback path.
 
$$y_i = (y_{i-1} + x_i) + a = (a + x_i) + y_{i-1}$$




- Pipelining is limited to 2 stages.

C-Slow Technique for Pipelining Loops

“C-slow” Technique

 - Essentially this means we go ahead and cut feedback path:



- This makes operations in adjacent pipeline stages independent and allows full cycle for each:


Multithreaded Processors use this.

add ₁	x+b	x+b	x+b	x+b	x+b	x+b
mult	ay	ay	ay	ay	ay	ay
add ₂	y	y	y	y	y	y

List Processor Design and Optimizations

5. Optimization, Architecture #4

□ Datapath:

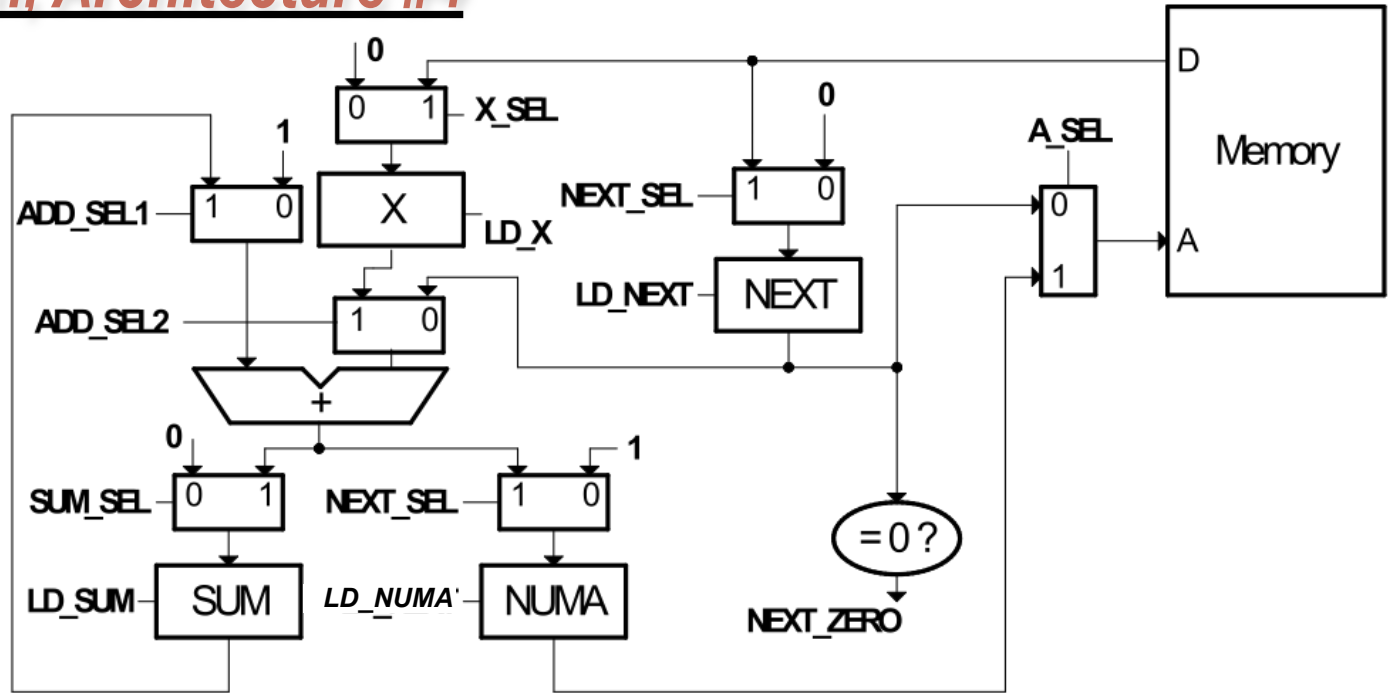

□ Incremental cost:

- Addition of another register & mux, adder mux, and control.

□ Performance: find max time of the four actions


1. $X \leftarrow \text{Memory}[\text{NUMA}]$,
 $\text{NUMA} \leftarrow \text{NEXT} + 1$;

$$0.5 + 1 + 10 + 1 + 0.5 = 13\text{ns}$$

$$\text{same for all} \Rightarrow T > 13\text{ns}, F < 77\text{MHz}$$

2. $\text{NEXT} \leftarrow \text{Memory}[\text{NEXT}]$,
 $\text{SUM} \leftarrow \text{SUM} + X$;

Modulo Scheduling List Processor

 

- Assuming a single adder and a single ported memory. Minimal schedule section length = 2. Because both memory and adder are used for 2 cycles during one iteration.

memory	next _i	
adder		numa _i

memory	next _i	x _{i-1}
adder		numa _i

wrap-around,
decrease subscript

memory	next _i	x _{i-1}
adder	sum _{i-2}	numa _i

wrap-around,
decrease subscript


- Finished schedule for 4 iterations:

Memory	next ₁		next ₂	x ₁	next ₃	x ₂	next ₄	x ₃	
adder		numa ₁		numa ₂	sum ₁	numa ₃	sum ₂	numa ₄	sum ₃

Carry Select Adder Design

Carry Select Adder

 Extending Carry-select to multiple blocks



What is the optimal # of blocks and # of bits/block?



- If blocks too small delay dominated by total mux delay
- If blocks too large delay dominated by adder ripple delay

\sqrt{N} stages of \sqrt{N} bits

$T \propto \text{sqrt}(N)$,
 Cost $\approx 2 \cdot \text{ripple} + \text{muxes}$

Carry Lookahead and Parallel Prefix Adders

Parallel Prefix Adder Example

  


$$\begin{aligned}
 G &= g_3 + g_2 p_3 + (g_1 + g_0 p_1) p_3 p_2 \\
 &= g_3 + g_2 p_3 + g_1 p_3 p_2 + g_0 p_3 p_2 p_1 \\
 &= c_4
 \end{aligned}$$

$$s_i = a_i \oplus b_i \oplus c_i = p_i \oplus c_i$$

Bit-serial Addder

Bit-Serial Addition

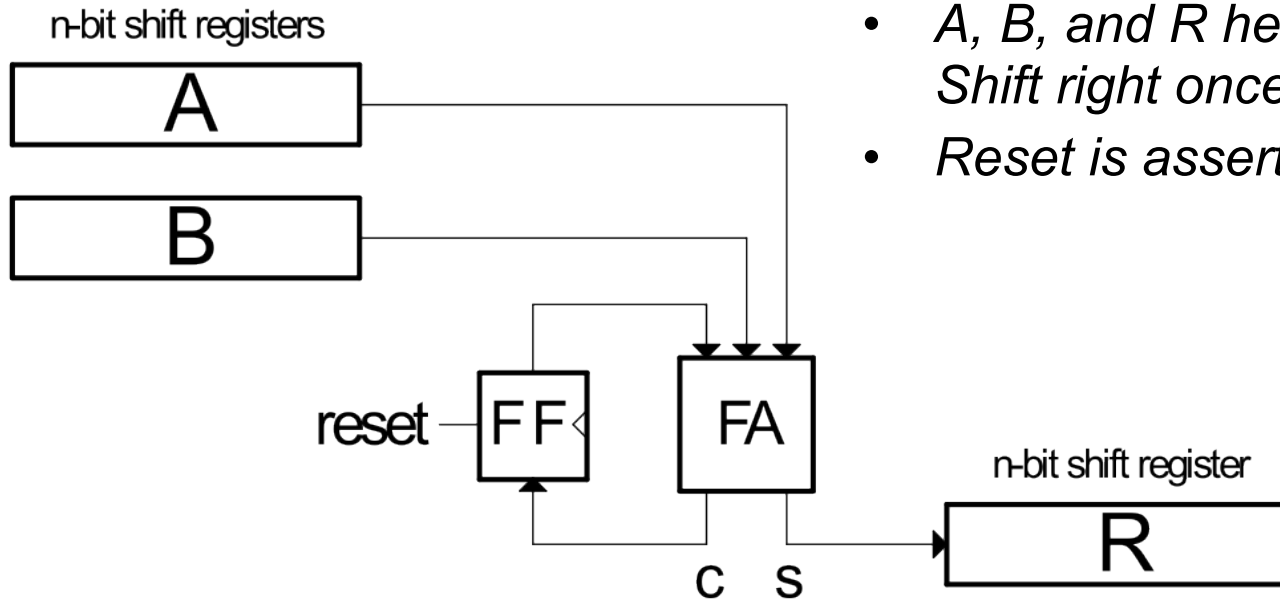

- *A, B, and R held in shift-registers. Shift right once per clock cycle.*
- *Reset is asserted by controller.*

- Addition of 2 n-bit numbers:
 - takes n clock cycles,
 - uses 1 FF, 1 FA cell, plus registers
 - the bit streams may come from or go to other circuits, therefore the registers might not be needed.


Combinational Multiplier (unsigned)

$$\begin{array}{r} X3 \quad X2 \quad X1 \quad X0 \\ * \quad Y3 \quad Y2 \quad Y1 \quad Y0 \\ \hline \end{array}$$

← multiplicand
← multiplier

$$\begin{array}{r} X3Y0 \quad X2Y0 \quad X1Y0 \quad X0Y0 \\ + \quad X3Y1 \quad X2Y1 \quad X1Y1 \quad X0Y1 \\ + \quad X3Y2 \quad X2Y2 \quad X1Y2 \quad X0Y2 \\ + \quad X3Y3 \quad X2Y3 \quad X1Y3 \quad X0Y3 \\ \hline z7 \quad z6 \quad z5 \quad z4 \quad z3 \quad z2 \quad z1 \quad z0 \end{array}$$

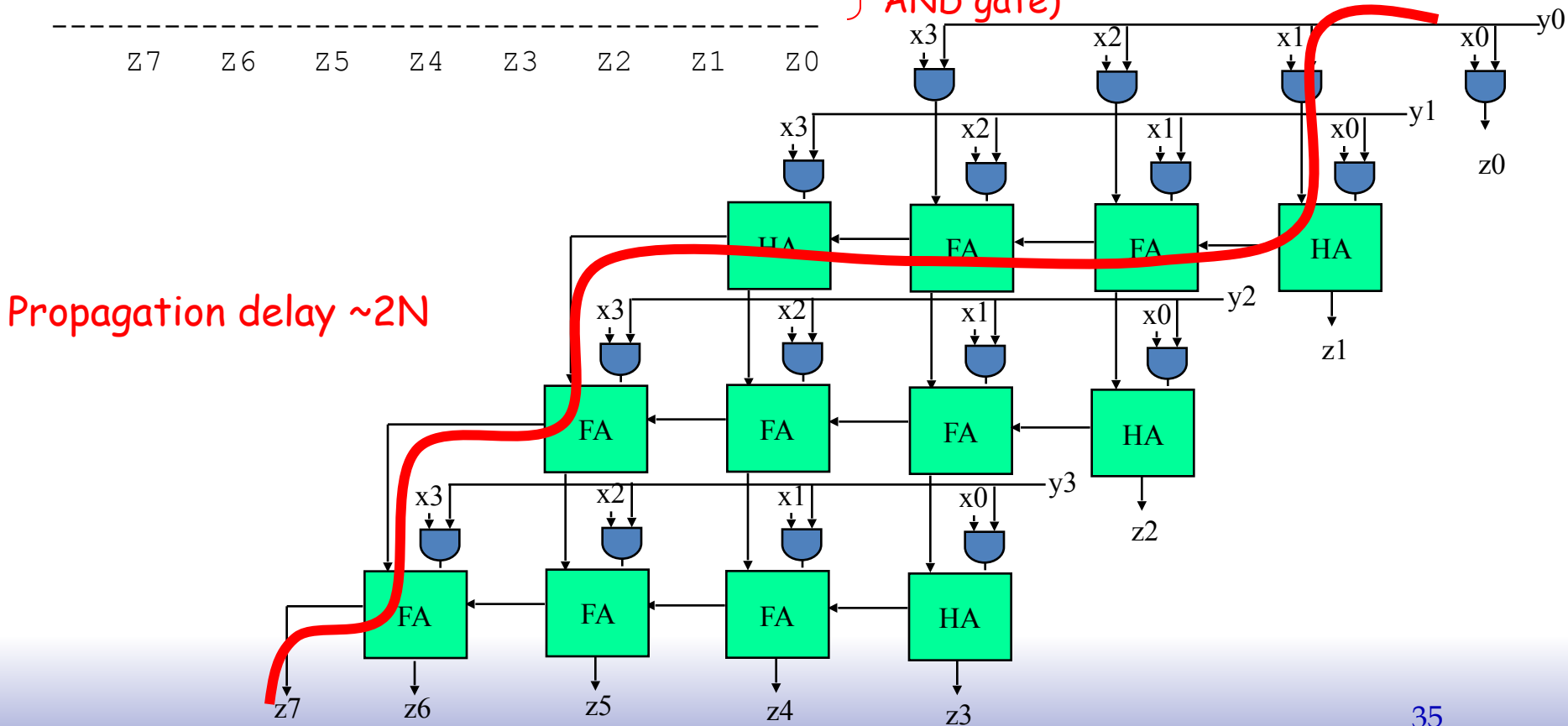Partial products, one for each bit in multiplier (each bit needs just one AND gate)



Carry-Save Addition

- Speeding up multiplication is a matter of speeding up the summing of the partial products.
- “Carry-save” addition can help.
- Carry-save addition passes (saves) the carries to the output, rather than propagating them.

- Example: sum three numbers, $3_{10} = 0011$, $2_{10} = 0010$, $3_{10} = 0011$


$$\begin{array}{r}
 3_{10} \quad 0011 \\
 + 2_{10} \quad 0010 \\
 \hline
 c \quad 0100 = 4_{10} \\
 s \quad 0001 = 1_{10} \\
 \hline
 3_{10} \quad 0011 \\
 c \quad 0010 = 2_{10} \\
 s \quad 0110 = 6_{10} \\
 \hline
 1000 = 8_{10}
 \end{array}$$

The top two additions (0011 + 0010 and 0011 + 0010) are grouped by a right-facing curly brace labeled "carry-save add".
 The bottom two additions (0011 + 0010 and 0011 + 0010) are grouped by a left-facing curly brace labeled "carry-propagate add".

- In general, *carry-save* addition takes in 3 numbers and produces 2.
 - Sometimes called a “3:2 compressor”: 3 input signals into 2 in a potentially lossy operation
- Whereas, *carry-propagate* takes 2 and produces 1.
- With this technique, we can avoid carry propagation until final addition


Signed Multiplication

2's Complement Multiplication

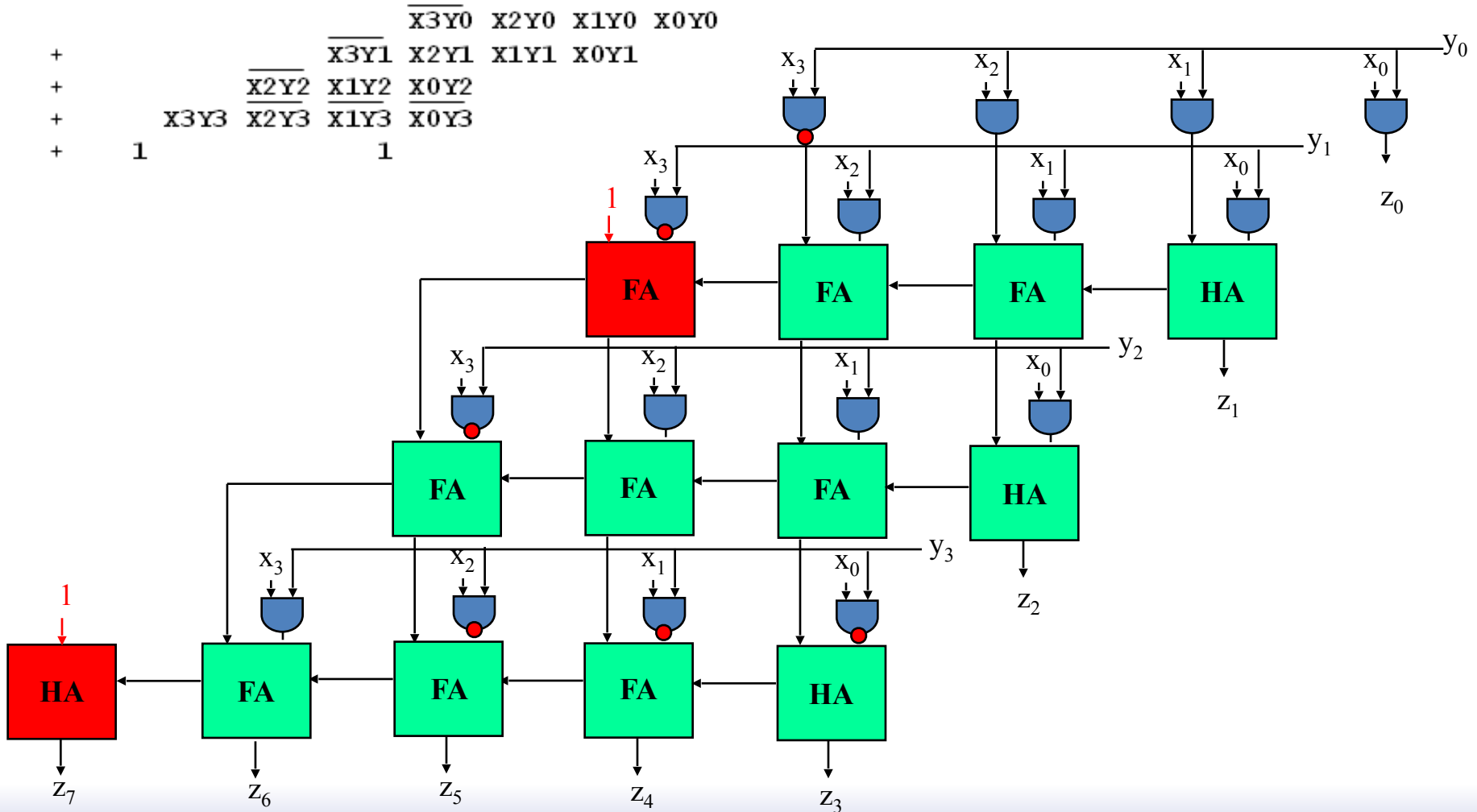

Bit-serial Multiplier

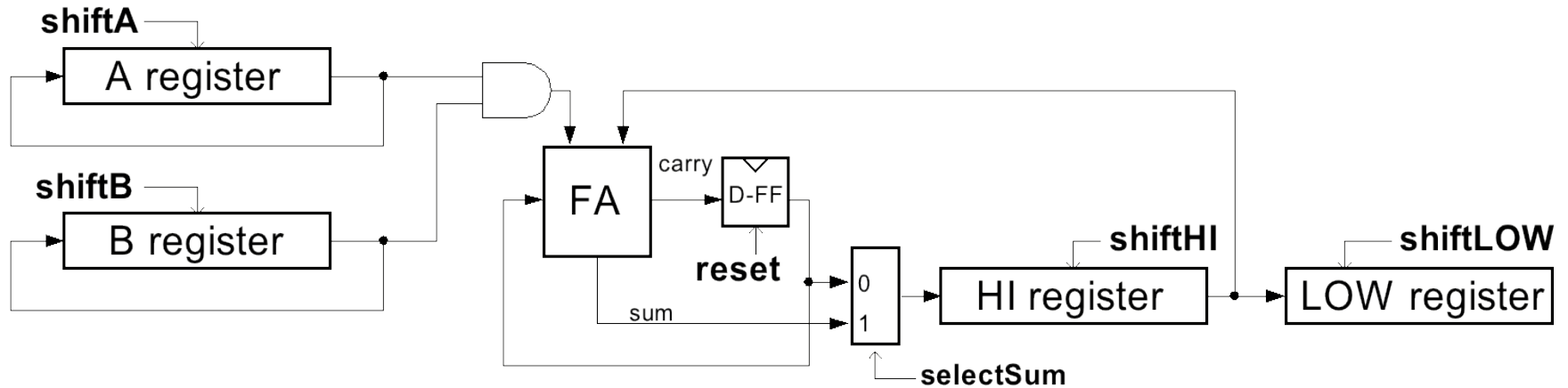- Bit-serial multiplier (n^2 cycles, one bit of result per n cycles):



- Control Algorithm:

```
repeat n cycles { // outer (i) loop
  repeat n cycles{ // inner (j) loop
    shiftA, selectSum, shiftHI
  }
  shiftB, shiftHI, shiftLOW, reset
}
```

Note: The occurrence of a control signal x means $x=1$. The absence of x means $x=0$.

Booth recoding

Booth Encoding Multiplication

(On-the-fly canonical signed digit encoding!)

current bit pair

from previous bit pair

B_{K+1}	B_K	B_{K-1}	action
0	0	0	add 0
0	0	1	add A
0	1	0	add A
0	1	1	add 2^*A
1	0	0	sub 2^*A
1	0	1	sub A
1	1	0	sub A
1	1	1	add 0

$$\begin{aligned}
 B_{K+1,K}^*A &= 0^*A \rightarrow 0 \\
 &= 1^*A \rightarrow A \\
 &= 2^*A \rightarrow 4A - 2A \\
 &= 3^*A \rightarrow 4A - A
 \end{aligned}$$

$$\leftarrow -2^*A + A$$

$$\leftarrow -A + A$$

A "1" in this bit means the previous stage needed to add 4^*A . Since this stage is shifted by 2 bits with respect to the previous stage, adding 4^*A in the previous stage is like adding A in this stage!

Canonic Signed Digit Representation

- CSD represents numbers using 1, $\bar{1}$, & 0 with the least possible number of non-zero digits.
 - Strings of 2 or more non-zero digits are replaced.
 - Leads to a unique representation.

- To form CSD representation might take 2 passes:

- First pass: replace all occurrences of 2 or more 1's:

$$01..10 \text{ by } 10..\bar{1}0$$

- Second pass: same as above, plus replace $01\bar{1}0$ by 0010 and $0\bar{1}10$ by $00\bar{1}0$

- Examples:

$$011101 = 29$$

$$100\bar{1}01 = 32 - 4 + 1$$

$$0010111 = 23$$

$$001100\bar{1}$$

$$010\bar{1}00\bar{1} = 32 - 8 - 1$$

$$0110110 = 54$$

$$10\bar{1}10\bar{1}0$$


$$100\bar{1}0\bar{1}0 = 64 - 8 - 2$$

- Can we further simplify the multiplier circuits?

Log and Barrel Shifters Design and Analysis


Log Shifter / Rotator

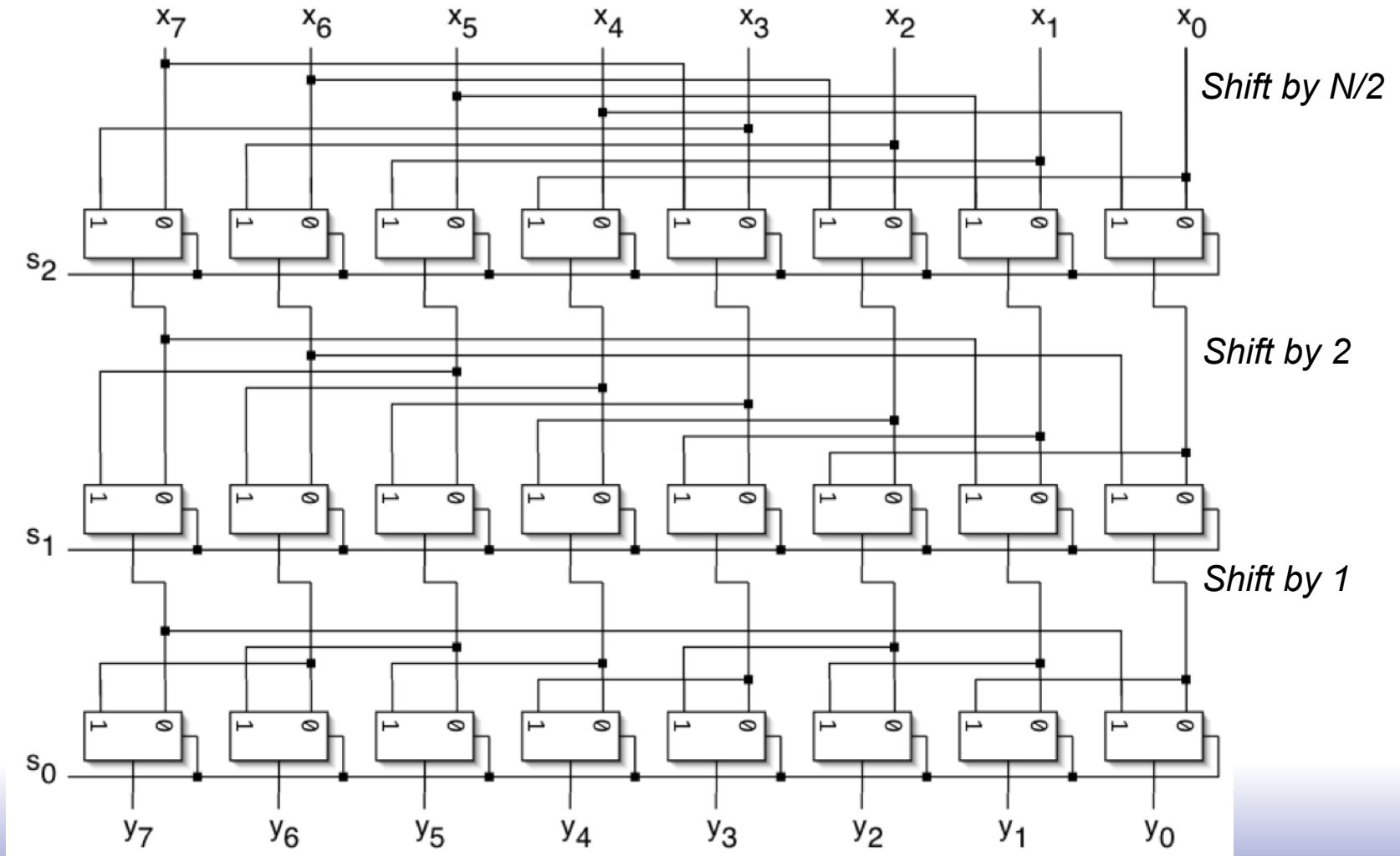- Log(N) stages, each shifts (or not) by a power of 2 places, $S=[s_2;s_1;s_0]$:



Barrel Shifter

 Log and Barrel Shifters Design and Analysis




Cost/delay?

- (don't forget the decoder)

Controller using Counters

Use of Counters in Controller Design

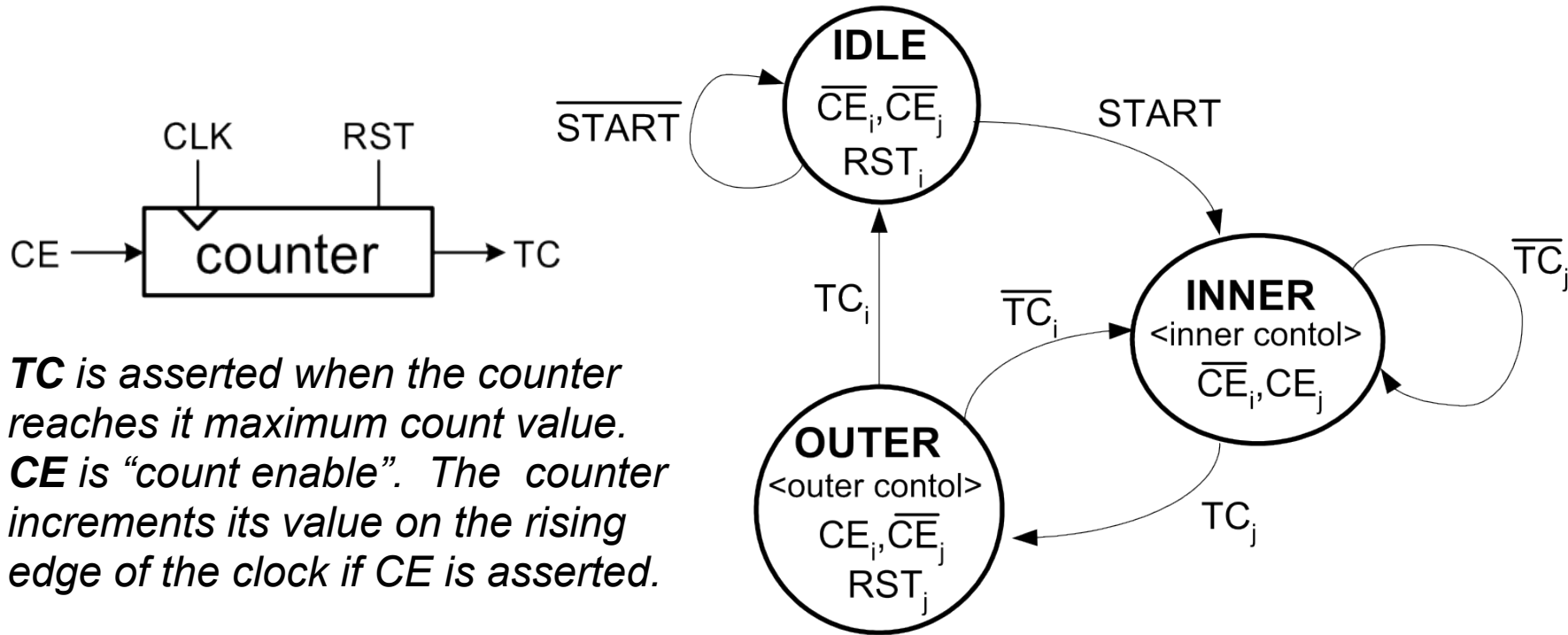- **State Transition Diagram:**
 - Assume presence of two binary counters. An “i” counter for the outer loop and “j” counter for inner loop.



Clock Constraints in Edge-Triggered Systems

If launching edge is late and receiving edge is early, the data will not be too late if:

$$t_{clk-q,max} + t_{logic,max} + t_{setup} < T_{CLK} - t_{JS,1} - t_{JS,2} + \delta$$

Minimum cycle time is determined by the maximum delays through the logic

$$t_{clk-q,max} + t_{logic,max} + t_{setup} - \delta + 2t_{JS} < T_{CLK}$$

Skew can be either positive or negative

Jitter t_{JS} usually expressed as peak-to-peak or $n \times$ RMS value

Clock Constraints in Edge-Triggered Systems

If launching edge is early and receiving edge is late:

$$t_{clk-q,min} + t_{logic,min} - t_{JS,1} > t_{hold} + t_{JS,2} + \delta$$

Minimum logic delay


$$t_{clk-q,min} + t_{logic,min} > t_{hold} + 2t_{JS} + \delta$$

(This assumes jitter at launching and receiving clocks are independent – which usually is not true)

Source of Clock Uncertainties



Clock Uncertainties

Sources of clock uncertainty

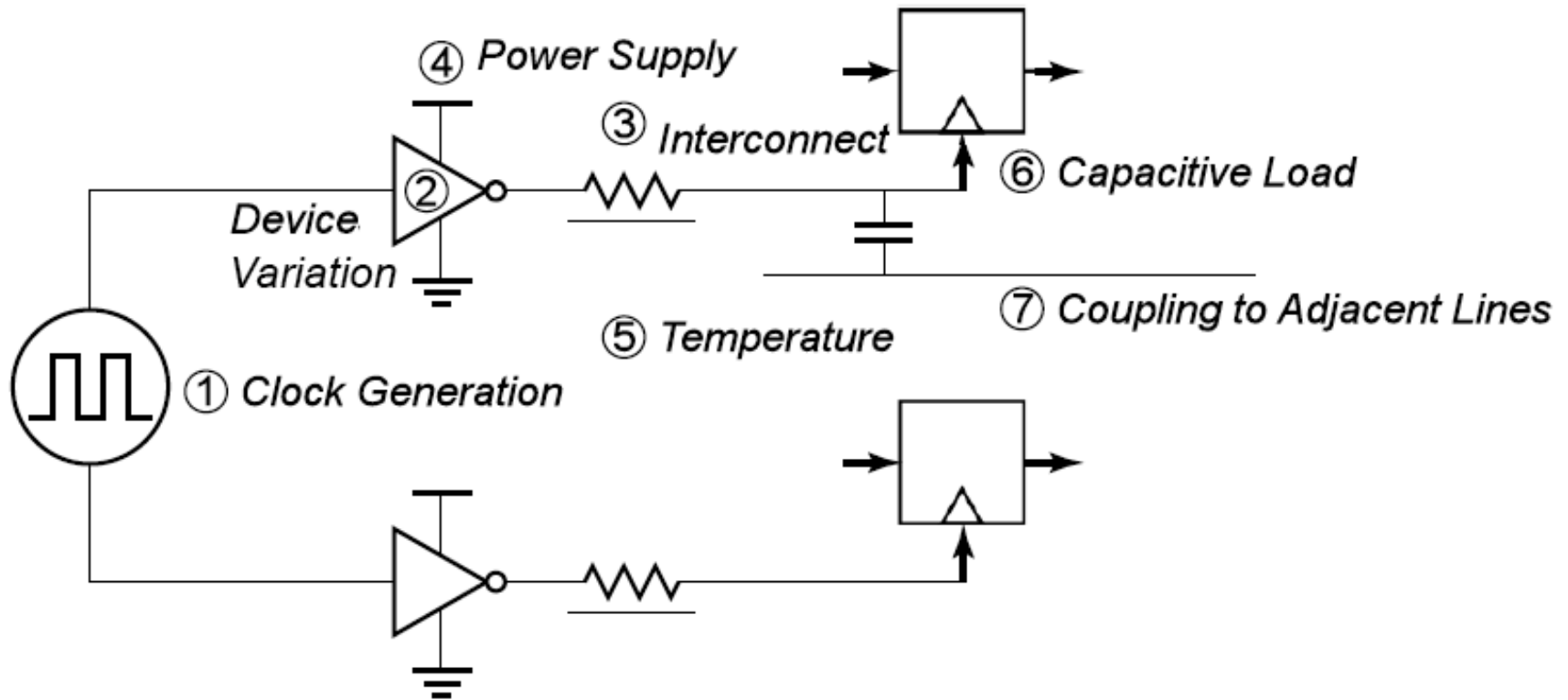

H-Tree


Principles of Good Clock Distribution

  

Equal wire length/number of buffers to get to every location

Power Supply Impedance

- ❑ No voltage source is ideal - $||Z|| > 0$
- ❑ Two principal elements increase Z:
 - Resistance of supply lines (IR drop)
 - Inductance of supply lines ($L \cdot di/dt$ drop)

 

Types of Faults in Digital Designs

- **Design Bugs** (function, timing, power draw)
 - detected and corrected at design time through testing and verification (simulation, static checks)
- **Manufacturing Defects** (violation of design rules, impurities in processing, statistical variations)
 - post production testing for sorting
 - spare on-chip resources for repair
- **Runtime Failures** (physical effects and environmental conditions)
 - assuming design is correct and no manufacturing defects

Hamming Error Correcting Code

- Use more parity bits to pinpoint bit(s) in error, so they can be corrected.
- Example: Single error correction (SEC) on 4-bit data
 - use 3 parity bits, with 4-data bits results in 7-bit code word
 - 3 parity bits sufficient to identify any one of 7 code word bits
 - overlap the assignment of parity bits so that a single error in the 7-bit word can be corrected
- **Procedure:** group parity bits so they correspond to subsets of the 7 bits:
 - p_1 protects bits 1,3,5,7
 - p_2 protects bits 2,3,6,7
 - p_3 protects bits 4,5,6,7

1 2 3 4 5 6 7
 p_1 p_2 d_1 p_3 d_2 d_3 d_4

Bit position number

001 = 1_{10}
011 = 3_{10}
101 = 5_{10}
111 = 7_{10}

p_1

010 = 2_{10}
011 = 3_{10}
110 = 6_{10}
111 = 7_{10}

p_2

100 = 4_{10}
101 = 5_{10}
110 = 6_{10}
111 = 7_{10}

p_3

Note:
number bits
from left to
right.

The End.

- ❑ Special thanks to our GSIs: Sean and Tan. And to Charles (reader).
- ❑ Good luck on the final.
- ❑ Thanks for a great semester!