



EECS 151/251A

Spring 2021

**Digital Design and Integrated
Circuits**

Instructor:

John Wawrzynek

**Lecture 7 & 8: Finite
State Machines**

Announcements

- ❑ Virtual Front Row for today 2/11:
 - ❑ Naomi Sagan
 - ❑ Peter Trost
 - ❑ William Hsu
 - ❑ Neil Kulkarni
 - ❑ Robert Puccinelli
- ❑ **Keep those questions/comments coming please! (they help determine your class participation points)**
- ❑ HW 3 due Monday (2/15).
- ❑ HW 2 being graded. Solution posted Friday.
- ❑ Comments on problem sets?





Finite State Machines



Finite State Machines (FSMs)

FSMs:

  - Can model behavior of *any sequential circuit*
- Useful representation for designing sequential circuits
- As with all sequential circuits: output depends on present *and* past inputs
 - effect of past inputs represented by the current *state*
- Behavior is represented by **State Transition Diagram**:
 - traverse one edge per clock cycle.



FSM Implementation

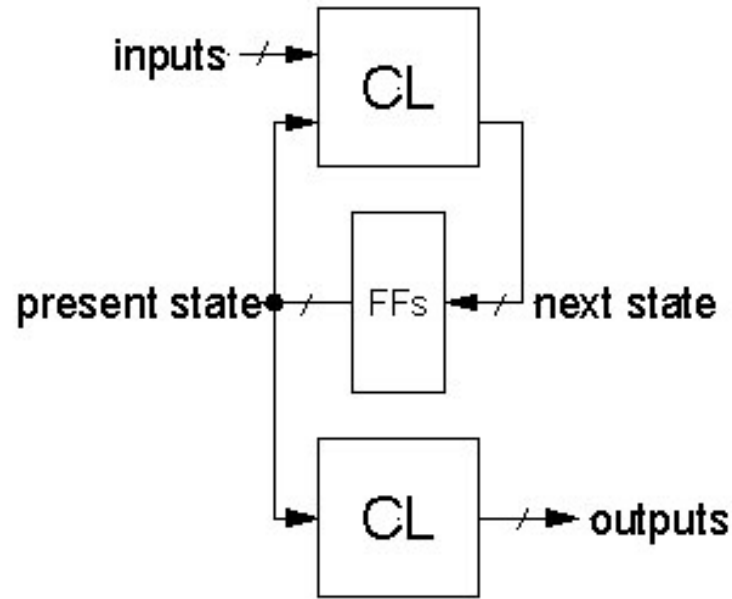 


- ❑ Flip-flops form *state register*
- ❑ number of states $\leq 2^{\text{number of flip-flops}}$
- ❑ CL (combinational logic) calculates next state and output
- ❑ **Remember: The FSM follows exactly one edge per cycle.**

Later we will learn how to implement in Verilog. Now we learn how to design “by hand” to the gate level.


FSM Example: Parity Checker

A string of bits has “even parity” if the number of 1's in the string is even.

 - Design a circuit that accepts a infinite serial stream of bits, and outputs a 0 if the parity thus far is even and outputs a 1 if odd:




 example: 0 0 1 1 1 0 1
 even even odd even odd odd even




Next we take this example through the “formal design process”. But first, can you guess a circuit that performs this function?

By-hand Design Process (a)

 

“State Transition Diagram”

 
- circuit is in one of two “states”.
- transition on each cycle with each new input, over exactly one arc (edge).
- Output depends on which state the circuit is in.



By-hand Design Process (b)

State Transition Table:

<i>present state</i>	<i>OUT</i>	<i>IN</i>	<i>next state</i>
<i>EVEN</i>	<i>0</i>	<i>0</i>	<i>EVEN</i>
<i>EVEN</i>	<i>0</i>	<i>1</i>	<i>ODD</i>
<i>ODD</i>	<i>1</i>	<i>0</i>	<i>ODD</i>
<i>ODD</i>	<i>1</i>	<i>1</i>	<i>EVEN</i>

 

Invent a code to represent states:

Let 0 = EVEN state, 1 = ODD state

<i>present state (ps)</i>	<i>OUT</i>	<i>IN</i>	<i>next state (ns)</i>
0	0	0	0
0	0	1	1
1	1	0	1
1	1	1	0

Derive logic equations from table (how?):

$$OUT = PS$$

$$NS = PS \text{ xor } IN$$

By-hand Design Process (c)


Logic equations from table:

$$OUT = PS$$

$$NS = PS \text{ xor } IN$$

□ Circuit Diagram:

 - XOR gate for NS calculation
- Flip-Flop to hold present state
- no logic needed for output in this example.



“Formal” By-hand Design Process

Review of Design Steps:

1. Specify **circuit function** (English)
2. Draw **state transition diagram**
3. Write down **symbolic state transition table**
4. Write down **encoded state transition table**
5. Derive **logic equations**
6. Derive **circuit diagram**


Register to hold state

Combinational Logic for Next State and Outputs



Another FSM Design Example


Combination Lock Example

 

- Used to allow entry to a locked room:
2-bit serial combination. Example 01,11:
 1. Set switches to 01, press ENTER
 2. Set switches to 11, press ENTER
 3. OPEN is asserted (OPEN=1).

If wrong code, ERROR is asserted (after second combo word entry).
Press Reset at anytime to try again.

Combinational Lock STD

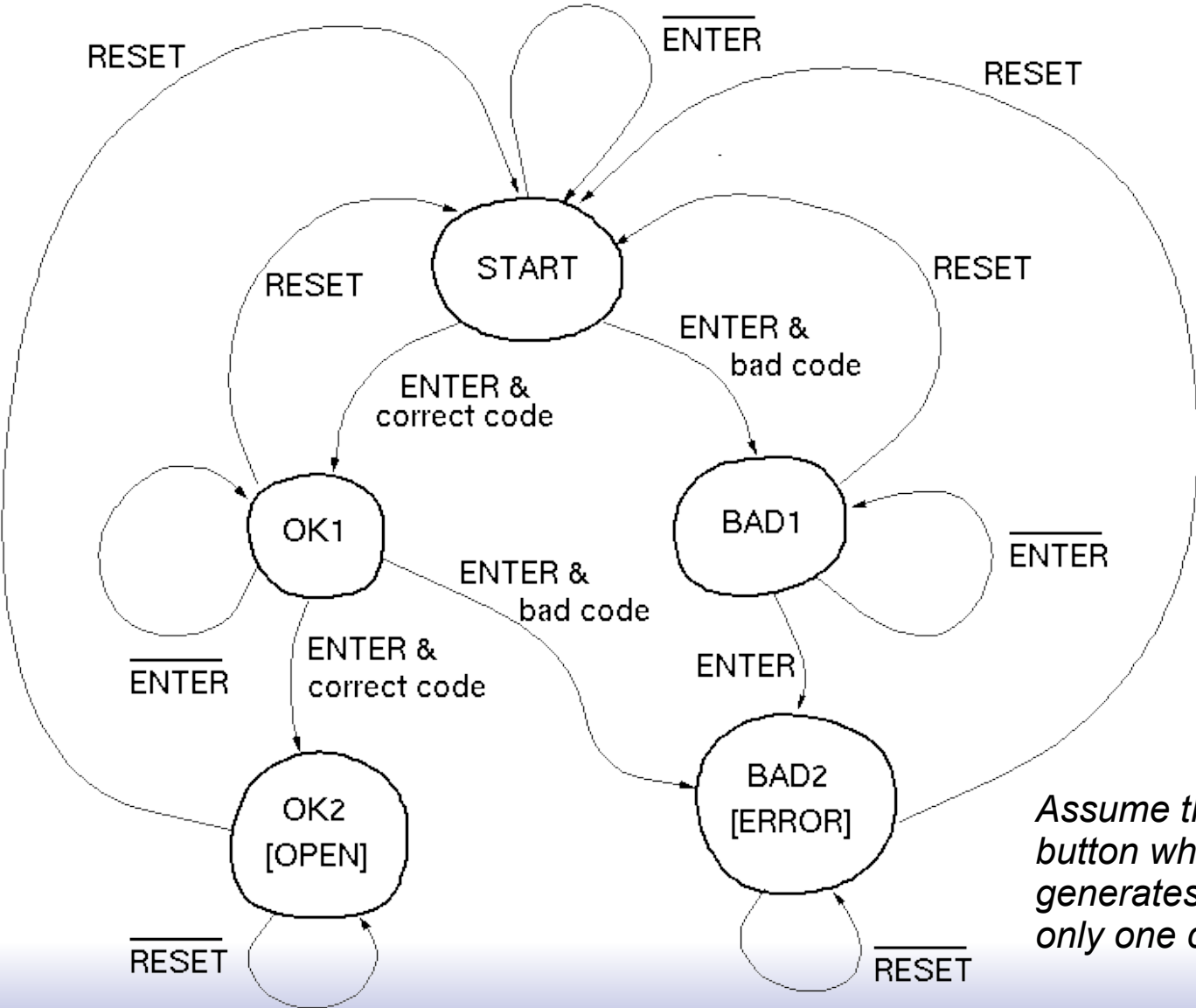


Assume the ENTER button when pressed generates a pulse for only one clock cycle.

Symbolic State Transition Table

RESET	ENTER	COM1	COM2	Preset State	Next State	OPEN	ERROR
0	0	*	*	START	START	0	0
0	1	0	*	START	BAD1	0	0
0	1	1	*	START	OK1	0	0
0	0	*	*	OK1	OK1	0	0
0	1	*	0	OK1	BAD2	0	0
0	1	*	1	OK1	OK2	0	0
0	*	*	*	OK2	OK2	1	0
0	0	*	*	BAD1	BAD1	0	0
0	1	*	*	BAD1	BAD2	0	0
0	*	*	*	BAD2	BAD2	0	1
1	*	*	*	*	START	0	0

 Decoder logic for checking combination (01,11):




* represents "wild card" - expands to all combinations


Encoded ST Table

ENTER	COM1	COM2	PS2	PS1	PS0	NS2	NS1	NS0
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0
0	1	1	0	0	0	0	0	0
1	0	0	0	0	0	1	0	0
1	0	1	0	0	0	1	0	0
1	1	0	0	0	0	0	0	1
1	1	1	0	0	0	0	0	1
0	0	0	0	0	1	0	0	1
0	0	1	0	0	1	0	0	1
0	1	0	0	0	1	0	0	1
0	1	1	0	0	1	0	0	1
1	0	0	0	0	1	1	0	1
1	1	0	0	0	1	1	0	1
1	0	1	0	0	1	0	1	1
1	1	1	0	0	1	0	1	1
0	0	0	0	1	1	0	1	1
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	0	1	1	0	1	1
1	0	0	0	1	1	0	1	1
1	0	1	0	1	1	0	1	1
1	1	0	0	1	1	0	1	1
1	1	1	0	1	1	0	1	1
0	0	0	1	0	0	1	0	0
0	0	1	1	0	0	1	0	0
0	1	0	1	0	0	1	0	0
0	1	1	1	0	0	1	0	0
1	0	0	1	0	0	1	0	1
1	0	1	1	0	0	1	0	1
1	1	1	1	0	0	1	0	1
0	0	0	1	0	1	1	0	1
0	0	1	1	0	1	1	0	1
0	1	0	1	0	1	1	0	1
0	1	1	1	0	1	1	0	1
1	0	0	1	0	1	1	0	1
1	0	1	1	0	1	1	0	1
1	1	0	1	0	1	1	0	1
1	1	1	1	0	1	1	0	1

 - **Assign states:**
START=000, OK1=001, OK2=011
BAD1=100, BAD2=101
- **Omit reset.** Assume that primitive flip-flops has reset input.
- **Rows not shown have don't cares in output.**
 Correspond to invalid PS values.




 
- **What are the output functions for OPEN and ERROR?**





Moore Versus Mealy Machines

FSM Implementation Notes

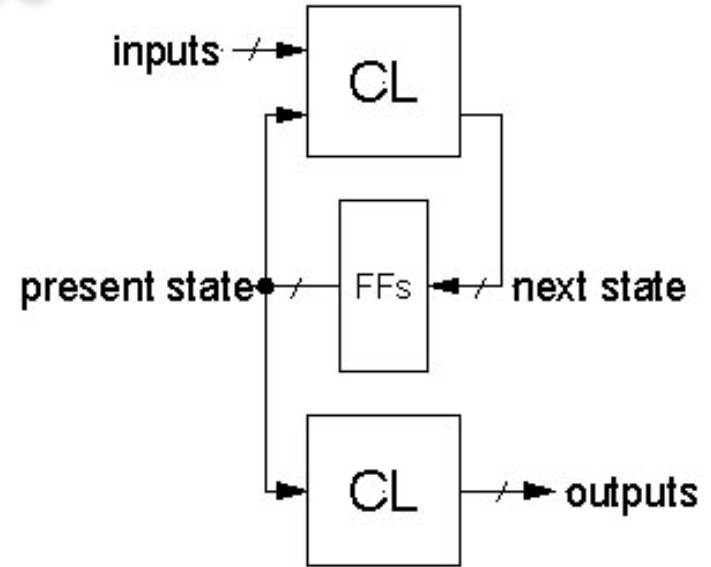 - All examples so far generate output based only on the present state, commonly called a “Moore Machine”:



  - If output functions include both present state and input then called a “Mealy Machine”:




Finite State Machines

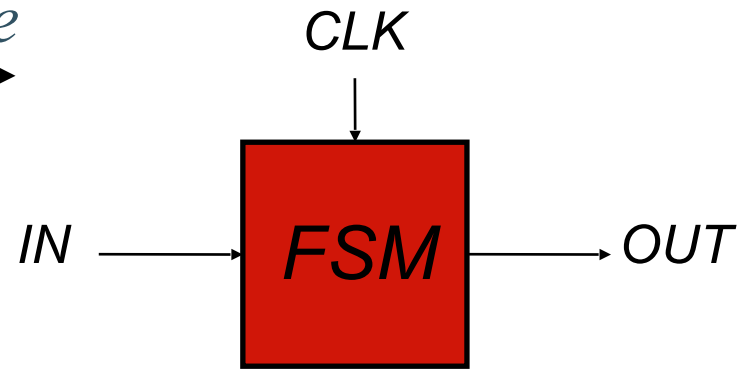Example: Edge Detector

Bits are received one at a time (one per cycle),


such as: 000111010 $\xrightarrow{\text{time}}$



Design a circuit that asserts its output for one cycle when the input bit stream changes from 0 to 1.

We'll try two different solutions: Moore then Mealy.

 State Transition Diagram Solution A - Moore




	<i>IN</i>	<i>PS</i>	<i>NS</i>	<i>OUT</i>
<i>ZERO</i>	0	00	00	0
	1	00	01	0
<i>CHANGE</i>	0	01	00	1
	1	01	11	1
<i>ONE</i>	0	11	00	0
	1	11	11	0

Solution A, circuit derivation

	IN	PS	NS	OUT
ZERO	0	00	00	0
	1	00	01	0
CHANGE	0	01	00	1
	1	01	11	1
ONE	0	11	00	0
	1	11	11	0

		PS				
		00	01	11	10	
IN	0	0	0	0	-	$NS_1 = IN PS_0$
	1	0	1	1	-	


		PS				
		00	01	11	10	
IN	0	0	0	0	-	$NS_0 = IN$
	1	1	1	1	-	

 

		PS				
		00	01	11	10	
IN	0	0	1	0	-	$OUT = \overline{PS_1} PS_0$
	1	0	1	0	-	

Solution B - Mealy

 
Output depends not only on PS but also on input, IN



Let ZERO=0,
ONE=1


IN	PS	NS	OUT
0	0	0	0
0	1	0	0
1	0	1	1
1	1	1	0
 
$$NS = IN, \text{ OUT} = IN \text{ PS}'$$



What's the intuition about this solution?

Edge detector timing diagrams

 


- *Solution A: both edges of output follow the clock*
- *Solution B: output rises with input rising edge and is asynchronous wrt the clock, output falls synchronous with next clock edge*

FSM Comparison

Solution A

Moore Machine

 
- *output function only of PS*
- *maybe more states*
- *synchronous outputs*
 - *Input glitches not send at output*
 - *one cycle “delay”*
 - *full cycle of stable output*



Solution B

Mealy Machine

 
- *output function of both PS & input*
- *maybe fewer states*
- *asynchronous outputs*
 - *if input glitches, so does output*
 - *output immediately available*
 - *output may not be stable long enough to be useful (below):*




If output of Mealy FSM goes through combinational logic before being registered, the CL might delay the signal and it could be missed by the clock edge (or violate set-up time requirement)

FSM Moore and Mealy Implementation Review

Moore Machine

 


Mealy Machine

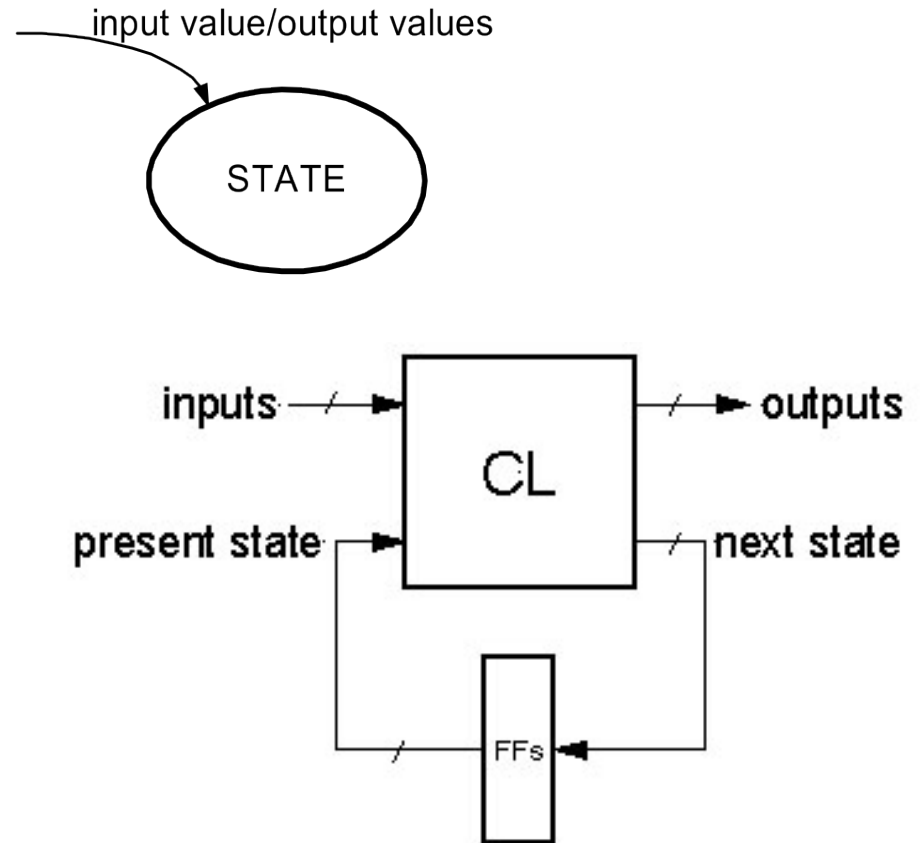


Final Notes on Moore versus Mealy

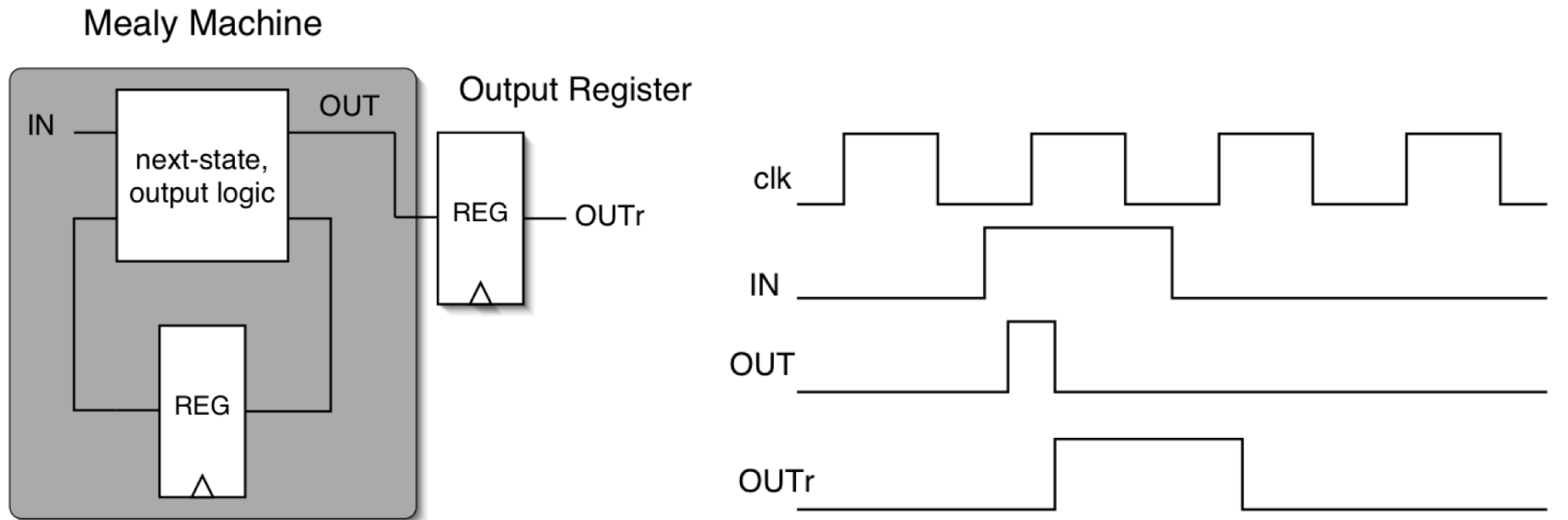1. A given state machine *could* have *both* Moore and Mealy style outputs. Nothing wrong with this, but you need to be aware of the timing differences between the two types.
2. The output timing behavior of the Moore machine can be achieved in a Mealy machine by “registering” the Mealy output values:



State Encoding

 

- ❑ In general:

of possible FSM states = $2^{\# \text{ of Flip-flops}}$

Example:


state1 = 01, state2 = 11, state3 = 10, state4 = 00

- ❑ However, often more than $\log_2(\# \text{ of states})$ FFs are used, to simplify logic at the cost of more FFs.
- ❑ Extreme example is one-hot state encoding.

State Encoding

- ❑ One-hot encoding of states.
- ❑ One FF per state.

Ex: 3 States


 


- ❑ Why one-hot encoding?
 - Simple design procedure.
 - Circuit matches state transition diagram (example next page).
 - Often can lead to simpler and faster “next state” and output logic.
- ❑ Why not do this?
 - Can be costly in terms of Flip-flops for FSMs with large number of states.
- ❑ FPGAs are “Flip-flop rich”, therefore one-hot state machine encoding is often a good approach.

One-hot encoded FSM

Think about moving a single token from state to state.

- Even Parity Checker Circuit:

  



Circuit generated through direct inspection of the STD.

- In General:



- FFs must be initialized for correct operation (only one 1)

One-hot encoded combination lock

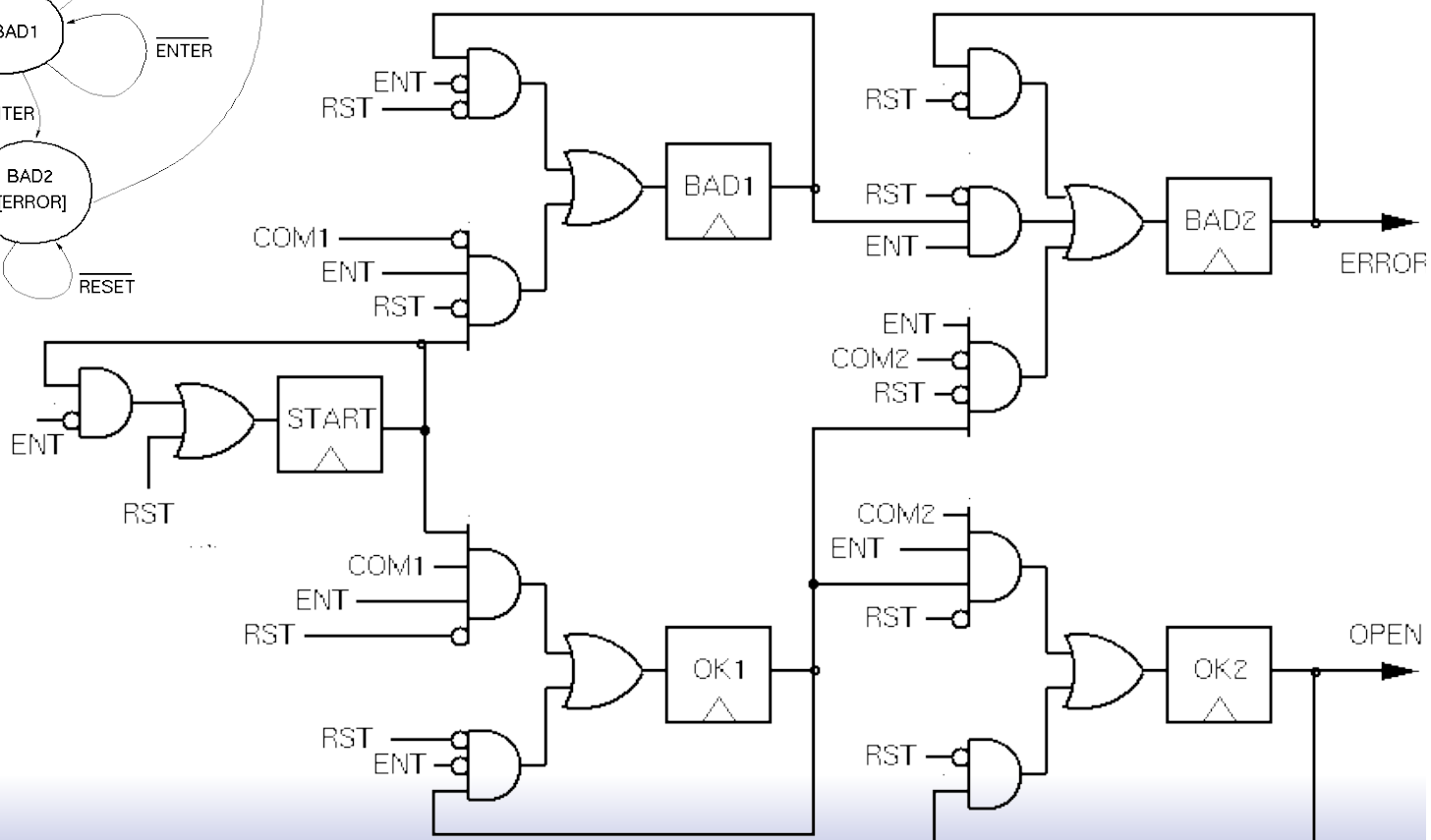 



FSMs in Verilog

General FSM Design Process with Verilog Implementation



Design Steps:

1. Specify **circuit function** (English)
 2. Draw **state transition diagram**
 3. Write down **symbolic state transition table**
 4. Assign encodings (bit patterns) to symbolic states
 5. Code as Verilog behavioral description
- ✓ Use parameters to represent encoded states.
 - ✓ Use register instances for present-state plus CL logic for next-state and outputs.
 - ✓ Use case for CL block. Within each case section (state) assign all outputs and next state value based on inputs. Note: For Moore style machine make outputs dependent only on state not dependent on inputs.

Finite State Machine in Verilog

Implementation Circuit Diagram

State Transition Diagram

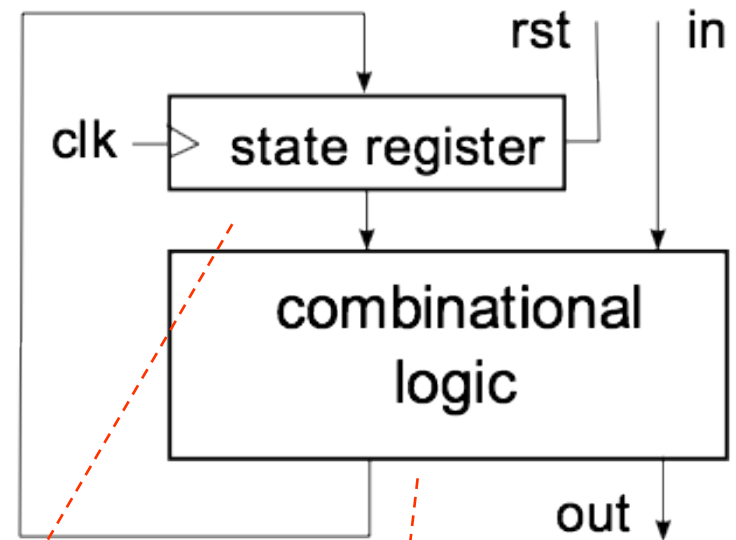 

Holds a symbol to keep value and next state based on input track of which bubble the FSM is in.

CL functions to determine output and current state.

$out = f(in, \text{current state})$

$next\ state = f(in, \text{current state})$

Finite State Machines

```
module FSM1(clk, rst, in, out);  
input clk, rst;  
input in;  
output out;
```

Must use reset to force to initial state.

reset not always shown in STD

```
// Defined state encoding:
```

```
localparam IDLE = 2'b00;
```

```
localparam S0 = 2'b01;
```

```
localparam S1 = 2'b10;
```

Constants local to this module.


```
reg out;  
reg [1:0] next_state;  
wire [1:0] present_state;
```

*out not a register, but assigned in always block
Combinational logic signals for transition.*

```
// state register
```

```
REGISTER_R #(.N(2), .INIT(IDLE)) state
```

 
```
(.q(present_state), .d(next_state), .rst(rst));
```



An always block should be used for combination logic part of FSM. Next state and output generation.

FSMs (cont.)

```
// always block for combinational logic portion
always @(present_state or in)
case (present_state)
// For each state def output and next
  IDLE  : begin
          out = 1'b0;
          if (in == 1'b1) next_state = S0;
          else next_state = IDLE;
        end
  S0    : begin
          out = 1'b0;
          if (in == 1'b1) next_state = S1;
          else next_state = IDLE;
        end
  S1    : begin
          out = 1'b1;
          if (in == 1'b1) next_state = S1;
          else next_state = IDLE;
        end
  default: begin
          next_state = IDLE;
          out = 1'b0;
        end
endcase
endmodule
```

 

Each state becomes a case clause.

For each state define:
Output value(s)
State transition

Use "default" to cover unassigned state. Usually unconditionally transition to reset state.


Mealy or Moore?

Edge Detector Example

Mealy Machine

```
REGISTER_R #(.INIT(ZERO) state  
(.q(ps), .d(ns), .rst(rst));
```


```
always @(ps in)  
  case (ps)  
    ZERO: if (in) begin  
            out = 1'b1;  
            ns = ONE;  
          end  
          else begin  
            out = 1'b0;  
            ns = ZERO;  
          end  
    ONE: if (in) begin  
            out = 1'b0;  
            ns = ONE;  
          end  
          else begin  
            out = 1'b0;  
            ns = ZERO;  
          end  
    default: begin  
              out = 1'bx;  
              ns = default;  
            end  
  end
```

 

Moore Machine


```
REGISTER_R #(.N(2), .INIT(ZERO)) state  
(.q(ps), .d(ns), .rst(rst));
```

```
always @(ps in)  
  case (ps)  
    ZERO: begin  
            out = 1'b0;  
            if (in) ns = CHANGE;  
            else ns = ZERO;  
          end  
    CHANGE: begin  
              out = 1'b1;  
              if (in) ns = ONE;  
              else ns = ZERO;  
            end  
    ONE: begin  
            out = 1'b0;  
            if (in) ns = ONE;  
            else ns = ZERO;  
          end  
    default: begin  
              out = 1'bx;  
              ns = default;  
            end  
  end
```

 


FSM CL block (original)

```
always @(present_state or in)
case (present_state)
  IDLE : begin
    out = 1'b0;
    if (in == 1'b1) next_state = S0;
    else next_state = IDLE;
  end
  S0 : begin
    out = 1'b0;
    if (in == 1'b1) next_state = S1;
    else next_state = IDLE;
  end
  S1 : begin
    out = 1'b1;
    if (in == 1'b1) next_state = S1;
    else next_state = IDLE;
  end
  default: begin
    next_state = IDLE;
    out = 1'b0;
  end
endcase
endmodule
```

 

The sequential semantics of the blocking assignment allows variables to be multiply assigned within a single always block.

FSM CL block rewritten

 

```
always @*
```

** for sensitivity list*

```
begin
```

```
next_state = IDLE;
```

```
out = 1'b0;
```

```
case (state)
```

```
  IDLE : if (in == 1'b1) next_state = S0;
```

```
  S0   : if (in == 1'b1) next_state = S1;
```

```
  S1   : begin
```

```
    out = 1'b1;
```

```
    if (in == 1'b1) next_state = S1;
```

```
  end
```

```
  default: ;
```

```
endcase
```

```
end
```

```
Endmodule
```

Normal values: used unless specified below.

Within case only need to specify exceptions to the normal values.

Note: The use of “blocking assignments” allow signal values to be “rewritten”, simplifying the specification.