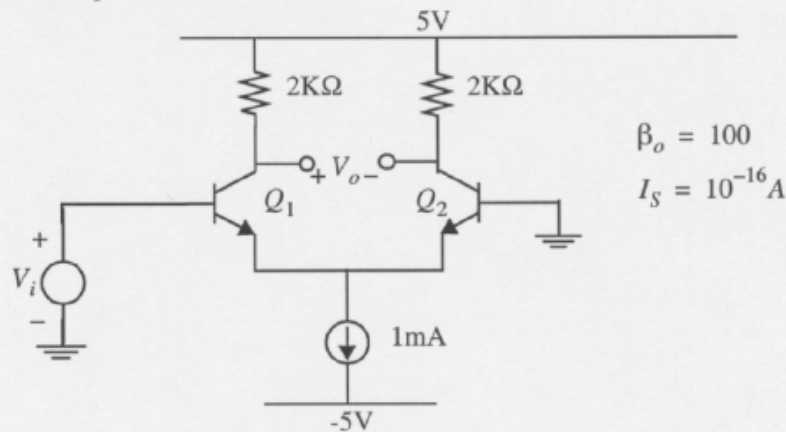


UNIVERSITY OF CALIFORNIA
College of Engineering
Department of Electrical Engineering
and Computer Sciences


Example Problem Set 1

EECS 142

1. A differential amplifier is shown below.



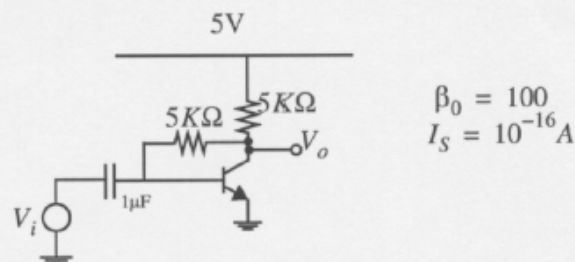- a) Use .DC in SPICE to compute the DC transfer characteristic from V_i to V_o for $V_i = \pm 200mV$ and use TF to obtain the small-signal voltage gain and input resistance. Verify with hand calculations.
 - b) Calculate HD_3 in V_o for $\hat{V}_i = 4mV$ and then 8mV o-peak sinusoidal. Compare with .TRAN and .FOURIER in SPICE.
 - c) Calculate the input interfering signal required to produce $IM_3 = 2\%$.
2. An amplifier is shown below.



- a) Calculate small-signal input resistance and voltage gain at $f = 1MHz$, and check with .AC on SPICE.
- b) Calculate HD_2 and HD_3 in V_o for $\hat{V}_i = 4mV$ and then 8mV o-peak sinusoidal. Compare with .TRAN and .FOURIER in SPICE. Use $f = 1MHz$.
- c) Calculate the input interfering signal required to produce $IM_3 = 2\%$.