 


UNIVERSITY OF CALIFORNIA
College of Engineering
Department of Electrical Engineering
and Computer Sciences


Example Problem Set 3

EECS 142


1. A receiver input stage is shown below. Calculate the maximum interfering signal voltage at V_i for $IM_3 < 1\%$.



 2. Calculate IM_2 and IM_3 in the circuit shown below, for two sinusoidal voltages of o-peak amplitude 300 mV each applied at V_i . Check with SPICE by simulating HD_2 and HD_3 .



3. A feedback amplifier is shown below.

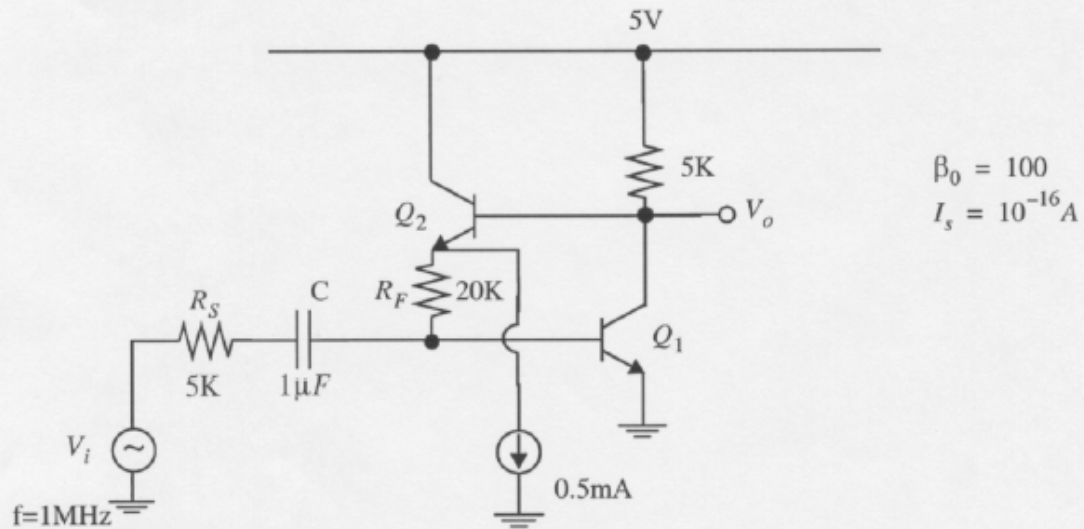

- Calculate the small-signal voltage gain of the circuit and the loop gain at $f = 1\text{MHz}$.
- Calculate HD_2 in V_o for a 1V peak-peak sinusoidal output voltage at $f = 1\text{MHz}$, assuming Q_1 is the major source of distortion. Check with SPICE.