

Example Problem Set 1

1. (a) $I_{CC} = I_{C2} = 0.5mA$

$$g_m = \frac{1}{52\Omega}$$

$$\frac{\Delta V_o}{\Delta V_i} = -g_m R_L = -\frac{2000}{52} = -38.5$$

$$R_i = 2r_{\pi 1} = 2\frac{\beta_o}{g_m} = 200 \times 52 = 10.4K\Omega$$

Large signal $V_o = (I_{C2} - I_{C1})R_L$

$$= \alpha_F I_{EE} R_L \tanh\left(\frac{-V_{id}}{2V_T}\right)$$

$$\cong 2 \tanh\left(\frac{-V_{id}}{52mV}\right)$$

(b) $HD_3 = \frac{1}{48}\left(\frac{\hat{V}_i}{V_T}\right)^2$

$$\hat{V}_i = 4mV \rightarrow HD_3 = \frac{1}{48}\left(\frac{4}{26}\right)^2 = 0.05\%$$

$$\hat{V}_i = 8mV \rightarrow HD_3 = 0.2\%$$


(c) $Im_3 = 3HD_3 = \frac{1}{16}\left(\frac{\hat{V}_i}{V_T}\right)^2 = 0.02$

$$\therefore \hat{V}_i = 14.7mV$$

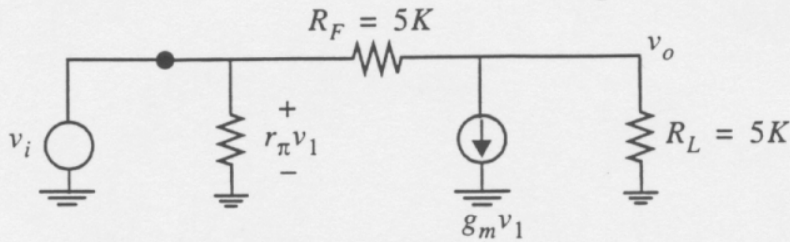2. (a) Bias $I_C \cong \frac{V_{CC} - V_{BE}}{R_L} = \frac{5 - 0.8}{5K} = 0.84mA$

Small signal

$$\left[f = 1MHz \quad \frac{1}{\omega C} \cong 0 \text{ for } C = 1\mu F \right]$$



$$\begin{aligned} \frac{v_o - v_i}{R_F} + g_m v_i + \frac{v_o}{R_L} &= 0 \\ \therefore v_o \left(\frac{1}{R_F} + \frac{1}{R_L} \right) &= -v_i \left(g_m - \frac{1}{R_F} \right) \\ \therefore \frac{v_o}{v_i} &\cong -g_m (R_L \parallel R_F) \\ &= -\frac{0.84}{26} \times 2500 = -81 \end{aligned}$$

$$\begin{aligned} R_i &= r_\pi \parallel \frac{R_F}{1 + A_v} \\ &= \frac{100 \times 26}{0.84} \parallel \frac{5000}{82} \\ &= 3.1K \parallel 61\Omega \\ &= 60\Omega \end{aligned}$$

(b) $\hat{V}_i = 4mV \quad HD_3 = \frac{1}{24} \left(\frac{\hat{V}_i}{V_T} \right)^2 = \frac{1}{24} \left(\frac{4}{26} \right)^2 = 0.1\%$

$$HD_2 = \frac{1}{4} \frac{\hat{V}_i}{V_T} = 3.8\%$$

$\hat{V}_i = 8mV \quad HD_3 = 0.4\% \quad HD_2 = 7.7\%$

(c) $Im_3 = \frac{1}{8} \left(\frac{\hat{V}_i}{V_T} \right)^2$

$$= 0.02$$

for $\hat{V}_i = 10.4mV$

hw1.1.lis

* Hw1.1: Differential amplifier

```

vcc vcc 0 5
vee vee 0 -5
lee 1 vee 1m

q1 vo+ vin 1 npn
q2 vo- 0 1 npn
r1 vcc vo+ 2k
r2 vcc vo- 2k

vin vin 0 0 ac (1 0) sin (0 4m 1e6)

.model npn npn bf=100 is=1e-16

.option post=2 nomod

.op
.vf v(vo+,vo-) vin
.dc vin -0.2 0.2 .01
.tran .001u 4u
.four 1e6 v(vo+,vo-)
.alter

vin vin 0 0 ac (1 0) sin (0 8m 1e6)
.end

```

```

*****
* Output file
*****
**** operating point status is all simulation time is 0.

+0.1 ==-750.9857m 0:vcc = 5.0000 0:vee = -5.0000
+0:vin = 0. 0:vo+ = 4.0099 0:vo- = 4.0099

**** bipolar junction transistors

```

```

element 0:q1 0:q2
model 0:npn 0:npn
lb 4.9505u 4.9505u
ic 495.0495u 495.0495u
vbe 750.9857m 750.9857m
vce 4.7609 4.7609
vbc -4.0099 -4.0099
vs -4.0099 -4.0099
power 2.3606m 2.3606m
betad 100.0000 100.0000
gm 19.2687m 19.2687m
rpl 5.1898k 5.1898k
rx 0. 0.
ro 4.009e+16 4.009e+16
cpl 0. 0.
cmu 0. 0.
cbx 0. 0.
ccs 0. 0.
betaac 100.0000 100.0000
ft 3.066e+12 3.066e+12

```

```

**** small-signal transfer characteristics

v(vo+,vo-)/vin = -38.5375
input resistance at vin = 10.3795k
output resistance at v(vo+,vo-) = 4.0000k

```

***** fourier analysis tnom= 25.000 temp= 25.000

fourier components of transient response v(vo+,vo-)

dc component = 9.113D-10

harmonic no	frequency (hz)	fourier component	normalized component	phase (deg)	normalized phase (deg)
1	1.0000x	153.9011m	1.0000	179.9992	0.
2	2.0000x	1.8250n	11.8581n	124.9733	-55.0258
3	3.0000x	80.4130u	522.4976u	-179.0223	-359.0215
4	4.0000x	1.8320n	11.9040n	159.9491	-20.0501
5	5.0000x	719.5668n	4.6755u	-133.2519	-313.2511
6	6.0000x	1.8438n	11.9805n	-165.0701	-345.0693
7	7.0000x	278.7932n	1.8115u	-103.2556	-283.2548
8	8.0000x	1.8604n	12.0884n	-130.0821	-310.0813
9	9.0000x	150.0341n	974.8730n	-73.9375	-253.9366

total harmonic distortion = 52.2523m percent

* Alter file

vin vin 0 0 ac (1 0) sin (0 8m 1e6)

.end

***** fourier analysis tnom= 25.000 temp= 25.000


fourier components of transient response v(vo+,vo-)

dc component = 1.879D-09

harmonic no	frequency (hz)	fourier component	normalized component	phase (deg)	normalized phase (deg)
1	1.0000x	306.4153m	1.0000	179.9991	0.
2	2.0000x	3.7632n	12.2812n	124.9756	-55.0236
3	3.0000x	620.5145u	2.0251m	-179.7488	-359.7479
4	4.0000x	3.7777n	12.3285n	159.9517	-20.0455
5	5.0000x	2.6965u	8.8002u	-155.8679	-335.8671
6	6.0000x	3.8019n	12.4078n	-165.0633	-345.0625
7	7.0000x	583.8513n	1.9054u	-104.2633	-284.2625
8	8.0000x	3.8362n	12.5195n	-130.0730	-310.0721
9	9.0000x	311.5393n	1.0167u	-74.3902	-254.3893

total harmonic distortion = 202.5097m percent

* DIFFERENTIAL AMPLIFIER
/08/25 13:49:56

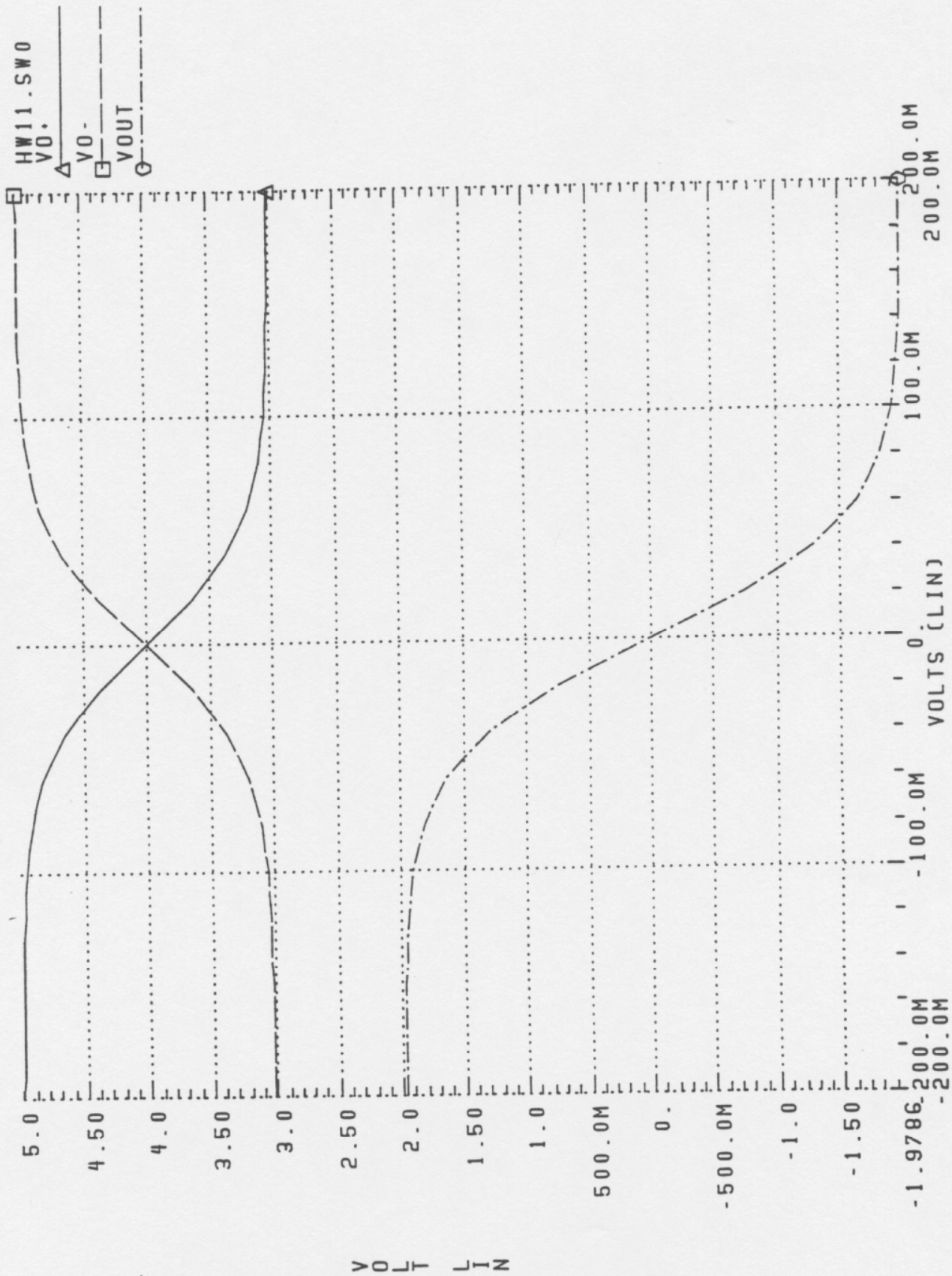



```
* hw1, problem 2
vcc vcc 0 5
r1 vcc vout 5k
r2 vout vln 5k
q1 vout vln 0 npn
vln vln 0 764.2789m sin(764.2789m 4m 1e6)
* Note: the capacitor can be ignored at f=1Mhz
.model npn npn bf=100 ls=1e-16
.option post=2 nomod
.op
.tf v(vout) vln
.tran .001u 4u
.four 1e6 v(vout)
.alter


vln vln 0 764.2789m sin(764.2789m 8m 1e6)
.end

*****
* Output file
*****
**** operating point status is all simulation time is 0.
+0.vcc = 5.0000 0:vln = 764.2789m 0:vout = 805.8072m
**** bipolar junction transistors
element 0:q1
model 0:npn
lb 8.3053u
lc 830.5329u
vbe 764.2789m
vce 805.8072m
vbc -41.5283m
vs -805.8072m
power 675.5970u
betad 100.0000
gm 32.3267m
rpi 3.0934k
rx 0.
ro 1.293e+15
cpi 0.
cmu 0.
cbx 0.
ccs 0.
betaac 100.0000
ft 5.145e+12
**** small-signal transfer characteristics
v(vout)/vln = -80.3168
input resistance at vln = 60.2895
output resistance at v(vout) = 2.5000k
**** fourier analysis
tnom= 25.000 temp= 25.000
```

```
*****
fourier components of transient response v(vout)
dc component = 7.932D-01
harmonic no frequency (hz) fourier component normalized phase (deg) normalized phase (deg)
1 1.0000x 322.2146m 1.0000 179.9992 0.
2 2.0000x 12.6038m 39.1163m 90.0014 -89.9978
3 3.0000x 320.7861u 995.5665u -514.9512m -180.5141
4 4.0000x 5.4180u 16.8147u -99.4745 -279.4737
5 5.0000x 1.3909u 4.3165u -131.9410 -311.9402
6 6.0000x 352.2095n 1.0931u 175.4571 -4.5420
7 7.0000x 556.7797n 1.7280u -103.0223 -283.0215
8 8.0000x 165.9884n 515.1487n -145.0923 -325.0914
9 9.0000x 302.3556n 938.3671n -73.4462 -253.4454
total harmonic distortion = 3.9129 percent

*****
* Alter file
*****
vln vln 0 764.2789m sin(764.2789m 8m 1e6)
**** fourier analysis
tnom= 25.000 temp= 25.000
****
fourier components of transient response v(vout)
dc component = 7.620D-01
harmonic no frequency (hz) fourier component normalized phase (deg) normalized phase (deg)
1 1.0000x 637.0103m 1.0000 179.9991 0.
2 2.0000x 38.5415m 60.5038m 89.9999 -89.9992
3 3.0000x 7.8376m 12.3038m -179.9474 -359.9465
4 4.0000x 8.2719m 12.9855m 90.0110 -89.9682
5 5.0000x 6.1863m 9.7115m -15.9811m -180.0151
6 6.0000x 4.1485m 6.5125m -90.0296 -270.0287
7 7.0000x 2.4212m 3.8008m 179.9895 -9.6436m
8 8.0000x 1.1068m 1.7375m 89.9373 -90.0619
9 9.0000x 228.1506u 358.1585u -543.1837m -180.5423
total harmonic distortion = 6.4304 percent
```

* HW1, PROBLEM 2
/08/25 14:17:45

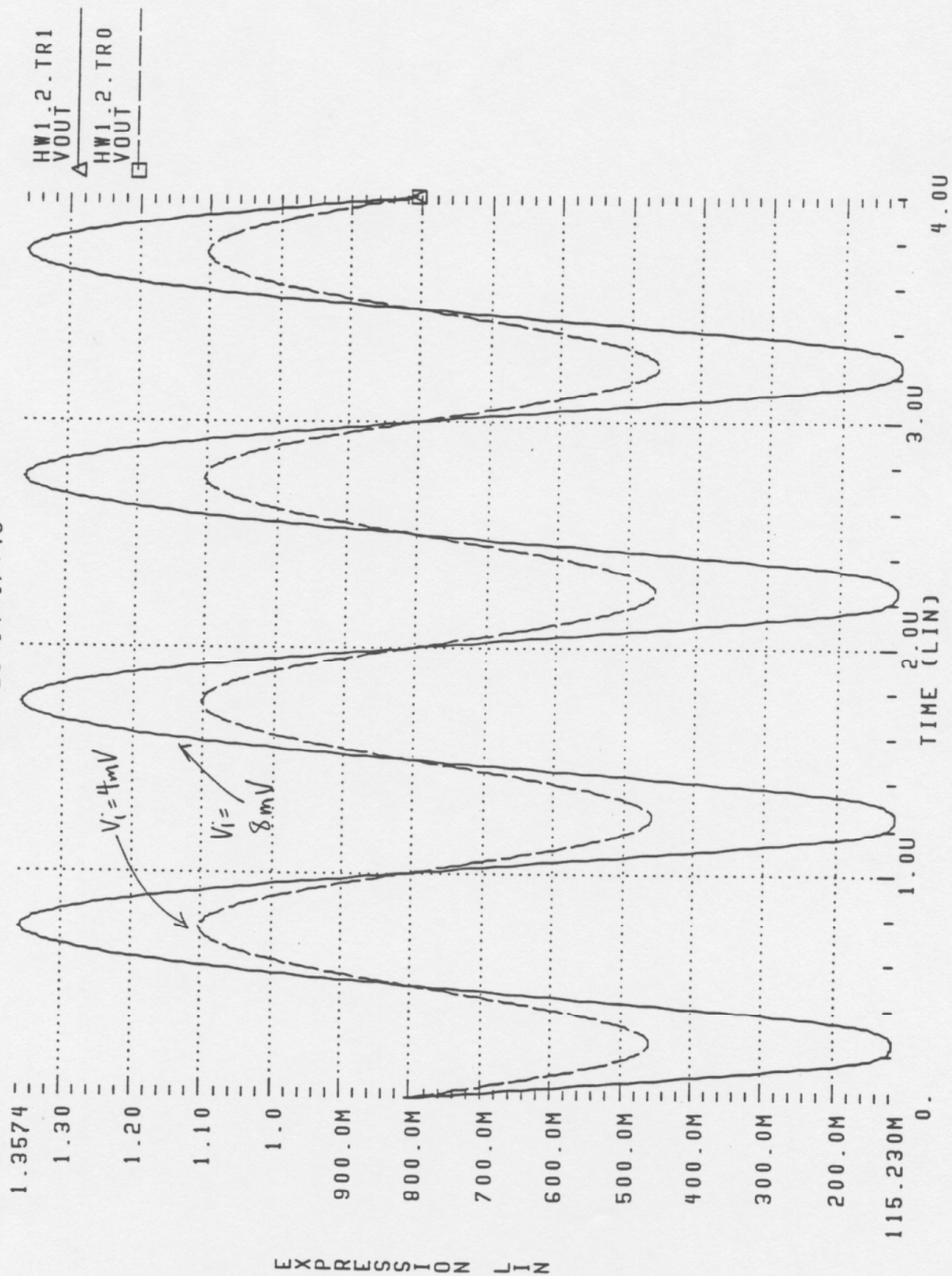

* HW1, PROBLEM 2
/08/26 13:40:07

