

Example Problem Set 4

1a) start by noting that for all the BJT's

$$I_C = 1.3 \text{ mA}, \quad V_{BC} \approx 1V \quad \therefore \quad g_m = 50 \text{ mS}$$

$$C_{\pi} = 572 \text{ fF}$$

$$C_M = 26 \text{ fF}$$

$$r_{\pi} = 2 \text{ k}\Omega$$

Next, we find the equivalent parameters for the degenerated diff-pair:

$$\text{note that } g_m R_E = 50 \text{ mS} \cdot 60 \Omega$$

$$= 3$$

$$g_m' = \frac{g_m}{1 + g_m R_E} = 12.5 \text{ mS}$$

$$C_{\pi}' = \frac{C_{\pi}}{1 + g_m R_E} = 143 \text{ fF}$$

$$C_M' = 26 \text{ fF}$$

$$r_{\pi}' = r_{\pi} \cdot (1 + g_m R_E) = 8 \text{ k}\Omega$$

Now, start with the 2nd stage: $A_{V2} = g_m' \cdot (R_L / C_M)$

since $R_L \ll r_o$, neglect r_o

$$= \frac{g_m' R_L}{1 + R_L C_M j\omega}$$

$$= \frac{2}{1 + j\omega \cdot 4 \times 10^{-12}}$$

(pole @ 38 GHz)

this stage presents a load to the previous stage of $j\omega C_{\pi}' \parallel \frac{1}{j\omega(C_M + A_{V2})} \parallel r_{\pi}' = \frac{1}{j\omega C_2} \parallel r_{\pi}'$


$$\text{where } C_2 = C_{\pi}' + C_M(1 + A_{V2}) = (143 + 78) \text{ fF} = \underline{221 \text{ fF}}$$

the first stage has a gain: $A_{V1} = g_m \cdot Z_L$

$$\text{where } Z_L = j\omega L \parallel R_p \parallel \frac{1}{j\omega C_L} \parallel r_{pi}' \parallel \frac{1}{j\omega C_2} \parallel \frac{1}{j\omega C_M} \parallel r_o$$

$R_p \ll r_{pi}' \ll r_o$, so neglect r_{pi}', r_o
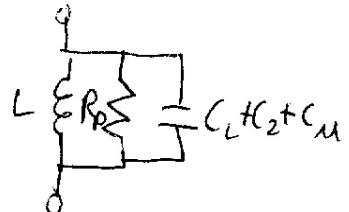
$$Z_L = \frac{1}{\frac{1}{j\omega C_L} + \frac{1}{R_p} + j\omega(C_L + C_2 + C_M)}$$



$$= \frac{j\omega L}{1 + j\omega \frac{L}{R_p} - \omega^2(L(C_L + C_2 + C_M))}$$

$$\text{So, } \omega_n = \frac{1}{\sqrt{L \cdot (C_L + C_2 + C_M)}} = 6.28 \times 10^9 \Rightarrow f_c = 16 \text{ Hz}$$

Now find R_p for this center frequency!

$$= Q \cdot L \cdot \omega = 4 \cdot 4 \mu H \cdot 6.28 \times 10^9 \approx 100 \Omega$$


$$Z_L = \frac{j\omega \cdot 4 \mu H}{1 + j\omega \frac{4 \mu H}{100 \Omega} - \omega^2 \left(\frac{1}{6.28 \times 10^9} \right)^2} = 100 \Omega \cdot \frac{\frac{j\omega \cdot 4 \mu H}{100 \Omega}}{1 + j\omega \frac{4 \mu H}{100 \Omega} - \omega^2 \left(\frac{1}{6.28 \times 10^9} \right)^2}$$

$$A_{V1} = g_m \cdot Z_L = 5 \cdot \frac{j\omega \cdot 40 \mu H / \Omega}{1 + j\omega \cdot 40 \mu H / \Omega - \left(\frac{\omega}{6.28 \times 10^9} \right)^2}$$


$$\boxed{\text{So peak gain} = 5 \cdot 2 = 10 \text{ at } 1 \text{ GHz}}$$

$$A_{V2} \approx 10 \cdot \frac{j\omega \cdot 40 \mu H / \Omega}{1 + j\omega \cdot 40 \mu H / \Omega - \left(\frac{\omega}{6.28 \times 10^9} \right)^2}$$

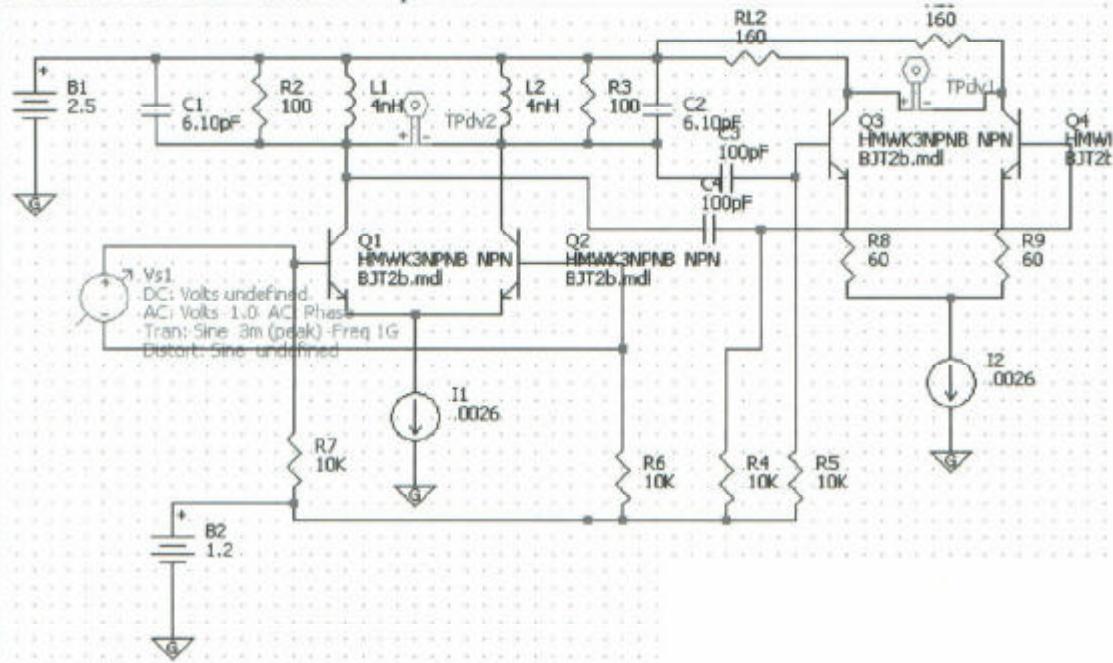Schematic for all simulations in problem 1:



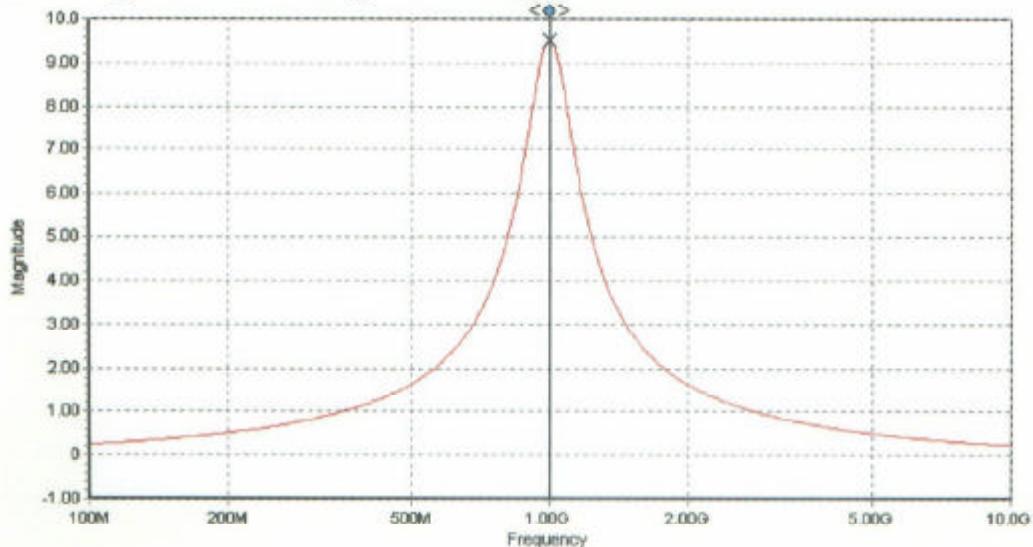AC simulation shows gain peaking at 1GHz, with a gain of 9.5 (slightly lower than calc due to slight resistive loading from 2nd stage)



b)

$$(i_1 - i_2) = I_{EE} \tanh\left(\frac{V/n}{2V_T}\right)$$

$\Downarrow I_{EE}$ we know: $\tanh(x) = \frac{e^x - e^{-x}}{e^x + e^{-x}}$

so find taylor coefficients:

$$\frac{d \tanh(x)}{dx} = \frac{(e^x + e^{-x})^2 - (e^x - e^{-x})^2}{(e^x + e^{-x})^2}$$

$$= 1 - \tanh^2(x)$$

$$\frac{d^2 \tanh(x)}{dx^2} = -2 \tanh(x) \left(\frac{d}{dx} (\tanh(x)) \right)$$

$$= -2 \tanh(x) (1 - \tanh^2(x))$$

$$\frac{d^3 \tanh(x)}{dx^3} = -2(1 - \tanh^2(x)) + 6 \tanh^2(x)(1 - \tanh^2(x))$$


so,

$d_1 = \frac{I_{EE}}{2V_T}$
$= 50 \text{ mS}$

$a_2 = 0$

$d_3 = \frac{-2}{(2V_T)^3} = \frac{-I_{EE}}{24V_T^3}$
$= -6160 \text{ mS}V^{-2}$

c) use feed-back:

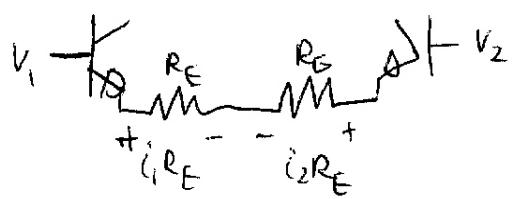

(Note we neglect fb effect

from Z_{mid} , since $Z_{mid} \leq 100\Omega$,
and $\frac{100\Omega}{\beta} \ll R_E$)

We know: with no feed back

$$(i_1 - i_2) = f(V_1 - V_2) \approx \frac{V_1 - V_2}{2V_T} - \frac{I_{EE}(V_1 - V_2)^3}{24V_T^3}$$

because $V_1 - V_2 = V_{be1} - V_{be2}$
but feed back means

$$\begin{aligned} V_1 - V_2 &= V_{be1} + i_1 R_E - i_2 R_E - V_{be2} \\ &= (V_{be1} - V_{be2}) + \underbrace{R_E(i_1 - i_2)}_{\text{feedback}} \end{aligned}$$

$$\text{so, } f = R_E$$

$$T = a_1 f = \frac{I_{EE}}{2V_T} R_E$$

$$\therefore b_1 = \frac{a_1}{1+T} = \frac{\frac{I_{EE}}{2V_T}}{1 + \frac{I_{EE}R_E}{2V_T}} = \frac{I_{EE}}{2V_T + I_{EE}R_E} = \boxed{12.5 \text{ ms}}$$

$$b_2 = \frac{a_2}{(1+T)^3} = 0$$

$$b_3 = \frac{a_3}{(1+T)^4} = \frac{-\frac{I_{EE}}{24V_T^3}}{\left(1 + \frac{I_{EE}R_E}{2V_T}\right)^4} = \frac{-I_{EE} \cdot \frac{2}{3}V_T}{(2V_T + I_{EE}R_E)^4} = \boxed{-24 \text{ ms/V}^2}$$

d) because we have set all of the frequencies (w_1, w_2 and therefore IM_3 term, $2w_1-w_2$, and $2w_2-w_1$) to be inband, we can use the cascaded approximation; note that we must rewrite a_1, a_3 to account for the load of the first stage:

$$a'_1 = 100q_1 = 100 \cdot 50 \text{ ms} = 5$$

$$a'_2 = 100 \cdot q_1 = 100 \cdot 50 \text{ ms} = 0$$

$$a'_3 = 100q_2 q_3 = 100 \cdot (-6160 \text{ ms/V}^2) = -616 \text{ V}^{-2}$$

Similarly we must find b_1', b_2' and b_3' by including the load of the 2nd stage:

$$b'_1 = 12.5 \text{ ms} \cdot 160 \Omega = 2$$

$$b'_2 = 0 \cdot 160 \Omega = 0$$

$$b'_3 = -24 \text{ ms/V}^2 \cdot 160 = -3.84 \text{ V}^{-2}$$

Now we can find c_1, c_2, c_3 :

$$c_1 = a'_1 \cdot b'_1 = 10$$

$$c_2 = 0 \cdot 0 = 0$$

$$c_3 = a'_1 \cdot b'_3 + a'_3 \cdot b'_1 \cancel{- 2b'_2 a'_1 a'_2} = -1714 \text{ V}^{-2}$$

$$\text{So, } IIP_3 = \sqrt{\frac{4}{3} \left| \frac{c_1}{c_3} \right|} = 0.088 \text{ V}$$

e) P_{1dB}: since compression is an in-band effect, we can use the cascaded approach, and, in fact, can use the result from part(d):

$$P_{1dB} = IIP_3 - 9.6 \text{ dB} = \boxed{0.024 \text{ V}}$$

HD₃: now we have a problem,

$$HD_3 = \frac{\text{mag(3rd harmonic)}}{\text{mag(fund)}}$$

but the 3rd harmonic is outside the pass-band of the 1st stage, so we cannot use the simple cascade approximation.

Instead, we know that 3rd harm output is made up of two parts, call them S₃₁, S₃₂, which are generated by the nonlinearity of the 1st and 2nd stages respectively.

S_{3out} = S₃₁ * G(3GHz) + S₃₂, that is, the output 3rd harmonic is the sum of 3rd harm from the 1st stage, times the gain of the 2nd, plus the ~~third~~ third harm from the 2nd stage.

$$S_{31} = \left(\frac{1}{4} b_3 \cdot V_{in}^3 \right) \circ Z_L (2\pi \cdot 30 \text{Hz})$$

$$= \frac{1}{4} (-6160 \text{mSv}^{-2}) (3 \text{mV})^3 \circ \frac{j(2\pi \cdot 3 \cdot 10^4 \text{Hz}) \cdot 4 \text{nH}}{1 + j \frac{4 \text{nH}}{100 \Omega} (2\pi \cdot 3 \cdot 10^4 \text{Hz}) - \left(\frac{2\pi \cdot 3 \cdot 10^4}{2\pi \cdot 1 \cdot 10^4} \right)^2}$$

$$= -41.8 \text{nA} \cdot \frac{j75.4}{1 + j(0.754) - 9}$$

$$= -36.6 \text{nV} + 388j \text{nV}$$

$$S_{32} = \left(\frac{1}{4} b_3 \cdot V_{mid}^3 \right) R_L$$

$$= \frac{1}{4} b_3 \cdot (5 \cdot V_{in})^3 R_L$$

(note that we are looking at the part of V_{mid} at the fundamental frequency)


$$= \frac{1}{4} (-24 \text{mSv}^{-2}) (15 \text{mV})^3 160 \Omega$$

$$= -3.24 \mu\text{V}$$

$$\begin{aligned} S_{3+tot} &= S_{32} + G_2 S_{31} = 3.24 \mu\text{V} + 2(-36.6 \text{nV} + j388 \text{nV}) \\ &= \underline{-3.3 \mu\text{V} + 0.78j \mu\text{V}} \end{aligned}$$


$$HD3 = \frac{|S_{3+tot}|}{S_1} = \frac{3.4 \mu\text{V}}{10.3 \text{mV}} = \frac{3.4 \times 10^{-6} \text{V}}{30 \times 10^{-3} \text{V}} \boxed{= 1.1 \times 10^{-4}}$$

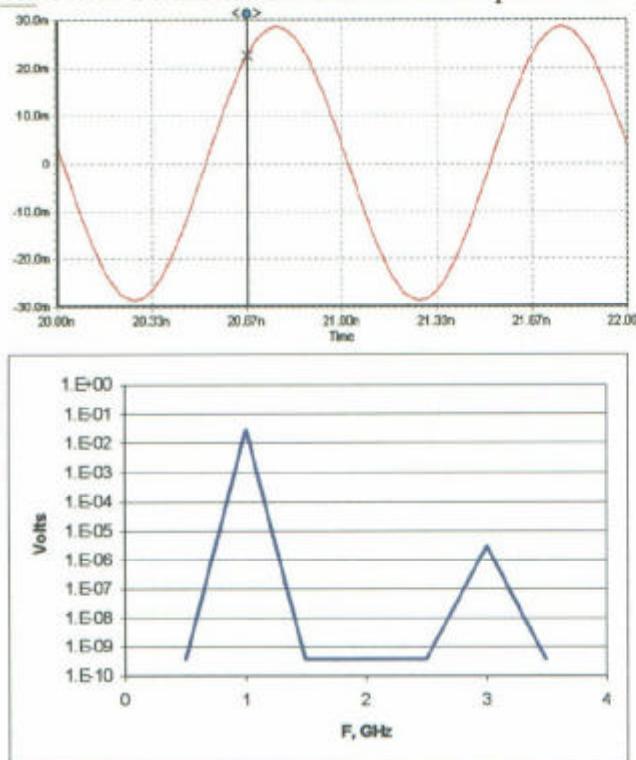Start with a transient simulation with input of 3mV, and do a Fourier transform:



Now we see that $f_{\text{fund}} = 28.5 \text{ mV}$, $3^{\text{rd}} = 3\mu\text{m}$, so $\text{HD3} = 10^{-4}$, as predicted

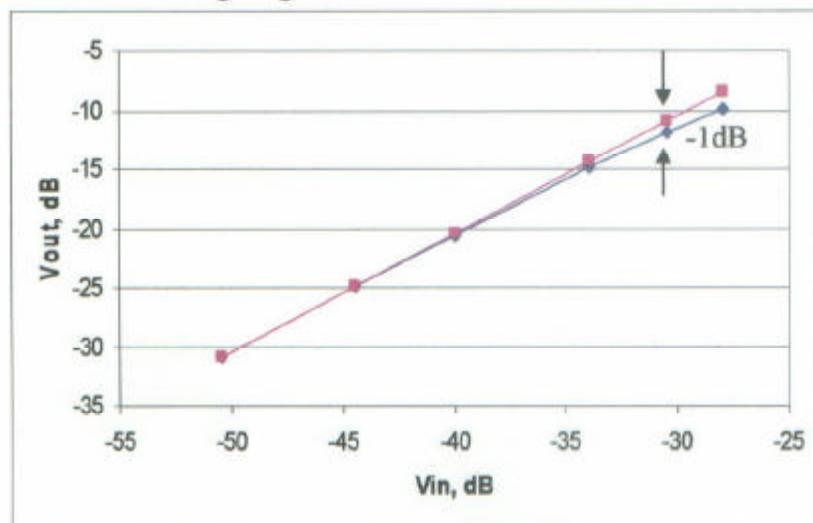Repeat the simulation for a variety of input voltages, and plot Fund vs the predicted fund based on small signal gain:



It can be seen that the P1dB is at $V_{\text{in}}=-30\text{dB}$, or **30mV** as predicted.