 


# High-Speed A/D Converter


- Flash Converter
  - Comparator
  - Binary Encoder
- Interpolation
- Folding

## Flash Converter

- Very fast: only 1 clock cycle per conversion
- High complexity:  $2^B - 1$  comparators
- High input capacitance




# Comparator

 


- Clock rate  $f_s$
- Resolution
- Overload Recovery
- Input capacitance (and linearity!)
- Power dissipation
- Common-mode rejection
- Kickback noise
- ...

# CMOS Comparator Example

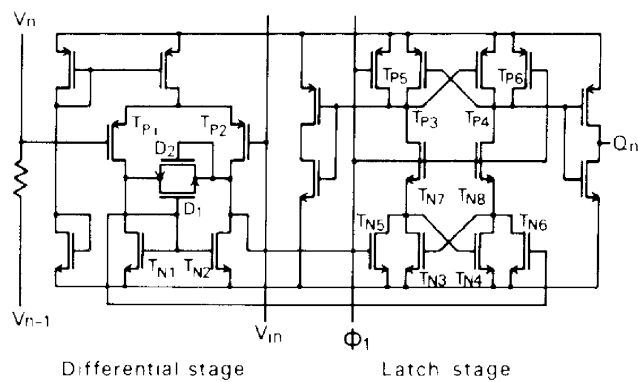


# Comparator with Auto-Zero

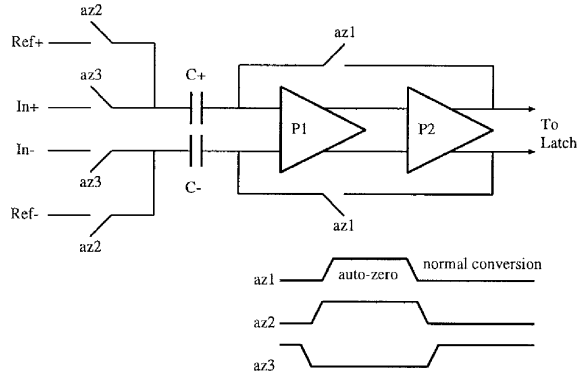

I. Mehr and L. Singer, "A 500-Msample/s, 6-Bit Nyquist-Rate ADC for Disk-Drive Read-Channel Applications," JSSC July 1999, pp. 912-20.




# Auto-Zero Implementation

 

I. Mehr and L. Singer, "A 55-mW, 10-bit, 40-Msample/s Nyquist-Rate CMOS ADC," JSSC March 2000, pp. 318-25.




# Flash Converter Errors

 

- Comparator input:
  - Offset
  - Nonlinear input capacitance
  - Kickback noise (disturbs reference)
  - Signal dependent sampling time
- Comparator output:
  - Sparkle codes (... 111101000 ...)
  - Metastability

# Sparkle Codes

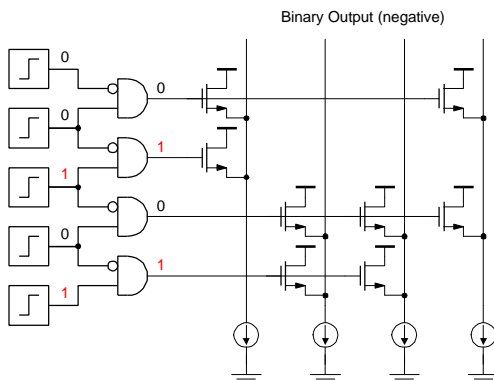


Correct Output:  
0110 ... 1000

Actual Output:  
1110

# Sparkle Tolerant Encoder

Binary Output (negative)

 


Protects against a *single* sparkle.

Ref: C. Mangelsdorf et al, "A 400-MHz Flash Converter with Error Correction," JSSC February 1990, pp. 997-1002.



# Meta Stability

Binary Output (negative)

 

Different gates interpret metastable output X differently

Correct Output: 0111 or 1000

Actual Output: 1111

Solutions:

- Latches (high power)
- Gray encoding

Ref: C. Portmann and T. Meng, "Power-Efficient Metastability Error Reduction in CMOS Flash A/D Converters," JSSC August 1996, pp. 1132-40.



# Gray Encoding

Thermometer Code							Gray			Binary		
T <sub>1</sub>	T <sub>2</sub>	T <sub>3</sub>	T <sub>4</sub>	T <sub>5</sub>	T <sub>6</sub>	T <sub>7</sub>	G <sub>3</sub>	G <sub>2</sub>	G <sub>1</sub>	B <sub>3</sub>	B <sub>2</sub>	B <sub>1</sub>
0	0	0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	1	0	0	1
1	1	0	0	0	0	0	0	1	1	0	1	0
1	1	1	0	0	0	0	0	1	0	0	1	1
1	1	1	1	0	0	0	1	1	0	1	0	0
1	1	1	1	1	0	0	1	1	1	1	0	1
1	1	1	1	1	1	0	1	0	1	1	1	0
1	1	1	1	1	1	1	1	0	0	1	1	1

$$G_1 = T_1 \overline{T_3} + T_5 \overline{T_7}$$

$$G_2 = T_2 \overline{T_6}$$

$$G_3 = T_4$$

- Each T<sub>i</sub> affects only one G<sub>i</sub>  
→ Avoids disagreement of interpretation by multiple gates
- Protects also against sparkles
- Follow Gray encoder by (latch and) binary encoder



# Reducing Complexity

E.g. 10-bit "straight" flash

- Input range: 0 ... 1V
- LSB = Δ: ~ 1mV
- Comparators: 1023 with offset << LSB
- Input capacitance: 1023 \* 100fF = 102pF
- Power: 1023 \* 3mW = 3W

Techniques:


- Interpolation
- Folding
- Folding & Interpolation
- Two-step, pipelining




# Interpolation

- Idea
  - Interpolation between preamp outputs
- Reduces number of preamps
  - Reduced input capacitance
  - Reduced area, power dissipation
- Same number of latches
- Important “side-benefit”
  - Decreased sensitivity to preamp offset
  - → improved DNL

# Simulink Model

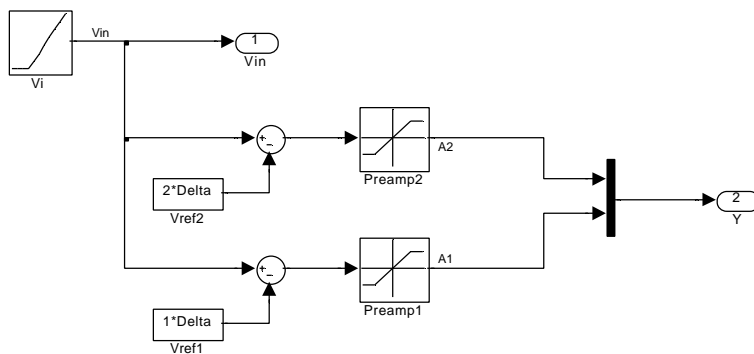

# Preamp Output

 


Zero crossings (to be detected by latches) at  $V_{in} =$

$$V_{ref1} = 1 \Delta$$

$$V_{ref2} = 2 \Delta$$

# Differential Preamp Output

 

Zero crossings at  $V_{in} =$


$$V_{ref1} = 1 \Delta$$

$$V_{ref12} = 0.5 \cdot (1+2) \Delta$$

$$V_{ref2} = 2 \Delta$$




# Interpolation in Flash ADC

 

Half as many reference voltages and preamps


# Resistive Interpolation

 

- Resistors produce additional levels
- With 4 resistors, the "interpolation factor"  $M=8$  (ratio of latches/pramps)


Ref: H. Kimura et al, "A 10-b 300-MHz Interpolated-Parallel A/D Converter," JSSC April 1993, pp. 438-446.

# DNL Improvement

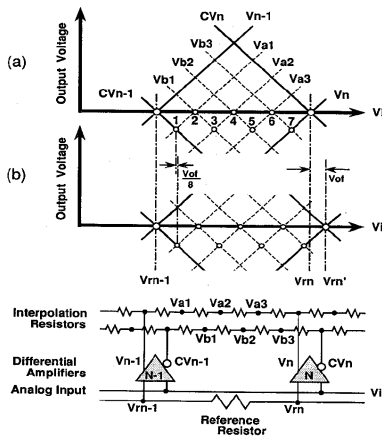

- Preamp offset distributed over  $M$  resistively interpolated voltages:  
→ impact on DNL divided by  $M$
- Latch offset divided by gain of preamp  
→ use "large" preamp gain ...

# Preamp Input Range

 


# Measured Performance

<b>Resolution</b>		<b>10 b</b>
<b>Maximum conversion frequency</b>		<b>300 MHz</b>
<b>Integral non-linearity</b>		<b><math>\pm 1.0</math> LSB</b>
<b>Differential non-linearity</b>		<b><math>\pm 0.4</math> LSB</b>
<b>SNR/THD</b>	<b>10MHz input</b>	<b>56/-59 dB</b>
	<b>50MHz input</b>	<b>48/-47 dB</b>
<b>Input capacitance</b>		<b>8 pF</b>
<b>Input range</b>		<b>2 V</b>
<b>Power supply</b>		<b>-5.2V</b>
<b>Power dissipation</b>		<b>4.0W</b>
<b>Chip size</b>		<b><math>9.0 \times 4.2</math> mm<sup>2</sup></b>
<b>Element count</b>		<b>36,000</b>
<b>Technology</b>		<b>1.0 <math>\mu</math>m bipolar:ft=25GHz</b>

Ref: H. Kimura et al, "A 10-b 300-MHz Interpolated-Parallel A/D Converter," JSSC April 1993, pp. 438-446.



# Folding Converter

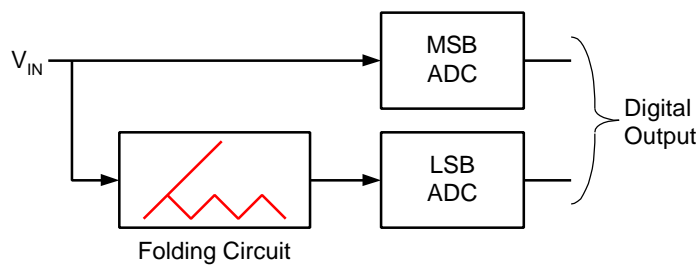


- Significantly fewer comparators than flash  $\sim 2^{B/2+1}$
- Fast
- Nonidealities in folder limit resolution to  $\sim 10$ Bits



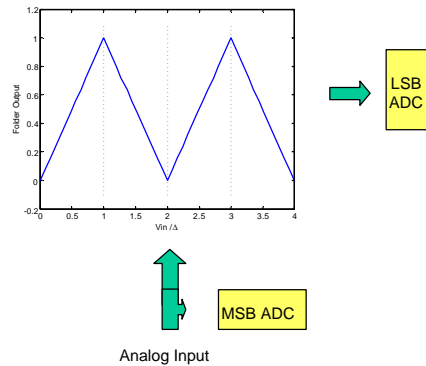
# Folding


- Folder maps input to smaller range
- MSB ADC determines which fold input is in
- LSB ADC determines position within fold
- Logic circuit combines LSB and MSB results




# Generating Folds

 

# Folding Circuit

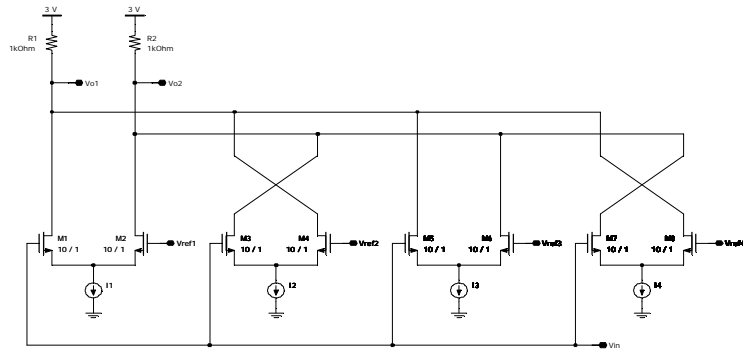


# CMOS Folder Output

 


Accurate only at zero-crossings

*Lowdown* →  
Most folding ADCs do not actually use the folds, but only the zero-crossings!

# Parallel Folders

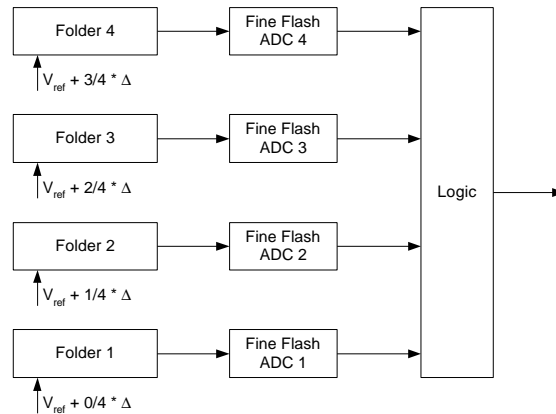


# Parallel Folder Outputs

 


- 4 Folders
- 8 Zero crossings
- → only 3 LSB bits
- Better resolution
  - More folders → huge complexity
  - Interpolation



# Folding & Interpolation

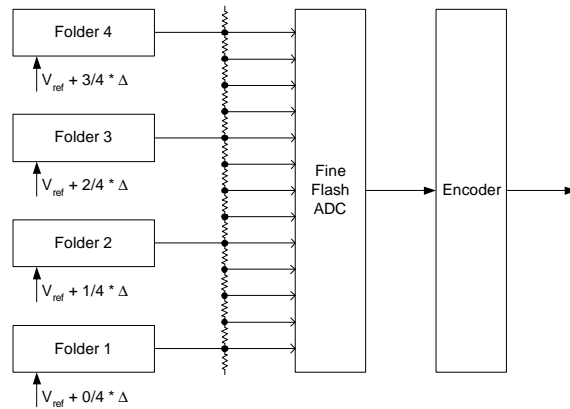

# Folder / Interpolator Output

 



# Folder / Interpolator Output

  

Interpolate only between closely spaced folds to avoid nonlinear distortion


## A 70-MS/s 110-mW 8-b CMOS Folding and Interpolating A/D Converter

  B. Nauta and G. Venes, JSSC Dec 1985, pp. 1302-8





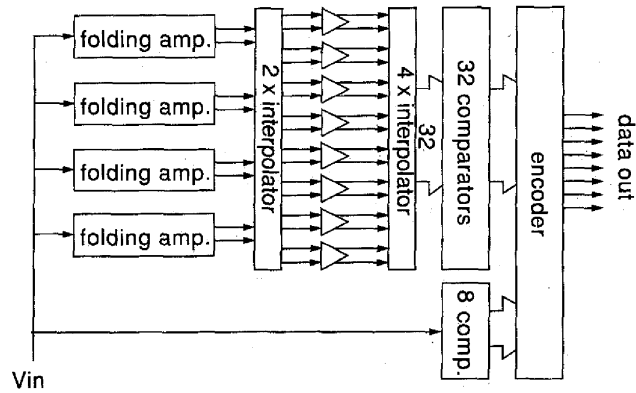
## A 70-MS/s 110-mW 8-b CMOS Folding and Interpolating A/D Converter


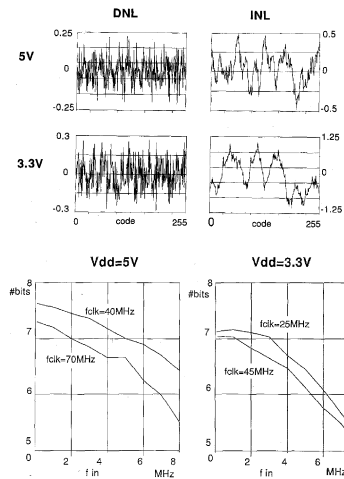
## A 70-MS/s 110-mW 8-b CMOS Folding and Interpolating A/D Converter



parameter	
resolution	8bit
input capacitance	4.8 pF
reference ladder resistance	720 $\Omega$
active area	0.7 mm <sup>2</sup>
technology	0.8 $\mu$ m, 1 poly, 2 metal, CMOS
supply voltage	$V_{dd}=5V$ $V_{dd}=3.3V$
analog input	2V <sub>pp</sub> 1.4V <sub>pp</sub>
Integral nonlinearity	$\pm 0.5LSB$ $\pm 1.0LSB$
Differential nonlinearity	$\pm 0.2LSB$ $\pm 0.3LSB$
max. clock frequency	70MHz    45MHz
power dissipation	110mW    45mW