


**UNIVERSITY OF CALIFORNIA**  
**College of Engineering**  
**Department of Electrical Engineering**  
**and Computer Sciences**

**B. E. BOSER**

**Midterm**  
**Friday, October 27, 2000**

**EECS 247**  
**FALL 2000**

 1. Find the following transfer functions (the amplifier is ideal):
  - a)  $H_1(z) = V_2(z) / V_1(z)$ , during phase 1, and
  - b)  $H_2(z) = V_3(z) / V_1(z)$ , for phase 1 input and phase 2 output.




2. The transfer function  $H(s)$  is realized as a switched capacitor ladder filter with LDI integrators.

$$H(s) = \frac{0.0010005 (s^2 + 1.235) (s^2 + 1.438) (s^2 + 2.408) (s^2 + 15.34)}{(s^2 + 0.4952s + 0.1505) (s^2 + 0.28s + 0.5605) (s^2 + 0.1106s + 0.8742) (s^2 + 0.0272s + 0.9987)}$$

a) Find the minimum clock frequency for the SC filter that is required to keep all zeros in the response.

b) What type of filter is  $H(s)$  realizing (low pass, band pass, etc)?

 3. The output  $V_o$  of the filter shown below is processed by an ideal sampler operating at  $f_s=1\text{MHz}$  (e.g. an ideal A/D converter).  $V_{in}$  is a sinusoid with 1V amplitude and  $f_x=1.3\text{MHz}$ . Calculate the amplitude and frequency of the sampled output.



4. Find the transfer function  $H(z)=V_2(z)/V_1(z)$  of the following SC circuit (for  $\Phi_1$ ):

