

University of California
College of Engineering
Department of Electrical Engineering and Computer Sciences

B. E. Boser

Homework 9 Solution

EECS 247
Fall 2003

The amplifier transfer function is

$$V_o = V_{\max} \tanh(A_v V_i)$$

$$\Rightarrow V_i = \frac{1}{A_v} \tanh^{-1}\left(\frac{V_o}{V_{\max}}\right) = \frac{1}{2A_v} \ln \frac{1 + \frac{V_o}{V_{\max}}}{1 - \frac{V_o}{V_{\max}}} \quad (1)$$

Using the nomenclature of slide 3, lecture 18, (1) becomes

$$V_{IN} = \frac{1}{A_v} \tanh^{-1}\left(\frac{V_{1OUT}}{V_{\max}}\right) = \frac{1}{2A_v} \ln \frac{1 + \frac{V_{1OUT}}{V_{\max}}}{1 - \frac{V_{1OUT}}{V_{\max}}} \quad (1a)$$

We will now find the integrator transfer function using the charge conservation principle. We choose $V_{CM} = 0$ and $C_{R1} = C_{R2} = C_{IN} = C_{FB} / 2$.

During ϕ_1 :

$$Q_{IN}(k-1) = C_{IN} V_{IN}(k-1) \quad (2)$$

$$Q_{R1}(k-1) = C_{R1} V_{REF} \quad (3)$$

$$Q_{R2}(k-1) = 0 \quad (4)$$

$$Q_{FB}(k-1) = [V_{IN}(k-1) - V_{1OUT}(k-1)]C_{FB}$$

$$\Rightarrow Q_{FB}(k-1) = \left[-\frac{1}{A_v} \tanh^{-1}\left(\frac{V_{1OUT}(k-1)}{V_{\max}}\right) - V_{1OUT}(k-1) \right] C_{FB} \quad (5)$$

During ϕ_2 , two cases are distinguished:

If the comparator output $D = -1$,

$$Q_{FB}(k) = Q_{FB}(k-1) - Q_{IN}(k-1) - Q_{R1}(k-1) + Q_{IN}(k) + Q_{R1}(k)$$

$$\left[-\frac{1}{A_v} \tanh^{-1}\left(\frac{V_{1OUT}(k)}{V_{\max}}\right) - V_{1OUT}(k) \right] C_{FB} - \left[-\frac{1}{A_v} \tanh^{-1}\left(\frac{V_{1OUT}(k-1)}{V_{\max}}\right) - V_{1OUT}(k-1) \right] C_{FB} =$$

$$= -C_{IN} V_{IN}(k-1) - C_{R1} V_{REF} + \frac{C_{IN}}{A_v} \tanh^{-1}\left(\frac{V_{1OUT}(k)}{V_{\max}}\right) + \frac{C_{R1}}{A_v} \tanh^{-1}\left(\frac{V_{1OUT}(k)}{V_{\max}}\right) \quad (6)$$

Equation (6) simplifies to

$$V_{IOUT}(D = -1) = \frac{0.5}{z-1}(V_{IN} + V_{REF}) + \frac{z}{z-1} \frac{1}{A_v} \left[\tanh^{-1}\left(\frac{V_{IOUT} z^{-1}}{V_{max}}\right) - 2 \tanh^{-1}\left(\frac{V_{IOUT}}{V_{max}}\right) \right] \quad (6a)$$

If the comparator output $D = 1$,

$$\begin{aligned} Q_{FB}(k) &= Q_{FB}(k-1) - Q_{IN}(k-1) - Q_{R2}(k-1) + Q_{IN}(k) + Q_{R2}(k) \\ \left[-\frac{1}{A_v} \tanh^{-1}\left(\frac{V_{IOUT}(k)}{V_{max}}\right) - V_{IOUT}(k) \right] C_{FB} - \left[-\frac{1}{A_v} \tanh^{-1}\left(\frac{V_{IOUT}(k-1)}{V_{max}}\right) - V_{IOUT}(k-1) \right] C_{FB} &= \\ = -C_{IN} V_{IN}(k-1) + \frac{C_{IN}}{A_v} \tanh^{-1}\left(\frac{V_{IOUT}(k)}{V_{max}}\right) + C_{R2} \left[V_{REF} + \frac{1}{A_v} \tanh^{-1}\left(\frac{V_{IOUT}(k)}{V_{max}}\right) \right] \end{aligned} \quad (7)$$

Equation (7) simplifies to

$$V_{IOUT}(D = 1) = \frac{0.5}{z-1}(V_{IN} - V_{REF}) + \frac{z}{z-1} \frac{1}{A_v} \left[\tanh^{-1}\left(\frac{V_{IOUT} z^{-1}}{V_{max}}\right) - 2 \tanh^{-1}\left(\frac{V_{IOUT}}{V_{max}}\right) \right] \quad (7a)$$

Combining (6a) and (7a) we get

$$V_{IOUT} = \underbrace{\frac{0.5}{z-1}(V_{IN} - DV_{REF})}_{\text{ideal term}} + \underbrace{\frac{z}{z-1} \frac{1}{A_v} \left[\tanh^{-1}\left(\frac{V_{IOUT} z^{-1}}{V_{max}}\right) - 2 \tanh^{-1}\left(\frac{V_{IOUT}}{V_{max}}\right) \right]}_{\text{term due to nonlinearity}} \quad (8)$$

The corresponding Sigma Delta is modeled in Simulink as shown in Figure 1.

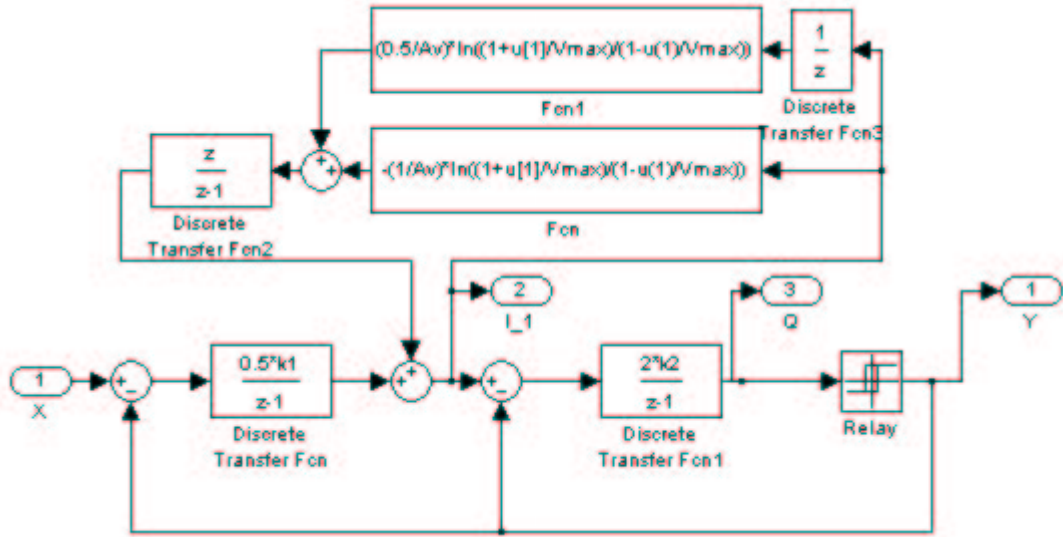


Figure 1. Sigma Delta Simulink model.

The in-band quantization noise using an ideal integrator is $-111dB$, as shown in Homework 8. Since only $3dB$ increase is accepted, the maximum acceptable value is $-108dB$, which corresponds to $A_v = 100$ according to the simulation. This value however leads to $SFDR < 95dB$. To meet this specification the amplifier gain is further increased to $A_v = 600$. The corresponding graphs are shown in Fig. 2 and 3.

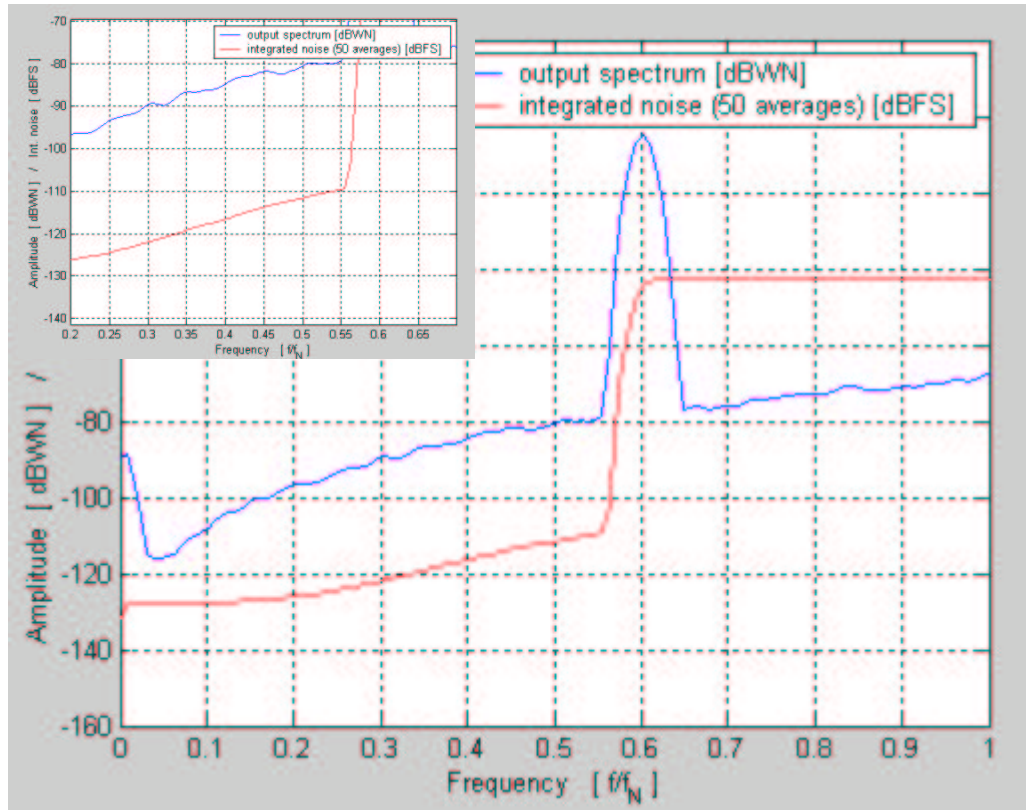


Figure 2. Quantization noise plot for gain = 600.

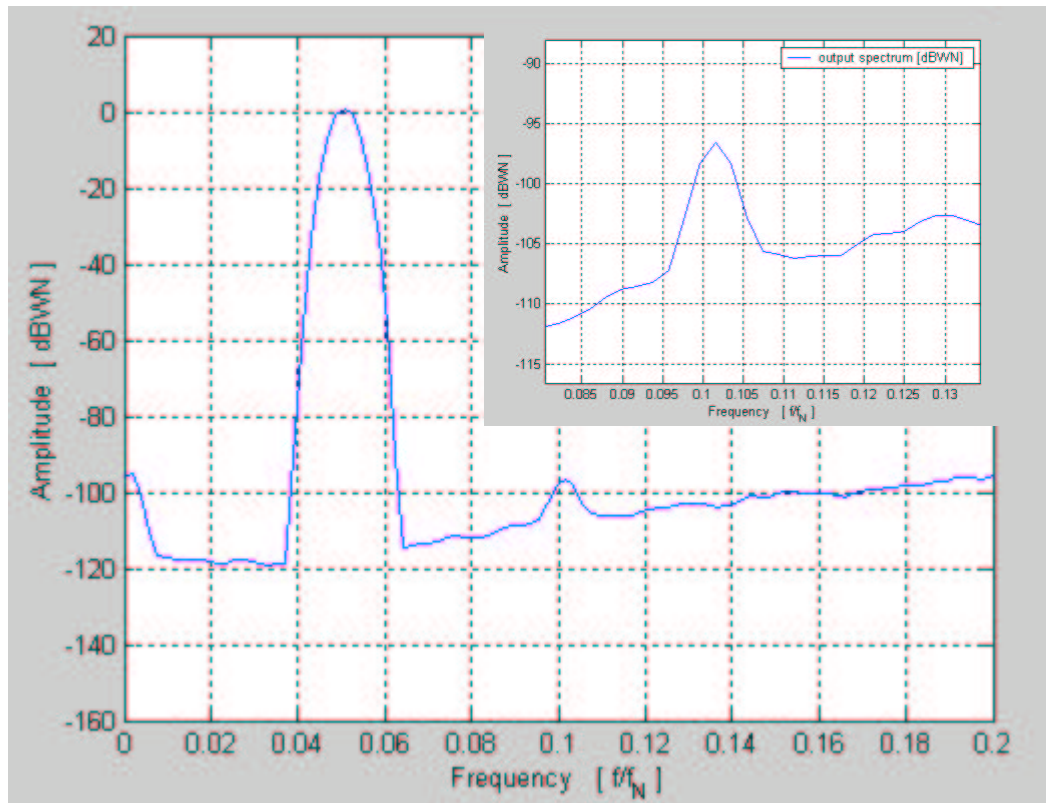


Figure 3. Harmonics plot for gain = 600.