

① Given: $N=4$, $\begin{cases} f_p = 500 \text{ kHz} & \text{Pass band Edge} \\ R_p = 0.3 \text{ dB} & \text{Pass band Atten.} \end{cases}$

Needed for Synthesis: $N, \omega_{-3\text{dB}}$

Butterworth:

$$|H(\omega)|^2 = \frac{1}{1 + (\omega/\omega_{-3\text{dB}})^{2N}} = \frac{1}{1 + \epsilon^2 (\omega/\omega_p)^{2N}}$$

with $\frac{1}{1 + \epsilon^2} = \left(10^{-R_p/20}\right)^2$ Passband Atten.

$$\left(\frac{\omega}{\omega_{-3\text{dB}}}\right)^{2N} = \epsilon^2 \left(\frac{\omega}{\omega_p}\right)^{2N}$$


$$\Rightarrow \frac{\omega_{-3\text{dB}}}{\omega_p} = \frac{1}{\epsilon^{1/N}}$$

$$\epsilon = \sqrt[10^{R_p/10} - 1]{} = 0.2674$$


$$\Rightarrow \omega_{-3\text{dB}} = 2\pi \cdot 500 \text{ kHz} \cdot \frac{1}{0.2674^{1/4}}$$

$$\underline{\underline{\omega_{-3\text{dB}} = 2\pi \cdot 695.3 \text{ kHz}}}$$

Implementation:

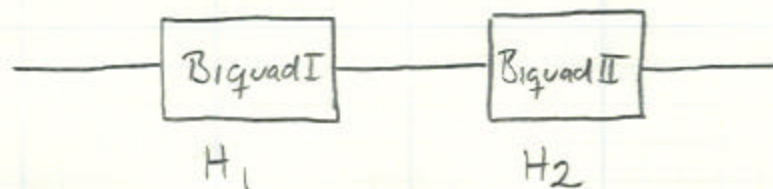
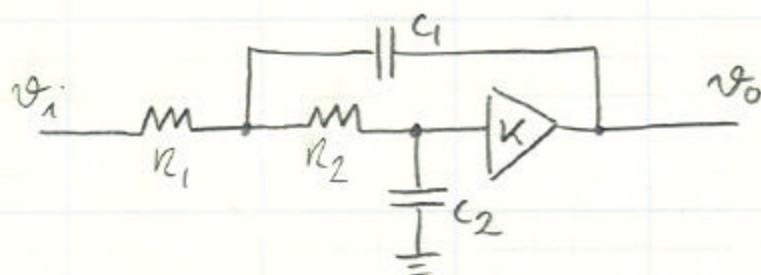
$$H(s) = \frac{G \omega_0^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$



$$\omega_0 = \frac{1}{\sqrt{R_1 C_1 R_2 C_2}} \quad G = K \quad Q = \frac{\omega_0}{\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1-K}{R_2 C_2}}$$

from Matlab:

$$\omega_{01} = 4.3687 \text{ Mrad/s}$$

$$\omega_{02} = 4.3687 \text{ Mrad/s}$$

$$Q_1 = 0.5412$$

$$Q_2 = 1.3066$$

$$G = K = 1, \text{ choose } R_1 = R_2 = R = R_{\max} = 100k \text{ (nom)}$$

$$\Rightarrow Q = \frac{\omega_0 R C_1}{2} \quad (\text{note that } Q \text{ does not change with systematic RC variations!})$$

$$C_1^+ = \frac{2Q}{\omega_0 R^+} \quad (\text{maximum component values})$$

$$\omega_0 = \frac{1}{R \sqrt{C_1 C_2}}$$

WORST CASE: $R = R^+ = 1.15 R$

$$C_1 = C_1^+ = 1.1 C_1$$


$$C_2 = C_2^+ = 1.1 C_2$$

$$\omega_0 = \frac{1}{1.1 \cdot 1.15} \frac{1}{R \sqrt{C_1 C_2}}$$

$$C_2^+ = \left(\frac{1}{\omega_0 R^+} \right)^2 \cdot \frac{1}{C_1^+} \quad (\text{maximum comp. values})$$

\Rightarrow COMPONENT VALUES SEE MATLAB PRINTOUT

MINIMUM SAMPLING FREQUENCY:

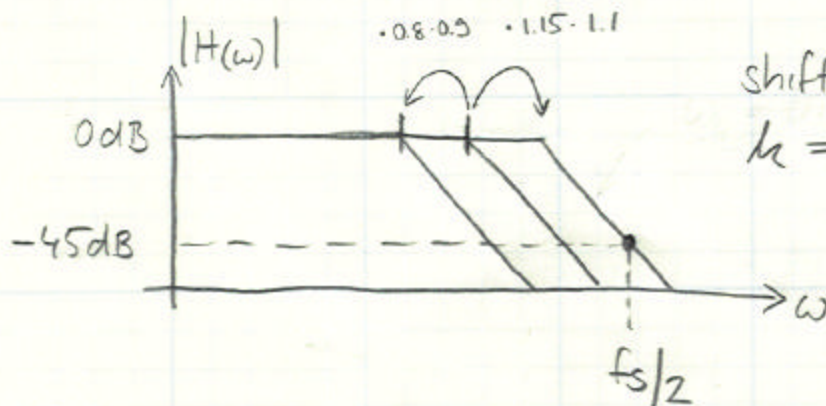

shift by

$$k = \frac{1}{0.8 \cdot 0.9} \cdot 1.15 \cdot 1.1 = 1.757$$

$$|H(f_s/2)|^2 = \frac{1}{1 + \left(\frac{f_s}{2f_{-3dB}^+} \right)^{2N}} \approx \left(\frac{2f_{-3dB}^+}{f_s} \right)^{2N}$$

$$f_s \geq \frac{2f_{-3dB}^+}{|H(f_s/2)|^{1/N}} = \frac{2 \cdot 1.757 \cdot 695.3 \text{ kHz}}{10^{-45/(20 \cdot 4)}}$$

$$f_s \geq 8.36 \text{ MHz}$$

MATLAB OUTPUT:

w01 =
4.3687e+006

w02 =
4.3687e+006

Q1 =
0.5412

Q2 =
1.3066

COMPONENT VALUES (MAX, NOM, MIN)

R =
1.0e+005 *
1.1500 1.0000 0.8500


C11 =
1.0e-011 *
0.2154 0.1959 0.1763

C12 =
1.0e-011 *
0.5201 0.4728 0.4256

C21 =
1.0e-011 *
0.1839 0.1672 0.1505

C22 =
1.0e-012 *
0.7617 0.6925 0.6232

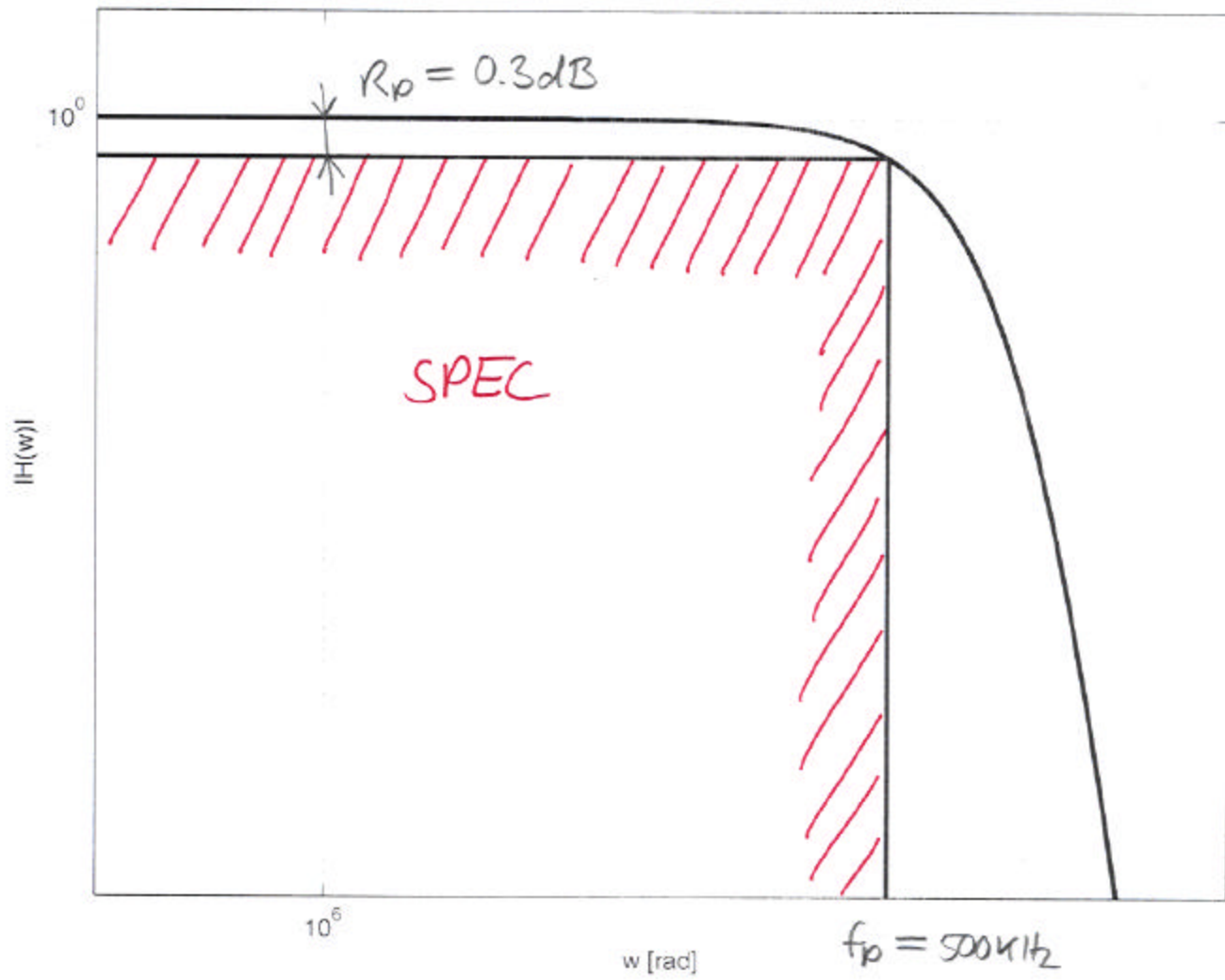EE247 HW2 Problem 1 - Passband Plot vs. Spec



% EE247 Homework#2 Problem 1

% Boris Murmann

% filter specification and synthesis

N = 4;

Wn = 2*pi*695.3e3; % -3dB frequency [rad] (hand calculated)

[Z, P, K] = butter(N, Wn, 's');

% Plot frequency response and check vs. spec

w1 = 2*pi*100e3;

w2 = 2*pi*1000e3;

wp = 2*pi*500e3;

Ap = 10^(-0.3/20);

Amin = 0.5;

[NUM, DEN] = zp2tf(Z, P, K);

[H, W] = freqs(NUM, DEN);

loglog(W, abs(H), 'LineWidth', 2);

axis([w1 w2 Amin 1.1]);

line([w1 wp], [Ap Ap], 'LineWidth', 2, 'Color', 'red');

line([wp wp], [Ap Amin], 'LineWidth', 2, 'Color', 'red');

title('EE247 HW2 Problem 1 - Passband Plot vs. Spec');

xlabel('w [rad]');

ylabel('|H(w)|');

grid;

% Break up into biquads

[NUM1, DEN1] = zp2tf([], P(1:2), 1);

[NUM2, DEN2] = zp2tf([], P(3:4), 1);

w01 = sqrt(DEN1(3));

w02 = sqrt(DEN2(3));

Q1 = w01/DEN1(2);

Q2 = w02/DEN2(2);

% Calculate components

Rnom=100e3;

MR=1.15;

MC=1.1;

mR=0.85;

mC=0.9;

% Maximum component values

R(1) = Rnom*MR;

C11(1) = 2*Q1/(w01*R(1));

C12(1) = 2*Q2/(w02*R(1));

C21(1) = (1/C11(1)) * (1/(w01*R(1)))^2;

C22(1) = (1/C12(1)) * (1/(w02*R(1)))^2;

% Nominal component values

R(2) = R(1)/MR;

C11(2) = C11(1)/MC;

C12(2) = C12(1)/MC;

C21(2) = C21(1)/MC;

C22(2) = C22(1)/MC;

% Minimum component values

R(3) = R(2)*mR;

C11(3) = C11(2)*mC;

C12(3) = C12(2)*mC;

C21(3) = C21(2)*mC;

C22(3) = C22(2)*mC;

R

C11

C12

C21

C22

* EE247 Homework#2 - Problem 1
* Spectre Input
* Boris Murmann

***** Circuit Description *****

simulator lang=spectre

vin (vi 0) vsource mag=1

b1nom (vi volnom) skbp res=100k cap1=1.959p cap2=1.672p k=1

b2nom (volnom vomom) skbp res=100k cap1=4.728p cap2=0.6925p k=1

b1min (vi volmin) skbp res=85k cap1=1.763p cap2=1.505p k=1

b2min (volmin vomom) skbp res=85k cap1=4.256p cap2=0.623p k=1

b1max (vi volmax) skbp res=115k cap1=2.154p cap2=1.839p k=1

b2max (volmax vomom) skbp res=115k cap1=5.201p cap2=0.762p k=1

subckt skbp (vi vo)

parameters cap res cap1 cap2 k

r1 (vi 1) resistor r=res

r2 (2 1) resistor r=res

c1 (1 vo) capacitor c=cap1

c2 (2 0) capacitor c=cap2

k1 (vo 0 2 0) vcvs gain=k

ends skbp

***** Control Statements *****

SimOptions options

+ rawfmt= psfbin

+ gmin= 1E-12

+ reltol= 1E-03

+ vabstol= 1E-06

+ iabstol= 1E-12

+ temp= 27

ACsweep ac start=100k stop=10M dec=100

Spexbre Output - Problem 1

$|H(f)|$

10^0

10^{-1}

10^{-2}

10^{-3}

10^{-4}

10^{-5}

100K

1M

freq (Hz)

→

MIN

NOM

MAX

RC

-45dB


10M

$f_s/2$

$= 8.36 \text{ MHz} / 2$

$\uparrow |H(f)|$

Spectre Output - Problem 1

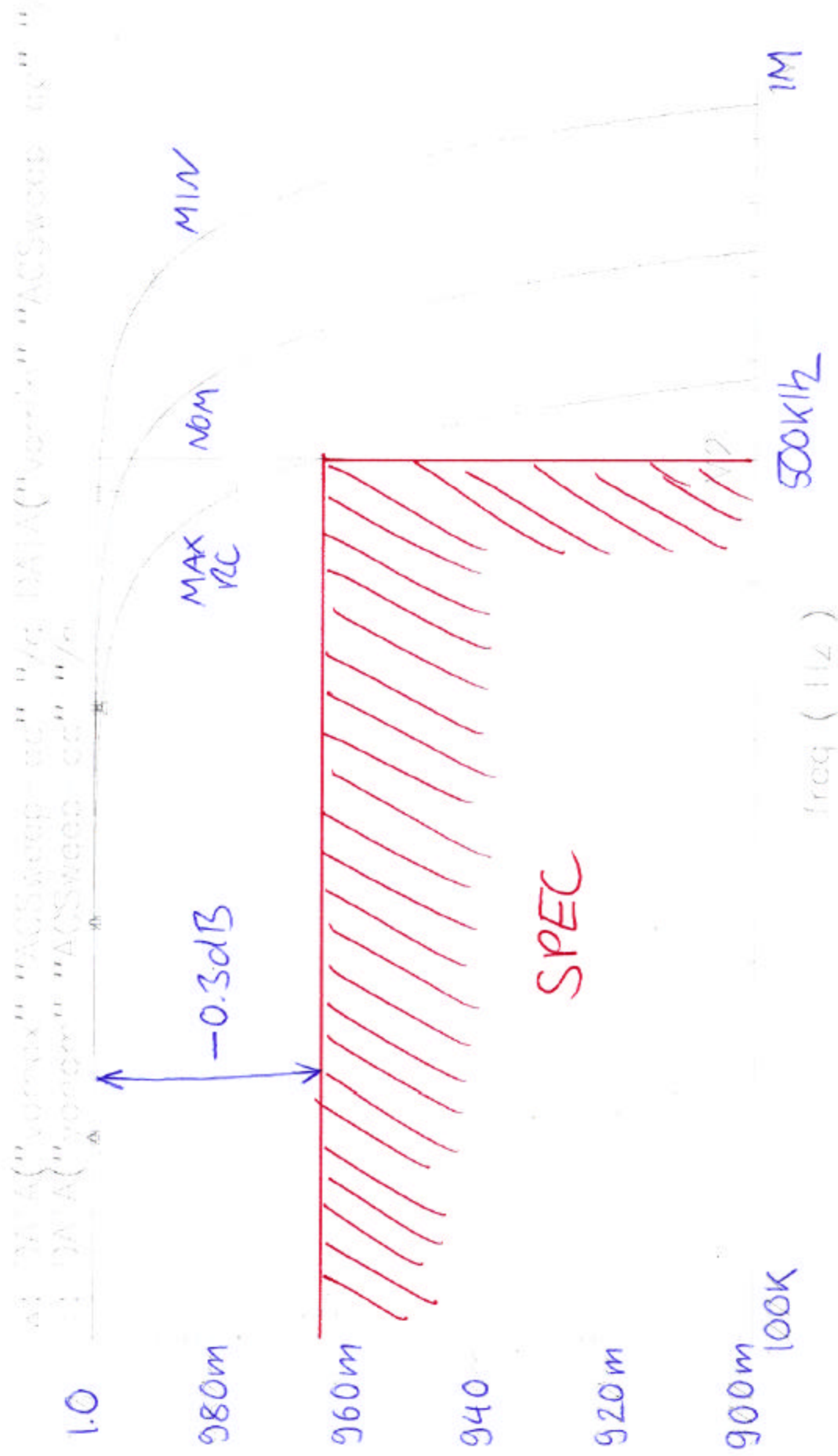

$$(2) \quad H_1(s) = \frac{-K_{oa}}{s + \omega_{oa}}$$

$$H_2(s) = \frac{K_{2b}s^2 + K_{ob}}{s^2 + \frac{\omega_{ob}}{Q}s + \omega_{ob}^2}$$

$K_{1b} = 0$ (complex conj. zeros)

From Matlab:

$$K \cdot \frac{(s-z_1)(s-z_2)}{(s-p_1)(s-p_2)(s-p_3)}$$

$\downarrow \qquad \qquad \downarrow$
 $H_2(s) \qquad \qquad H_1(s)$

- $H_1(s=0) = -\frac{K_{oa}}{\omega_{oa}} \stackrel{!}{=} -1$ (want unity gain)


$$\omega_{oa} = \frac{-1}{p_3} \quad ; \quad K_{oa} = \omega_{oa}$$

- use `zp2tf` ($[z_1, z_2], [p_1, p_2], K/K_{oa}$)

$$\Rightarrow \omega_{ob}, Q, K_{ob}, K_{2b}$$

$$\left. \begin{array}{l} \rightarrow \omega_{oa} = 3.29 \text{ Mrad/s} = K_{oa} \\ \rightarrow \omega_{ob} = 6.3 \text{ Mrad/s} \\ \quad Q = 2.21 \\ \quad K_{ob} = 3.97 \cdot 10^{15} \\ \quad K_{2b} = 0.13 \frac{1}{\text{rad}^2} \end{array} \right\} \begin{array}{l} \underline{\underline{H_1(s)}} \\ \underline{\underline{H_2(s)}} \end{array}$$

Implementation:

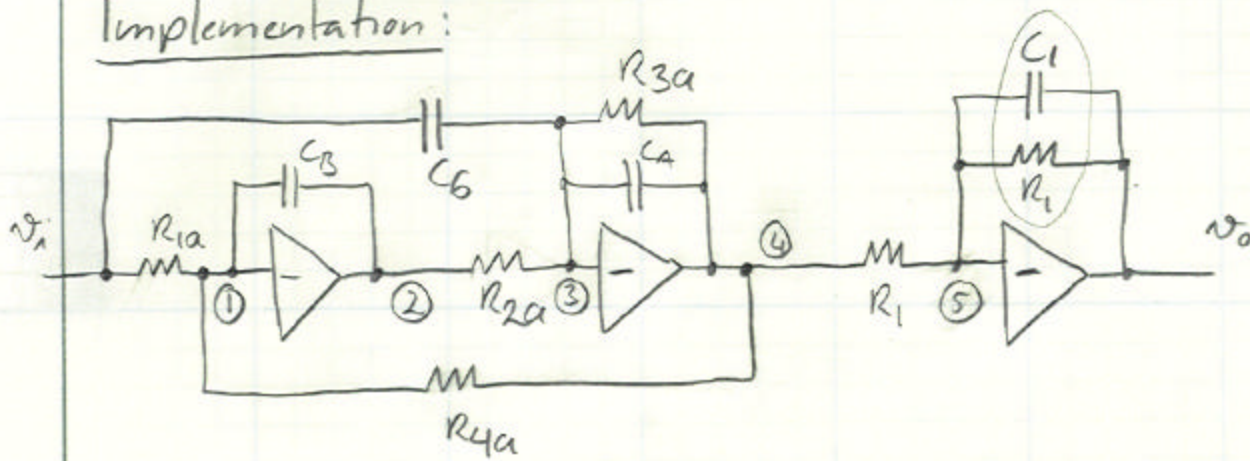

- $C_1 = \frac{1}{\omega_{oa} R_1} = 303.9 \text{ fF}$ with $R_1 = R_{\max} = 100\text{k}$

- \rightarrow iteratively scale C_A, C_B until all $R < R_{\max}$
using Matlab:

$$R_{1a} = 79.37\text{k}$$

$$R_{2a} = -39.68\text{k}$$

$$R_{3a} = 87.54\text{k}$$

$$R_{4a} = 79.37\text{k}$$


$$C_A = 400\text{fF}$$

$$C_B = 200\text{fF}$$


$$C_6 = 52.8\text{fF} \checkmark > 50\text{fF}$$

\rightarrow Simulation Results see attached

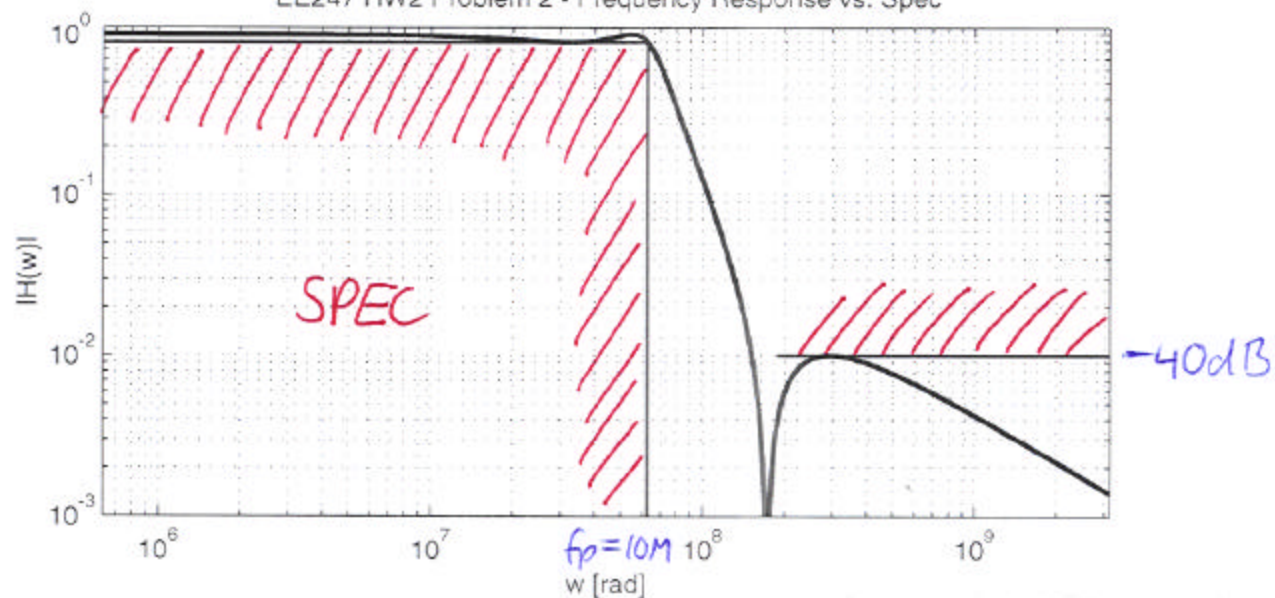EE247 HW2 Problem 2 - Frequency Response vs. Spec



EE247 HW2 Problem 2 - Passband Zoom

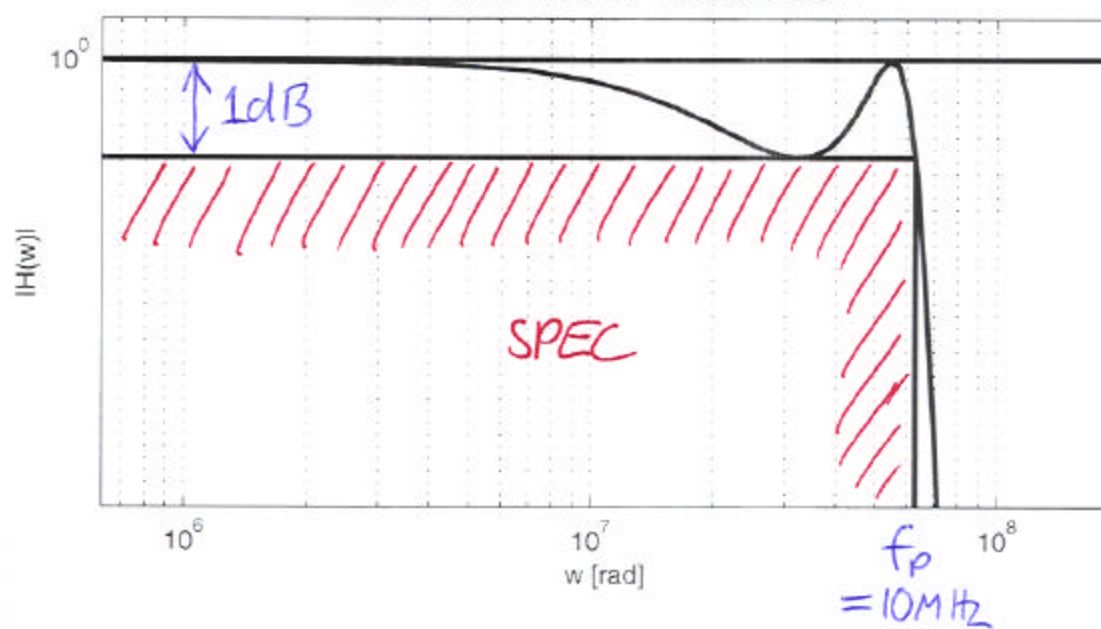

% EE247 Homework#2 Problem 2

% Boris Murmann

% filter specification and synthesis

```
clear;
N = 3;
Rp = 1;
Rs = 40;
Wn = 2*pi*10e6; % cutoff frequency [rad]
[Z, P, K] = ellip(N, Rp, Rs, Wn, 's');
```

% Plot frequency response and check vs. spec

% Plot range

```
w1 = 2*pi*100e3;
w2 = 2*pi*500e6;
wp = Wn;
ws = 2*pi*30e6;
Ap = 10^(-Rp/20);
As = 10^(-Rs/20);
Amin = 10^((-Rs-20)/20);
[NUM, DEN] = zp2tf(Z, P, K);
[H, W] = freqs(NUM, DEN, w1:(w2-w1)/1000:w2);
```

subplot(2,1,1)

```
loglog(W, abs(H), 'LineWidth', 2);
```

```
axis([w1 w2 Amin 1.1]);
```

% horizontal passband line

```
line([w1 wp], [Ap Ap], 'LineWidth', 1, 'Color', 'red');
```

```
%line([w1 ws], [1 1], 'LineWidth', 1, 'Color', 'red');
```

% horizontal stopband line

```
line([ws w2], [As As], 'LineWidth', 1, 'Color', 'red');
```

% vertical passband line

```
line([wp wp], [Ap Amin], 'LineWidth', 1, 'Color', 'red');
```

% vertical stopband line

```
%line([ws ws], [1 As], 'LineWidth', 1, 'Color', 'red');
```

```
title('EE247 HW2 Problem 2 - Frequency Response vs. Spec');
```

```
xlabel('w [rad]');
```

```
ylabel('|H(w)|');
```

```
grid;
```

subplot(2,1,2)

```
loglog(W, abs(H), 'LineWidth', 2);
```

```
axis([w1 ws Ap-0.3 1.05]);
```

% horizontal passband line

```
line([w1 wp], [Ap Ap], 'LineWidth', 2, 'Color', 'red');
```

```
line([w1 ws], [1 1], 'LineWidth', 2, 'Color', 'red');
```

% horizontal stopband line

```
line([ws w2], [As As], 'LineWidth', 2, 'Color', 'red');
```

% vertical passband line

```
line([wp wp], [Ap Amin], 'LineWidth', 2, 'Color', 'red');
```

% vertical stopband line

```
%line([ws ws], [1 As], 'LineWidth', 2, 'Color', 'red');
```

```
title('EE247 HW2 Problem 2 - Passband Zoom');
```

```
xlabel('w [rad]');
```

```
ylabel('|H(w)|');
```

```
grid;
```

% Calculate Coefficients

% First order section

% Desired DC Gain is G2=1

```
G1=1;
```

```
w0a=-P(3)
```

```
K0a=G1*w0a
```


% Second order section

% DC Gain is also one, by using K/K0b as the K parameter in zp2tf

```
[NUM1, DEN1] = zp2tf([Z(1:2)], P(1:2), K/K0a);
```

```
w0b=sqrt(DEN1(3))
```


Spectre Output - Problem 2

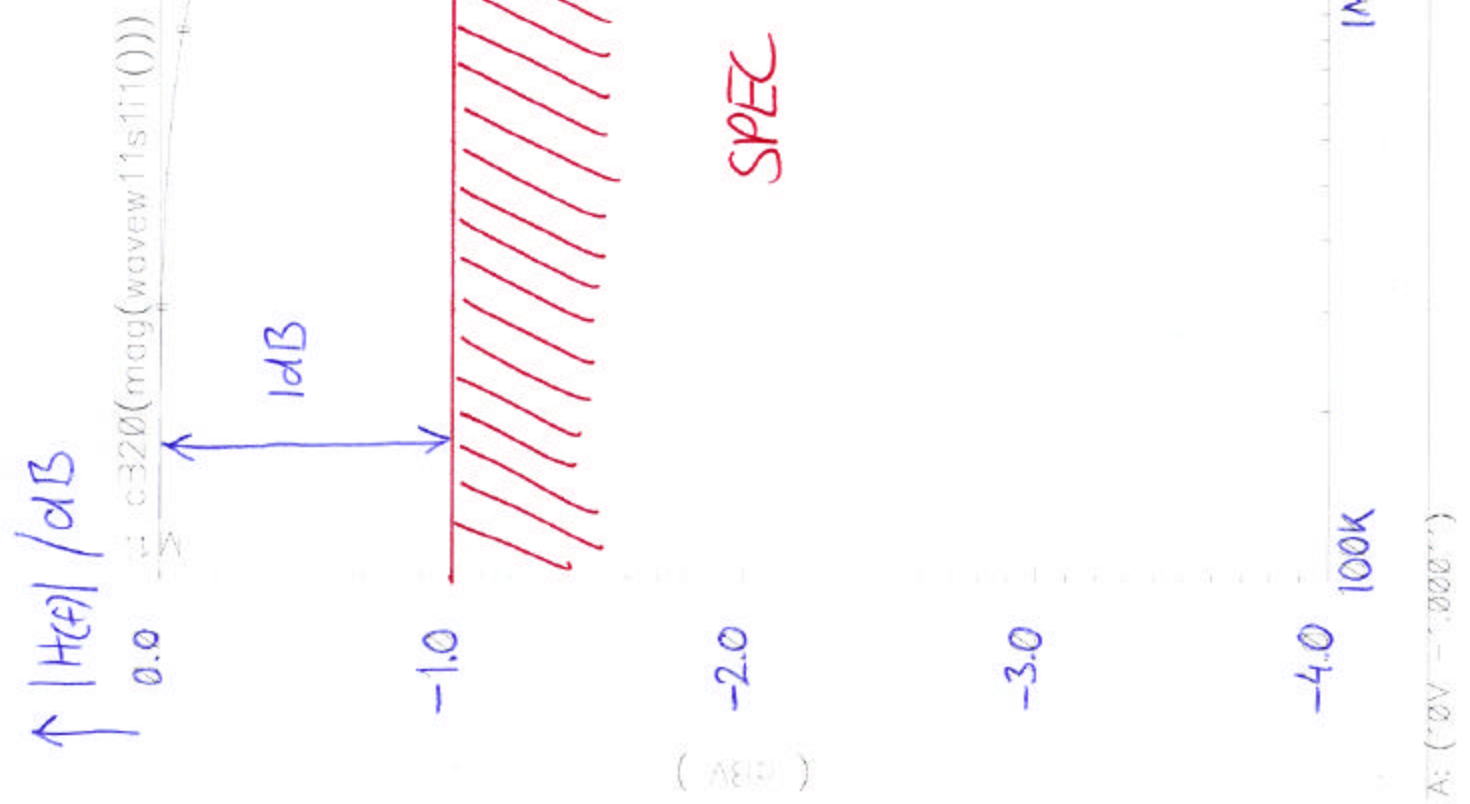

$\uparrow |H(\omega)|/dB$

Spectre Output - Problem 2

1: c320(mag(wavew11s1i1()))

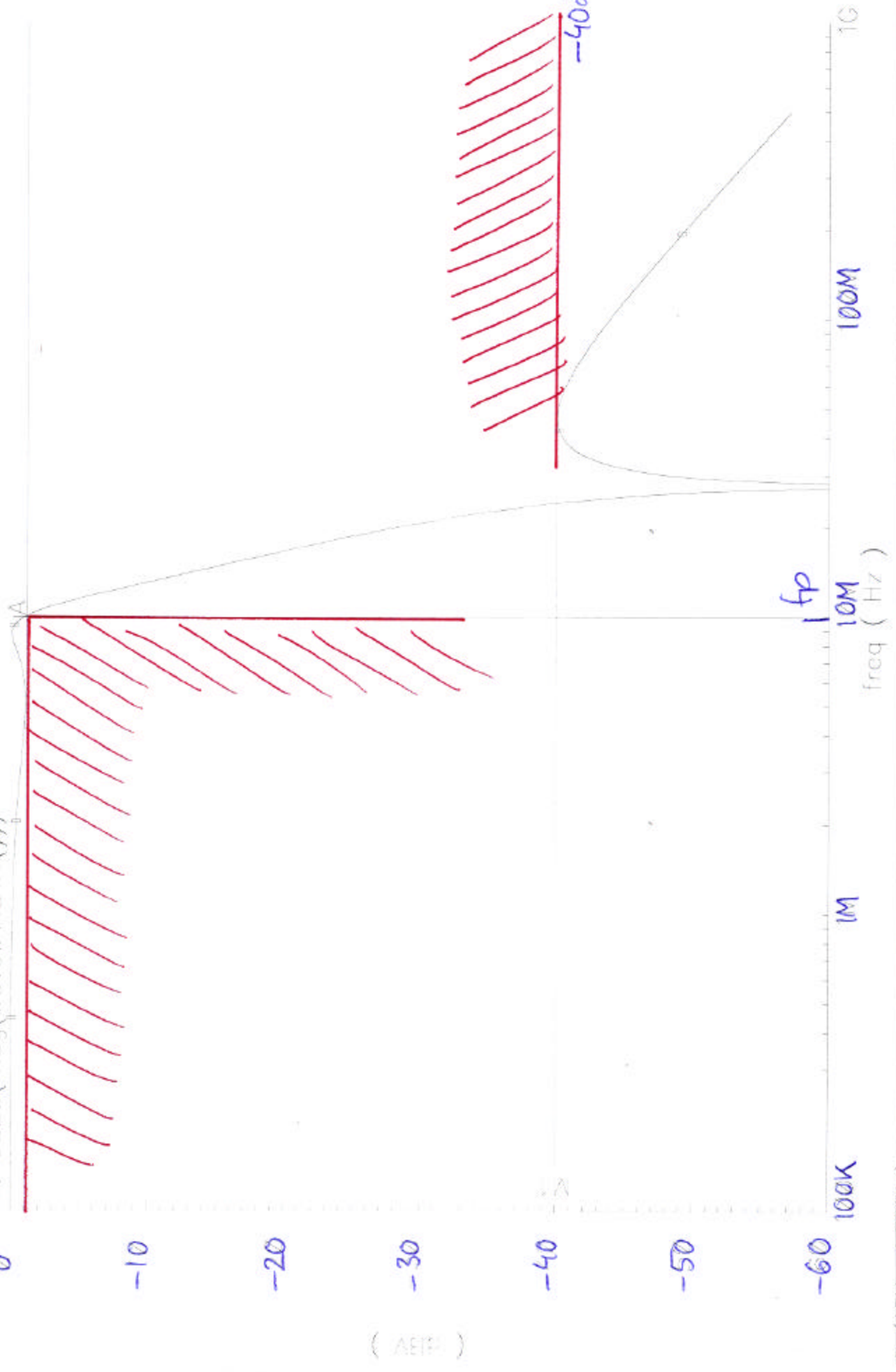

A: (10V - 1000000)

* EE247 Homework#2 - Problem 2
* Spectre Input
* Boris Murmann

***** Circuit Description *****

* component values from matlab
parameters

+R1 = 100k
+C1 = 3.0389e-013
+CA = 4.0000e-013
+CB = 2.0000e-013
+R1a = 7.9366e+004
+R2a = -3.9683e+004
+R3a = 8.7539e+004
+R4a = 7.9366e+004
+C6 = 5.2853e-014

vin (vi 0) vsource mag=1

r1x (vi 1) resistor r=R1a
r2x (2 3) resistor r=R2a
r3x (3 4) resistor r=R3a
r4x (1 4) resistor r=R4a
cax (3 4) capacitor c=CA
cbx (1 2) capacitor c=CB
c6x (vi 3) capacitor c=C6
amp1(2 0 1 0) vcvs gain=-1e6
amp2(4 0 3 0) vcvs gain=-1e6

r1l (4 5) resistor r=R1
r12 (5 v0) resistor r=R1
clx (5 v0) capacitor c=C1
amp3(v0 0 5 0) vcvs gain=-1e6

***** Control Statements *****

SimOptions options

+ rawfmt= psfbin
+ gmin= 1E-12
+ reltol= 1E-03
+ vabstol= 1E-06
+ iabstol= 1E-12
+ temp= 27

ACsweep ac start=100k stop=500Meg dec=100