

UNIVERSITY OF CALIFORNIA**College of Engineering****NTU 776CA (EECS 247)****Midterm (120 minutes)****October 15-19, 2001**

Exam is open-book, open-notes. Clearly mark results with box around. No credit for ambiguous solutions. Show derivations. Return this cover page. Good luck!

Name: Solution

PROBLEM	SCORE
1	
2	
Total	

(Total # of pages = 7
including this one)

1. [40] Consider the following Z-domain filter transfer function.


$$H(z) = \frac{1 - z^{-1}}{2 + z^{-1}}$$

- Find the poles and zeros of $H(z)$. [10]
- Sketch the frequency response of the filter between $-\pi$ and π . Is it highpass, lowpass, or bandpass? [10]
- Draw a fully differential circuit that realizes this transfer function using LDI integrators and switched capacitors. Assume you have non-overlapping two-phase clocks available. Your answer will be graded on the number of components used in your circuit. [20]

Hint: you may realize negative numbers with fully differential circuits.

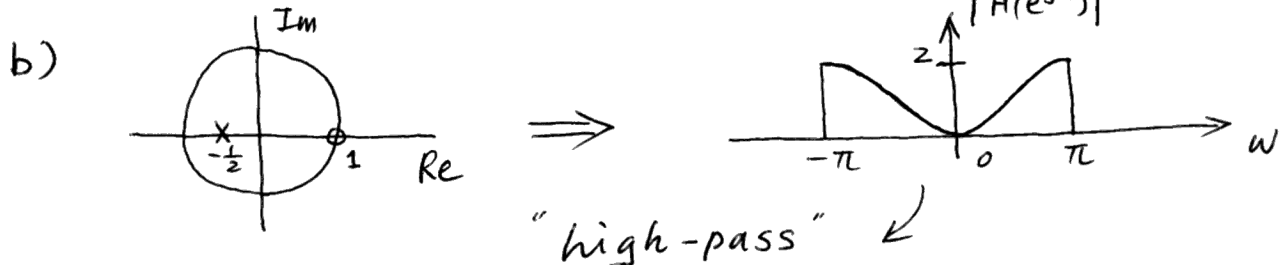a) zero : $1 - z^{-1} = 0 \Rightarrow z = 1$

pole : $2 + z^{-1} = 0 \Rightarrow z = -\frac{1}{2}$



c) $\frac{Y(z)}{X(z)} = H(z) = \frac{1 - z^{-1}}{2 + z^{-1}}$

$$\Rightarrow Y(z)(2 + z^{-1}) = X(z)(1 - z^{-1})$$


$$2Y(n) + Y(n-1) = X(n) - X(n-1]$$

$$Y(n) = -\frac{1}{2}Y(n-1) + \frac{1}{2}[X(n) - X(n-1)] \quad (*)$$

#1. c) cont'd

we need 1 LDI, 2 caps (one switched)

single-ended prototype

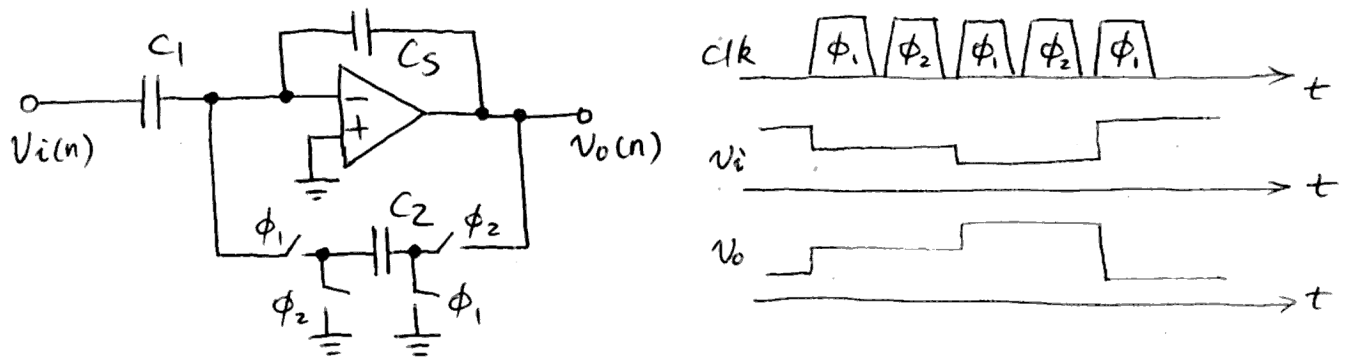

Derive TF using charge conservation principle.

$$@ \phi_2: v_i(n-1)C_1 + v_o(n-1)(C_2 + v_o(n-1)C_S) = \Sigma Q$$

$$@ \phi_1: v_i(n)C_1 + \phi + v_o(n)C_S = \Sigma Q'$$

but $\Sigma Q = \Sigma Q'$, so


$$v_i(n-1)C_1 + v_o(n-1)C_2 + v_o(n-1)C_S = v_i(n)C_1 + v_o(n)C_S$$

$$\Rightarrow v_o(n) = \left(\frac{C_2 + C_S}{C_S} \right) v_o(n-1) + \frac{C_1}{C_S} [v_i(n-1) - v_i(n)]$$


compare this with (*), we have

$$C_1 = -\frac{1}{2}C_S, \quad C_2 = -\frac{3}{2}C_S$$

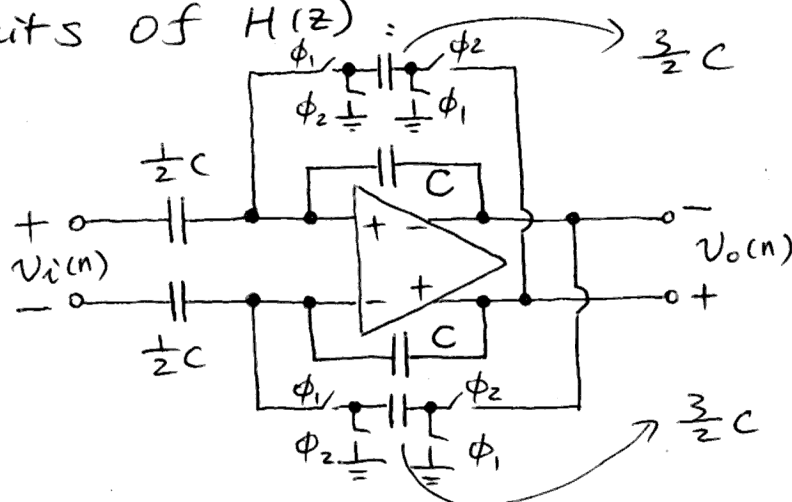This leads to the final implementation using differential circuits of $H(z)$:




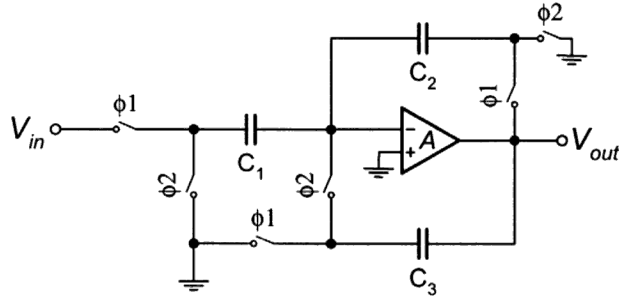2. [60] Performance of switched-capacitor circuits often suffers from nonidealities of op amps, i.e., finite bandwidth, finite gain, offset etc. The following predictive SC amplifier is claimed to be able to compensate the finite-gain effect of the op amp. Assume the op amp gain is A (frequency independent). ϕ_1 and ϕ_2 are non-overlapping two-phase clocks. V_{in} and V_{out} updates when $\phi_1=1$.



- Derive the Z-domain voltage transfer function $V_{out}(z)/V_{in}(z)$ with finite A . [20]
- Explain why the predictive SC amplifier works. What is the limitation of this compensation scheme? You may explain intuitively and justify your answer with the result you obtain in a). [20]
Hint: think about when the frequency of V_{in} approaches f_{clk} , the clock frequency.
- Someone also claims this compensation scheme can remove the input offset of the op amp. Can you prove that? [20]

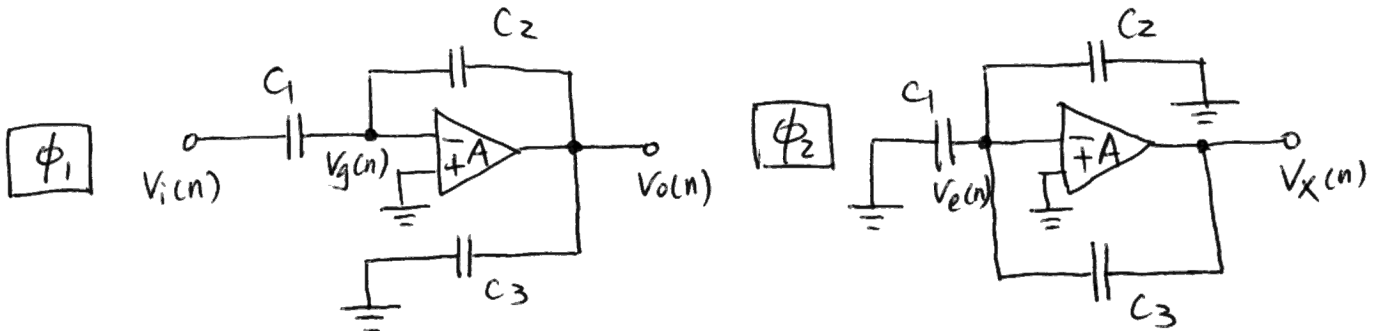a) Redraw the ckt in ϕ_1 & ϕ_2 respectively.



We will use the charge conservation law to derive the VTF. We need to take A into account in the process.

#2. a) cont'd

step 1 start in ϕ_2 , time $(n-1)$. Assume C_1 & C_2 are fully discharged. Then in time n , we balance the charge.

$$\begin{array}{ccc} \boxed{\phi_2} (n-1) & & \boxed{\phi_1} (n) \\ \sum Q = \phi \equiv \sum Q = [V_i(n) - V_g(n)]C_1 + [V_o(n) - V_g(n)]C_2 \\ \Rightarrow & \boxed{V_o(n) = - \left\{ \frac{C_1}{C_2 + \frac{C_1 + C_2}{A}} \right\} V_i(n)} & (*) \end{array}$$

$$\text{or } \frac{V_o(n)}{V_i(n)} = - \frac{C_1}{C_2 + \frac{C_1 + C_2}{A}} \quad \text{"finite-gain effect"}$$

step 2 start in ϕ_2 , time (n) , work into ϕ_1 , time $(n+1)$.

$$\begin{array}{ccc} \boxed{\phi_2} (n) & & \boxed{\phi_1} (n+1) \\ -C_1 V_e(n) - C_2 V_e(n) + [V_x(n) - V_e(n)]C_3 & & [V_i(n+1) - V_g(n+1)]C_1 + [V_o(n+1) - V_g(n+1)]C_2 \\ = V_o(n)C_3 & & = -C_1 V_e(n) - C_2 V_e(n) \end{array}$$

$$\begin{array}{ccc} \Downarrow & & \Downarrow \\ V_e(n) = -V_o(n) \frac{C_3}{C_1 + C_2 + C_3 + AC_3} & & V_i(n+1)C_1 + V_o(n+1) \left(C_2 + \frac{C_1 + C_2}{A} \right) \\ \text{or } V_e(n) = - \frac{V_o(n)}{A + \frac{C_1 + C_2 + C_3}{C_3}} & & = -V_e(n) (C_1 + C_2) \end{array}$$

$$\Downarrow$$

$$V_i(n+1)C_1 + V_o(n+1) \left(C_2 + \frac{C_1 + C_2}{A} \right) = V_o(n) \frac{C_1 + C_2}{A + \frac{C_1 + C_2 + C_3}{C_3}}$$

#2

 \Rightarrow

$$\frac{V_o}{V_i}(z) = \frac{-C_1}{c_2 + \frac{C_1+C_2}{A} - \frac{z^{-1}(C_1+C_2)}{A + \frac{C_1+C_2+C_3}{C_3}}}$$

(*)

if $\frac{C_1+C_2+C_3}{C_3} \ll A$ holds, we may write:

$$\frac{1}{A + \frac{C_1+C_2+C_3}{C_3}} \approx \frac{1}{A} - \underbrace{\left(\frac{C_1+C_2+C_3}{C_3} / A^2 \right)}_{\text{ignore for } A \gg 1}$$

This leads to ,

$$\Rightarrow \frac{V_o}{V_i}(z) \approx \frac{-C_1}{c_2 + \frac{C_1+C_2}{A}(1-z^{-1})} = H(z)$$

b) if $f_{in} \ll f_{clk}$, then $z \approx 1$ (low-freq input)


$$\Rightarrow \frac{V_o}{V_i}(z) \approx -\frac{C_1}{C_2}$$

The gain dependent term $\frac{C_1+C_2}{A}(1-z^{-1})$ vanishes for low-freq input. This explains why this SC amplifier is called "predictive" since signals that are slow are easy to be predicted from sample to sample. So, ϕ_1 is amplifying phase, while ϕ_2 is predicting phase.

Caution as f_{in} approaches f_{clk} , we see in the right plot that z approaches -1 .

$$\Rightarrow \frac{V_o}{V_i}(z) \approx \frac{-C_1}{c_2 + \left(\frac{C_1+C_2}{A} \right) \cdot 2}$$

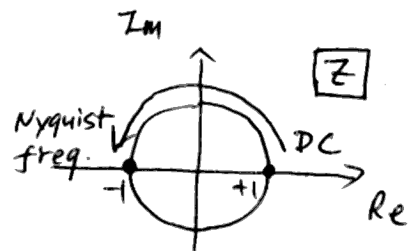Now, we actually enhance the error due to finite gain.



This is the limitation of this scheme.

#2

c) This is simple. Assume A is large.

$$\boxed{\phi_2} (n-1)$$

$$\boxed{\phi_1} (n)$$

$$\Sigma Q = -V_{os} (C_1 + C_2) \equiv \Sigma Q = [V_{i(n)} - V_{g(n)}] C_1 + [V_{o(n)} - V_{g(n)}] C_2$$

$$\Rightarrow -V_{os} (C_1 + C_2) = V_{i(n)} C_1 + V_{o(n)} C_2 - V_{g(n)} (C_1 + C_2)$$

but $V_{g(n)} = V_{os}$, so the LHS and the last term in RHS cancel, we have,

$$\emptyset = V_{i(n)} C_1 + V_{o(n)} C_2$$

$$\text{or } \frac{V_{o(n)}}{V_{i(n)}} = - \frac{C_1}{C_2}$$

no V_{os} effect.