




UNIVERSITY OF CALIFORNIA
College of Engineering
Department of Electrical Engineering
and Computer Sciences

B. E. BOSER

Midterm
Friday, October 27, 2000

EECS 247
FALL 2000

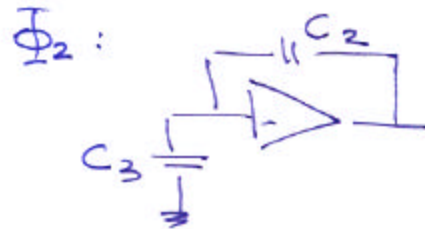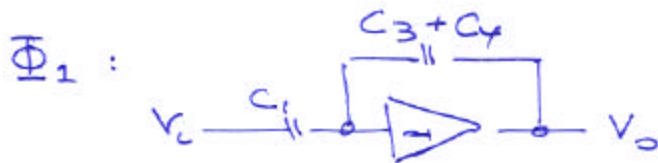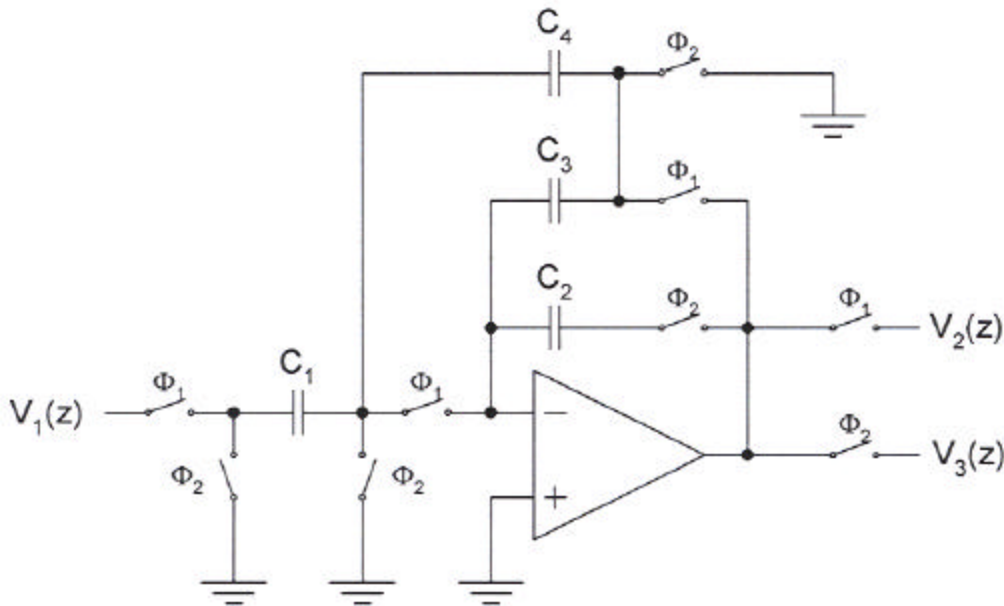1. Find the following transfer functions (the amplifier is ideal):
a) $H_1(z) = V_2(z) / V_1(z)$, during phase 1, and
b) $H_2(z) = V_3(z) / V_1(z)$, for phase 1 input and phase 2 output.



(a) $H_1(z) = - \frac{C_1}{C_3 + C_4} \parallel$

(b) $Q_3 = -V_i \cdot \frac{C_1 \cdot C_3}{C_3 + C_4} \cdot z^{-1}$

$Q_2 = C_2 \cdot V_o = C_2 \cdot V_o \cdot z^{-1} + Q_3$

$\Rightarrow H_2(z) = - \frac{C_1 \cdot C_3}{C_3 + C_4} \cdot \frac{1}{C_2} \cdot \frac{z^{-1}}{1 - z^{-1}} \parallel$

Useful in large capacitor spread situations.

2. The transfer function $H(s)$ is realized as a switched capacitor ladder filter with LDI integrators.

$$H(s) = \frac{0.0010005 (s^2 + 1.235) (s^2 + 1.438) (s^2 + 2.408) (s^2 + 15.34)}{(s^2 + 0.4952s + 0.1505) (s^2 + 0.28s + 0.5605) (s^2 + 0.1106s + 0.8742) (s^2 + 0.0272s + 0.9987)}$$

- a) Find the minimum clock frequency for the SC filter that is required to keep all zeros in the response.
b) What type of filter is $H(s)$ realizing (low pass, band pass, etc)?

$$(a) \quad f_{c, \max} = \frac{f_s}{\pi}$$


$$\Rightarrow f_s \geq \pi \cdot f_{z, \max} = \frac{\sqrt{15.34}}{2} = \underline{\underline{1.96 \text{ Hz}}}$$

$$(b) \quad H(s) \Big|_{s=0} = 0.8912 \quad \text{or} \quad -1 \text{ dB}$$

$$H(s) \Big|_{s \rightarrow \infty} = 0.0010005 \quad \text{or} \quad -60 \text{ dB}$$

\Rightarrow LPF

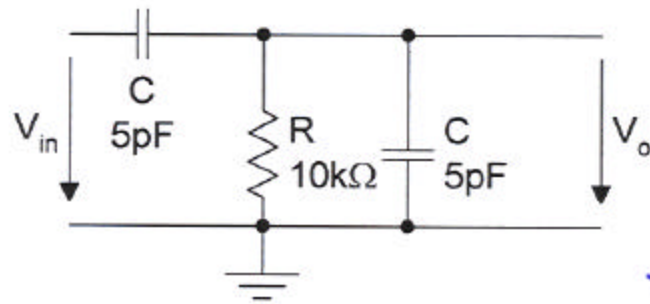3. The output V_o of the filter shown below is processed by an ideal sampler operating at $f_s = 1 \text{ MHz}$ (e.g. an ideal A/D converter). V_{in} is a sinusoid with 1V amplitude and $f_x = 1.3 \text{ MHz}$. Calculate the amplitude and frequency of the sampled output.



$$\tau = RC = 50 \text{ nsec.}$$


$$H(s) = \frac{s\tau}{1 + 2s\tau}$$

$$|H(\omega)|^2 = \frac{(\omega\tau)^2}{1 + (2\omega\tau)^2}$$

$$|H(\omega = 2\pi f_x)| = 0.3163 \text{ V} = \text{Amplitude}$$

$$300 \text{ kHz} = \text{Frequency}$$

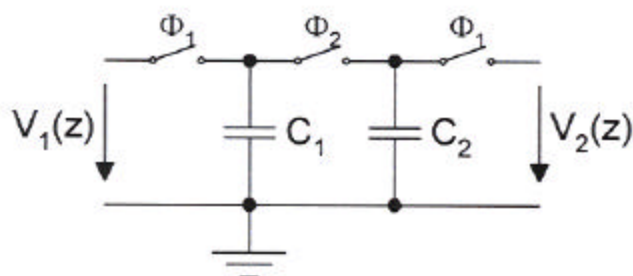4. Find the transfer function $H(z) = V_2(z)/V_1(z)$ of the following SC circuit (for Φ_1):



$$\Phi_2: \quad Q_T = Q_1^{(1)} + Q_2^{(1)} \\ = C_1 \cdot V_1 \cdot z^{-1} + C_2 \cdot V_2 \cdot z^{-1}$$

b

$$V_2(z) = \frac{Q_T}{C_1 + C_2} \\ = \frac{C_1}{C_1 + C_2} \cdot V_1 \cdot z^{-1} + \frac{C_2}{C_1 + C_2} \cdot V_2 \cdot z^{-1}$$

$$V_2 \cdot \left(1 - \frac{C_2}{C_1 + C_2} \cdot z^{-1}\right) = V_1 \cdot z^{-1} \cdot \frac{C_1}{C_1 + C_2}$$

$$\Rightarrow H(z) = \frac{z^{-1} \cdot \frac{C_1}{C_1 + C_2}}{1 - \frac{C_2}{C_1 + C_2} \cdot z^{-1}}$$

(low pass filter).