

UNIVERSITY OF CALIFORNIA
College of Engineering
Department of Electrical Engineering and Computer Sciences
NTU IC-776CA

Homework For Fun **EECS 247**
B. E. BOSER **Spring 2004**
Solution will be posted before final exam

You are to design a 2nd order sigma-delta modulator. Use the structure shown below. The DAC output levels are at $\pm V_{\text{ref}}$.

- a) Modeling the quantizer as an additive white noise source, derive an equation for the SQNR as a function of oversampling ratio M . What oversampling ratio is required for 100dB SQNR? Round to the next higher power of two. What would be the minimum sampling frequency f_s to achieve a 20kHz signal bandwidth (assume a brick-wall filter)?
- b) Verify the dynamic range with simulation. Use a small (e.g. -40dB) sinusoidal input and extrapolate to 0dB (see slide 19 in Lecture 16). Scale the horizontal axis such that 0dB corresponds to the power of a sinusoid with peak-to-peak amplitude $\pm V_{\text{ref}}$.
- c) Plot the root-locus of the modulator as a function of effective quantizer gain G_{eff} . For what range of G_{eff} is the modulator stable?
- d) Plot G_{eff} as a function of input power, using the same scale as in (b). What is the maximum input level for which the modulator is stable?
- e) Scale the modulator internal nodes such that the peak integrator outputs do not exceed the DAC output levels for inputs up to -2dB. Plot the peak integrator outputs as a function of input amplitude for the scaled modulator.

