

**UNIVERSITY OF CALIFORNIA**  
**College of Engineering**  
**NTU 776CA (EECS 247)**

**Midterm (120 minutes)**

**October 15-19, 2001**

Exam is open-book, open-notes. Clearly mark results with box around. No credit for ambiguous solutions. Show derivations. Return this cover page. Good luck!

**Name:** \_\_\_\_\_

<b>PROBLEM</b>	<b>SCORE</b>
1	
2	
<b>Total</b>	


1. [40] Consider the following Z-domain filter transfer function.

$$H(z) = \frac{1 - z^{-1}}{2 + z^{-1}}$$

- a) Find the poles and zeros of  $H(z)$ . [10]
- b) Sketch the frequency response of the filter between  $-\pi$  and  $\pi$ . Is it highpass, lowpass, or bandpass? [10]
- c) Draw a fully differential circuit that realizes this transfer function using LDI integrators and switched capacitors. Assume you have non-overlapping two-phase clocks available. Your answer will be graded on the number of components used in your circuit. [20]

*Hint: you may realize negative numbers with fully differential circuits.*

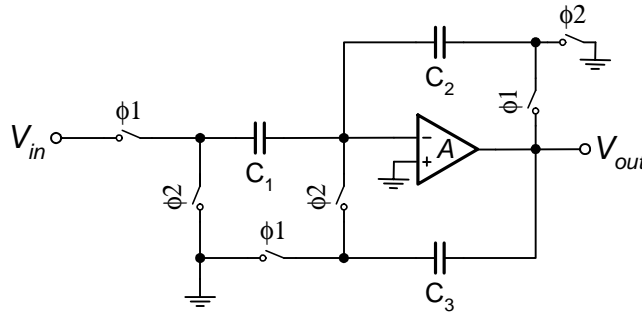2. [60] Performance of switched-capacitor circuits often suffers from nonidealities of op amps, i.e., finite bandwidth, finite gain, offset etc. The following predictive SC amplifier is claimed to be able to compensate the finite-gain effect of the op amp. Assume the op amp gain is  $A$  (frequency independent).  $\phi_1$  and  $\phi_2$  are non-overlapping two-phase clocks.  $V_{in}$  and  $V_{out}$  updates when  $\phi_1=1$ .



- Derive the Z-domain voltage transfer function  $V_{out}(z)/V_{in}(z)$  with finite  $A$ . [20]
- Explain why the predictive SC amplifier works. What is the limitation of this compensation scheme? You may explain intuitively and justify your answer with the result you obtain in a). [20]

*Hint: think about when the frequency of  $V_{in}$  approaches  $f_{clk}$ , the clock frequency.*

- Someone also claims this compensation scheme can remove the input offset of the op amp. Can you prove that? [20]