

UNIVERSITY OF CALIFORNIA
 College of Engineering
 Department of Electrical Engineering and Computer Sciences
 NTU 247

B. E. Boser

Homework 3
 Due Monday, February 19, 2007

NTU 247
 Spring 2007

1. A full-scale sine wave with frequency $f_x = 7\text{MHz}$ is input to a DAC clocked at $f_s = 20\text{MHz}$. Calculate the frequency and amplitude (relative to full-scale input) of all tones in the DAC output up to $f = 50\text{MHz}$. Assume the DAC output for each sample is held for 30ns and returned to zero for 20ns. Ignore quantization noise and other non-idealities.

2. For the differential switched-capacitor integrator below, find the z-domain output/input transfer function assuming:

- a) Output is sampled in Φ_1 ;
- b) Output is sampled in Φ_2 ;
- c) For output sampled in Φ_2 , find the continuous-time equivalent for the integrator time-constant using the output expression derived. Assume $f_{\text{Signal}} / f_{\text{Sampling}} \ll 1$.

