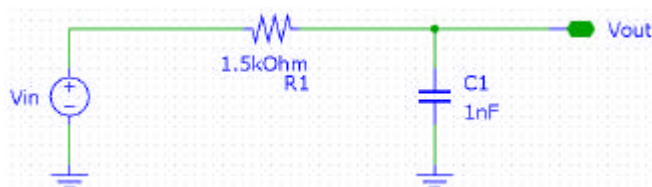


Introduction to Filters

- Filtering = frequency-selective signal processing
 - It's the most common type of signal processing
 - Examples:
 - Extract desired signal from many (radio)
 - Separating signal and noise
 - Amplifier bandwidth limitations
- Where to start
 - Perfectionist: ideal (low-pass) filter
 - Engineer: continuous time, first-order low-pass filter

First-Order RC Filter (LPF1)



Steady-state frequency response:

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{1}{1 + \frac{s}{\omega_o}}$$

with $\omega_o = \frac{1}{RC} = 2\pi \times 100kHz$


Poles and Zeros

$$H(s) = \frac{1}{1 + \frac{s}{\omega_0}}$$


Pole : $p = -\omega_0$

Zero : $z \rightarrow \infty$

s-plane (pzmap):

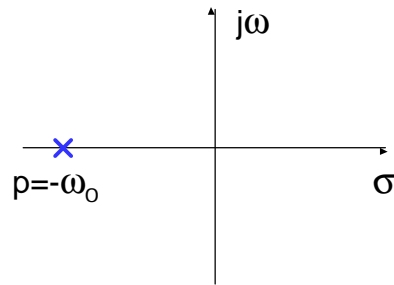

Magnitude Response

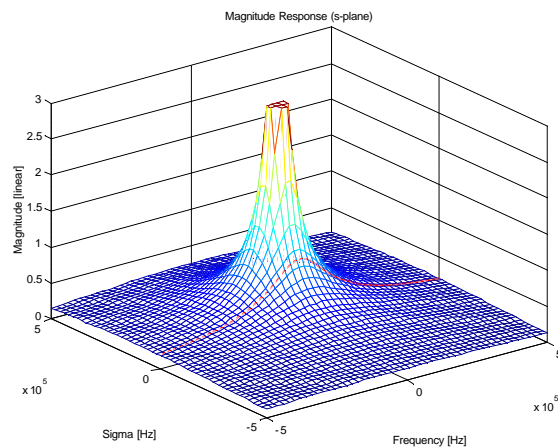

Frequency Response

Asymptotes:

- 20 dB/dec rolloff
- 90 degrees phase shift per 2 decades


$$|H(s = j\omega)|_{\omega=0} = 1$$

$$|H(s = j\omega)|_{\omega \rightarrow \infty} = 0$$

Matlab code (L02_bode_lpf1.m):

```
wo = 2*pi*100e3;  
s = tf('s');  
h = 1 / (1+s/wo);  
bodehz(h, logspace(1, 10, 100));
```

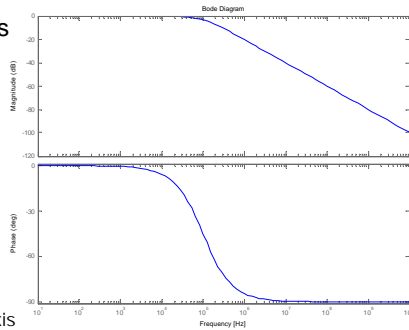Note: bodehz is same as bode, but frequency axis is in Hz, rather than rad/s.




Parasitics

Can we really get 100dB attenuation at 10GHz?

- Probably not
- Parasitics limit the performance of analog components
- E.g.
 - Shunt capacitance
 - Feed-through capacitance
 - Finite inductor, capacitor Q



LPF2

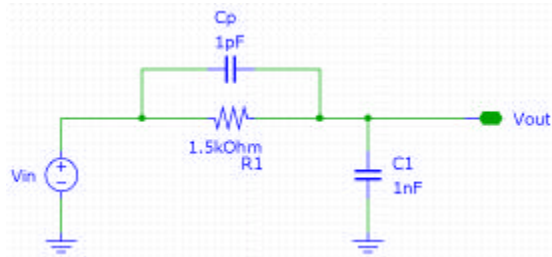


$$H(s) = \frac{1 + sRC_p}{1 + sR(C + C_p)}$$

$$\text{Pole : } p = -\frac{1}{R(C + C_p)} \approx -\frac{1}{RC}$$

$$\text{Zero : } z = -\frac{1}{RC_p}$$

Frequency Response

$$\begin{aligned} |H(j\omega)|_{\omega=0} &= 1 \\ |H(j\omega)|_{\omega \rightarrow \infty} &= \frac{C_p}{C + C_p} \\ &\approx \frac{C_p}{C} \\ &= 10^{-3} \\ &= -60dB \end{aligned}$$

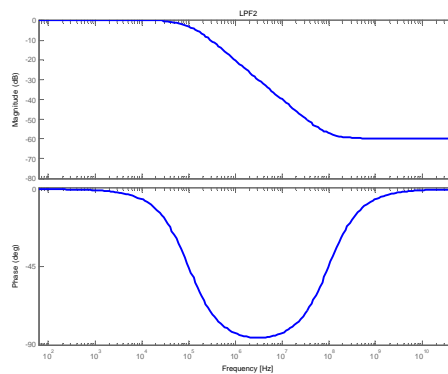

- Why not just make C larger?
- Beware of other parasitics not included in this model ...

Continuous Time Analog

- Analog passive components aren't ideal
 - Extra real poles/zeros result from parasitics
 - Parasitic effects begin to appear “50dB beyond” desired component characteristics
 - Common sense helps you anticipate them
- Digital filters do not suffer from these effects

Second-Order LPF

- Improved attenuation (compared to 1st order)
- Complex poles (rather than multiple real ones)
 - Why?
 - Visualize 3D s-plane plot!
- Biquadratic (2nd order) transfer function:

$$H(s) = \frac{1}{1 + \frac{s}{\omega_p Q_p} + \frac{s^2}{\omega_p^2}}$$
$$\begin{aligned} |H(j\omega)|_{\omega=0} &= 1 \\ |H(j\omega)|_{\omega \rightarrow \infty} &= 0 \\ |H(j\omega)|_{\omega=\omega_p} &= Q_p \end{aligned}$$

Biquad Poles

$$H(s) = \frac{1}{1 + \frac{s}{w_p Q_p} + \frac{s^2}{w_p^2}}$$

has poles at $s = -\frac{w_p}{2Q_p} \left(1 \pm \sqrt{1 - 4Q_p^2}\right)$

for $Q_p \leq \frac{1}{2}$ poles are real, complex otherwise

Complex Poles


$$Q_p > \frac{1}{2}$$

$$s = -\frac{w_p}{2Q_p} \left(1 \pm j\sqrt{4Q_p^2 - 1}\right)$$

Distance from origin in s-plane:


$$\begin{aligned} d^2 &= \left(\frac{w_p}{2Q_p}\right)^2 (1 + 4Q_p^2 - 1) \\ &= w_p^2 \end{aligned}$$

s-Plane

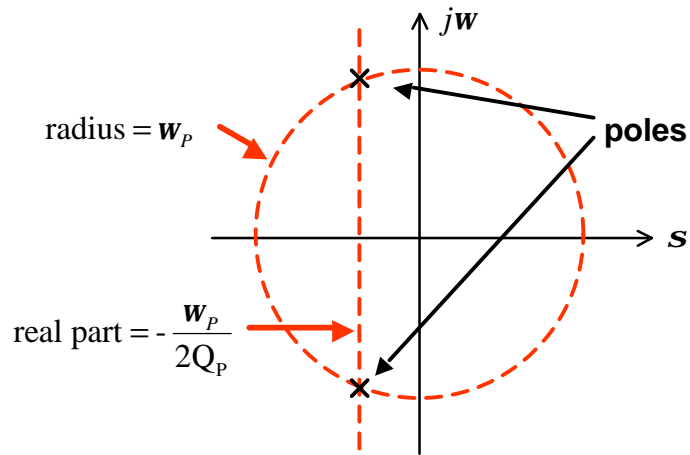


LPF3

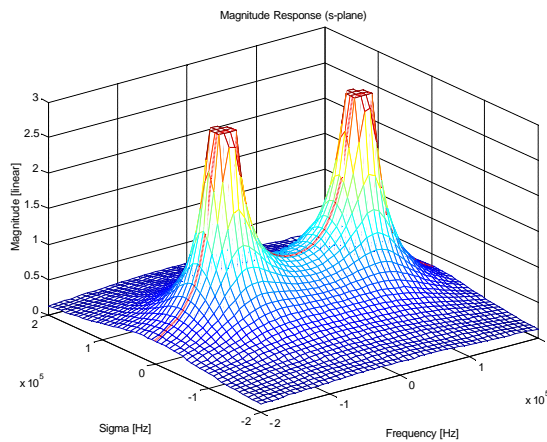
$$w_p = 2p \times 100k\text{Hz}$$
$$Q_p = 10$$



Frequency Response

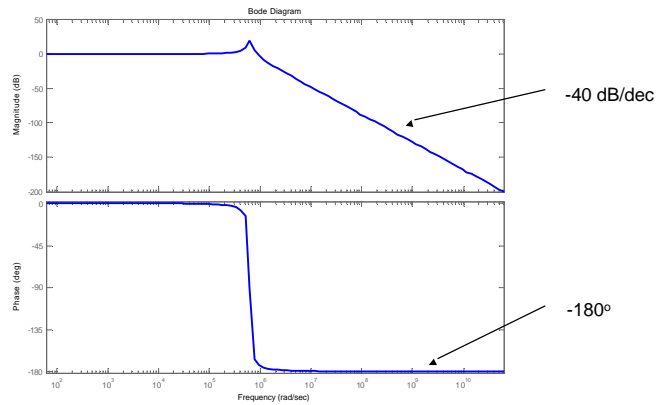


Varying Q ... Magnitude

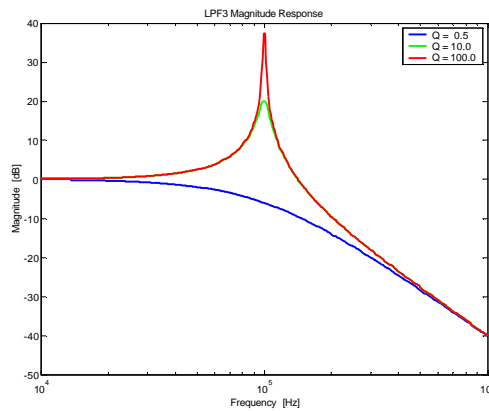

Gain at ω_p :

$20 \log Q$ [dB]

Phase

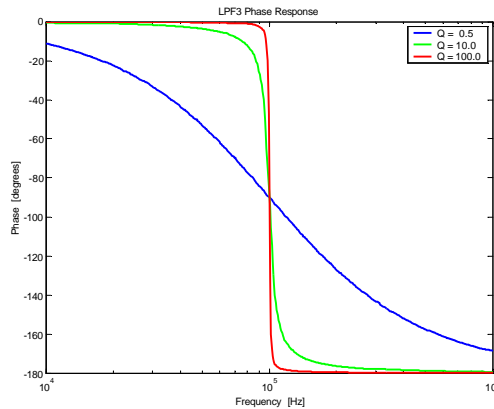


Slope at ω_p :
-45 Q deg/decade

Implementation of Biquads

- Passive RC: only real poles
- Terminated LC
 - “lowest power” (well ... it’s passive!)
 - No noise (except load and source)
- Active Biquad
 - Filter texts give you dozens of topologies. Who needs or wants that many choices?
 - Single-opamp biquad: Sallen-Key
 - Two-opamp biquad: Tow-Thomas

Sallen-Key LPF

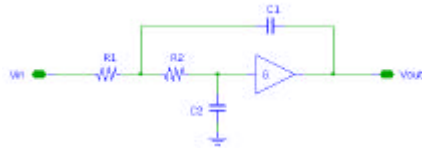

$$H(s) = \frac{G}{1 + \frac{s}{\omega_p Q_p} + \frac{s^2}{\omega_p^2}}$$

$$\omega_p = \frac{1}{\sqrt{R_1 C_1 R_2 C_2}}$$

$$Q_p = \frac{\omega_p}{\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1-G}{R_2 C_2}}$$

- Single gain element
- “Parasitic sensitive”
- Versions for LPF, HPF, BP, ...

Ref: K. L. Su, “Analog Filters,” Chapman & Hall, 1996, pp. 215.

Component Sizing Choice 1

4 unknowns: R_1, R_2, C_1, C_2

2 knowns: ω_p, Q_p

→ problem is underdetermined


Choice 1: minimum component spread

$$C_1 = C_2 = 1nF$$

$$R_1 = R_2 = \frac{1}{\omega_p C_1} = 1.6k\Omega$$

$$G = 3 - \frac{1}{Q_p} = 2.9$$

SK Magnitude Response 1

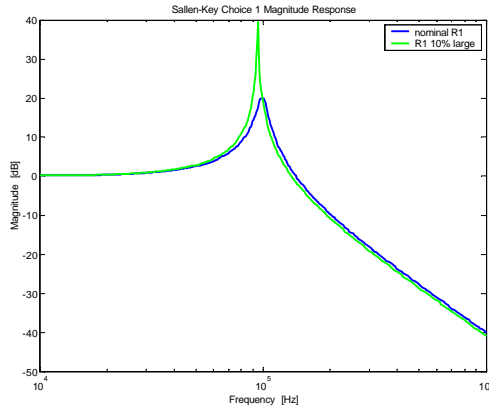

10% increase of R_1
more than doubles Q_p !

→ The circuit is very sensitive
to component variations.

Component Sizing Choice 2

Choice 2: minimum sensitivity

$$G = 1$$

$$R_1 = R_2 = 2k\Omega$$

$$C_1 = \frac{2Q_p}{\omega_p R_1} = 16nF$$

$$C_2 = \frac{1}{2Q_p \omega_p R_1} = 40pF$$


Note also:

$$\frac{C_1}{C_2} = 4Q_p^2 = 400$$

Huge element spread →

This topology is suitable only for
low-Q filter implementations.

SK Magnitude Response 2

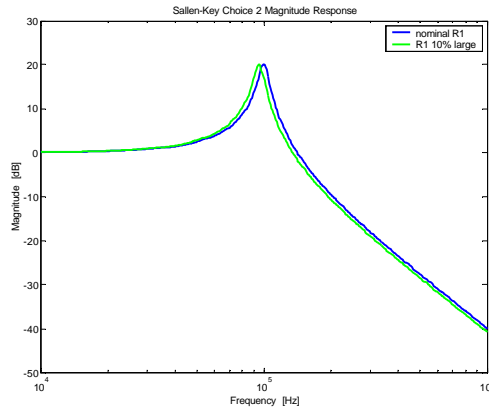

10% increase of R_1 has only small effect on response!

→ The circuit is NOT very sensitive to component variations.

Sensitivity

Definition $\frac{\Delta y}{y} = S_x^y \frac{\Delta x}{x}$

with $S_x^y = \frac{x}{y} \frac{dy}{dx}$

Example $\frac{\Delta Q_p}{Q_p} = S_{R_1}^{Q_p} \frac{\Delta R_1}{R_1}$

Choice 1 $S_{R_1}^{Q_p} = Q_p - 0.5 = 9.5$

$\frac{\Delta Q_p}{Q_p} \approx 9.5 \frac{\Delta R_1}{R_1} = 95\%$

Choice 2 $S_{R_1}^{Q_p} = 0$

- Implementation and component sizing have huge impact on sensitivity
- High-sensitivity circuits are problems in practice
- No theory for finding a low-sensitivity architecture
- Ladder filters are usually low sensitivity
- Use proven circuits & check!

Common sense: Sensitivity is a first order approximation, correct only for infinitesimally small errors

Summary

- Frequency Response
 - Poles and zeros are like tent poles and pegs
 - Frequency response is evaluated on $j\omega$ axis
 - Poles and zeros close to $j\omega$ axis dominate response
- Practical Implementation Constraints
 - Components are not ideal
 - Avoid solutions requiring large element spread
 - Beware of high-sensitivity architectures