

# N247 HW1 Solution

## 1 Question 1

$$Q = \frac{\omega_0}{BW} = \frac{1MHz}{250KHz} = 4$$

## 2 Question 3

The equations simplify to

$$\omega_0 = \frac{\sqrt{2}}{RC} \quad (1)$$

$$Q = \frac{\sqrt{2}}{4 - K} \quad (2)$$

$$G = \frac{K}{4 - K} \quad (3)$$

For C=1pF, we find

$$R = \frac{\sqrt{2}}{\omega_0 C} \approx 220K\Omega \quad (4)$$

$$K = 4 - \frac{\sqrt{2}}{Q} \approx 3.65 \quad (5)$$

$$G = \frac{K}{4 - K} = 10.42 \quad (6)$$

The sensitivity of the Quality Factor to the value of K can be calculated as

$$S_K^Q = \frac{\partial Q}{\partial K} \frac{K}{Q} = K \cdot \frac{\partial \log(Q)}{\partial K} = \frac{K}{4 - K} = G = 10.42 \quad (7)$$

Spectre simulations results: Command used the bandwidth and center frequency are reported in SK.ocn(see website). Comment: the variation in Q is larger than predicted by sensitivity analysis. The reason is nonlinear dependence of Q on K. The last column of the table above reports calculated values of Q with changing K, considering the nonlinear relation. The agreement with simulations is almost perfect.

K	$\omega_0$ [Hz]	BW	Q	G[dB]	Q(calc)
3.65	1M	255K	4	20.67	4
3.65*1.05	1M	117.2K	8.44	27	8.44
3.65*0.95	1M	376K	2.65	16.27	2.5

Tab. 1: Simulation Results

### 3 Question 4

Simulating with 4 50fF stray capacitors I obtained:  $\omega_0 = 912KHz$ ,  $Q = 2.82$ ,  $PG = 17dB$

### 4 Question 5

Since the sensitivity of Q to K for this example is approximately 10 , in order to control Q within 10% we need to control K within 1%. Since for an amplifier with finite gain  $A_v$ ,  $K \approx K_{id}(1 - K_{id}/A_v)$ ,  $K_{id}/A_v \leq .01$  or  $A_v \geq 364$ . Since  $A_v^{Min} = 2/3A_{v0}$ ,  $A_{v0} \geq 560$ .