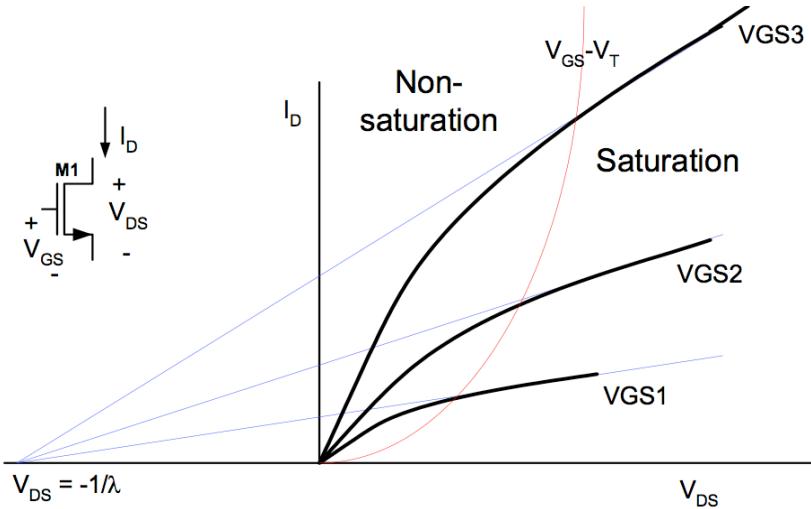


1. MOSFET Equations

a) N-channel MOSFET

Cut Off	$V_{GS} \leq V_T$	$I_{DS} = 0$
Linear	$V_{GS} > V_T, V_{DS} \leq V_{GS} - V_T$	$I_{DS} = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_T)V_{DS} - \frac{V_{DS}^2}{2} \right] (1 + \lambda V_{DS})$
Saturation	$V_{GS} > V_T, V_{DS} > V_{GS} - V_T$	$I_{DS} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$




The simplest model in SPICE (Level 1 or default model) uses the above equations.

Parameter	SPICE Parameter	Units	Typical Values
$\mu_n C_{ox}$	KP	A/V ²	200 μ
V_{T0}	VTO	V	0.5 – 1.0
λ	LAMBDA	V ⁻¹	0.05 – 0.005

b) P-channel MOSFET

Cut Off	$V_{SG} \leq V_T $	$I_{SD} = 0$
Linear	$V_{SG} > V_T , V_{SD} \leq V_{SG} - V_T $	$I_{SD} = \mu_p C_{ox} \frac{W}{L} \left[(V_{SG} - V_T)V_{SD} - \frac{V_{SD}^2}{2} \right] (1 + \lambda V_{SD})$
Saturation	$V_{SG} > V_T , V_{SD} > V_{SG} - V_T $	$I_{SD} = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - V_T)^2 (1 + \lambda V_{SD})$

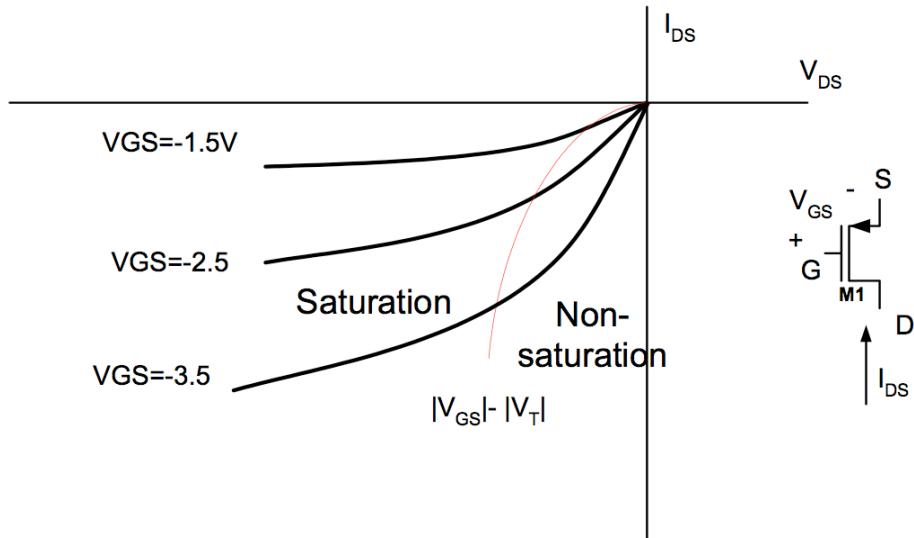

Example)

$$\begin{aligned} V_S &= 4 \text{ V}, V_G = 2 \text{ V}, V_D = 1 \text{ V} \\ V_T &= -0.8 \text{ V}, \lambda = 0, K_p = 100 \mu\text{A/V}^2 \\ W &= 10 \mu\text{m}, L = 2 \mu\text{m} \end{aligned}$$

Find MOSFET type, operation region, I_{DS} .

- Solution

$$|V_{DS}| > |V_{GS}| - |V_T| \Rightarrow \text{saturation}$$

$$I_{SD} = \frac{100\mu}{2} \frac{10\mu}{2\mu} (2 - |-0.8|)^2 (1 + 0) = 360 \mu\text{A}$$

$$I_{DS} = -360 \mu\text{A}$$

2. MOSFET Circuits

Example) The PMOS transistor has $V_T = -2 \text{ V}$, $K_p = 8 \mu\text{A/V}^2$, $L = 10 \mu\text{m}$, $\lambda = 0$.

Find the values required for W and R in order to establish a drain current of 0.1 mA and a voltage V_D of 2 V .


- Solution

$$V_D = V_G \Rightarrow V_{SD} > V_{SG} - |V_T| \Rightarrow \text{saturation}$$

$$|I_{DS}| = \frac{1}{2} K_p \frac{W}{L} (V_{SG} - |V_T|)^2 (1 + \lambda V_{SD}) = \frac{8\mu}{2} \frac{W}{10\mu} (3 - 2)^2 (1 + 0) = 0.1 \text{ mA}$$

$$I_R = \frac{V_D}{R} = \frac{2}{R} = 0.1 \text{ mA}$$
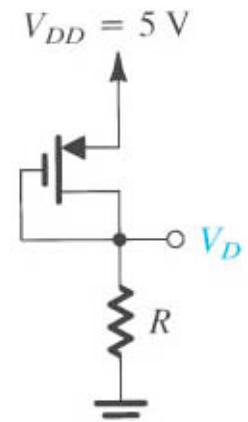
$$W = 250 \mu\text{m}, \quad R = 20 \text{ k}\Omega$$



Example) The PMOS transistor has $V_T = -1$ V, $K_p = 8 \mu\text{A/V}^2$, $W/L = 25$, $\lambda = 0$.

For $I = 100 \mu\text{A}$, find the V_{SD} and V_{SG} for $R = 0, 10\text{k}, 30\text{k}, 100\text{k}$.

- Solution


$\lambda = 0$ (no channel length modulation)

1) $R = 0$

$$V_D = V_G \Rightarrow V_{SD} > V_{SG} - |V_T| \Rightarrow \text{saturation}$$

$$I_{SD} = \frac{1}{2} K_p \frac{W}{L} (V_{SG} - |V_T|)^2 = \frac{8\mu}{2} \cdot 25 \cdot (V_{SG} - 1)^2 = 100\mu$$

$$V_{SG} = 2V \quad V_{SD} = 2V$$

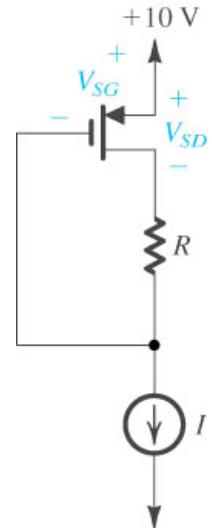

2) $R = 10k$

$$V_D - V_G = IR = 100\mu \cdot 10k = 1 \Rightarrow V_{SD} = V_{SG} - |V_T| \Rightarrow \text{saturation or linear}$$

$$I_{SD} = \frac{1}{2} K_p \frac{W}{L} (V_{SG} - |V_T|)^2 = \frac{8\mu}{2} \cdot 25 \cdot (V_{SG} - 1)^2 = 100\mu$$

$$V_{SG} = 2V \quad V_{SD} = 1V$$

3) $R = 30k$

$$V_D - V_G = IR = 100\mu \cdot 30k = 3 \Rightarrow V_{SD} < V_{SG} - |V_T| \Rightarrow \text{linear}$$

$$I_{SD} = K_p \frac{W}{L} ((V_{SG} - |V_T|) V_{SD} - \frac{V_{SD}^2}{2}) = 8\mu \cdot 25 \cdot ((V_{SD} + 3 - 1) V_{SD} - \frac{V_{SD}^2}{2}) = 100\mu$$

$$V_{SD} \approx 0.24V \quad V_{SG} = 3.24V$$

4) $R = 100k$

$$V_D - V_G = IR = 100\mu \cdot 100k = 10 \Rightarrow V_{SD} < V_{SG} - |V_T| \Rightarrow \text{linear}$$

$$I_{SD} = K_p \frac{W}{L} ((V_{SG} - |V_T|) V_{SD} - \frac{V_{SD}^2}{2}) = 8\mu \cdot 25 \cdot ((V_{SD} + 10 - 1) V_{SD} - \frac{V_{SD}^2}{2}) = 100\mu$$

$$V_{SD} \approx 0.06V \quad V_{SG} = 10.06V$$