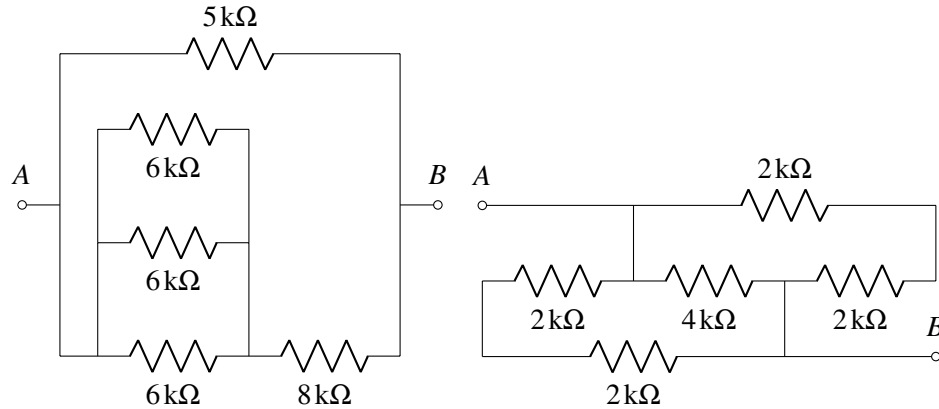



1. Series and Parallel Combinations

For the resistor networks shown below, find an equivalent resistance between the terminals A and B using the resistor combination rules for series and parallel resistors.




2. Voltage and Current Dividers

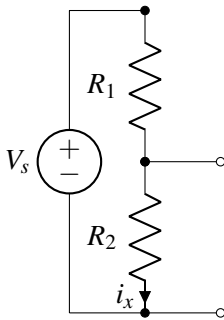(a) For the circuit below, find the voltage V_{out} in terms of the resistances R_1 , R_2 and V_s .




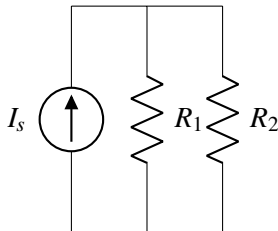(b) For the circuit below, find the current through R_2 .



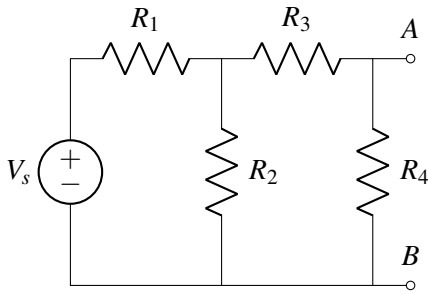3. KVL and KCL

For the circuit shown below, $V_s = 5V$, $R_1 = R_2 = 4k\Omega$ and $R_3 = R_4 = 2k\Omega$.



- For the circuit above write KVL equations for each loop and KVL equations for each node.
- Solve for the voltage between A and B using resistor combination rules and divider rules.