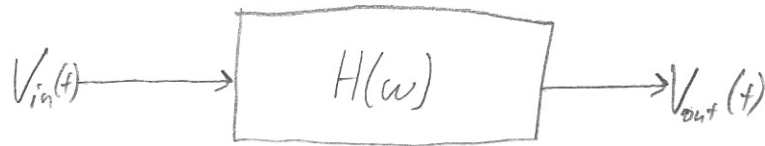


Warmup

1)



$$H(\omega) = \frac{5}{1 - j\omega \cdot 10^{-4}} \quad V_{in}(t) = \cos(10t) + \cos(20000t)$$

Find $V_{out}(t)$.SolutionFind $|H(\omega)|$, $\angle H(\omega)$ at each frequency of interest:

$$|H(10)| \approx 5 \quad \angle H(10) \approx 0$$


$$|H(2 \cdot 10^4)| = \frac{5}{\sqrt{1^2 + 2^2}} = \sqrt{5} \quad \angle H(2 \cdot 10^4) = 0 - \arctan(-5) \approx 1.37$$

$$V_{out}(t) = 5 \cos 10t + \sqrt{5} \cos(20000t + 1.37)$$

2) Write down one question/confusion from Homework 7.


Discuss Questions from Homework, Lecture

Recall: Vector Subtraction

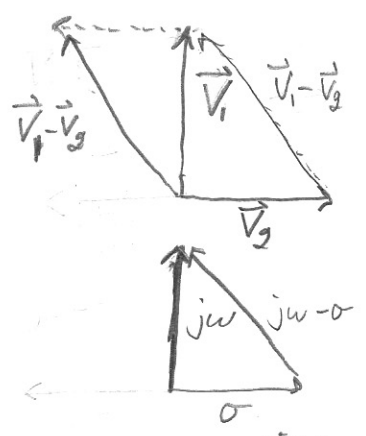


"All-pass" x-o plot

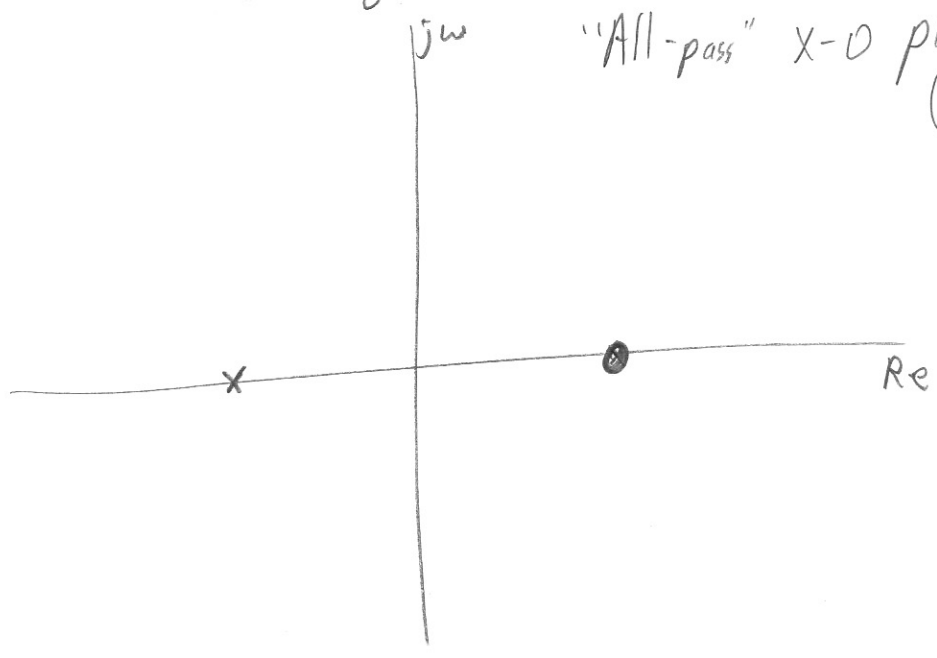("o"; (zeroes) correspond to terms in the numerator;
"x"s (poles) correspond to terms in the denominator)




Worksheet: All-pass filter analysis.

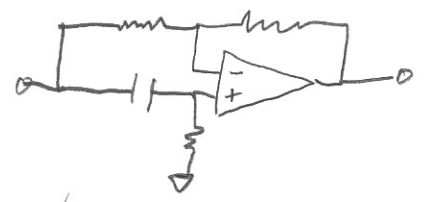
Wrap-up: We can conceptually analyze the circuit another way...



$\omega \rightarrow \infty, Z_c = 0$

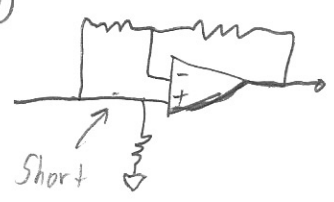

$\omega = 0; Z_c = \infty$

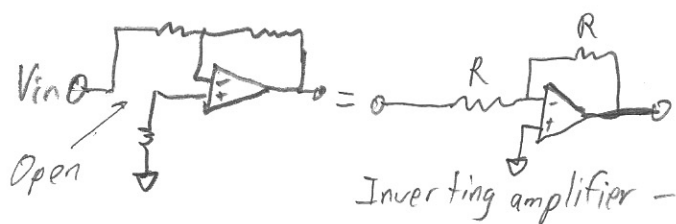

Inverting amplifier - 180° phase shift!



Non-inverting amp; No phase shift!