

RC Circuits / Differential Equations

OUTLINE

- Review: CMOS logic circuits & voltage signal propagation
- Model: RC circuit → differential equation for $V_{\text{out}}(t)$
- Derivation of solution for $V_{\text{out}}(t)$ → propagation delay formula

EE16B, Fall 2015

Meet the Guest Lecturer





Prof. Tsu-Jae King Liu



- Joined UCB EECS faculty in 1996
- Courses taught: 40, 105, 130, 143, 290D, 375
- Research in nanoelectronic & nanomechanical devices

The MOSFET

  Metal-Oxide-Semiconductor
Field-Effect Transistor:




  - Current flowing between the heavily doped SOURCE & DRAIN regions is controlled by the voltage on the GATE electrode
 - N-channel & P-channel MOSFETs operate in a complementary manner
- Handwritten notes: *negatively charged electrons (e⁻)*, *positively charged "holes" (h⁺)*, *ON: V_G > V_S + V_{TH}*, *V_G < V_S - V_{TH}*




The CMOS Inverter

CIRCUIT

 

✓ Low static power consumption, since one transistor is always off in steady state

SWITCH MODELS

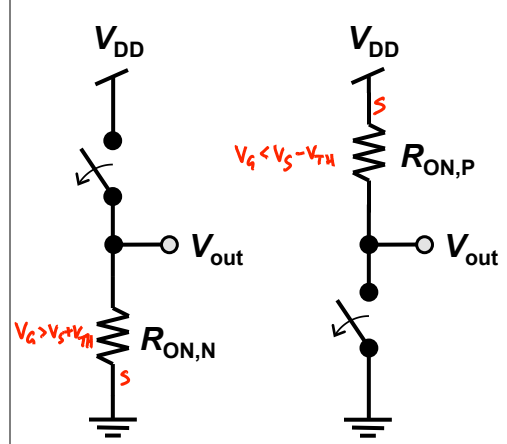


$V_{IN} = V_{DD}$ $V_{IN} = 0V$

Handwritten note: *V₀₀ = V_{TH}*

Pull-Down and Pull-Up Devices

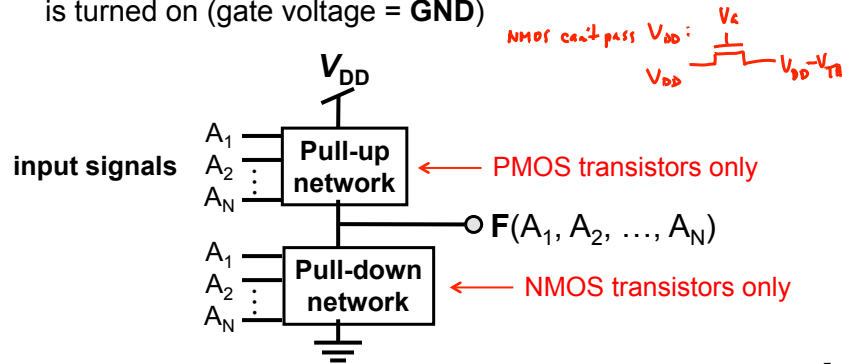- In CMOS logic gates, **NMOS** transistors are used to connect the output to **GND**, whereas **PMOS** transistors are used to connect the output to **V_{DD}**.
 - An NMOS transistor functions as a **pull-down device** when it is turned on (gate voltage = **V_{DD}**)
 - A PMOS transistor functions as a **pull-up device** when it is turned on (gate voltage = **GND**)





5

Voltage Signal Propagation

- When an input voltage of a logic gate is changed, there is a **propagation delay** before the output of the logic gate changes, due to capacitive loading at the output.

CMOS inverter chain

  


Propagation delay is measured between the 50% transition points of the input and output signals.

6

RC Circuit Model for High-Low Transition

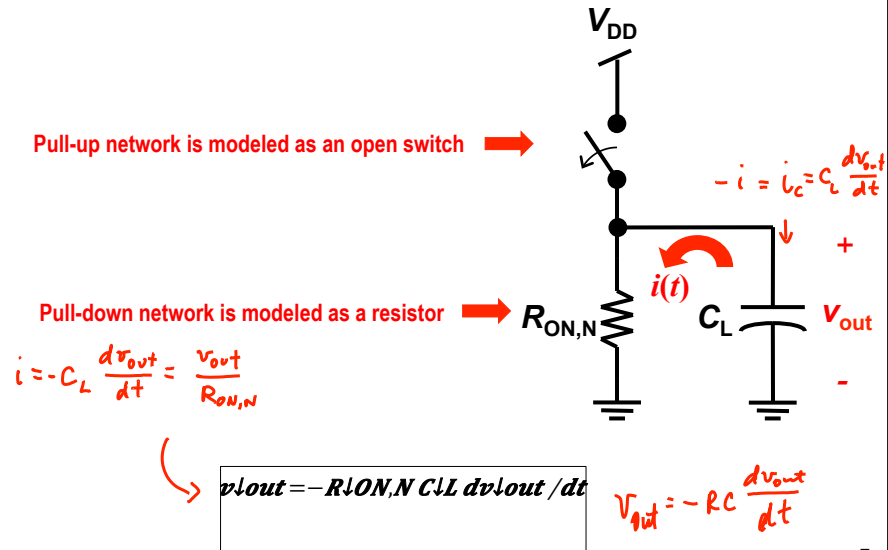Initially $V_{out} = V_{DD}$; then NMOSFET(s) connect(s) V_{out} to GND:




7

Output Load Capacitance of a Logic Gate


- The output load capacitance of a logic gate comprises several components:
 - pn-junction capacitance
for both NMOS and PMOS transistors
 - capacitance of connecting wires
 - input capacitances of the “fan-out” gates

★ $C_{gate,N}, C_{gate,P}$

 

8

Derivation of RC Model

 

9

Derivation of $V_{out}(t)$ for High-Low Transition

Approach #1: By separation of variables $V_{out} = -RC \frac{dV_{out}}{dt}$

$$dt = -RC \left(\frac{1}{v_{out}} \right) dv_{out}$$

$$\int dt = -RC \int \frac{1}{v_{out}} dv_{out}$$

$$t + C_1 = -RC \ln v_{out} \Rightarrow -\frac{t}{RC} + \frac{C_1}{RC} = \ln v_{out}$$

\nearrow
 constant

$$\Rightarrow v_{out} = \exp\left(-\frac{t}{RC} + \frac{C_1}{RC}\right) = e^{-t/RC} e^{C_1/RC} = C e^{-t/RC}$$

Initial Condition: At $t=0$, $V_{out} = V_{DD} = C$

$$v_{out}(t) = V_{DD} e^{-t/RC}$$

10

Derivation of $V_{out}(t)$ for High-Low Transition

Approach #2: With eigenfunctions $V_{out} = -RC \frac{dV_{out}}{dt}$

$$V_{out} = -RC f(V_{out})$$

$$-\frac{1}{RC} V_{out} = f(V_{out}) \rightarrow V_{out} \text{ is an eigenfunction of } f(\cdot)$$

Only an exponential function has a derivative proportionate to itself

$$\rightarrow V_{out} = K e^{t/\tau} \quad \text{where } \tau \text{ is a constant "time constant"}$$

↑
scalar factor



Plug into Diff. Eqn.: $K e^{t/\tau} = -RC \frac{d}{dt}(K e^{t/\tau}) = -RC \left(\frac{K}{\tau}\right) e^{t/\tau}$

$$\Rightarrow \frac{-RC}{\tau} = 1 \Rightarrow \tau = -RC \quad V_{out} = K e^{-t/RC} = V_{DD} e^{-t/RC}$$

↑
initial condition

11

Derivation of Formula for t_{pHL}

$$V_{out}(t) = V_{DD} e^{-t/R_{ON,N}C_L}$$


At $t = t_{pHL}$:

$$V_{out} = \frac{V_{DD}}{2} = V_{DD} e^{-t_{pHL}/RC}$$

$$\frac{1}{2} = e^{-t_{pHL}/RC} \Rightarrow 2 = e^{t_{pHL}/RC}$$

$$\ln(2) = t_{pHL}/RC$$
 
$$\Rightarrow t_{pHL} = RC \ln(2) = \underline{\underline{0.69 RC}}$$



12

RC Circuit Model for Low-High Transition


Initially $V_{out} = 0$; then PMOSFET(s) connect(s) V_{out} to V_{DD} :

Pull-up network is modeled as a resistor $\rightarrow R_{ON,P}$

$$i = \frac{V_{DD} - V_{out}}{R_{ON,P}}$$

Pull-down network is modeled as an open switch \rightarrow

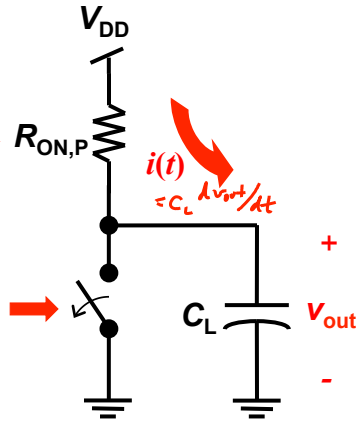
$$i = \frac{V_{DD} - V_{out}}{R_{ON,P}} = C_L \frac{dV_{out}}{dt}$$




$$V_{DD} - v_{out} = R_{ON,P} C_L \frac{dv_{out}}{dt}$$

13

Derivation of RC Model

 

Redraw:

 

Define $v'_{out} = v_{out} - V_{DD}$


v'_{out}

Solution to Diff Eqn is the same as before since $\frac{dv'_{out}}{dt} = \frac{d(v_{out} - V_{DD})}{dt} = \frac{dv_{out}}{dt}$

14

Derivation of $V_{out}(t)$ for Low-High Transition

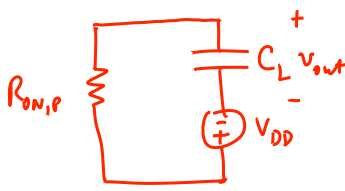Initially, $V_{out} = 0$ and $V_{out}' = 0 - V_{DD} = -V_{DD}$



$V_{out}' = V_{out} - V_{DD}$


$$V_{out}' = V_{out}'(t=0) e^{-t/R_{ON,P}C_L}$$

$$V_{out} - V_{DD} = -V_{DD} e^{-t/R_{ON,P}C_L}$$

$$V_{out} = V_{DD} \left[1 - e^{-t/R_{ON,P}C_L} \right]$$

15

Derivation of Formula for t_{pLH}
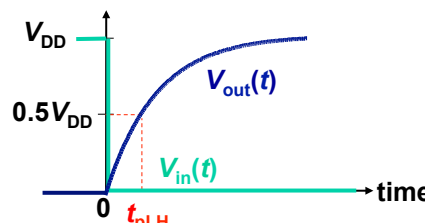
$$V_{out}(t) = V_{DD} \left(1 - e^{-t/R_{ON,P}C_L} \right)$$


At $t = t_{pLH}$:

$$V_{out} = \frac{V_{DD}}{2} = V_{DD} \left(1 - e^{-t_{pLH}/RC} \right)$$


$$e^{-t_{pLH}/RC} = \frac{1}{2} \Rightarrow e^{t_{pLH}/RC} = 2$$

$$t_{pLH}/RC = \ln(2)$$

$$t_{pLH} = \ln(2)RC = 0.69RC$$

16

Minimizing Propagation Delay

 

A fast CMOS logic circuit is built by

- 1. Keeping the output capacitance C_L small**
 - Minimize the area of drain pn junctions.
 - Lay out devices to minimize interconnect capacitance.
 - Avoid large fan-out.
- 2. Decreasing the equivalent resistance of the transistors**
 - Decrease gate length L_G
 - Increase transistor width W
 - ... but this increases pn junction area and hence C_L
- 3. Increasing V_{DD}**
 - trade-off with power consumption...

17

Classroom Analogy

