
RC Circuits

Michel M. Maharbiz

Vivek Subramanian

Response Terminology

Source dependence

Natural response – response in absence of sources

Forced response – response due to external source

Complete response = Natural + Forced

Time dependence



Transient response – time-varying response (temporary)

Steady state response – time-independent or periodic
(permanent)


Complete response = Transient + Steady State

Transient Response

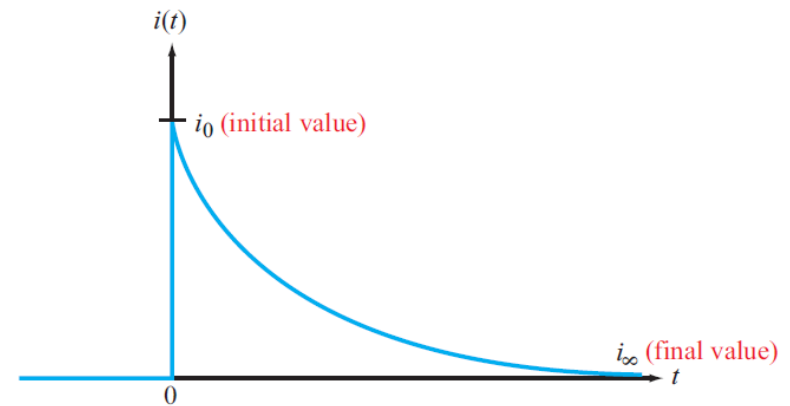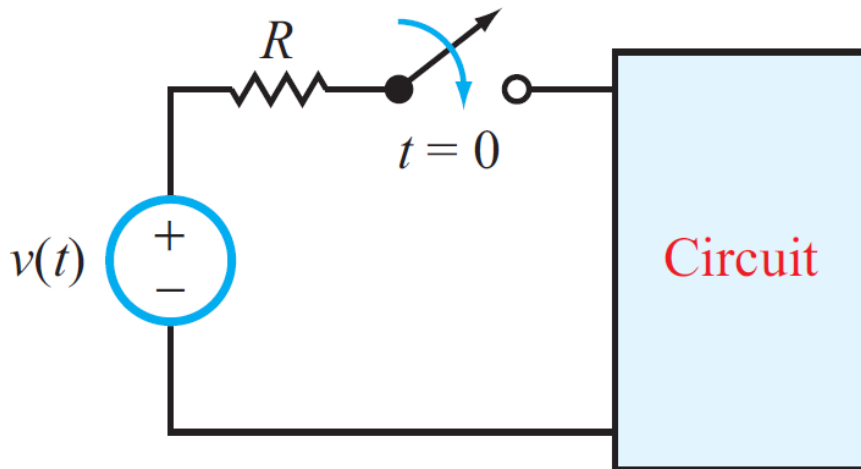The transient response represents the initial reaction immediately after a sudden change, such as closing or opening a switch to connect a source to the circuit.




(a) dc transient response

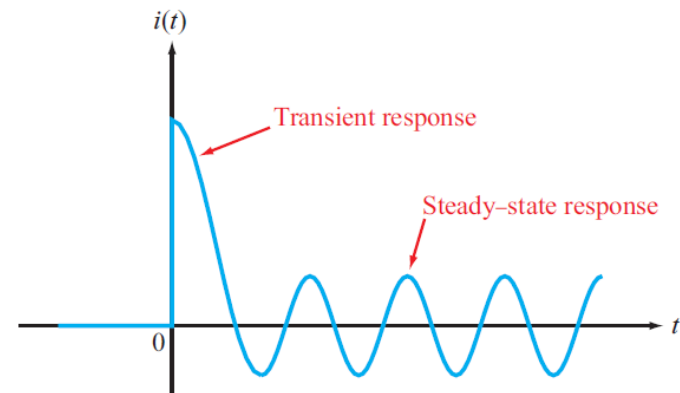

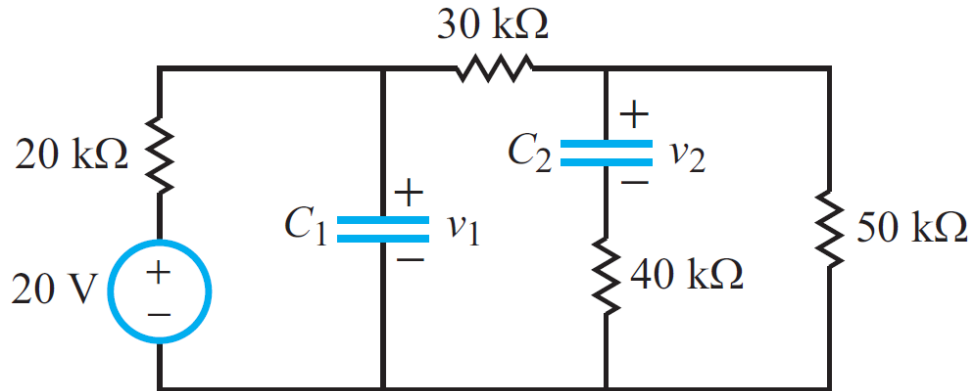
(b) Combined response to ac excitation

RC Circuits at DC

- At dc no currents flow through capacitors: **open circuits**


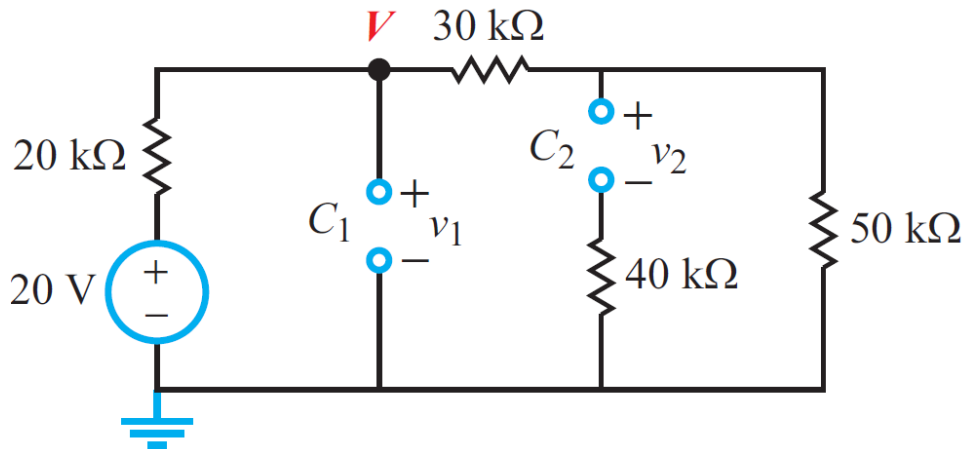
$$\frac{V - 20}{20 \times 10^3} + \frac{V}{(30 + 50) \times 10^3} = 0,$$




which gives $V = 16$ V. Hence,

$$v_1 = V = 16 \text{ V.}$$


Through voltage division, v_2 across the 50-kΩ resistor is given by

$$v_2 = \frac{V \times 50\text{k}}{(30 + 50)\text{k}} = \frac{16 \times 50}{80} = 10 \text{ V.}$$


Natural Response of Charged Capacitor

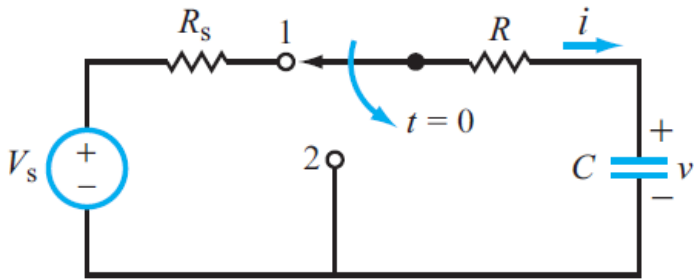

(a) RC circuit

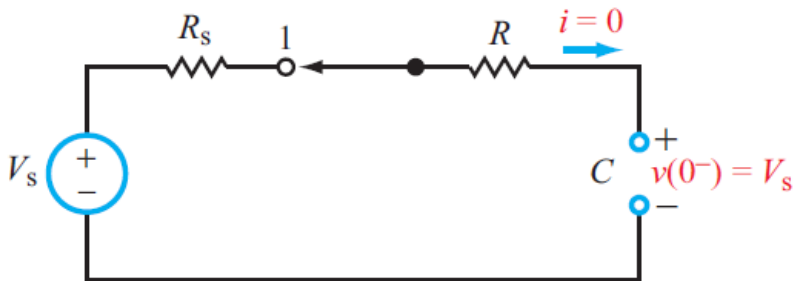

(b) At $t = 0^-$

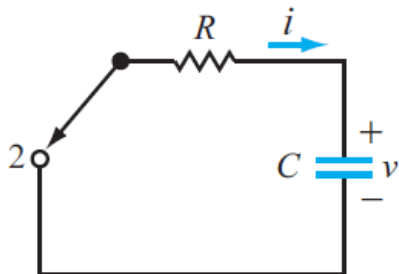

(c) At $t \geq 0$

(a) $t = 0^-$ is the instant just before the switch is moved from terminal 1 to terminal 2

(b) $t = 0$ is the instant just after it was moved; $t = 0$ is synonymous with $t = 0^+$

since the voltage across the capacitor cannot change instantaneously, it follows that

$$v(0) = v(0^-) = V_s.$$

$$Ri + v = 0 \quad (\text{for } t \geq 0),$$

where i is the current through and v is the voltage across the capacitor. Since $i = C \, dv/dt$,

$$RC \frac{dv}{dt} + v = 0.$$

Upon dividing both terms by RC , Eq. (5.69) takes the form

$$\frac{dv}{dt} + av = 0 \quad (\text{source-free}),$$

where

$$a = \frac{1}{RC}.$$

Solution to the differential equation

The standard procedure for solving Eq. (5.70) starts by multiplying both sides by e^{at} ,

$$\frac{dv}{dt} e^{at} + ave^{at} = 0. \quad (5.72)$$

Next, we recognize that the sum of the two terms on the left-hand side is equal to the expansion of the differential of (ve^{at}) ,

$$\frac{d}{dt}(ve^{at}) = \frac{dv}{dt} e^{at} + ave^{at}. \quad (5.73)$$

Hence, Eq. (5.72) becomes

$$\frac{d}{dt}(ve^{at}) = 0. \quad (5.74)$$

Integrating both sides, we have

$$\int_0^t \frac{d}{dt}(ve^{at}) dt = 0, \quad (5.75)$$

Solution to the differential equation

. Performing the integration gives

$$ve^{at} \Big|_0^t = 0$$

or

$$v(t) e^{at} - v(0) = 0. \quad (5.76)$$

Solving for $v(t)$, we have

$$\begin{aligned} v(t) &= v(0) e^{-at}, \\ &= v(0) e^{-t/RC} \quad (\text{for } t \geq 0), \end{aligned} \quad (5.77)$$


$$v(t) = v(0) e^{-t/\tau} \quad (\text{natural response}),$$

with

$$\tau = RC \quad (\text{s}),$$


τ is called the **time constant** of the circuit.

Natural Response of Charged Capacitor

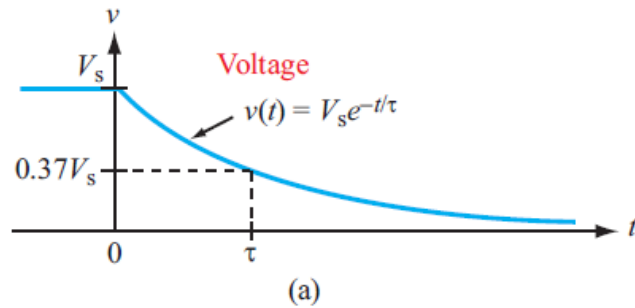

$$i(t) = C \frac{dv}{dt} = C \frac{d}{dt}(V_s e^{-t/\tau})$$

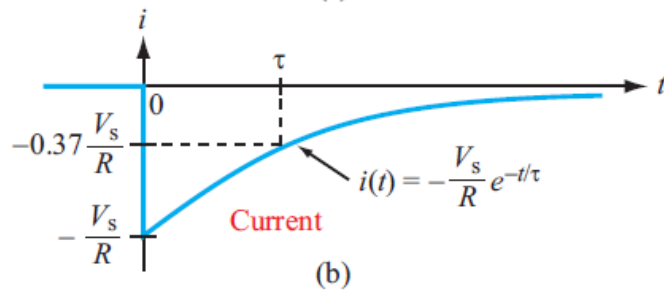
$$= -C \frac{V_s}{\tau} e^{-t/\tau} \quad (\text{for } t \geq 0),$$




which simplifies to

$$i(t) = -\frac{V_s}{R} e^{-t/\tau} u(t) \quad (\text{for } t \geq 0)$$

(natural response).

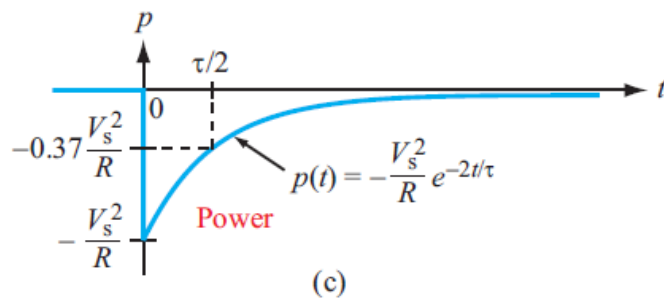

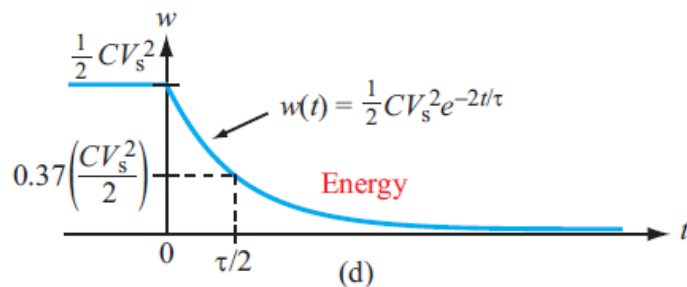
$$p(t) = i v = -\frac{V_s}{R} e^{-t/\tau} \times V_s e^{-t/\tau}$$




$$= -\frac{V_s^2}{R} e^{-2t/\tau} \quad (\text{for } t \geq 0).$$


General Response of RC Circuit

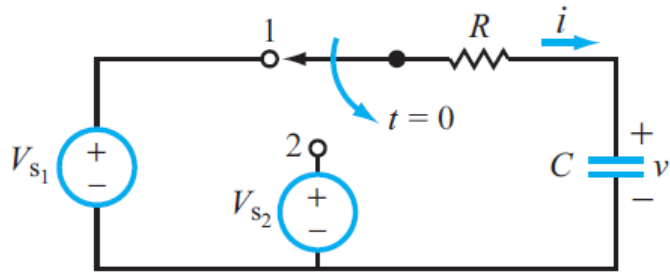

(a) RC circuit

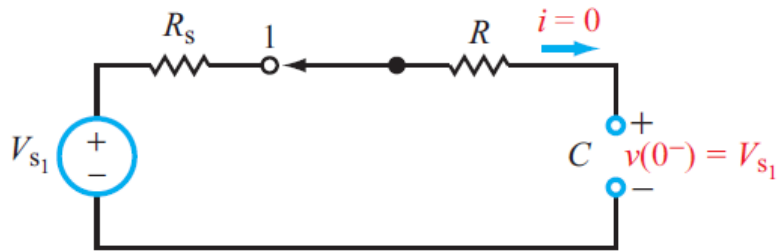

(b) At $t = 0^-$

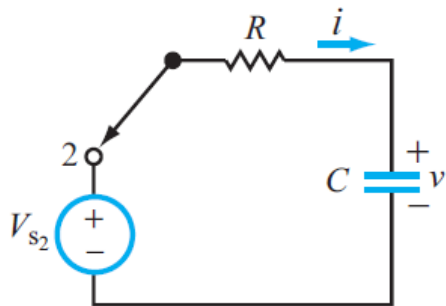

(c) At $t \geq 0$

$$v(0) = v(0^-) = V_{s1}. \quad (5.86)$$

For $t \geq 0$, the voltage equation for the loop in Fig. 5-30(c) is

$$-V_{s2} + iR + v = 0. \quad (5.87)$$

Upon using $i = C \, dv/dt$ and rearranging its terms, Eq. (5.87) can be written in the differential-equation form

$$\frac{dv}{dt} + av = b, \quad (5.88)$$

where

$$a = \frac{1}{RC} \quad \text{and} \quad b = \frac{V_{s2}}{RC}. \quad (5.89)$$

Solution of

$$\frac{dv}{dt} + av = b,$$

$$\frac{d}{dt}(ve^{at}) = be^{at}.$$

Integrating both sides,

$$\int_0^t \frac{d}{dt}(ve^{at}) dt = \int_0^t be^{at}$$

gives

$$ve^{at} \Big|_0^t = \frac{b}{a} e^{at} \Big|_0^t.$$

Upon evaluating the functions at the two limits, we have

$$v(t) e^{at} - v(0) = \frac{b}{a} e^{at} - \frac{b}{a},$$

and then solving for $v(t)$, we have

$$v(t) = v(0) e^{-at} + \frac{b}{a} (1 - e^{-at}).$$

As $t \rightarrow \infty$, $v(t)$ reduces to

$$v(\infty) = \frac{b}{a} = V_{s2}.$$

Solution of

$$\frac{dv}{dt} + av = b,$$

We have:

$$v(t) = v(0) e^{-at} + \frac{b}{a} (1 - e^{-at}). \quad v(\infty) = \frac{b}{a} = V_{s2}.$$

By reintroducing the time constant $\tau = RC = 1/a$ and replacing b/a with $v(\infty)$, we can rewrite Eq. (5.94) in the general form:

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau} \quad (\text{for } t \geq 0)$$

(switch action at $t = 0$).

If the switch action causing the change in voltage across the capacitor occurs at time T_0 instead of at $t = 0$, Eq. (5.96) assumes the form

$$v(t) = v(\infty) + [v(T_0) - v(\infty)]e^{-(t-T_0)/\tau} \quad (\text{for } t \geq T_0)$$

(switch action at $t = T_0$),