


---

# ***RC Circuit Examples***


Michel M. Maharbiz

Vivek Subramanian


# Example: Determine Capacitor Voltage

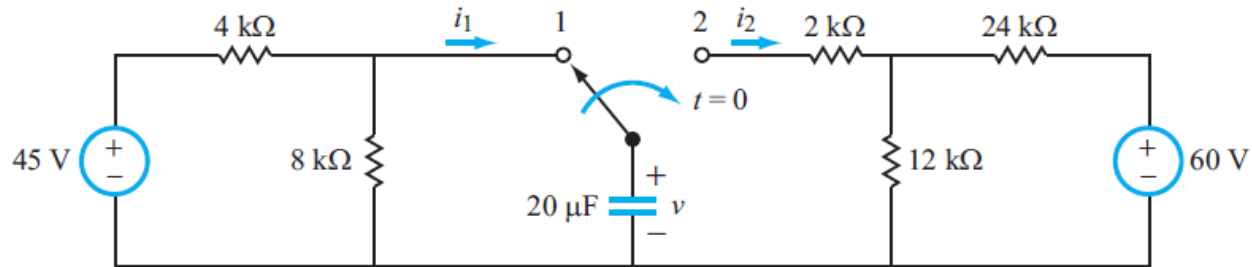

(a) Original circuit

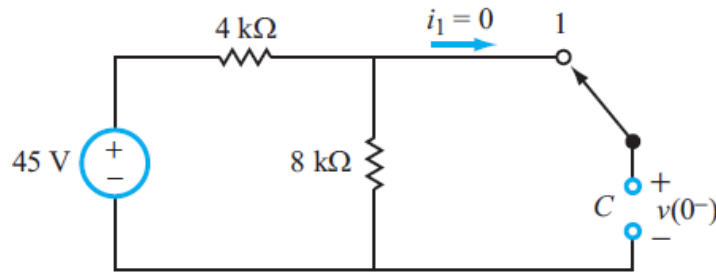


Circuit

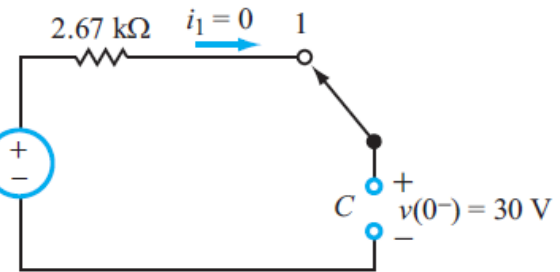


Thévenin equivalent

(b) At  $t = 0^-$

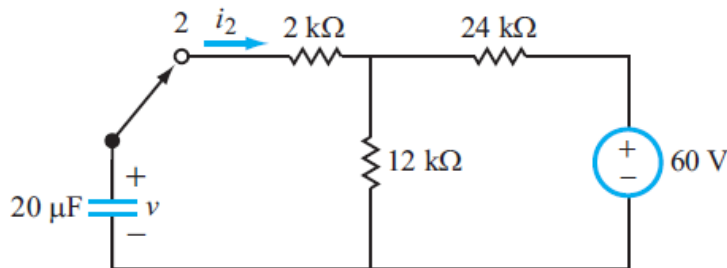


Circuit

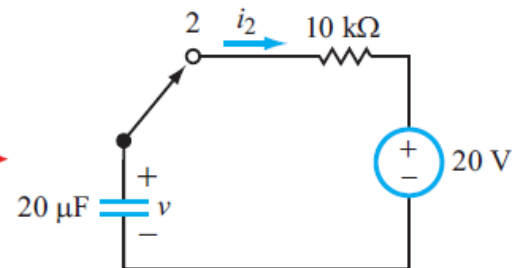

Thévenin equivalent

(c) At  $t \geq 0$

# Solution

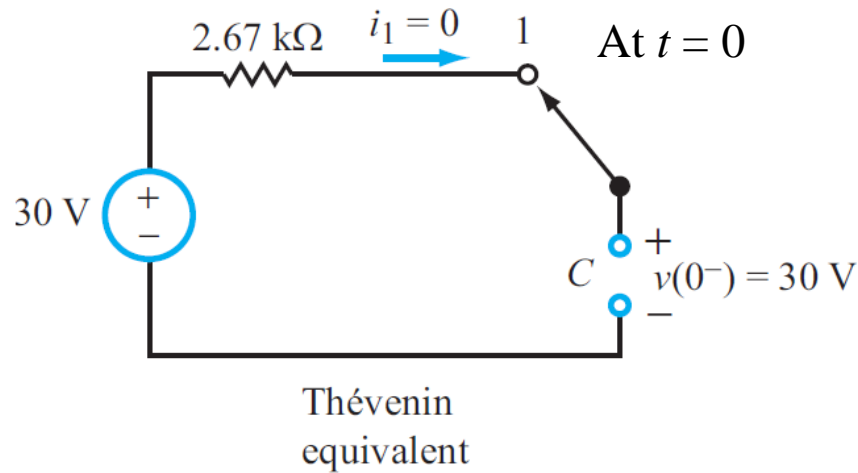

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau}$$

$$v(0) = v(0^-) = 30 \text{ V}$$

$$v(\infty) = \left( \frac{12\text{k}}{12\text{k} + 24\text{k}} \right) \times 60 = 20 \text{ V}$$

$$R = R_{\text{Th}} = 2 \text{ k}\Omega + 12 \text{ k}\Omega \parallel 24 \text{ k}\Omega$$


$$= 2 \text{ k}\Omega + \frac{12\text{k} \times 24\text{k}}{12\text{k} + 24\text{k}} = 10 \text{ k}\Omega.$$

Hence,


$$\tau = RC = 10 \times 10^3 \times 20 \times 10^{-6} = 0.2 \text{ s}.$$

Substituting the values we obtained for  $v(0)$ ,  $v(\infty)$ , and  $\tau$  in Eq. (5.99) leads to

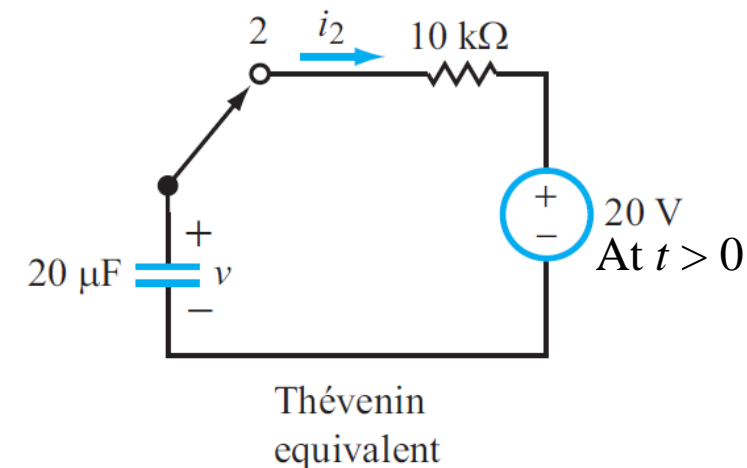
$$v(t) = (20 + 10e^{-5t}) \text{ V} \quad (\text{for } t \geq 0).$$




# Example: Charge/Discharge Action

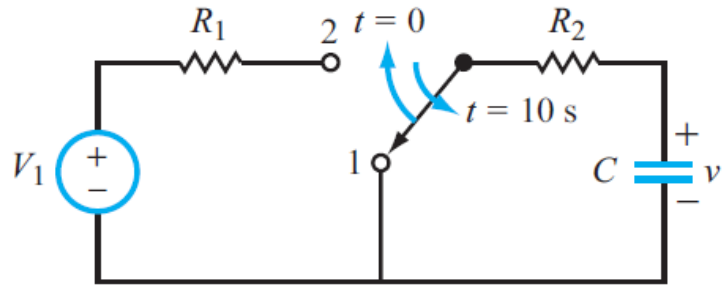

(a) Actual circuit

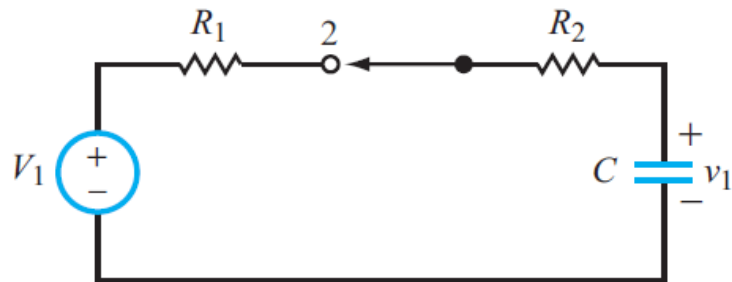

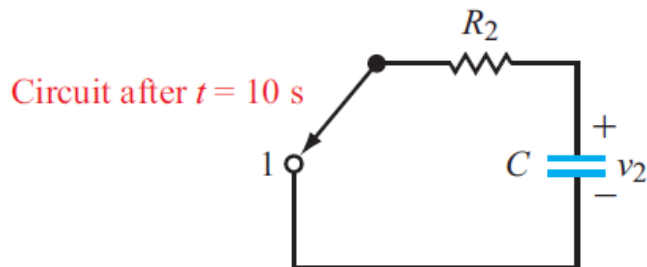(b) Circuit during  $0 \leq t \leq 10$  s



(c)

Given that the switch in Fig. 5-32 was moved to position 2 at  $t = 0$  (after it had been in position 1 for a long time) and then returned to position 1 at  $t = 10$  s, determine the voltage response  $v(t)$  for  $t \geq 0$  and evaluate it for  $V_1 = 20$  V,  $R_1 = 80$  k $\Omega$ ,  $R_2 = 20$  k $\Omega$ , and  $C = 0.25$  mF.


**Time Segment 1:**  $0 \leq t \leq 10$  s

When the switch is in position 2 (Fig. 5-32(b)), the resistance of the circuit is  $R = R_1 + R_2$ . Hence, the time constant during this first time segment is


$$\begin{aligned}\tau_1 &= (R_1 + R_2)C \\ &= (80 + 20) \times 10^3 \times 0.25 \times 10^{-3} = 25 \text{ s.}\end{aligned}$$

$$\begin{aligned}v_1(t) &= v_1(\infty) + [v_1(0) - v_1(\infty)]e^{-t/\tau_1} \\ &= 20(1 - e^{-0.04t}) \text{ V} \quad (\text{for } 0 \leq t \leq 10 \text{ s}).\end{aligned}$$


# Example (cont.)

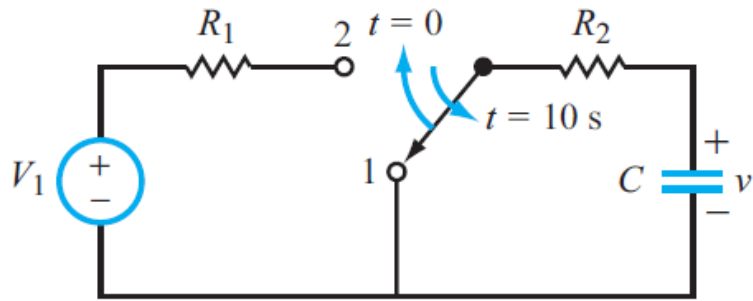

(a) Actual circuit

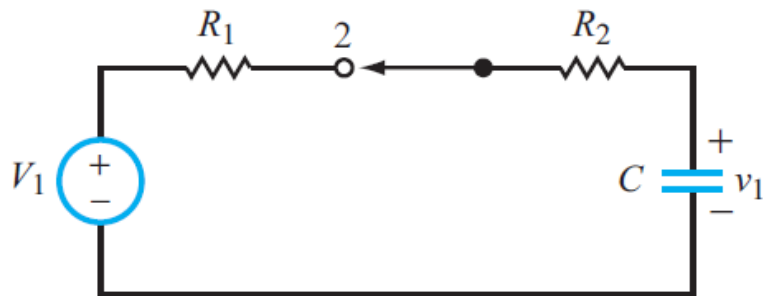

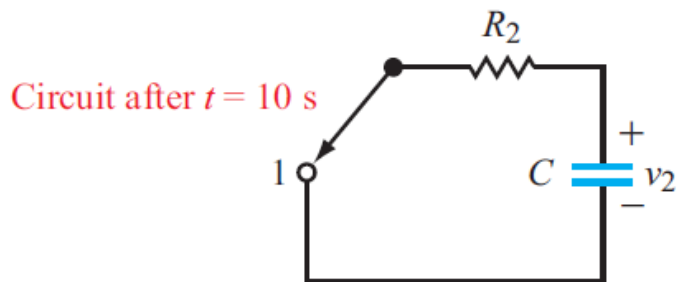(b) Circuit during  $0 \leq t \leq 10$  s



(c)

**Time Segment 2:**  $t \geq 10$  s

Voltage  $v_2(t)$ , corresponding to the second time segment (Fig. 5-32(c)), is given by Eq. (5.98) with a new time constant  $\tau_2$  as

$$v_2(t) = v_2(\infty) + [v_2(10) - v_2(\infty)]e^{-(t-10)/\tau_2}.$$

The new time constant is associated with the capacitor circuit remaining after returning the switch to position 1,

$$\begin{aligned} \tau_2 &= R_2 C \\ &= 20 \times 10^3 \times 0.25 \times 10^{-3} = 5 \text{ s}. \end{aligned}$$




The initial voltage  $v_2(10)$  is equal to the capacitor voltage  $v_1$  at the end of time segment 1, namely

$$\begin{aligned} v_2(10) &= v_1(10) = 20(1 - e^{-0.04 \times 10}) \\ &= 6.59 \text{ V}. \end{aligned}$$

With no voltage source present in the  $R_2C$  circuit, the charged capacitor will dissipate its energy into  $R_2$ , exhibiting a *natural response* with a final voltage of  $v_2(\infty) = 0$ . Consequently,

$$\begin{aligned} v_2(t) &= v_2(10) e^{-(t-10)/\tau_2} \\ &= 6.59e^{-0.2(t-10)} \text{ V} \quad (\text{for } t \geq 10 \text{ s}). \end{aligned}$$

# Example: Rectangular Pulse

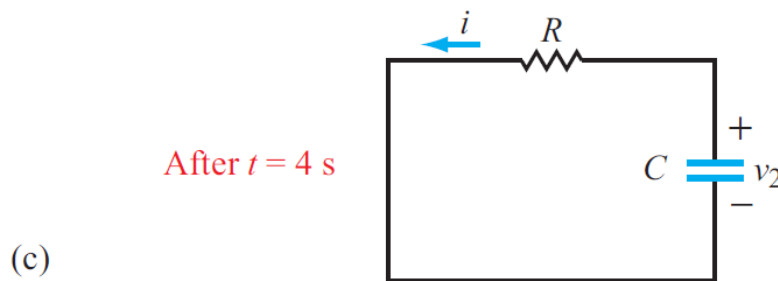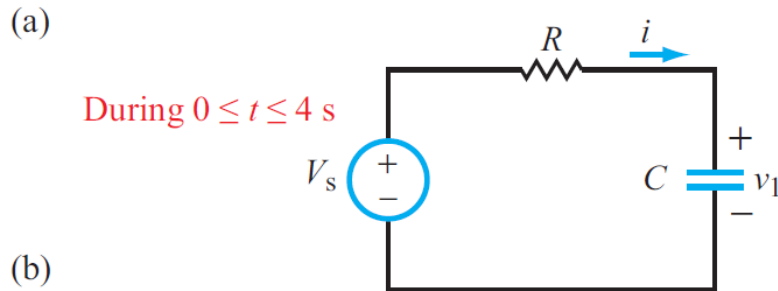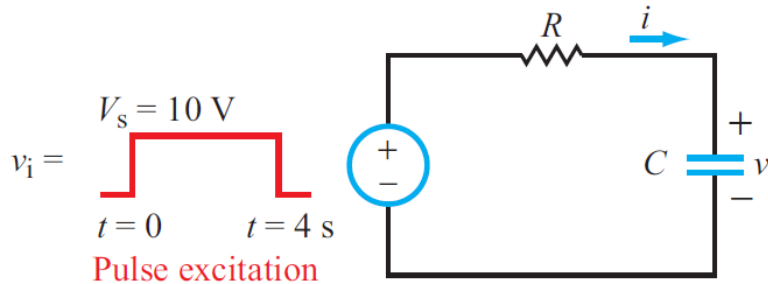

$$v_i(t) = V_s u(t) - V_s u(t - 4).$$

Since the circuit is linear, we can apply the superposition theorem to determine the capacitor response  $v(t)$ . Thus,

$$v(t) = v_1(t) + v_2(t),$$

$$v_1(t) = v_1(\infty) + [v_1(0) - v_1(\infty)]e^{-t/\tau}$$

$$= V_s(1 - e^{-t/\tau}) \quad (\text{for } t \geq 0).$$

For  $V_s = 10 \text{ V}$  and  $\tau = RC = 25 \times 10^3 \times 0.2 \times 10^{-3} = 5 \text{ s}$ ,

$$v_1(t) = 10(1 - e^{-0.2t}) \text{ V} \quad (\text{for } t \geq 0).$$


The second step function has an amplitude of  $-V_s$  and is delayed in time by 4 s. Upon reversing the polarity of  $V_s$  and replacing  $t$  with  $(t - 4)$ , we have

$$v_2(t) = -10[1 - e^{-0.2(t-4)}] \text{ V} \quad (\text{for } t \geq 4 \text{ s}).$$


The total response for  $t \geq 0$  therefore is given by

$$v(t) = v_1(t) + v_2(t)$$
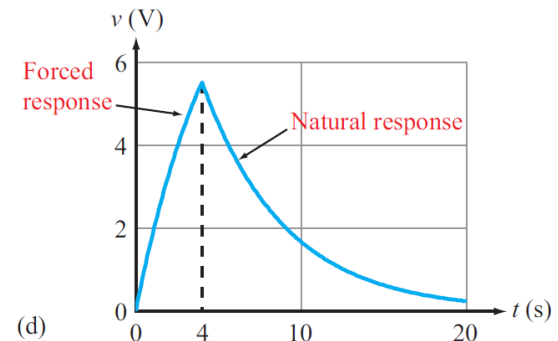
$$= 10[1 - e^{-0.2t}] - 10[1 - e^{-0.2(t-4)}] u(t - 4) \text{ V}$$



# RC Op-Amp Circuits: *Ideal Integrator*

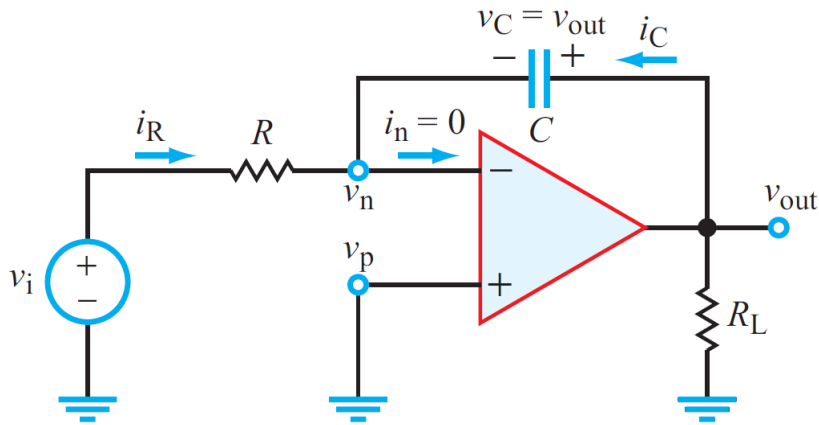

The output voltage  $v_{out}$  of such an integrator circuit is directly proportional to the time integral of the input signal  $v_i$ .

$$i_R = \frac{v_i}{R}. \quad (5.123)$$

Given that  $v_n = 0$ , the voltage  $v_C$  across  $C$  is simply  $v_{out}$ , and the current flowing through it is

$$i_C = C \frac{dv_{out}}{dt}. \quad (5.124)$$

At node  $v_n$ ,

$$i_R + i_C - i_n = 0. \quad (5.125)$$

In view of the second op-amp constraint, namely  $i_n = i_p = 0$ , it follows that

$$i_C = -i_R \quad (5.126)$$

or

$$\frac{dv_{out}}{dt} = -\frac{1}{RC} v_i. \quad (5.127)$$


Upon integrating both sides of Eq. (5.127) from a reference time  $t_0$  to time  $t$ , we have

$$\int_{t_0}^t \left( \frac{dv_{out}}{dt} \right) dt = -\frac{1}{RC} \int_{t_0}^t v_i dt, \quad (5.128)$$

which leads to

$$v_{out}(t) = -\frac{1}{RC} \int_{t_0}^t v_i dt + v_{out}(t_0). \quad (5.129)$$
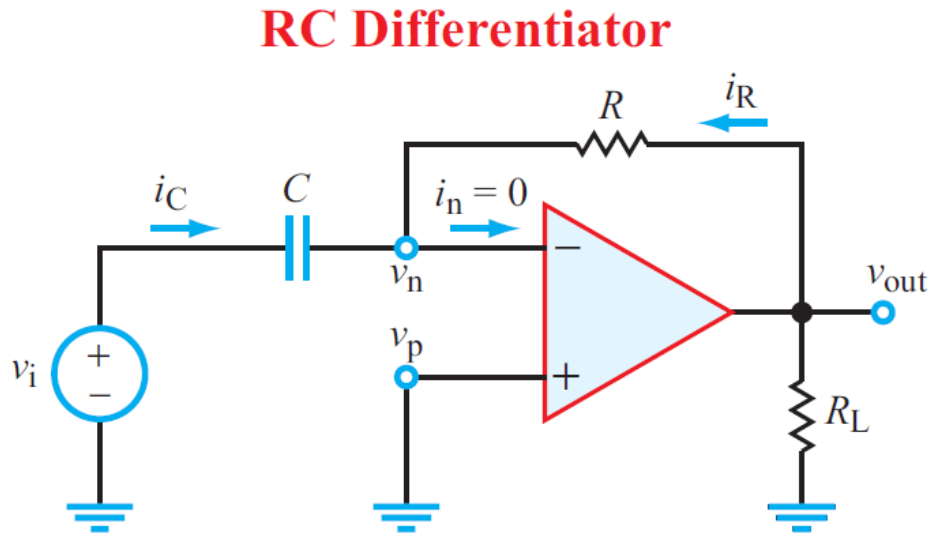
# RC Op-Amp Circuits: *Ideal Differentiator*



$$i_C = C \frac{dv_i}{dt},$$

$$i_R = \frac{v_{out}}{R},$$

$$i_C = -i_R.$$

$$v_{out} = -RC \frac{dv_i}{dt},$$