
More AC Analysis

Michel M. Maharbiz

Vivek Subramanian

Impedance and Admittance

Impedance is
voltage/current

$$\mathbf{Z} = R + jX$$

R = resistance = $\text{Re}(\mathbf{Z})$

X = reactance = $\text{Im}(\mathbf{Z})$

Admittance is
current/voltage


$$\mathbf{Y} = \frac{1}{\mathbf{Z}} = G + jB$$

G = conductance = $\text{Re}(\mathbf{Y})$


B = susceptance = $\text{Im}(\mathbf{Y})$

Resistor	$\mathbf{Z} = R$	$\mathbf{Y} = 1/R$
Inductor	$\mathbf{Z} = j\omega L$	$\mathbf{Y} = 1/j\omega L$
Capacitor	$\mathbf{Z} = 1/j\omega C$	$\mathbf{Y} = j\omega C$



Impedance Transformation

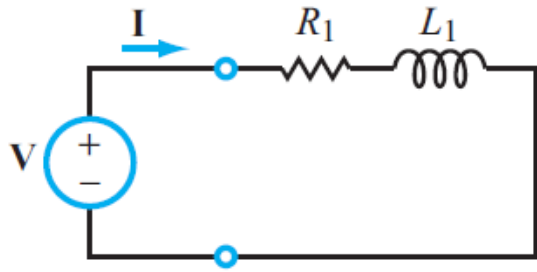

(a) RL

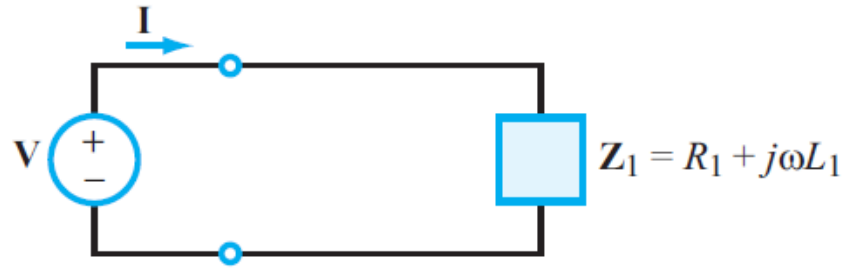


Voltage & Current Division

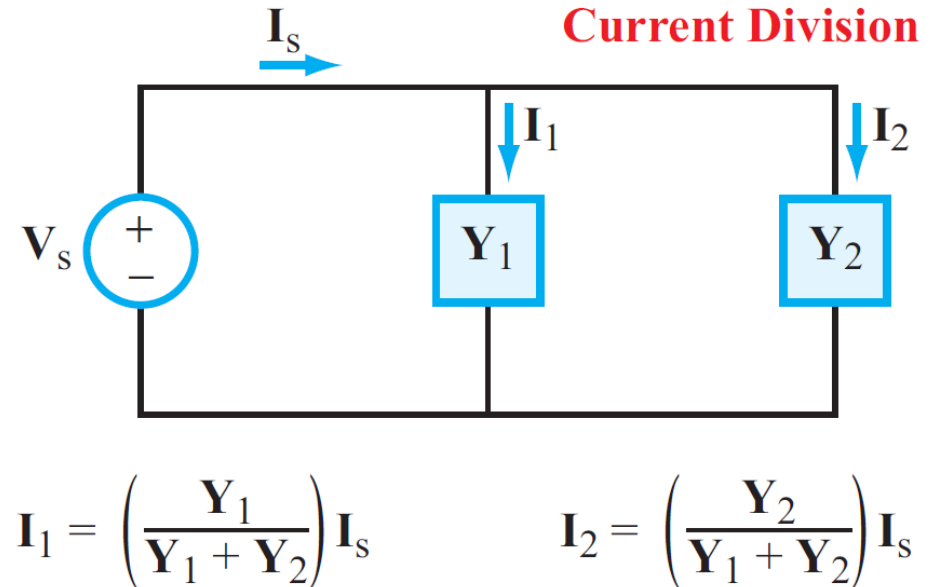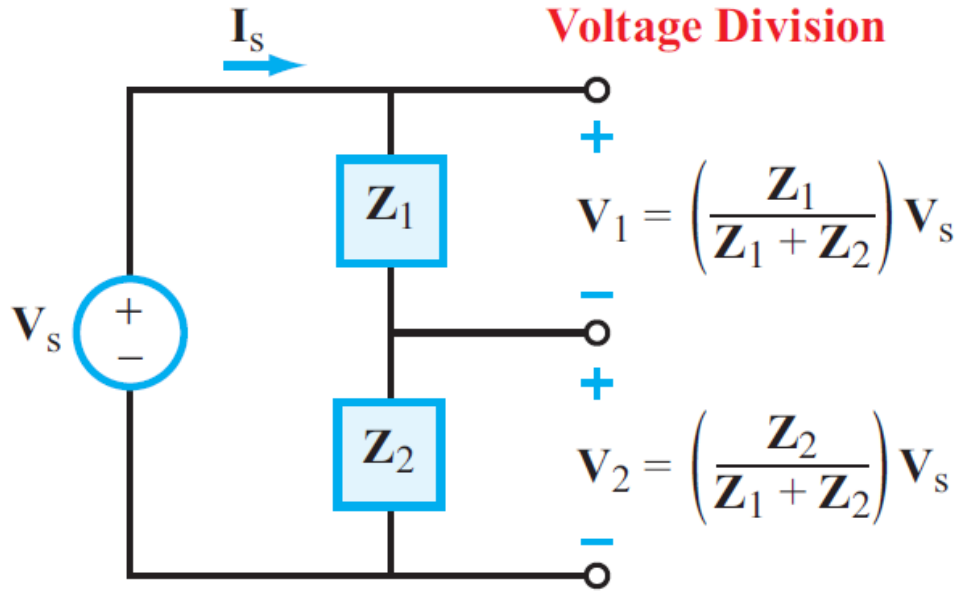

Linear circuit techniques



- We can now apply all the techniques we learned before (for dc circuits in the time domain) to ac circuits in the phase domain:
 - Superposition
 - Thevenin / Norton Equivalents

Example: Thévenin Circuit

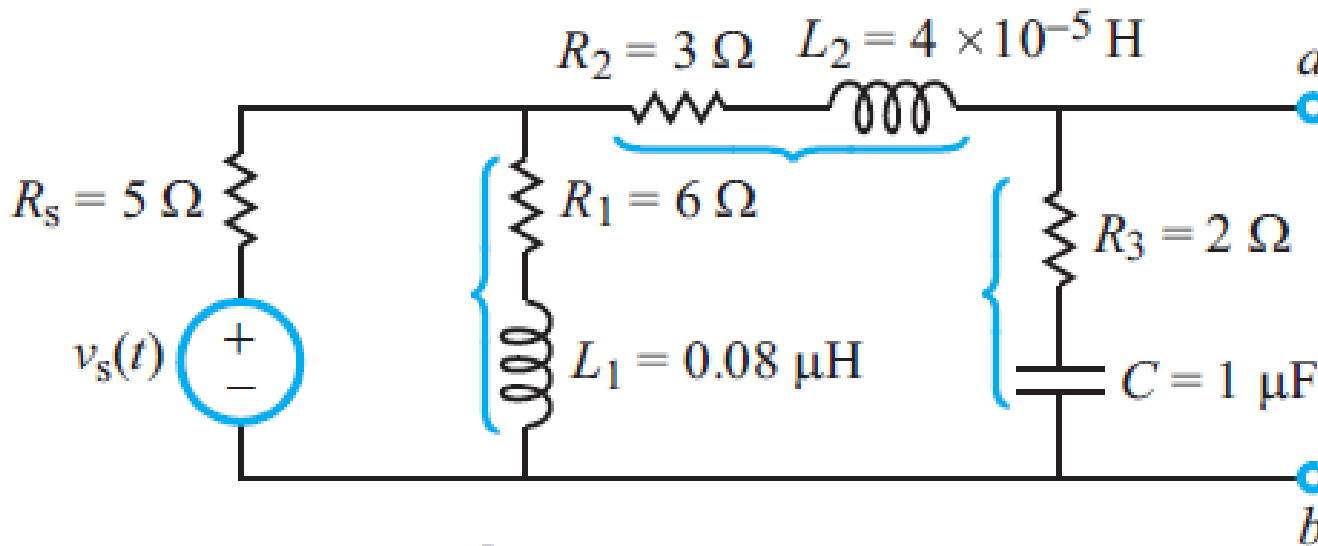


(a) $v_s(t) = 10 \cos 10^5 t \text{ (V)}$

Example: Thévenin Circuit

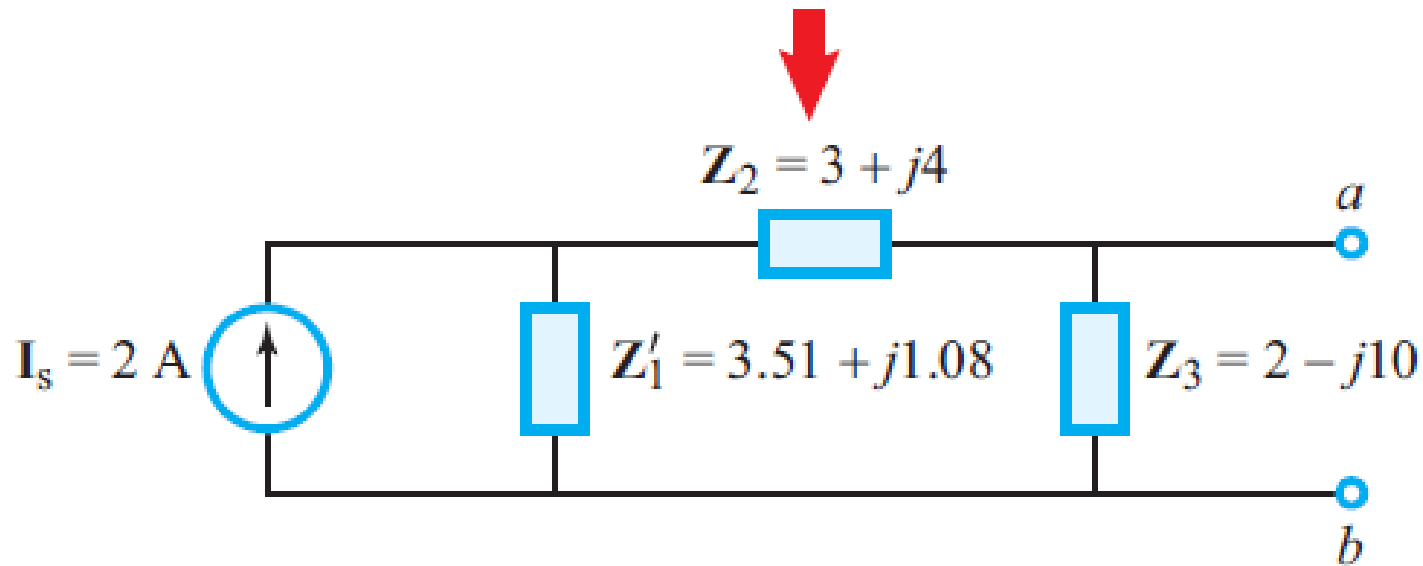
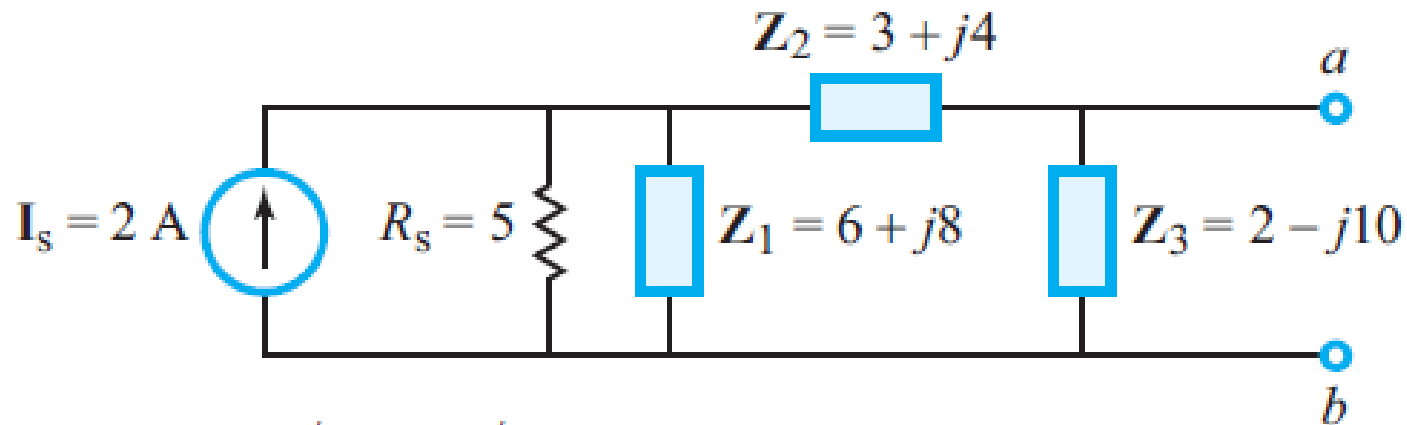


(c) $Z'_1 = R_s \parallel Z_1$

Example: Thévenin Circuit

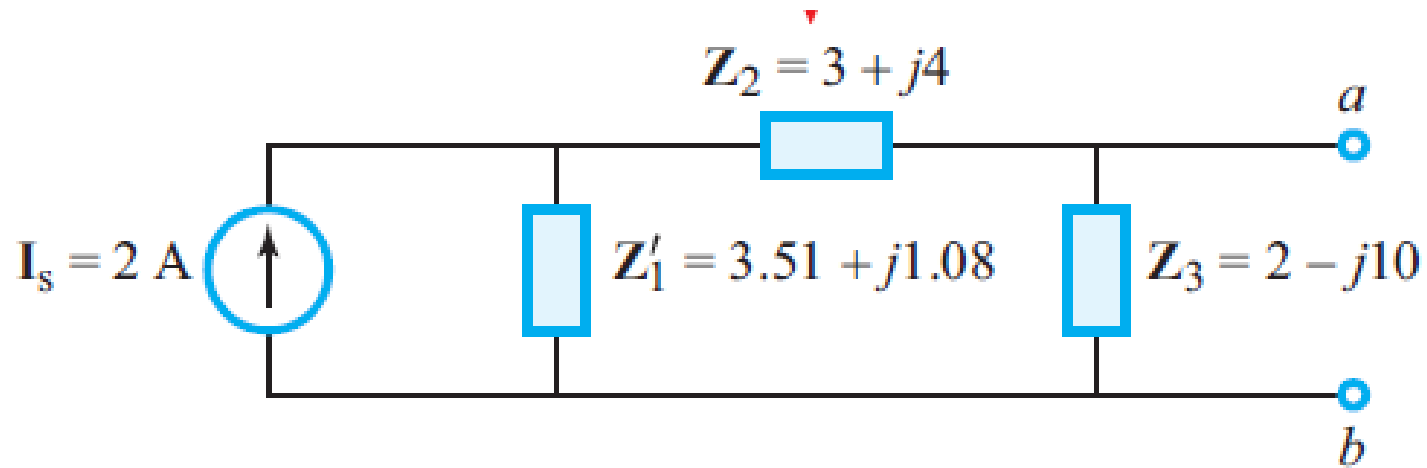


Example: Thévenin Circuit

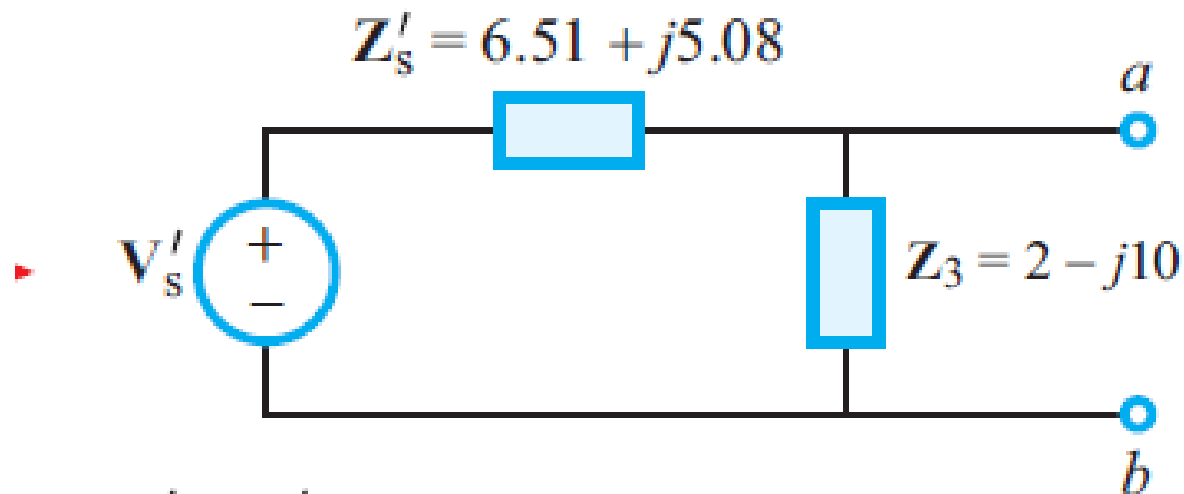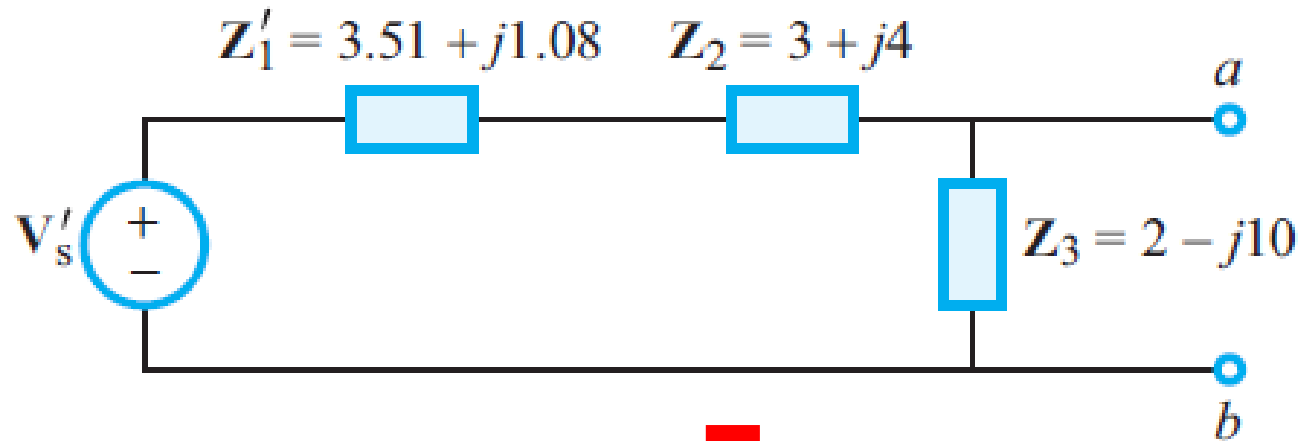

(e) $Z'_s = Z'_1 + Z_2$

Example: Thévenin Circuit

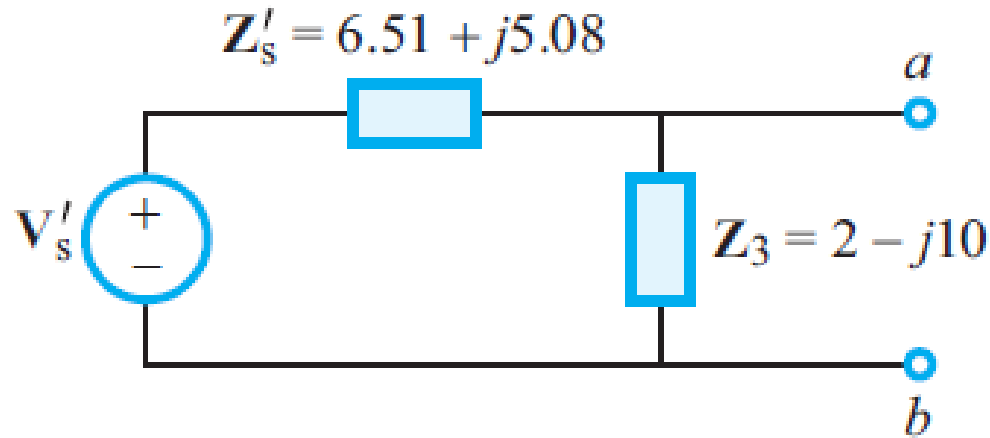

$$Z_{Th} = Z'_s \parallel Z_3$$

$$\frac{(6.51 + j5.08)(2 - j10)}{(6.51 + j5.08) + (2 - j10)} = (8.42 - j1.59) \Omega$$


$$R_{Th} = 8.42 \Omega,$$

$$C_{Th} = \frac{1}{1.59\omega} = 6.29 \mu\text{F}$$


Solving using Phasor Diagrams

- The relationships between current and voltage for L and C are:

Capacitor

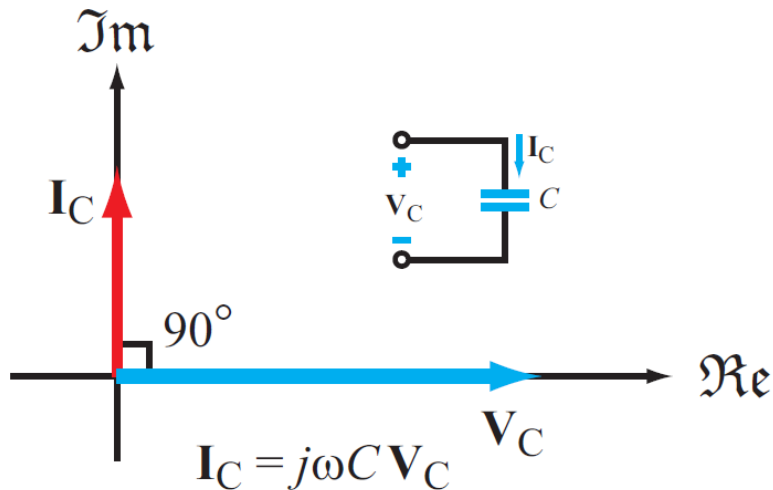


Inductor

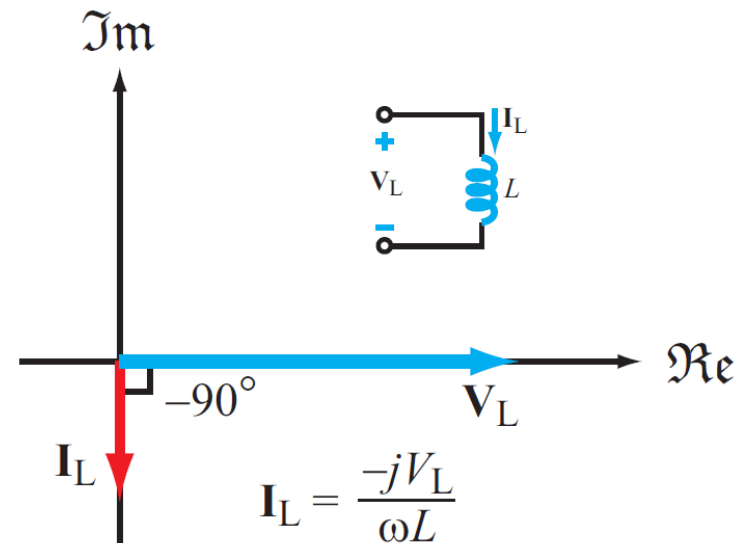

- The relationship between current and voltage for R is trivial, obviously

Solving using Phasor Diagrams

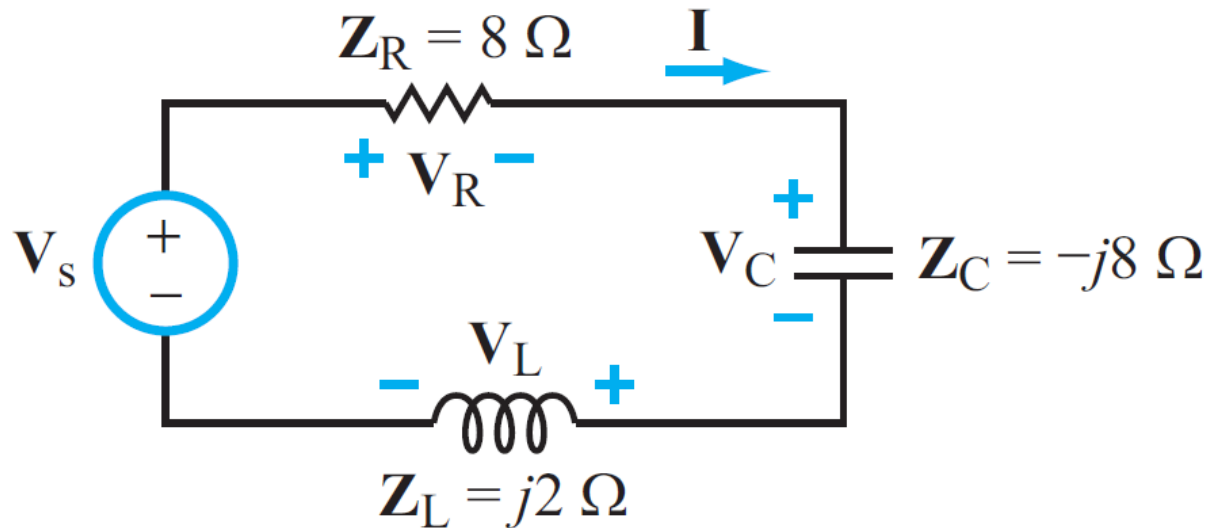- Consider the following circuit, with $V_s = 20e^{j30}$



$$\mathbf{I} = \frac{\mathbf{V}_s}{R + j\omega L - \frac{j}{\omega C}}$$

Solving using Phasor Diagrams

- We can find the individual voltages graphically:
 $I = 2e^{j66.87^\circ}$ A

