
Frequency Response

Michel M. Maharbiz

Vivek Subramanian

Frequency Response

Transfer function of a circuit or system describes the **output response** to an **input excitation** as a function of the angular frequency ω .

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_{\text{out}}(\omega)}{\mathbf{V}_{\text{in}}(\omega)} \quad \text{Voltage Gain}$$

$$\mathbf{H}(\omega) = M(\omega) e^{j\phi(\omega)},$$

where by definition,

$$M(\omega) = |\mathbf{H}(\omega)|, \quad \phi(\omega) = \tan^{-1} \left\{ \frac{\Im[\mathbf{H}(\omega)]}{\Re[\mathbf{H}(\omega)]} \right\}$$

Magnitude

Phase


Other Transfer Functions

Current gain: $\mathbf{H}_I(\omega) = \frac{\mathbf{I}_{\text{out}}(\omega)}{\mathbf{I}_{\text{in}}(\omega)},$


Transfer impedance: $\mathbf{H}_Z(\omega) = \frac{\mathbf{V}_{\text{out}}(\omega)}{\mathbf{I}_{\text{in}}(\omega)},$

Transfer admittance: $\mathbf{H}_Y(\omega) = \frac{\mathbf{I}_{\text{out}}(\omega)}{\mathbf{V}_{\text{in}}(\omega)}.$


Examples

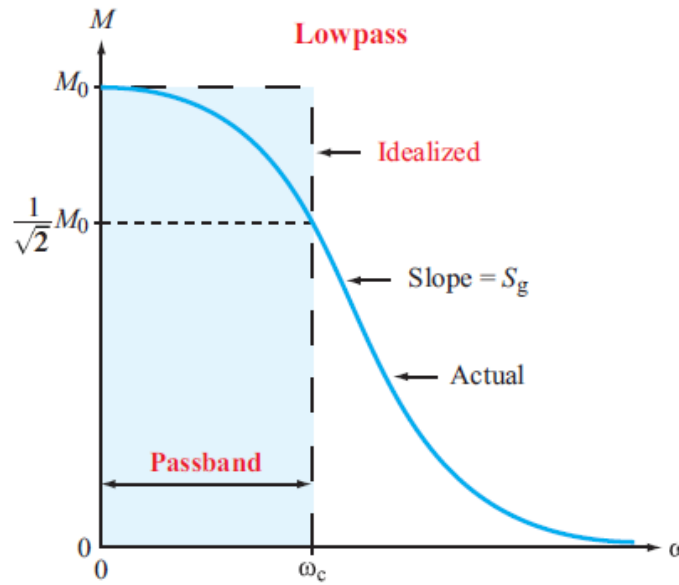


(a) Lowpass filter

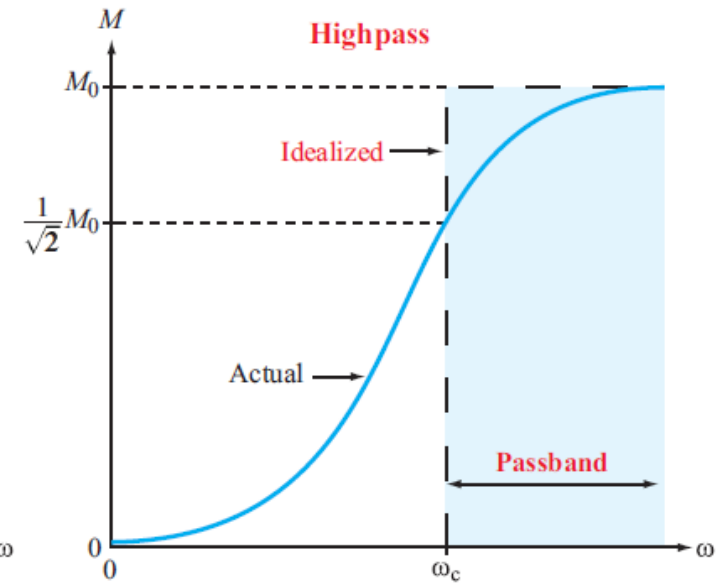

(b) Highpass filter

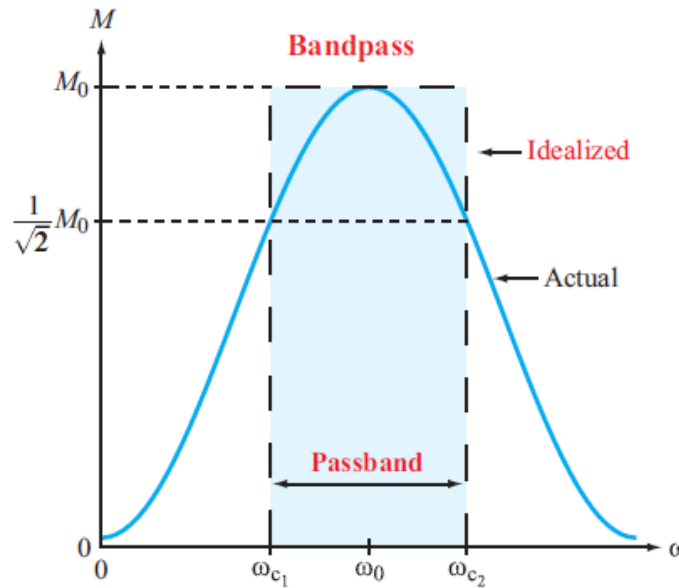


(c) Bandpass filter

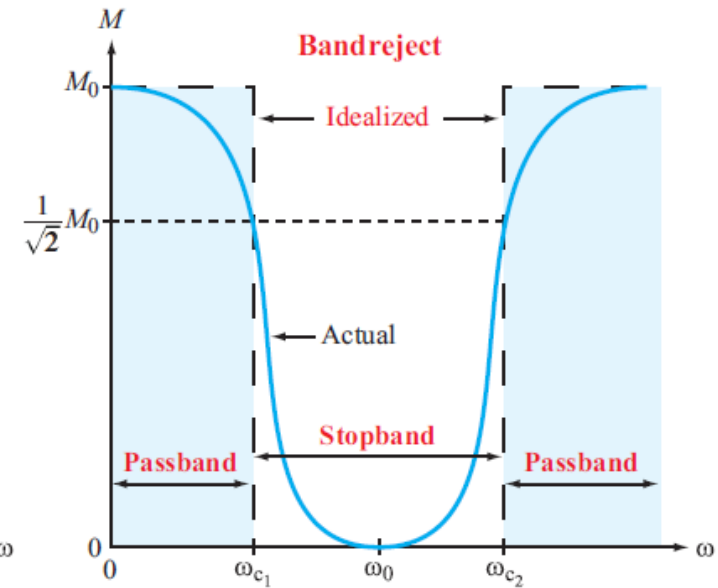

(d) Bandreject filter

Example: Low pass filter

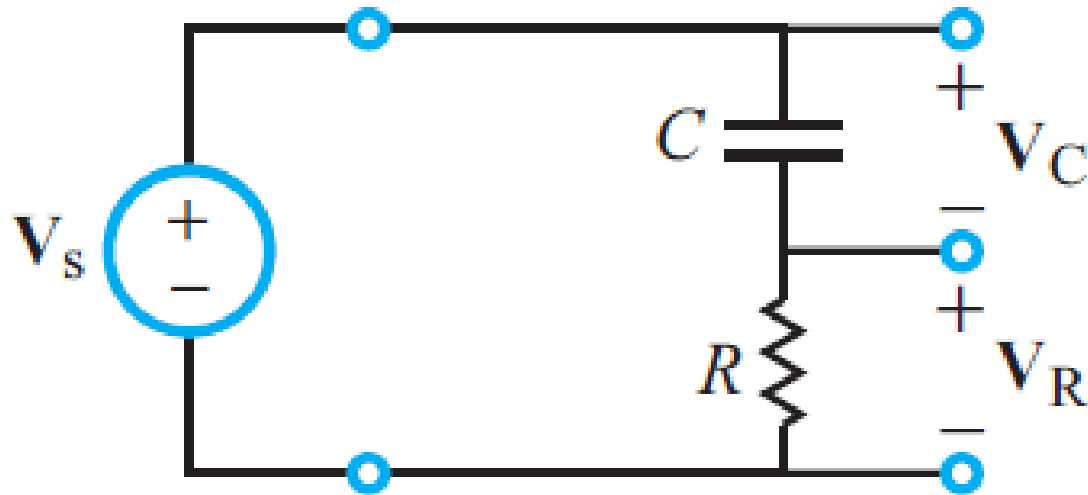

(a) RC circuit

Application of voltage division gives

$$V_C = \frac{V_s Z_C}{R + Z_C} = \frac{V_s / j\omega C}{R + \frac{1}{j\omega C}}.$$

$$\mathbf{H}_C(\omega) = M_C(\omega) e^{j\phi_C(\omega)},$$


$$M_C(\omega) = |\mathbf{H}_C(\omega)| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

The transfer function corresponding to V_C is

$$\mathbf{H}_C(\omega) = \frac{V_C}{V_s} = \frac{1}{1 + j\omega RC},$$

$$\phi_C(\omega) = -\tan^{-1}(\omega RC).$$

Example: Low pass filter

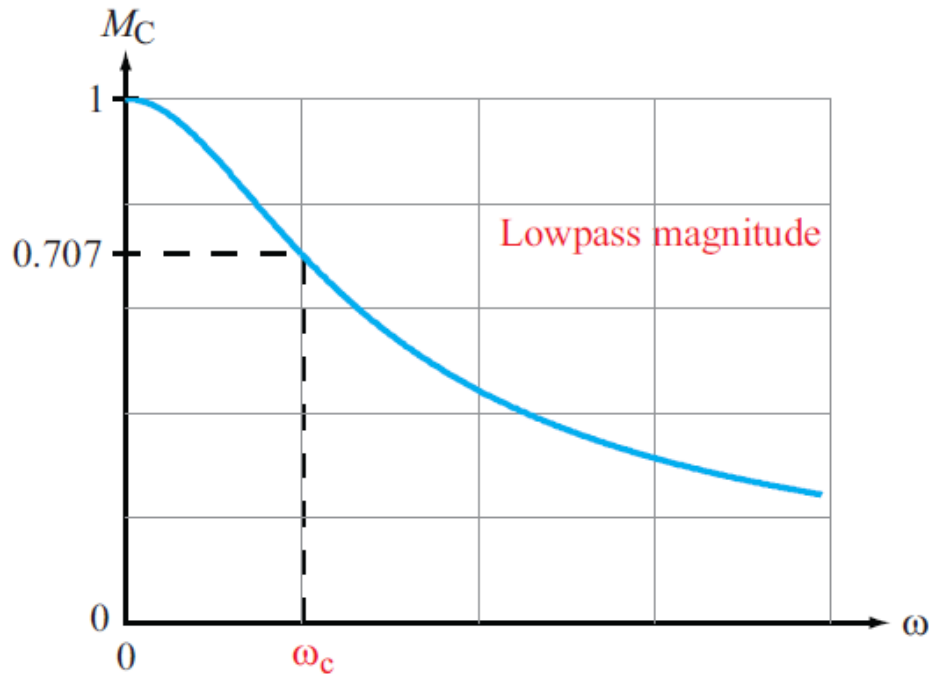

$$\mathbf{H}_C(\omega) = M_C(\omega) e^{j\phi_C(\omega)},$$

$$M_C(\omega) = |\mathbf{H}_C(\omega)| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

$$\phi_C(\omega) = -\tan^{-1}(\omega RC).$$

$$\mathbf{H}_C(\omega) = \frac{V_C}{V_s} = \frac{1}{1 + j\omega RC},$$

Corner Frequency ω_c

The corner frequency ω_c is defined as the angular frequency at which $M(\omega)$ is equal to $1/\sqrt{2}$ of the reference peak value,

$$M(\omega_c) = \frac{M_0}{\sqrt{2}} = 0.707M_0. \quad (9.5)$$


To determine corner frequency:

$$M_C^2(\omega_c) = \frac{1}{1 + \omega_c^2 R^2 C^2} = \frac{1}{2},$$

leads to

$$\omega_c = \frac{1}{RC}.$$

Example: High pass filter

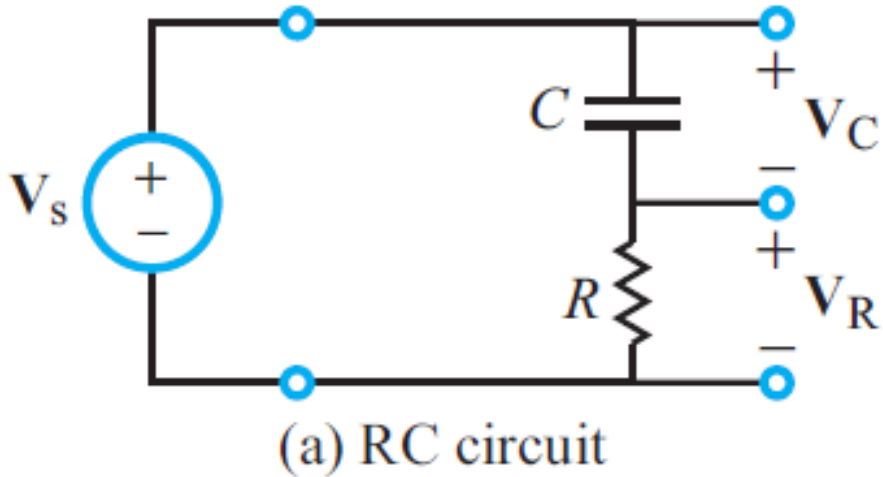


$$\mathbf{H}_R(\omega) = \frac{\mathbf{V}_R}{\mathbf{V}_s} = \frac{j\omega RC}{1 + j\omega RC}.$$

The magnitude and phase angle of $\mathbf{H}_R(\omega)$ are given by

$$M_R(\omega) = |\mathbf{H}_R(\omega)| = \frac{\omega RC}{\sqrt{1 + \omega^2 R^2 C^2}}$$

and
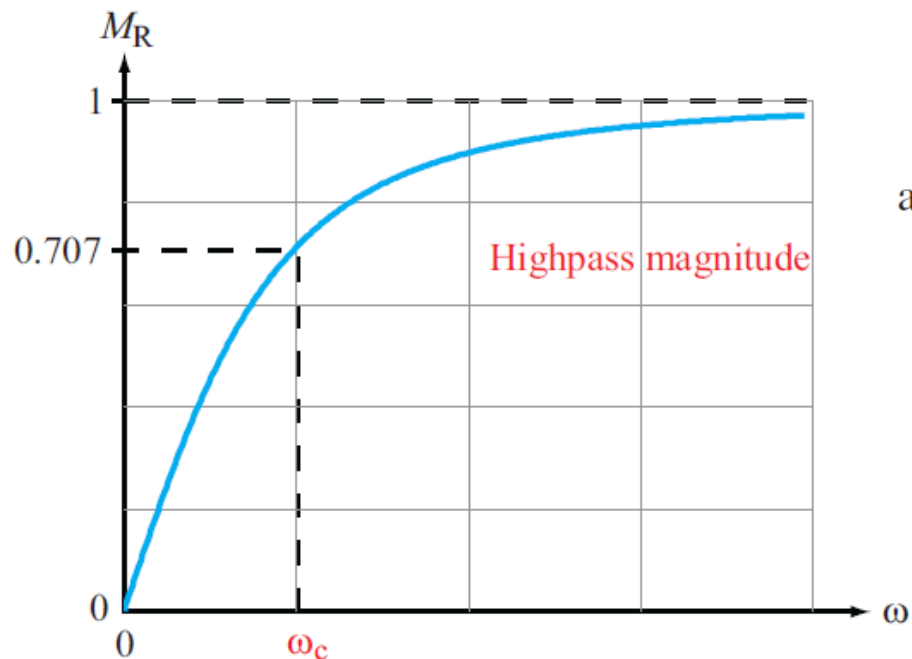
$$\phi_R(\omega) = \frac{\pi}{2} - \tan^{-1}(\omega RC).$$



Another example: an RLC circuit



$$\mathbf{I} = \frac{\mathbf{V}_s}{R + j(\omega L - \frac{1}{\omega C})}$$

$$= \frac{j\omega C \mathbf{V}_s}{(1 - \omega^2 LC) + j\omega RC}$$

$$\mathbf{H}_{BP}(\omega) = \frac{\mathbf{V}_R}{\mathbf{V}_s} = \frac{R\mathbf{I}}{\mathbf{V}_s} = \frac{j\omega RC}{(1 - \omega^2 LC) + j\omega RC}$$

$$M_{BP}(\omega) = |\mathbf{H}_{BP}(\omega)| = \frac{\omega RC}{\sqrt{(1 - \omega^2 LC)^2 + \omega^2 R^2 C^2}}$$
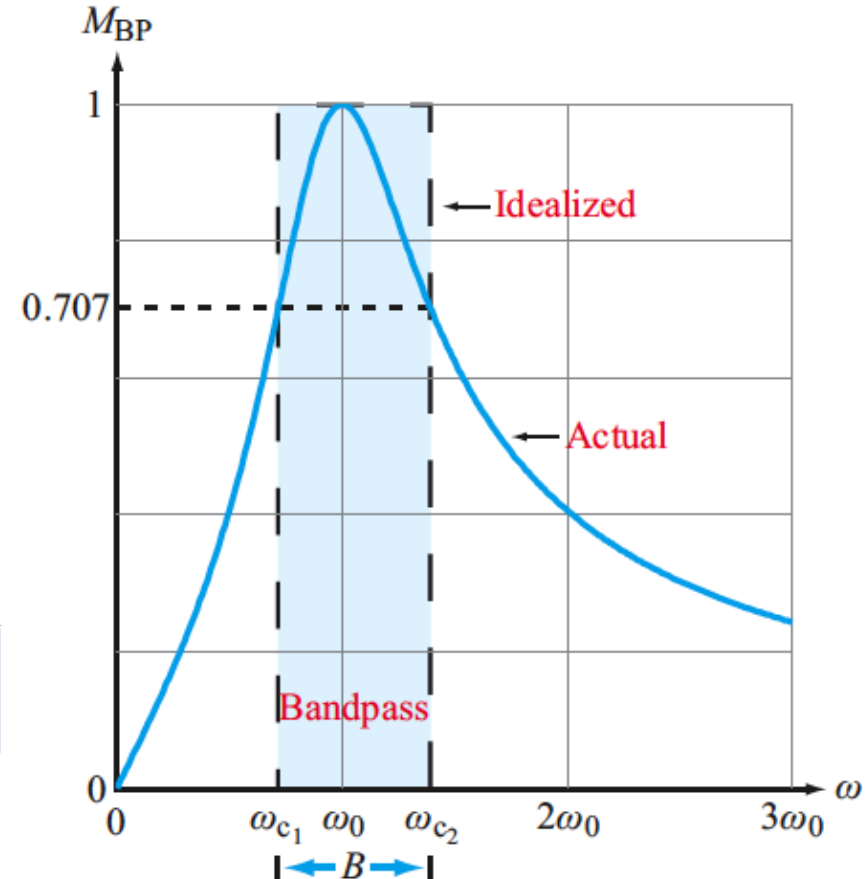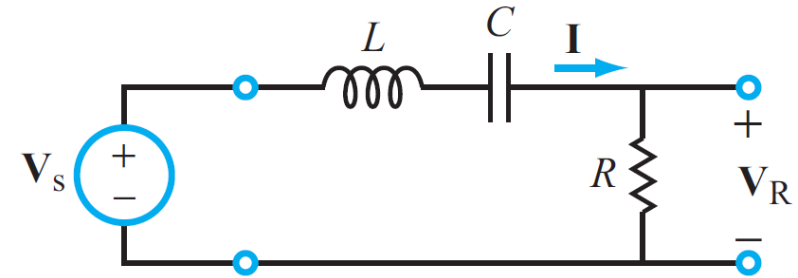
$$\phi_R(\omega) = 90^\circ - \tan^{-1} \left[\frac{\omega RC}{1 - \omega^2 LC} \right]$$



$$\omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}},$$

$$\omega_0 = \frac{1}{\sqrt{LC}}.$$

$$\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}.$$

$$B = \omega_{c2} - \omega_{c1} = \frac{R}{L}.$$